

260

(260)

-: HAND WRITTEN NOTES:-

OF

(4)

Electrical ENGG

-: SUBJECT:-

**NETWORK THEORY**

②

## Network Theory

1. Basics
2. Steady State AC Circuits (Resonance).
3. Theorems (obj & conv).
4. Transients ( " )
5. Two port ( " )
6. Graph theory and magnetic circuits
7. Filters
8. Synthesis (obj)

### Books

1. Fundamentals of Electric Circuits. (PDF)  
By Alexander Sadiku.
2. Engg Circuit Analysis  
By Hayt Kemmerly.
3. Networks and Systems  
By Roy Choudhary.
4. Network Analysis — Van Valkenburg.




the basic quantity in the circuit is charge, The charges of the  $e^-$  is given by  $-1.602 \times 10^{-19} \text{ C}$ . (4)

a flow of electrons is called as current (or)

the time rate of change is also called as current.

$$I = \frac{dQ}{dt} \text{ C/s (or) A}$$

$I \rightarrow$  conventional current.

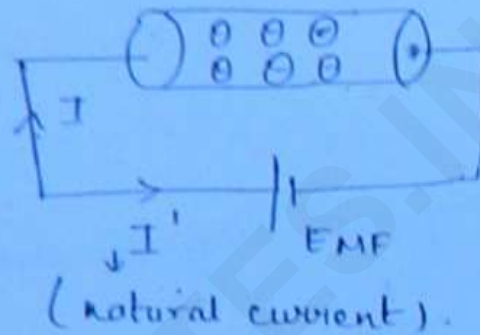

In the network theory, while developing KVL & KCL equation conventional current is used.

To move the  $e^-$  from one point to other point in particular direction, external force is required.




In the circuit, external force is provided by EMF and it is given by.

$$V = \frac{dW}{dQ} \text{ J/C (or) Volt.}$$




The time rate of energy is called as power

$$P = \frac{dW}{dt} \text{ J/s (or) Watt.}$$
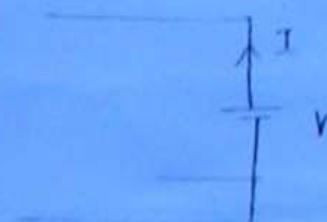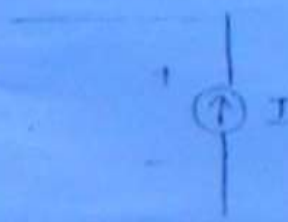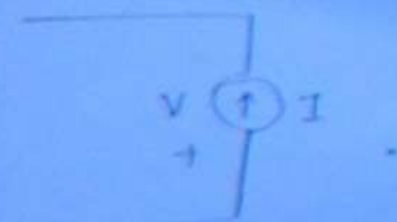
$$P = \frac{dW}{dQ} \frac{dQ}{dt} \Rightarrow \boxed{P = VI}$$





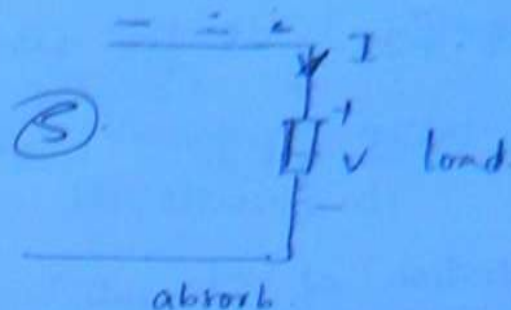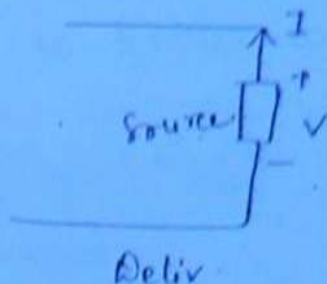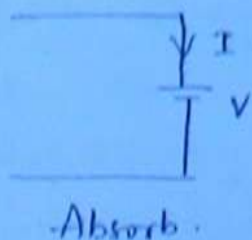

Note :

1. When current is entering at positive terminal element is absorbing power.
2. When current is leaving from the +ve terminal, element is delivering the power.

Q. Find power of each element, of the circuit shown.


$$V_1 - V_2 = 2V$$

$$V_2 = 10 - 2 = 8V$$

$$V_2 = 8V$$

$$V_3 - V_1 = 3$$

$$V_3 = 13V$$

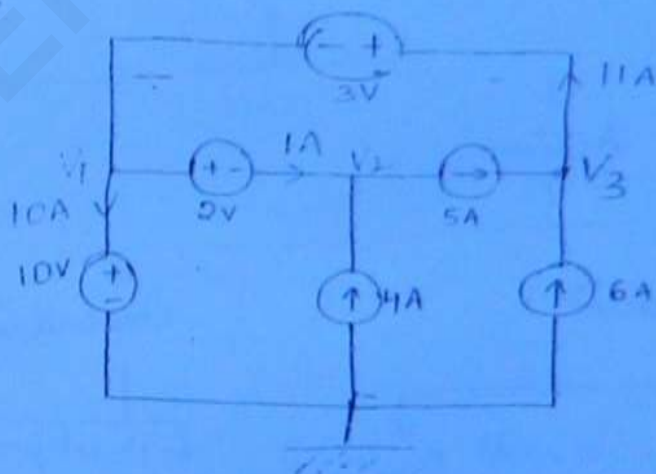

$$P_4 = 8 \times 4 = 32W \quad (\text{Del})$$

$$P_6 = 13 \times 6 = 78W \quad (\text{Del})$$

$$P_5 = 5 \times 5 = 25W \quad (\text{Del})$$

$$P_3 = 11 \times 3 = 33W \quad (\text{abs.})$$

$$P_{10V} = 10 \times 10 = 100W \quad (\text{abs.})$$

$$P_2 = 2 \times 1 = 2W \quad (\text{abs.})$$

$$(P_T)_{\text{abs}} = (P_T)_{\text{Del}} = 135W$$


the capacity to do the work is called as Energy.

$$W = \int_0^t P dt \quad \text{Watt-sec (or) J.}$$


(6)

## Classification of Elements

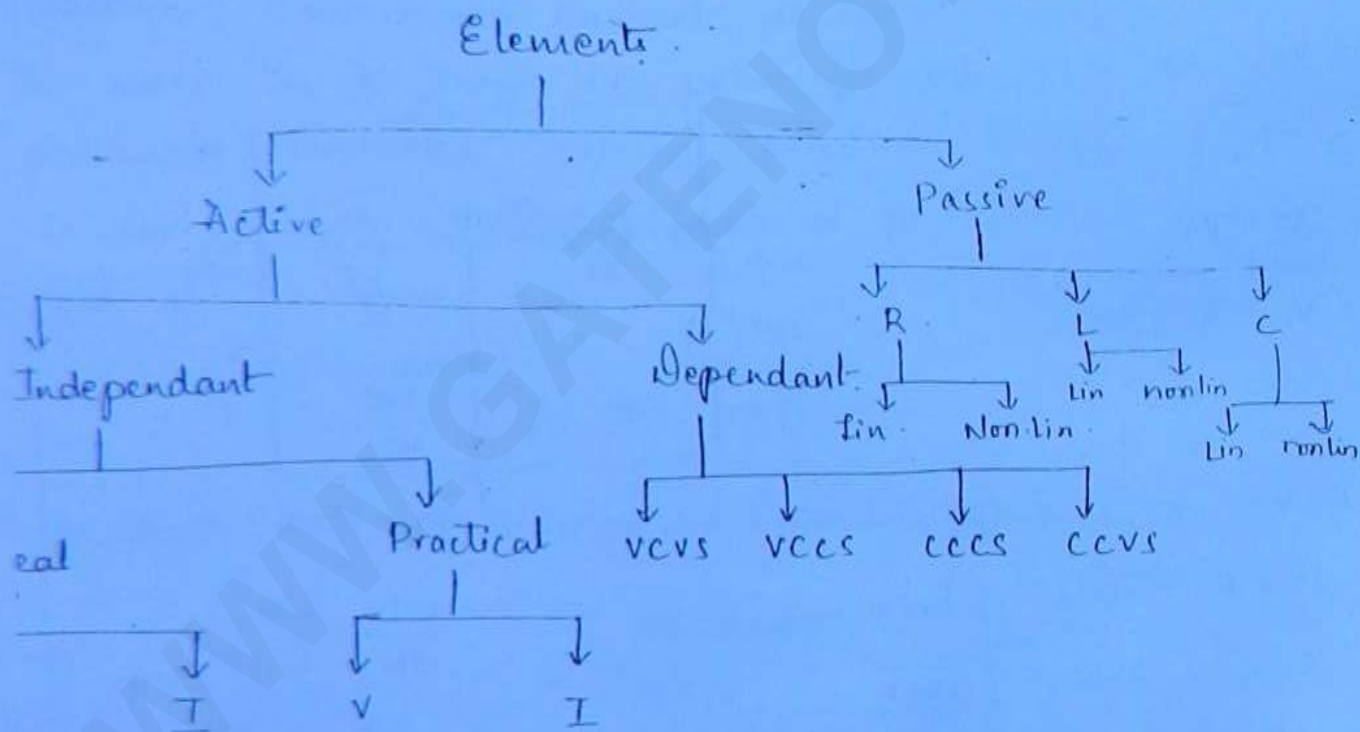1. Active and Passive Elements.
2. Unidirectional & Bidirectional Elements.
- Linear and non linear elements.
- Time variant and invariant elements.
- Lumped and distributed Elements.



Active Elements :- when element is capable of delivering Energy independently for infinite time (or) when the element is having property of internal amplification then the element is called as active element.

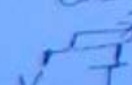Ex.  Independent source  
Transistor

## Passive Elements

⑦

When the element is not capable of delivering energy independently for infinite time, then the element is called as passive element.

Ex.  $R, L, \& C$ , bulb, transformer.

Resistance is a property of the resistor. It opposes flow of current. By doing so, it converts electrical energy to heat energy.

$$P = I^2 R$$



$$W = I^2 R t$$

↓  
(heat)

$$R = \frac{\rho L}{a}$$

$\Omega$

$F \rightarrow \Omega m$

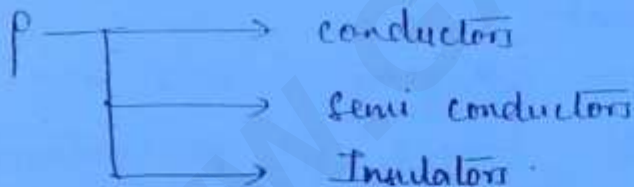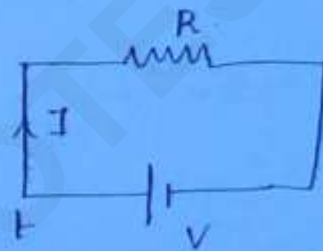

When resistivity ( $\rho$ ) of a conductor,  $\rho = 0$ , then it is called super conductor.

Ex. At 4.15K Mercury acts as a superconductor.

$$R_t = R_0 (1 + \alpha_0 t)$$

Where,

$R_0$  = resistance of the material at  $0^\circ C$

$\alpha_0$  : temperature coefficient per  $^\circ C$ .

$t$  : change in temperature.



## Ohm's law.

(8)


→ Ohm's law states that, at constant temperature, current density is directly proportional to electric field intensity.

$$J \propto E$$

$$J = \sigma E$$

$$\frac{I}{A} = \frac{1}{\rho} \cdot \frac{V}{l}$$

$$\frac{V}{I} = \frac{\rho l}{A} = R.$$

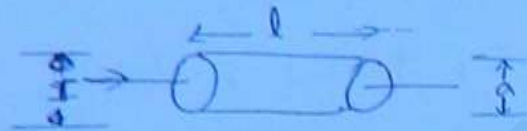

$$R = \frac{\rho l}{A}$$


$$J = \frac{I}{A}$$

$$E = \frac{V}{l}$$

$$\sigma = \frac{1}{\rho} \quad \text{mho/m.}$$

→ At constant temperature, potential difference across an element is directly proportional to the current flowing across the element.

$$V \propto i$$

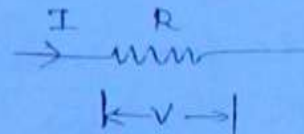

$$V = R I.$$

$$R = V/I = \text{constant.}$$

Ohm's law can be applied when temperature and conductivity of the material are constant.

Ohm's law

1<sup>st</sup> form →  $J = \sigma E$

$$G = \frac{1}{R} \quad \text{mho (or } \Omega^{-1})$$

2<sup>nd</sup> form →  $V = i R$




3<sup>rd</sup> form →  $i = G V$

4<sup>th</sup> form →  $V = \frac{dQ}{dt} R.$

→ When element properties and characteristics are independent on the direction of the current, then the element is called as bi directional element.

→ When element obeys the ohm's law, then the element is called as linear resistor.

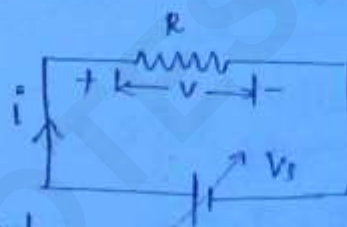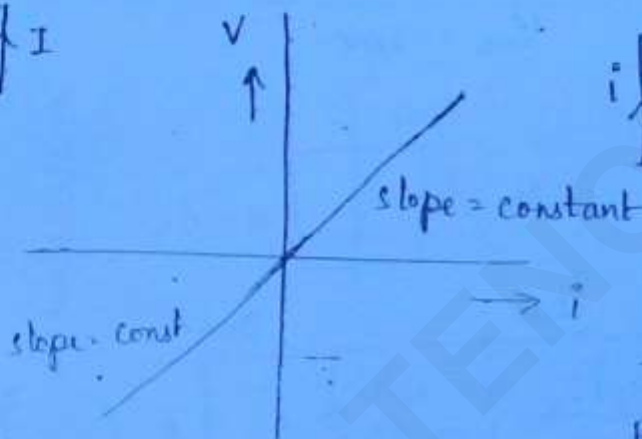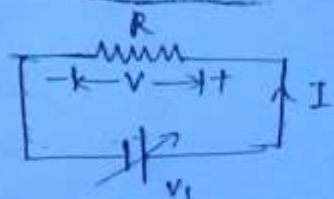~~Every~~ Every linear element should obey the bi-directional property. But not vice versa.





$$i \uparrow 10\% \Rightarrow V \uparrow 10\%$$

$$i \uparrow 90\% \Rightarrow V \uparrow 90\%$$

$$R = \frac{V}{I} = \text{Constant}$$

→ When element properties and characteristic depends on direction of the current, then the element is called as unidirectional element.

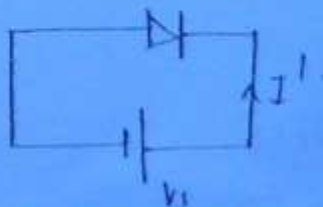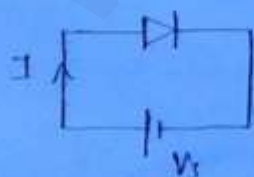→ When element does not obey the Ohm's Law, then the element is called as non linear resistor.




$$|I| \neq |I'|$$

## Open circuit O.C.

(10)


### Properties of O.C. (Ideal)

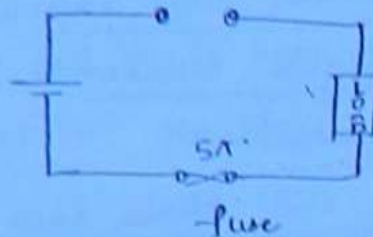

$$R = \infty$$

$$I = 0$$

$$V = \infty \text{ (non-possible)}$$

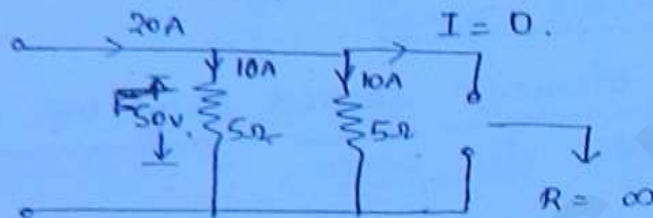


## Short circuit (S.C.)

### Properties of S.C. (Ideal)


$$R = 0$$

$$I = \infty$$

$$V = 0$$

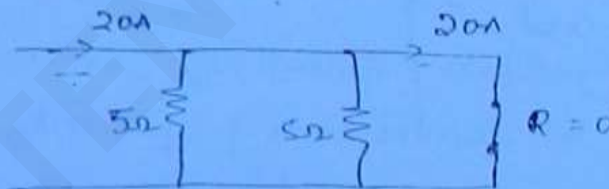

## Inductor

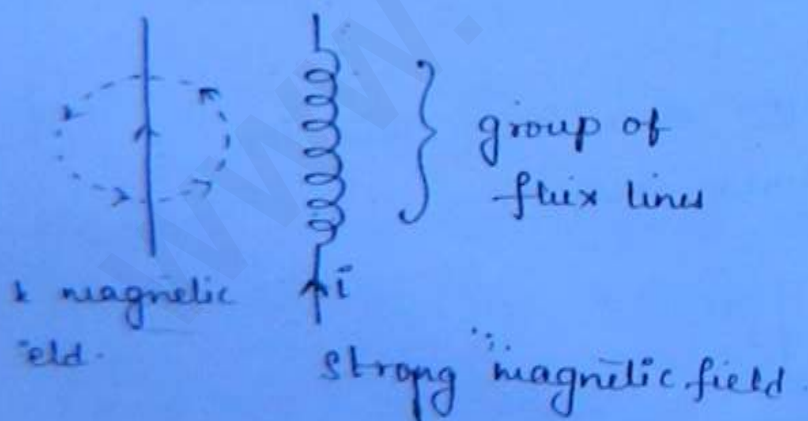

flux direction —  
right hand thumb  
rule

## Faraday's 1st law

When conductor cuts a magnetic lines of the force, an e.m.f is induced in the conductor.

The e.m.f induced is  $\propto \frac{d\Phi}{dt}$








1. emf is induced (c).

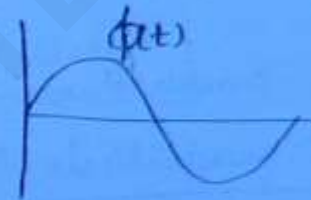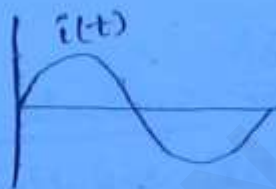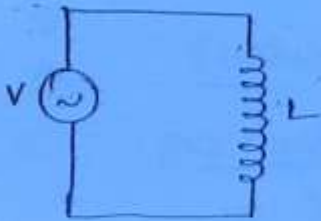2.  $e \propto \frac{d\phi}{dt}$

$$e = -N \frac{d\phi}{dt}$$

This is dynamically induced emf, Ex. - generator.



$e \propto \frac{d\phi}{dt}$

→ This is statically induced emf,  
Ex. Transformer (T/F)

$$e = -N \frac{d\phi}{dt} \rightarrow \text{Lenz law}$$

where -ve sign indicates, based on

Lenz law, induced voltage opposes its cause of existence.

$$\psi = N\phi$$

→ flux linkage.

$$V = \frac{d\psi}{dt}$$

$$\left. \begin{array}{l} \phi \propto i \\ \psi \propto \phi \end{array} \right\}$$

$$\psi \propto i \rightarrow \boxed{\psi = Li}$$

$$\psi = N\phi$$

$$V = \frac{d\psi}{dt}$$

$$\phi \propto i$$

$$\psi \propto i$$

$$V = L \frac{di}{dt}$$


$$L = \frac{V}{(di/dt)}$$

(12)

$$\begin{aligned} \psi &= N\phi \\ \psi &= Li \end{aligned} \quad \}$$

$$L = \frac{N\phi}{I} \text{ H.}$$


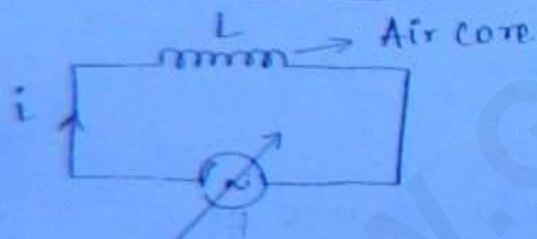
→ when inductance of the inductor independent on current magnitude then the inductor is called as linear inductor. Ex: Air core inductor.



$$L = \frac{N\phi}{I} = \text{constant.}$$

$$i \uparrow 10\%, \quad \phi \uparrow 10\%$$
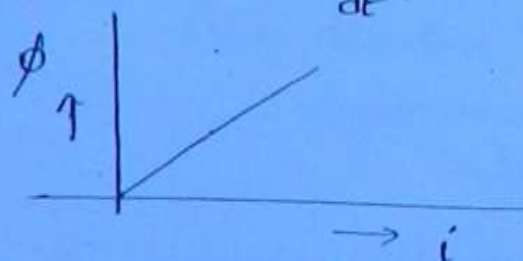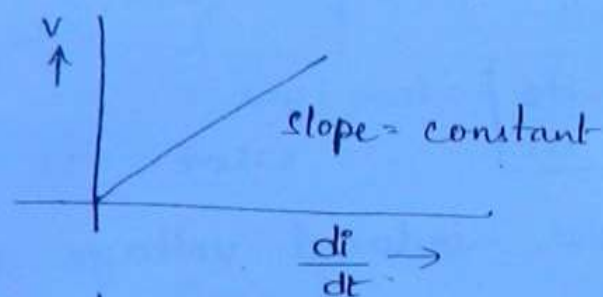
$$i \uparrow 90\%, \quad \phi \uparrow 90\%$$



$$V = L \frac{di}{dt} \Rightarrow \therefore L = \frac{V}{(di/dt)}$$

when inductance of the inductor depends on current magnitude, then the inductor is called as non linear inductor. Ex: IRON CORE inductor.

38.

$$V_{La} = \frac{e_1 + e_2(t)}{3}$$

(77)

$$= \frac{1}{3} \left( \sqrt{3} \cos(\omega t + 30^\circ) + \sqrt{3} \sin(\omega t + 60^\circ) \right)$$

$$= \frac{1}{3} \cdot \sqrt{3} \left[ \cos(\omega t + 30^\circ) + \cos(\omega t + 60 - 90^\circ) \right]$$

convert it to either cos or sine.

$$= \frac{1}{\sqrt{3}} \left[ \cos(\omega t + 30^\circ) + \cos(\omega t - 30^\circ) \right]$$

$$= \frac{1}{\sqrt{3}} \left[ 1 \angle 30^\circ + 1 \angle -30^\circ \right] = 1 \text{ V} \cdot 1 \angle 0^\circ$$

$$= 1 \cos(\omega t + 0^\circ) = \underline{\underline{\cos \omega t}}$$

43.

$$V = \sqrt{V_R^2 + V_L^2}$$

$$250 = \sqrt{V_R^2 + 150^2} \Rightarrow V_R = 200 \text{ V}$$

$$I = \frac{V_R}{R} = \frac{200}{100} = 2 \text{ A} \Rightarrow I_{\text{rms}} = 2 \text{ A}$$

$$X_L = \frac{V_L}{I} = \frac{150}{2} = 75 \Rightarrow \omega L = 75$$

$$L = \frac{75}{300} = 0.25 \text{ H}$$



45.

let current thru 60V, =  $i^1$

$$i^1 + i^2 = 12 \Rightarrow i^2 = 12 - i^1 = 12 \text{ A}$$

Ans: 10A

46.

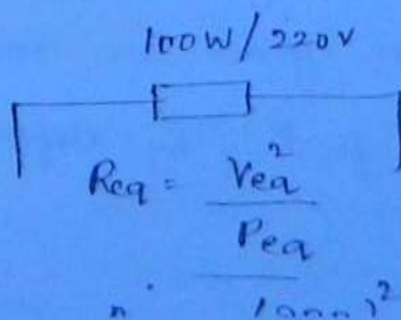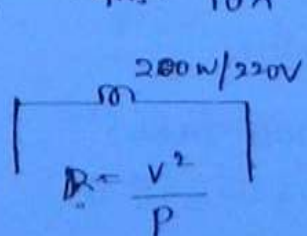

$$R_{eq} = nR$$

$$n = 2$$

n = no. of bulbs



$$L = \frac{N^2}{l/\mu_0\mu_r}$$

(74)

$$S = \frac{l}{\mu_r\mu_0}$$

$$L = \frac{N^2}{S}$$

$$S = \frac{\text{MMF}}{\phi} = \frac{NI}{\phi} \quad \text{AT/Weber}$$

$$L = \frac{N^2}{S} = \frac{N^2 \phi}{NI} = \frac{N \phi}{I}$$

law form  $\rightarrow$

$$V = L \frac{di}{dt}$$

work done  $\rightarrow$

$$i = \frac{1}{L} \int_{-\infty}^t v dt$$

$$P = \vec{v} \cdot \vec{i}$$

$$P = L \frac{di}{dt} i$$

$$W = \int P dt$$

$$W = \frac{1}{2} Li^2$$

or dissipation in an ideal inductor = 0.

Inductor stores Energy in the form of magnetic field. (Kinetic Energy).

conclusion:


For dc supply at steady state, inductor acts as a short circuit.

$$V = L \frac{di}{dt}$$

Steady state  $\rightarrow di/dt = 0$

$$V = 0$$




$\downarrow$   
S.C.

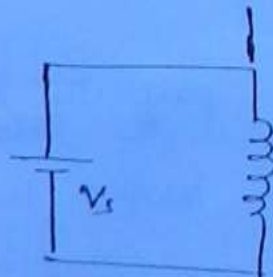

- Inductor does not allow sudden change of current & since to allow sudden change of current infinite voltage is required and time constant of the circuit should be equal to zero.

(i)  $V = L \frac{di}{dt} = \infty \quad \text{if } \frac{di}{dt} \rightarrow 0$

(ii) Time constant =  $L/R$ .

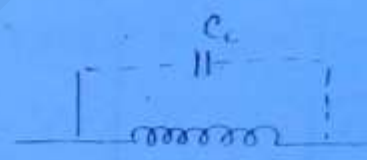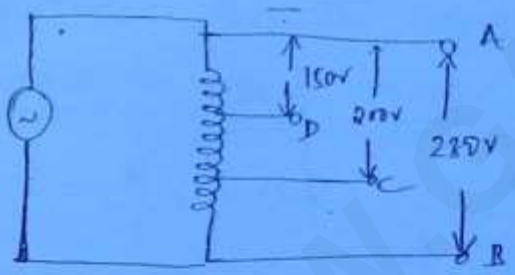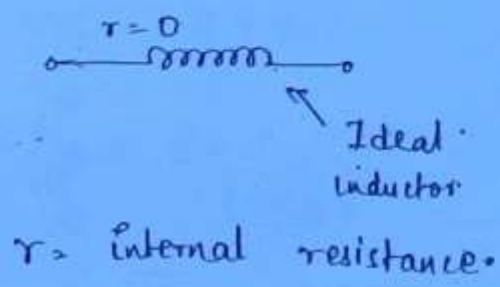

$C_c = \text{inter turn capacitance}$   
(or)  
Self capacitance.

$X_c = 1/2\pi f C$


Interturn capacitance is present when inductor is operated either at high frequency or high voltage.

### Capacitor

$Q \propto V$

$Q = CV$

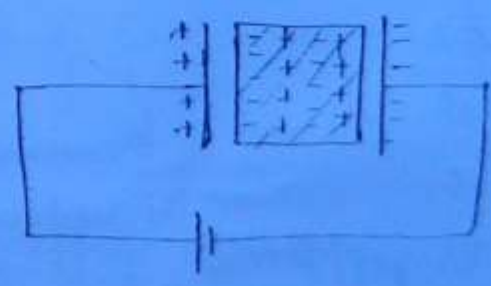$C = \frac{Q}{V} \quad \text{C/V (or) F}$



$$Q = CV$$

(16)

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

$$i = C \frac{dV}{dt}$$

$$C = i / (dV/dt)$$

$$i = C \frac{dV}{dt}$$

Ohm's law  
7<sup>th</sup> form.

$$P = Vi$$

$$P = C \frac{dV}{dt} V$$

$$W = \int P dt$$

$$W = \frac{1}{2} CV^2$$

$$V = \frac{1}{C} \int_{-\infty}^t i dt$$

8<sup>th</sup> form.

Energy stored in the  
form of electric field.

Power dissipation in ideal capacitor = 0.

> Capacitor stores energy in the form of electric field.  
(potential energy).

$$C = \frac{\epsilon A}{d}$$

$$\epsilon = \epsilon_0 \epsilon_r$$

$$\epsilon_0 = 8.85 \text{ pF/m}$$

\*

Permittivity is the property of  
the medium in which electric  
field exists.

A → area of cross section of each conducting plate

d → distance b/w 2 conducting plates





→ when capacitance of the capacitor independent on the voltage magnitude, then the capacitor is called as linear capacitor.

$$C = \frac{Q}{V} = \text{constant.}$$

$V \uparrow 10\%$ ,  $Q \uparrow 10\%$ .


$V \uparrow 90\%$ ,  $Q \uparrow 90\%$ .
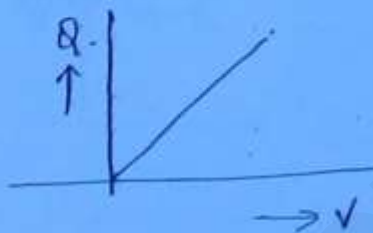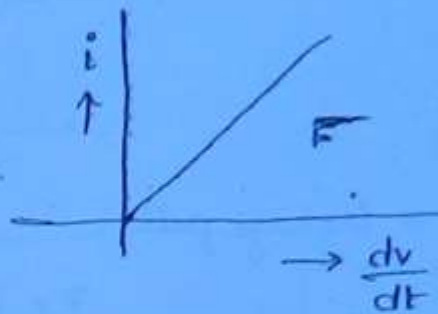
$$i = C \frac{dv}{dt} \Rightarrow C = \frac{i}{(dv/dt)}$$



→ when capacitance of the capacitor depends on voltage magnitude, then the capacitor is called as non-linear capacitor. Ex. Varactor diode.


$$C = \frac{Q}{V} = \text{variable.}$$

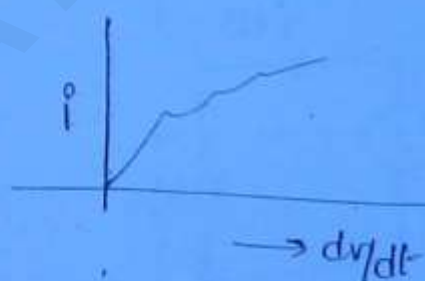

### Conclusions.

→ 1. For dc supply, at steady state, capacitor acts as O.C.

$$i = C \frac{dv}{dt} \Big|_{\text{steady state}} \frac{dv}{dt} = 0 \Rightarrow i = 0 \therefore \text{O.C.}$$

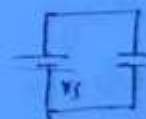


$$2. \text{ (i) } i = C \frac{dv}{dt}$$


Capacitor doesnot allow sudden change of voltages.

$\therefore$  for "sudden change of voltages"  $\infty$  current is required.

But practically it is not possible.

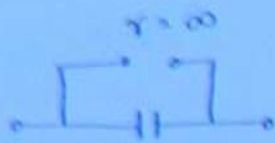

← ideal capacitor.

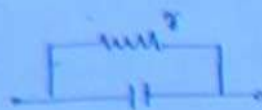

← practical.

$r \approx M\Omega$

in inductor  $r \approx m\Omega$ .





leakage path

$r =$  leakage path resistance.



## Active Elements
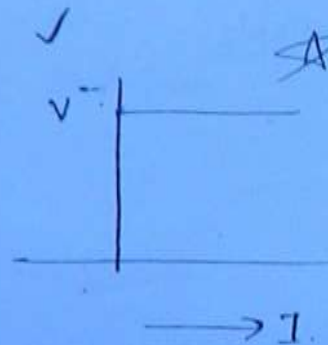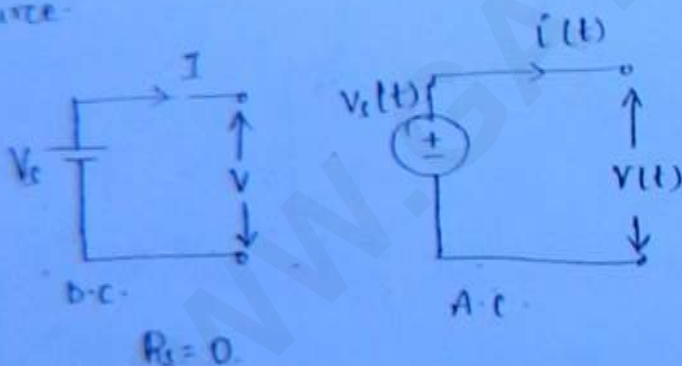
### Voltage Source

Ideal Voltage Source delivers energy at the specified voltage  $v(t)$ , which is independent on current delivered by this source.



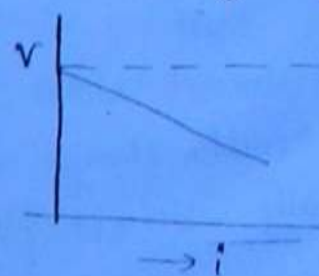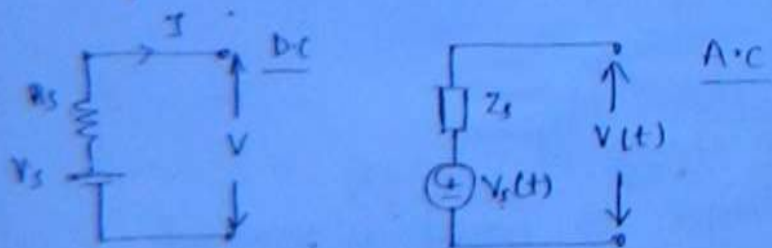
Practical voltage source delivers energy at specified voltage  $v(t)$ , which depends on current delivered by the source.






$$V_s = V + IR_s \Rightarrow V = V_s - IR_s$$
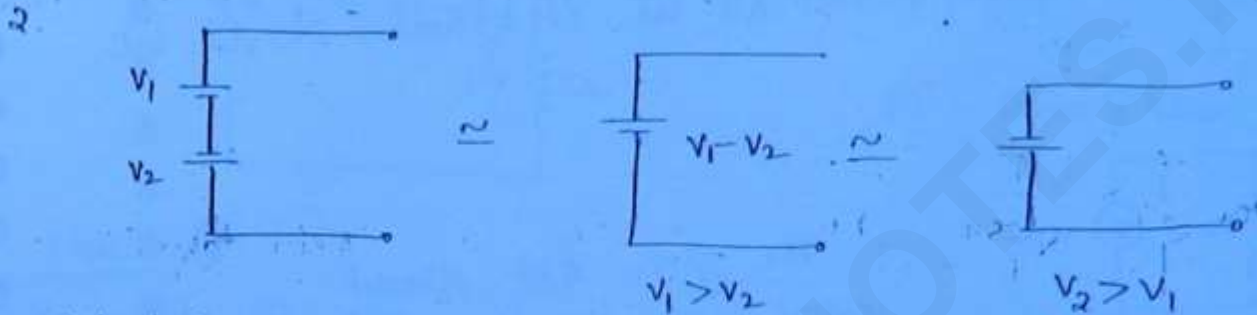
### Note:

Independent voltage and current source do not obey the ohm's law  
since voltage and current characteristic is non-linear.




Ideal source.

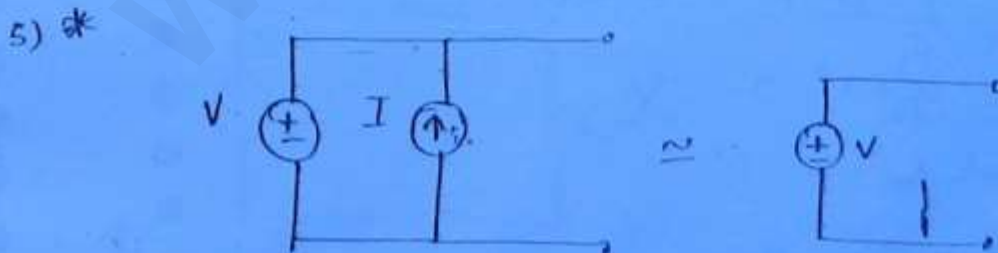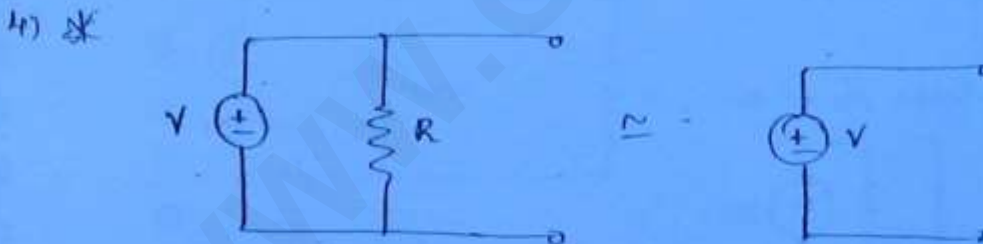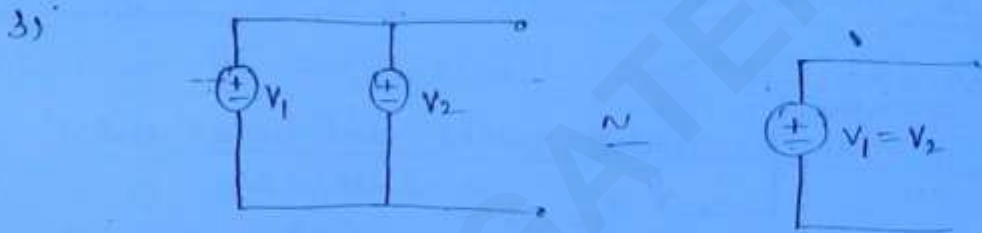



\*\*\*

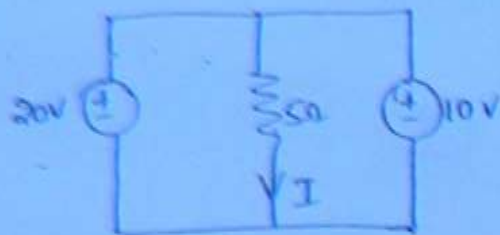
Find the value of  $I$  for this ckt. shown.





- (a) 2A (b) 4A (c) 6A  
(d) none.

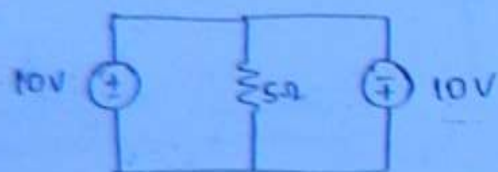(20)

Wrt KVL voltage across all the // branches should be equal.




→ The given ckt doesn't satisfy KVL.

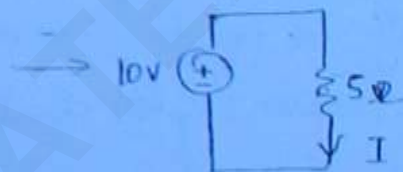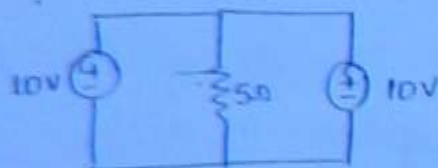

$$\Rightarrow I = 10/5 = 2A$$


using superposition

Case (i)

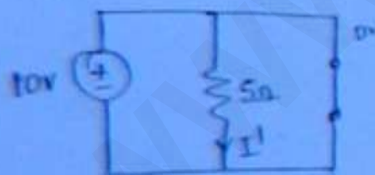

$$I' = 0$$

Case (ii)

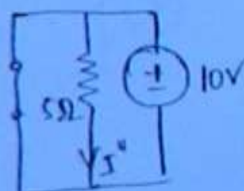


$$I'' = 0$$

$$I = I' + I'' = 0 \quad \times$$

10V & 0V can be

or the above circuit superposition theorem cannot be applied since, case 1 & case 2 circuits are not satisfying KVL.

Q.

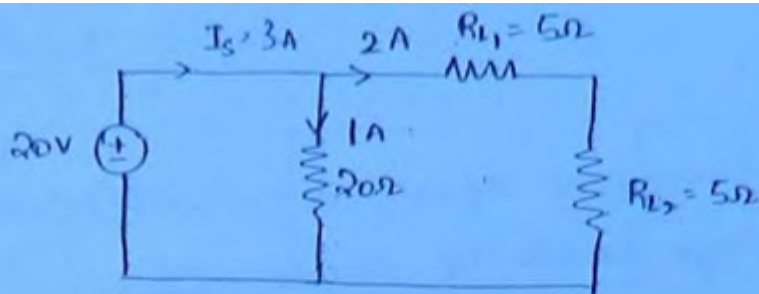


(2)

$$I_S = 3$$

$$P_S = 20 \times 3 = 60W$$

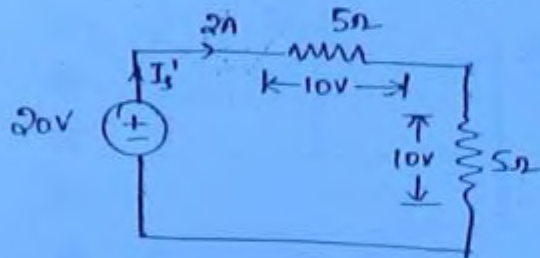or per eq. ckt (4) neglect  $R = 20\Omega$




$$I_S' = 2$$

$$P_S' = 20 \times 2 = 40W$$

Note: ✱


- (i) In the above circuit  $20\Omega$  resistance can be neglected while calculating either load current or load voltage.
- (ii) In the above circuit  $20\Omega$  resistance cannot be neglected while calculating either source current or power.

Q.

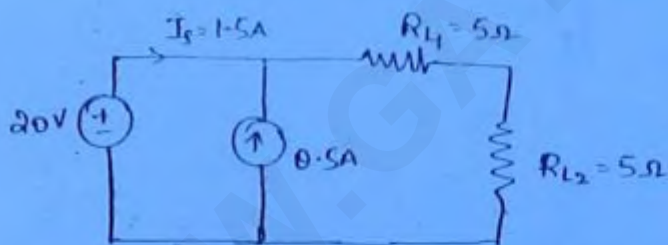

$$I_S = 1.5$$

$$P_S = 20 \times 1.5 = 30W$$

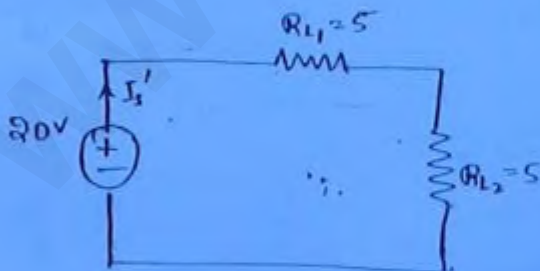

$$I_S' = 2$$

$$P_S' = 20 \times 2 = 40W$$


- Note: ✱
- (i) In the above ckt, current source can be neglected while calculating either load current or load voltage.
  - (ii) In the above circuit, current source cannot be neglected while calculating either voltage source current or power.



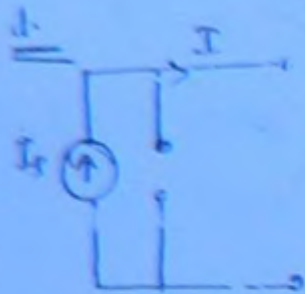
## Current sources.

Ideal current source delivers energy at specified current ( $I$ ), which is independent on voltage across the source. (22)


Internal resistance of ideal current source  $= \infty$ .





D.C.  $R_s = \infty$

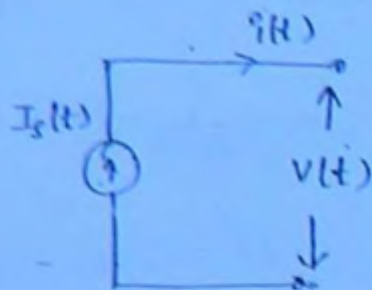

A.C.

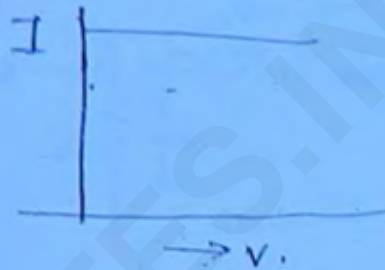

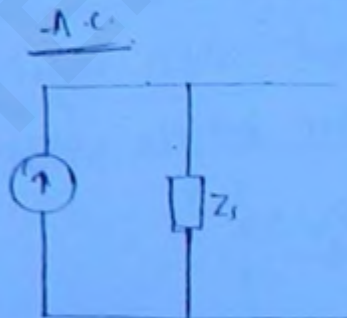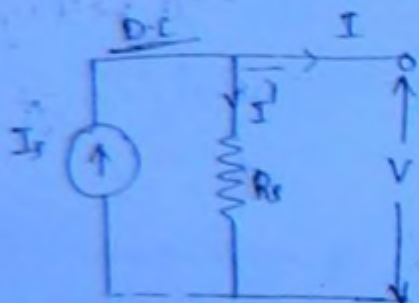
Real current source delivers energy at specified current ( $I$ ), which depends on voltage across the source.



$$I_s = I' + I$$

$$I = I_s - I'$$




$$I = I_s - \frac{V}{R_s}$$

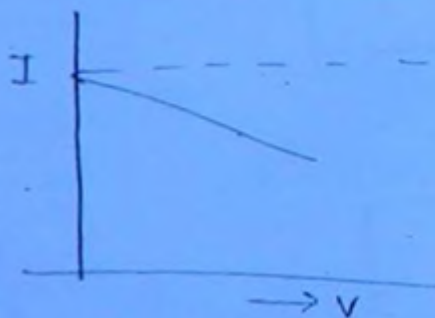


In the real time system no independent current source exist.



# Equivalent circuits:

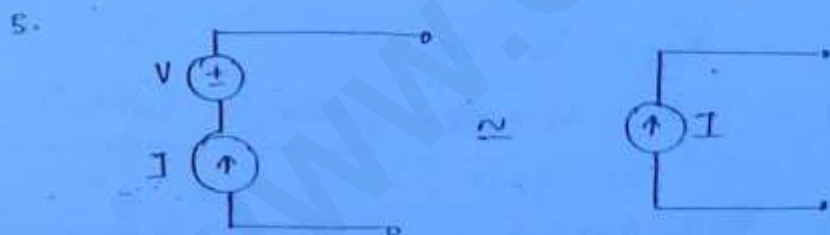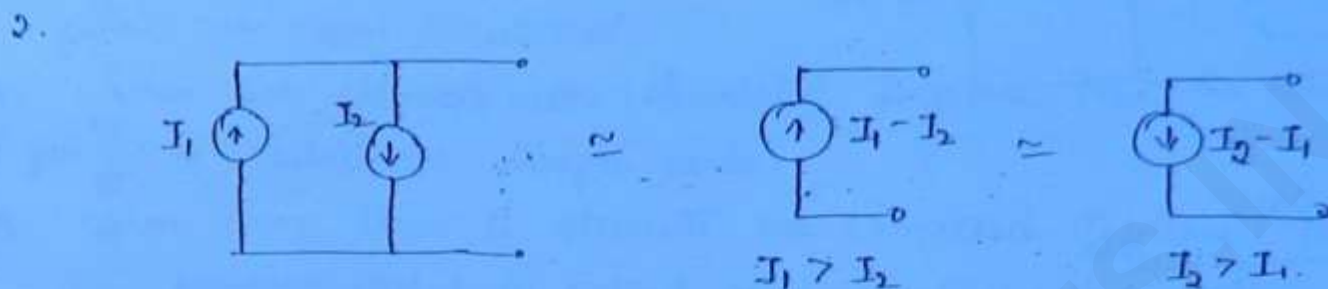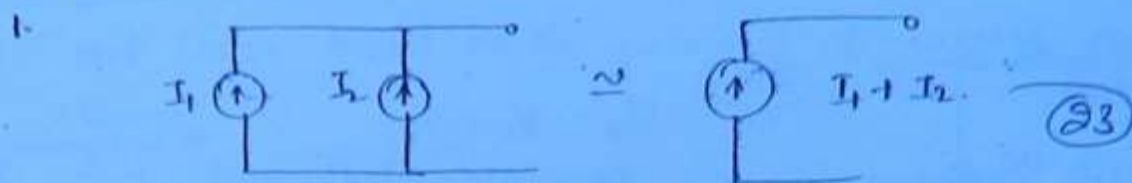

Ex 1

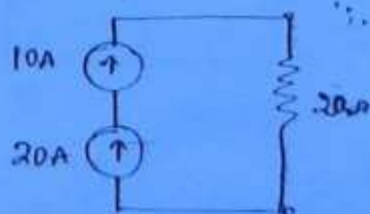


(A) 10A, (b) 20A, (c) 30A ~~(d) none~~  
not satisfying KCL.

Ex



not satisfying KCL.

B.

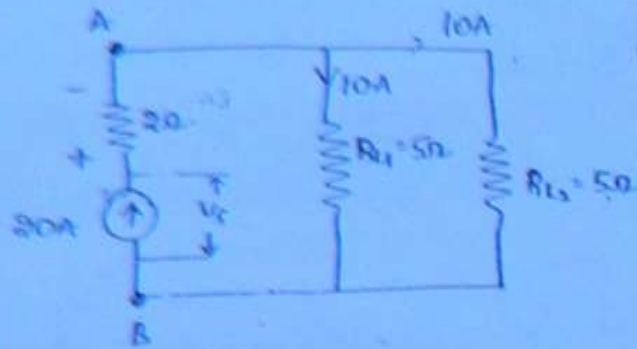

(24)


$$V_{AB} = V_s - 40$$

$$50 = V_s - 40$$

$$V_s = 90$$

$$P_s = 90 \times 20$$

neglecting 20Ω,

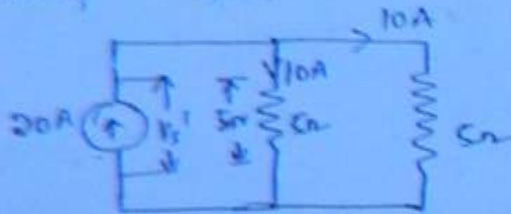


$$V_s' = 50V$$

$$50$$

$$P_s' = 50 \times 20$$

In the above circuit 20Ω resistance can be neglected while calculating either load current or load voltage.

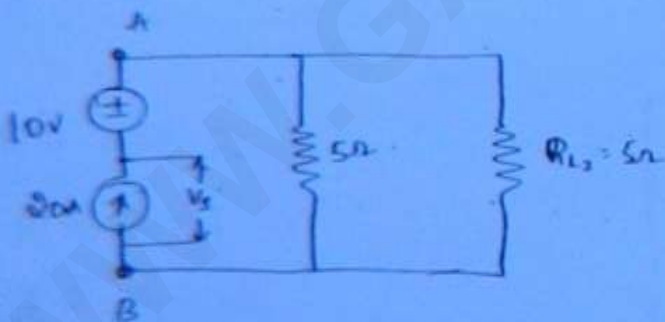In the above circuit 20Ω resistance cannot be neglected while calculating either source voltage or source power.




$$V_{AB} = V_s + 10$$

$$50 = V_s + 10$$

$$V_s = 40V$$

$$P_s = 40 \times 20$$

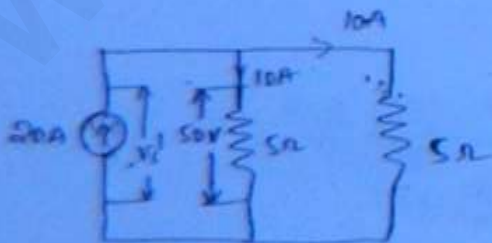

$$V_s' = 50V$$


$$P_s' = 50 \times 20$$

E: 1) In the above circuit voltage source can be neglected while calculating either load current or load voltage.

In the above circuit voltage source cannot be neglected


## KCL

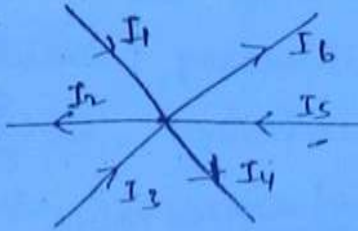1. KCL works based on the principle of law of conservation of charge. (25)
2. KCL states that algebraic sum of currents meeting at a point is equal to zero.
3. When two elements are connected together then the common point is called as simple node.
4. When more than 2 elements are connected together, then the common point is called as principle node.




$$I_1 - I_2 + I_2 - I_4 + I_5 - I_6 = 0$$

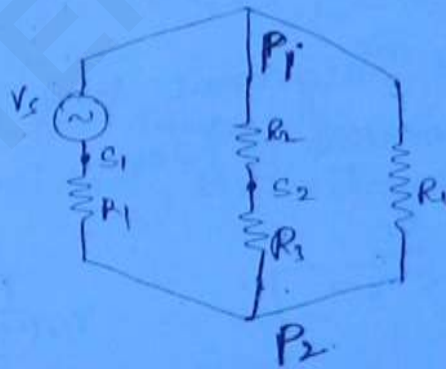Node  $\begin{cases} \text{simple} \\ \text{principle} \end{cases}$




## Current dividing rules

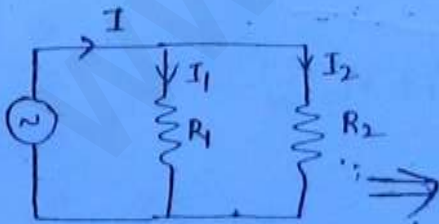

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

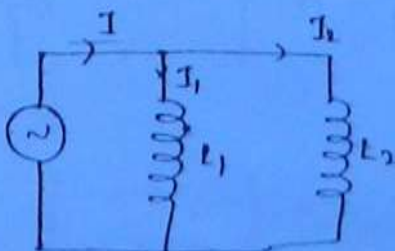
$$I_1 = \frac{I \cdot R_2}{R_1 + R_2} ; I_2 = \frac{I \cdot R_1}{R_1 + R_2}$$



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$
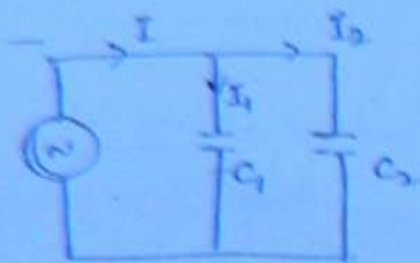
$$I_1 = \frac{I \cdot L_2}{L_1 + L_2} ; I_2 = \frac{I \cdot L_1}{L_1 + L_2}$$






$$C_{eq} = C_1 + C_2$$

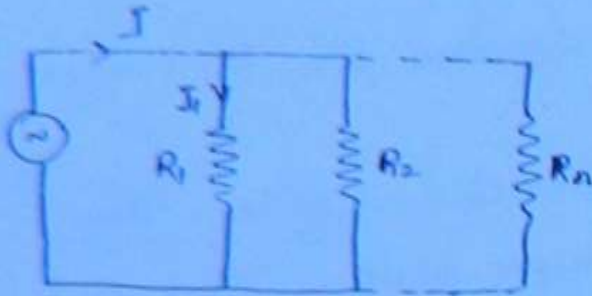(26)

$$I_1 = I \cdot \frac{C_1}{C_1 + C_2} ; I_2 = I \cdot \frac{C_2}{C_1 + C_2}$$




$$I_1 = I \cdot \frac{1/R_1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

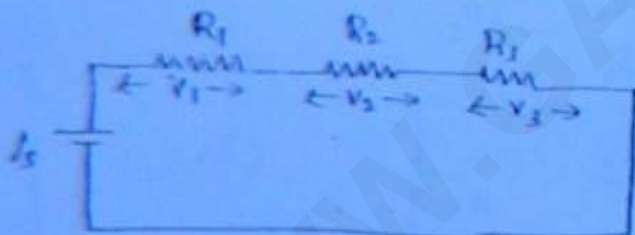
## KVL

KVL works based on the principle of law of Conservation of energy.

KVL states that the algebraic sum of the voltages in a closed loop is equal to zero.




$$V_1 + V_2 + V_3 - V_S = 0$$

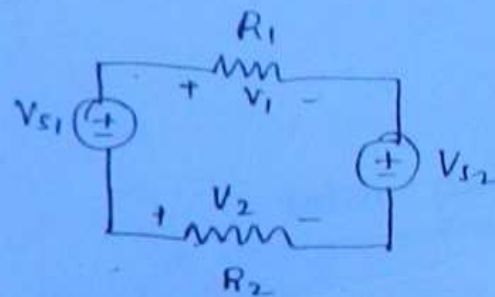

$$V_2 + V_{S1} = V_1 + V_{S2}$$

Find  $V_1$  &  $V_2$  of the ckt shown.

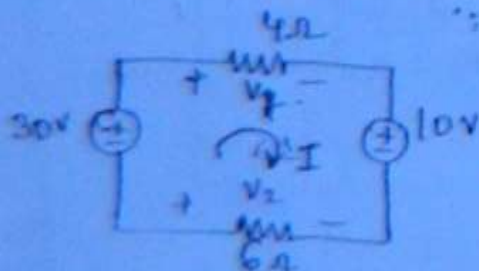

$$30 - V_1 - 10 + V_2 = 0$$

$$V_1 - V_2 = 20 \rightarrow (1)$$

$$V_1 = 4I, V_2 = -6I$$

$$4i + 6i = 20$$


## Conclusions.

1. Field theory can be applied either for low frequency or high frequency circuits. (accurate results are obtained).
2. Network theory can be applied only for low frequency circuits.
3. KVL & KCL fails for high frequency circuits.

(27)


## Lumped & Distributed parameters.

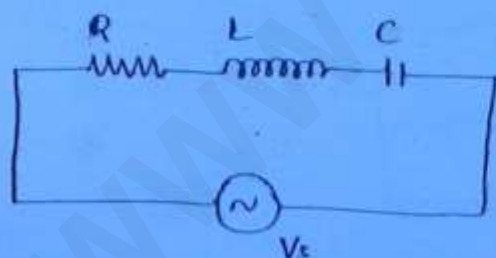1. KVL & KCL fails for distributed parameters. Since in distributed parameters electrically, it is not possible to separate resistance, inductance and capacitance effect.
2. Ohm's law can be applied for lumped (linear) and distributed parameters.
3. KVL & KCL equations used for lumped parameters circuit.  
(linear, non linear, unidirectional, bidirectional, time variant, and invariant elements).




$$V_s = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$



lumped (linear)

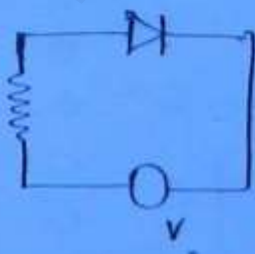

→ lumped (non linear).

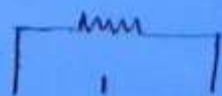

→ lumped

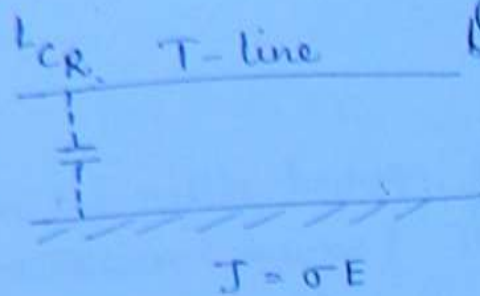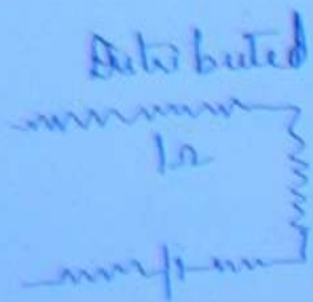


Distributed

(28)

$$J = \sigma E$$



Find equivalent inductance wrt A & B.

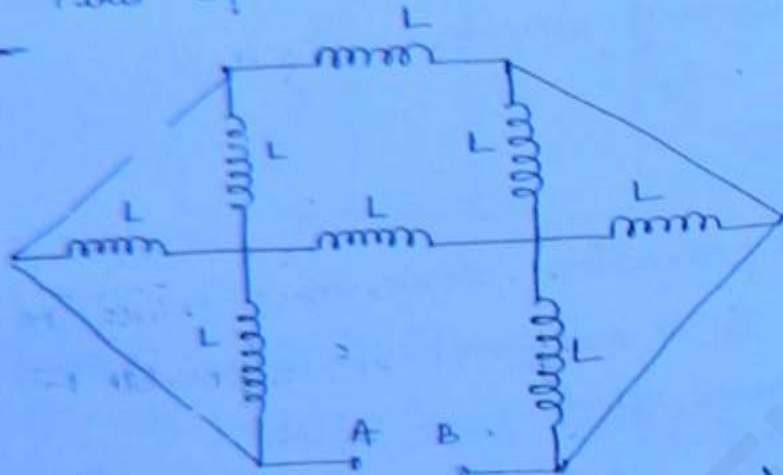

Handwritten calculations:

$$\frac{2L \cdot L}{3L} = \frac{2L}{3}$$


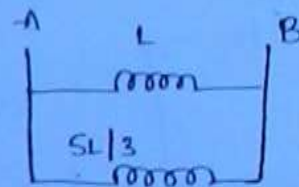
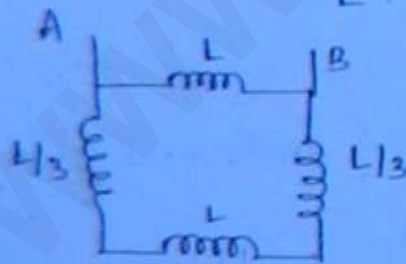
$$\frac{2L}{3} + \frac{2L}{3} = \frac{4L}{3}$$



$$L_{eq} = \frac{5L}{8}$$


$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

Find equivalent capacitance wrt A & B.

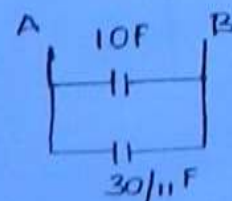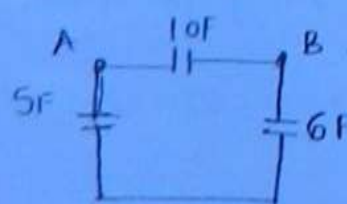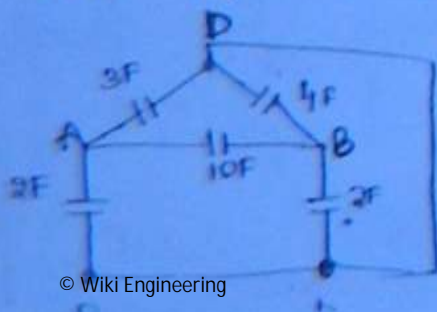




Q.

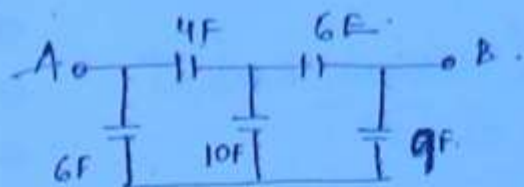



Find  $C_{eq}$  wrt A & B.

(29)

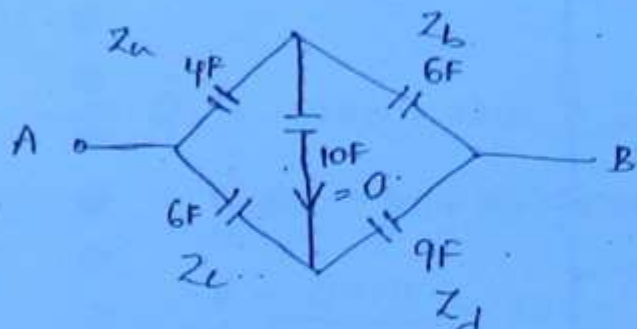

Balanced bridge  $\Rightarrow$


$$4 \times 9 = 6 \times 6$$

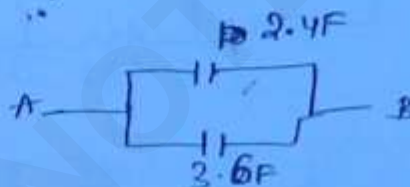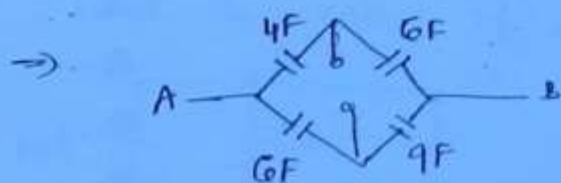

$$C_{eq} = 6.0F$$

Q.

Find eq. resistance wrt A & B.

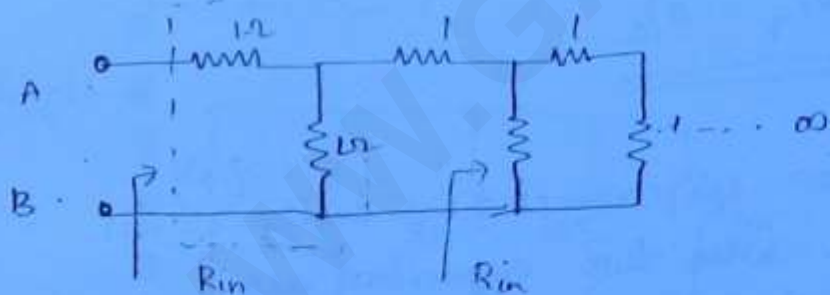

$$R_{eq} = 1 + \frac{R_{eq}}{1 + R_{eq}}$$

$$R_{eq} = \frac{1 + R_{eq} + 1}{1 + R_{eq}}$$

$$R_{eq} + 2 = 1 + R_{eq}$$


$$R^2 - R - 1 = 0$$

$$\frac{1 \pm \sqrt{1+4}}{2} = \frac{1 \pm \sqrt{5}}{2}$$

$$R_{in} = 1 + \frac{R_{in}}{1 + R_{in}}$$


$$R_{in}^2 - R_{in} - 1 = 0$$

$$R_{in} = \frac{1 + \sqrt{5}}{2}$$

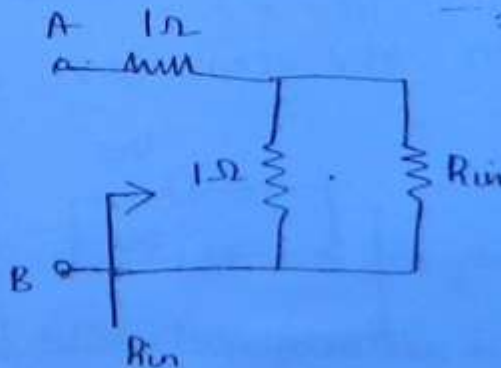

Find eq. resistance wrt. A & B. (assume each resistor is  $R\Omega$ )

(30)

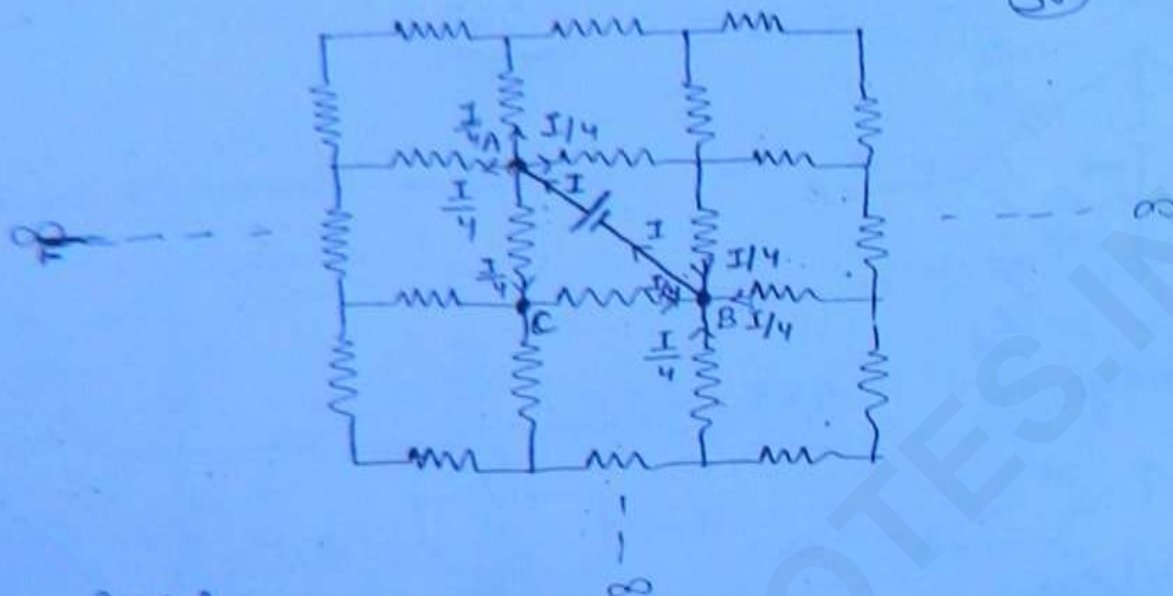



ACBA

$$V = R \cdot \frac{I}{4} + \frac{I}{4} \cdot R = \frac{R \cdot I}{2}$$

$$\Rightarrow \frac{V}{I} = \frac{R}{2} \Rightarrow \underline{\underline{R_{eq} = R/2}}$$

Two capacitors of  $40\mu F$  &  $20\mu F$  are connected in series to a source voltage of  $90V$ . When two capacitors are charged fully, they are connected in parallel. Find voltage across capacitors in parallel connection.

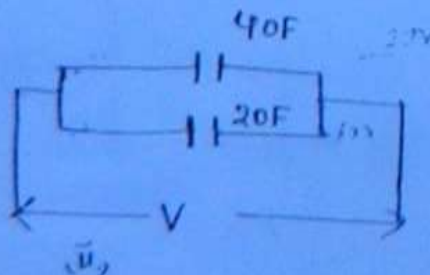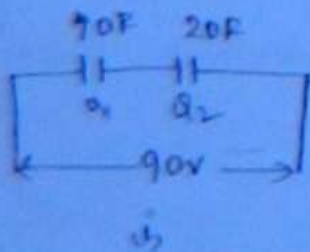- (a)  $40V$  (b)  $45V$  (c)  $30V$  (d)  $60V$



$$\frac{90}{1/40 + 1/20} = 60$$

$$V_1 = \frac{90 \times 20}{60} = 30V$$

$$V_2 = \frac{90 \times 40}{60} = 60V$$

i)  $C_{eq} = \frac{40 \times 20}{40 + 20} = \frac{40}{3}$

(31)

$Q = C_{eq} \cdot V \Rightarrow Q = \frac{40}{3} \times 90 = 1200 \text{ C}$


ii)  $\Rightarrow Q_T = 1200 + 1200 = 2400 \text{ C} \quad \star \star$

$C_{eq} = 20 + 40 = 60 \text{ F}$



$V = \frac{2400}{60} = 40 \text{ V}$

31

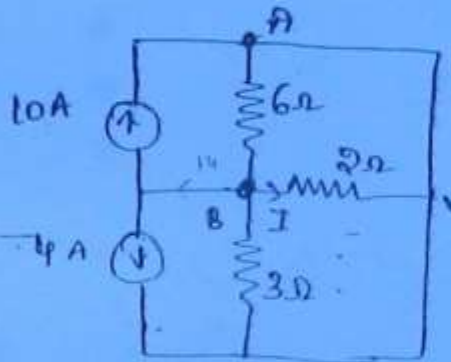Q.  $\star$  Find the value of  $I$  for the ckt shown.



Eq. ckt


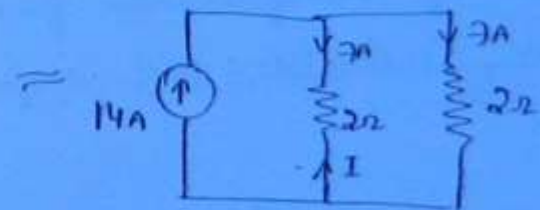
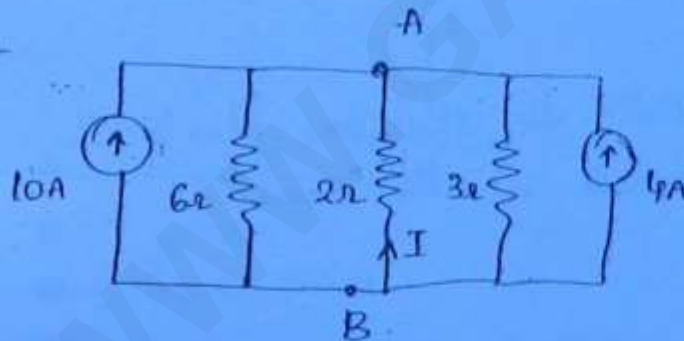


$I = -7 \text{ A}$

Note :-

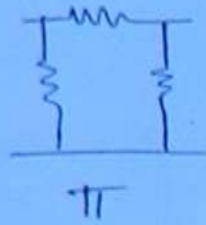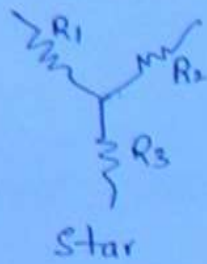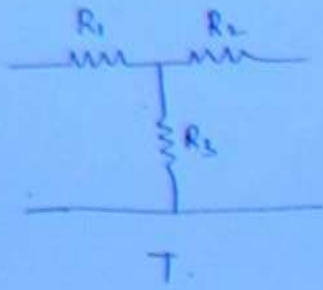
When elements are connected neither in series nor in parallel, to reduce the network, Star delta transformation is used.





delta to star
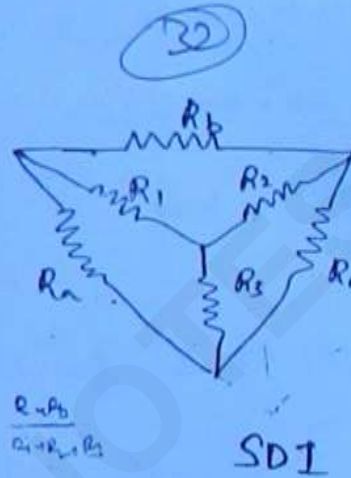
$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}, \quad R_2 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_3 = \frac{R_c R_a}{R_a + R_b + R_c}$$



Star to delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}, \quad R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, \quad R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


procedure of Transformation from delta to star (or) star to delta resistors, inductors and impedances is the same.

capacitors

delta to star

$$C_1 = \frac{1/C_a \cdot 1/C_b}{1/C_a + 1/C_b + 1/C_c}$$
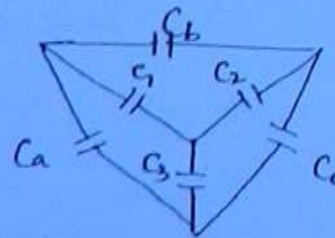
$$C_2 = \frac{1/C_b \cdot 1/C_c}{1/C_a + 1/C_b + 1/C_c}, \quad C_3 = \frac{1/C_a \cdot 1/C_c}{1/C_a + 1/C_b + 1/C_c}$$




## Star to delta

$$\frac{1}{C_a} = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2} \frac{1}{C_3} + \frac{1}{C_3} \frac{1}{C_1}}{\frac{1}{C_2}} \quad (33)$$


$$\frac{1}{C_b} = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2} \frac{1}{C_3} + \frac{1}{C_3} \frac{1}{C_1}}{\frac{1}{C_3}} \quad \frac{1}{C_c} = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2} \frac{1}{C_3} + \frac{1}{C_3} \frac{1}{C_1}}{\frac{1}{C_1}}$$

Q. Find eq. resistance wrt A & B.

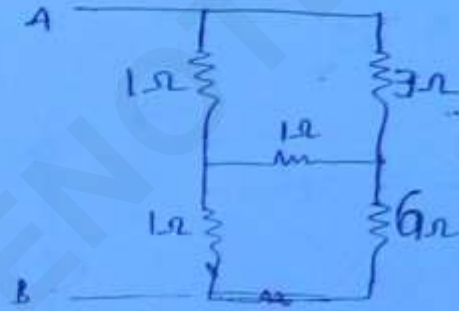

Convert  $1\Omega, 1\Omega, 1\Omega \rightarrow \Delta$

Sol

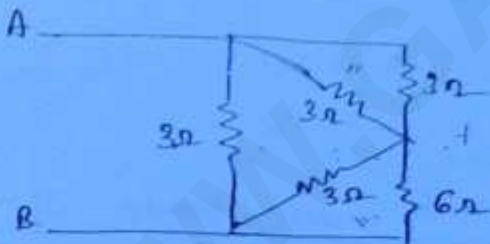

$$R_a = \frac{(1 \times 1) + (1 \times 1) + (1 \times 1)}{1}$$

$$R_a = 3\Omega$$

$$\parallel R_b = R_c = 3\Omega$$


$$\frac{1.5}{1.5 \times 3} = 0.5$$

$$R_{ab} = 1.6\Omega$$

Note

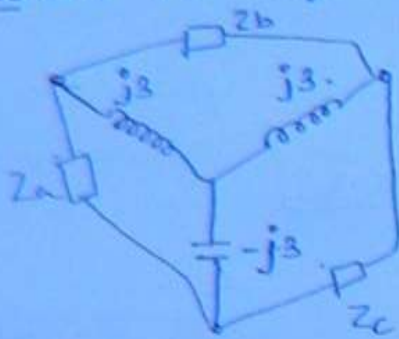1. when resistors of equal value are transformed from  $\gamma \rightarrow \Delta$ , resistance is increased by 3-times SDI
2. when capacitors of equal value are transformed from  $\gamma \rightarrow \Delta$ , capacitance decreases by 3-times DSI

Draw the eq.  $\Delta$  network for the network shown.




(34)


$$Z_a = \frac{(j3)(j3) + (j3)(-j3) + (j3)(-j3)}{(j3)} = -j3$$

$$Z_b = \frac{(j3)(-j3)}{-j3} = j3$$

$$Z_c = \frac{(j3)(-j3)}{j3} = -j3$$

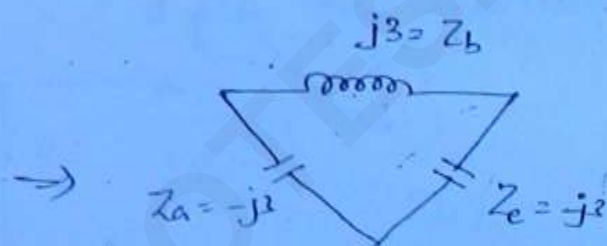


### Source Transformation

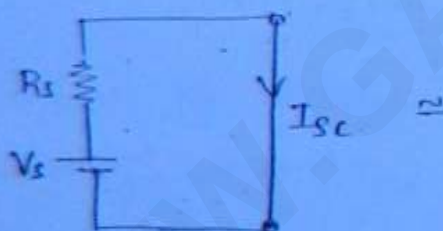

$$I_s = I_{sc} = \frac{V_s}{R_s}$$


$$R_s = R_s$$

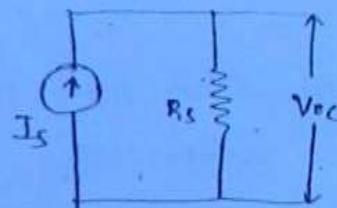



$$V_s = V_{oc} = I_s R_s$$

$$R_s = R_s$$

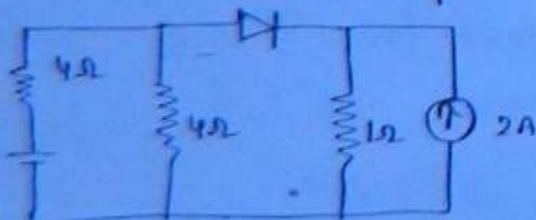
Find current of ideal diode of the ckt shown.





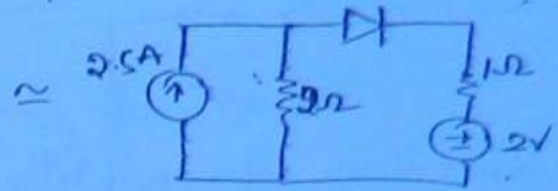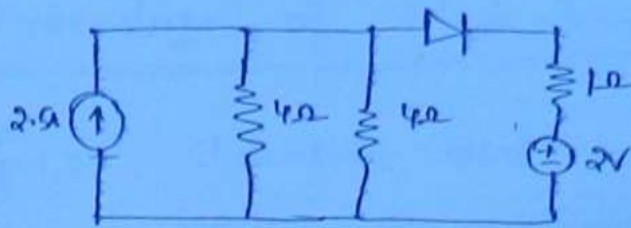


32

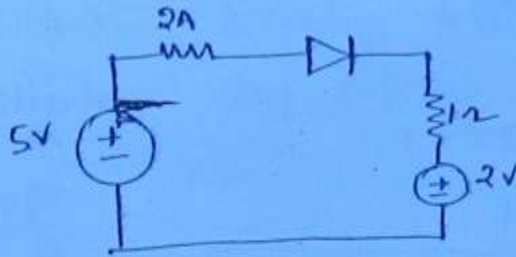


$$\Rightarrow i = \frac{5-2}{2+1} = 1A$$


### Dependant Sources

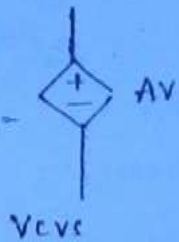


A → no unit

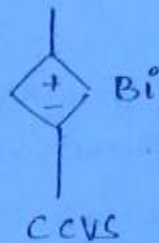

B → Ω  
 $V = iR$

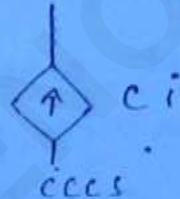


C → no unit

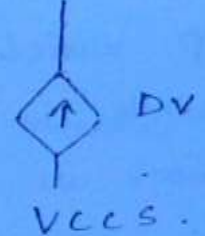

D → mho (or) S  
 $i = V/R = GV$


→ All the above are linear dependant sources.

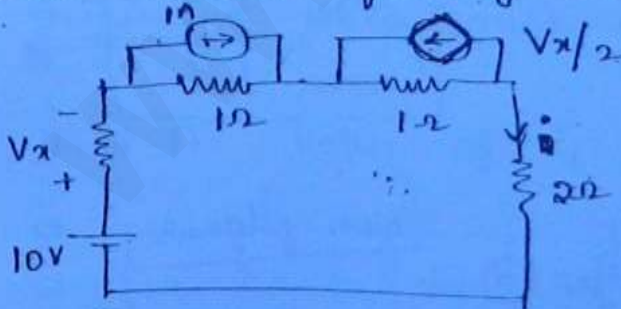Q. Find current flowing through 2Ω resistor



Note : ★★

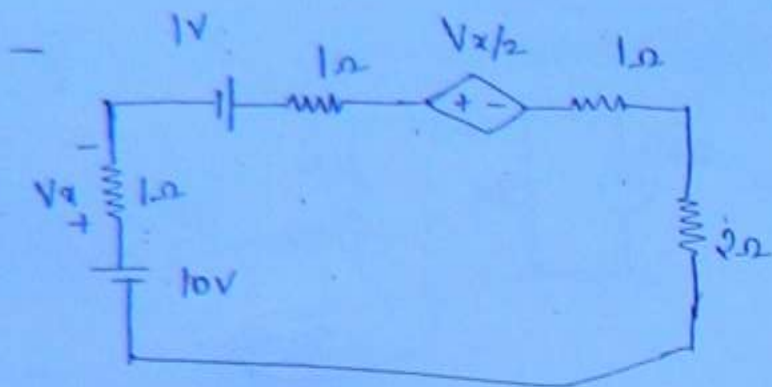while applying source transformation for dependant source, whenever dependant source magnitude depends without disturbing its dependent transformation.



(36)

$$I = \frac{10 + 1 - V_x/2}{1 + 1 + 1 + 2}$$

$$I = 9A$$

$$V_x = (I)$$


$$V_x = I$$

↖


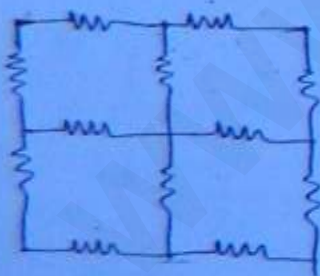
## Mesh Analysis

Mesh is a loop which doesnot consist of any inner loop. When the network is drawn on plane without any crossover, then the network is called as planar network.


Mesh analysis can be applied only for planar networks.



planar network

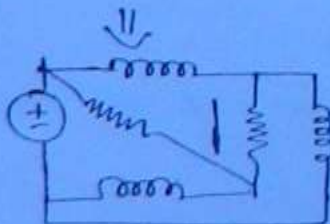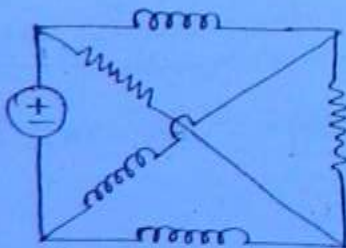

non planar

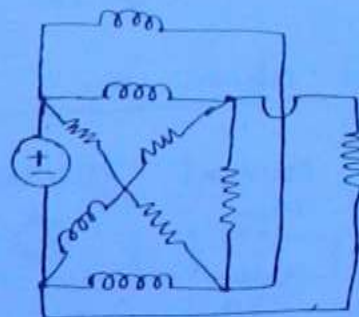


non planar



# Procedure of Mesh Analysis

- Step 1: Identify total number of meshes.  
Step 2: Assign the current direction for each mesh.  
Step 3: Develop KVL equation for each mesh. (37)  
Step 4: By solving ~~KVL~~ equations, find loop currents.

Ex.

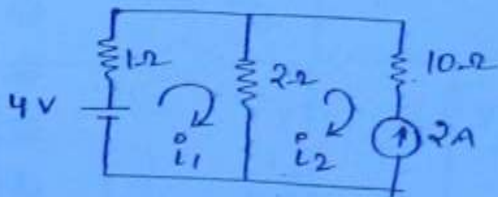

$$-4 + 3i_1 - 2i_2 = 0$$

$$i_2 = -2$$

$$i_1 = 0$$

Note.

Total no. of eqns = Total no. of meshes.

$$e = m = 2$$


b = Total number of branches

N = Total no. of nodes.

$$e = b - (N - 1) \quad **$$

\* In the above circuit, to find the loop current, minimum one equation is required.

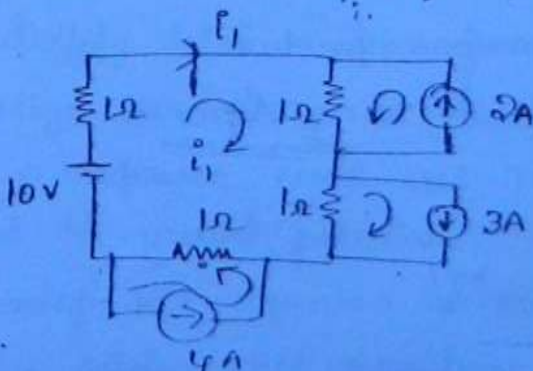Q. Find the value of  $i_1$  of this circuit shown.



$$-10 + i_1 + i_2 + 2 + i_1 + 3 + i_1 + 4 = 0$$

$$10 + 4i_1 + 3 \cdot 0$$

$$i_1 = 7/4$$




$$0 = -10 + 4\bar{I}_1 + (1 \times 2) - (1 \times 3) + 4 \times 1$$

$$\bar{I}_1 = 7/4 \text{ A}$$

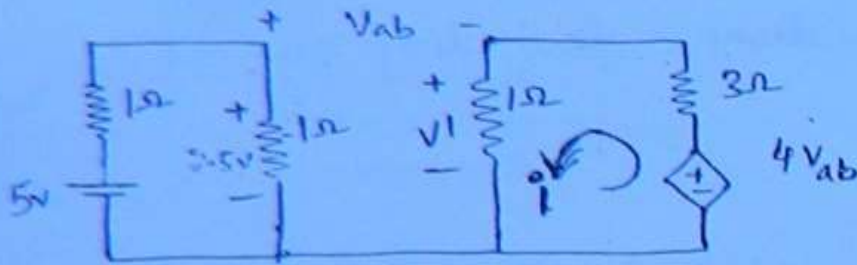(38)

Find the value of  $i$  of the circuit shown.



$$\bar{I} = \frac{4V_{ab}}{3+1} = V_{ab}$$


$$V' = (1 \times I) \Rightarrow V' = I = V_{ab}$$

$$-2.5 + V_{ab} + V' = 0$$

$$-2.5 + V_{ab} + V_{ab} = 0 \Rightarrow V_{ab} = 1.25 \text{ V}$$

$$\bar{I} = 1.25 \text{ A}$$

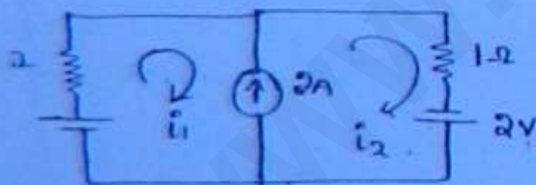Find  $i_1$  &  $i_2$  of the circuit shown?



When current source branch is common for two meshes, it is possible to find solution by using super node technique.

$$-5 + (1 \times I_1) + (1 \times I_2) - 2 = 0 \rightarrow \text{KVL}$$


$$I_2 - I_1 = 2 \rightarrow \text{KCL}$$

mesh  $\rightarrow$  KVL + ohm's law

\* \* Super mesh  $\rightarrow$  KVL + KCL + ohm's law.

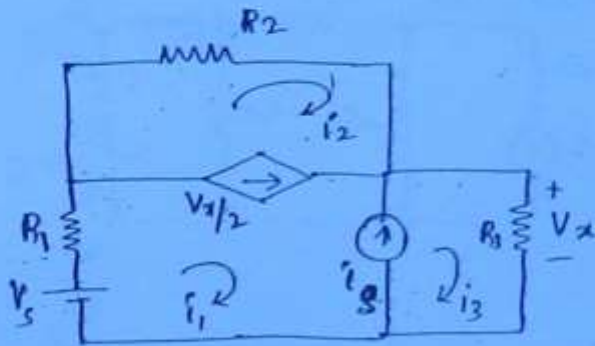(39)

Q. Develop mesh equations of the circuit shown.



$$-V_s + i_1 R_1 + i_2 R_2 + i_3 R_3 = 0 \rightarrow \text{KVL}$$

$$i_1 - i_2 = \frac{V_x}{2} \rightarrow \text{KCL}$$

$$i_3 - i_1 = i_s \rightarrow \text{KCL}$$


### Nodal Analysis

$\rightarrow$  Nodal analysis can be applied for planar and non-planar networks.

### Procedure of nodal analysis.

1. Identify total number of nodes.
2. Assign the voltage at each node, one of the nodes is taken as a reference node and reference node potential should be equal to ground potential.
3. develop KCL equation at each non reference node.
4. By solving KCL equations find node voltages.


mesh only  
if planar

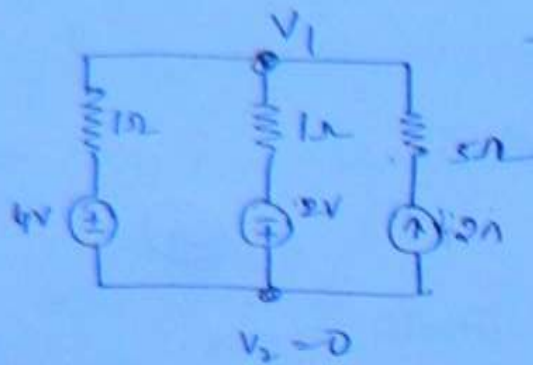

$$\frac{V_1 - 4}{1} + \frac{V_1 + 2}{1} = 2 \Rightarrow V_1 = 2V.$$


Total no. of eqns  $\boxed{C = N - 1}$

$N =$  no. of nodes.

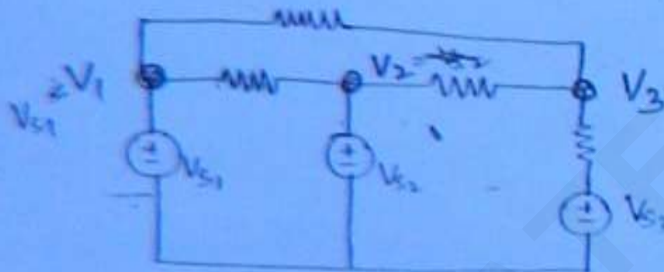

To find node voltages in the above circuit, minimum one equation is required.

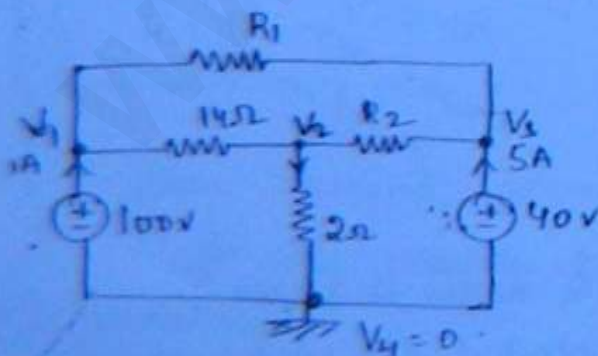Find  $R_1$  &  $R_2$  of this circuit shown.



node 4  $\rightarrow I = 5 + 10 = 15A$

$$V_2 = 15 \times 2 = 30V$$

$$V_1 = 100V$$

$$V_3 = 40V$$

node 1  $\rightarrow 10 = \frac{V_1 - V_2}{14} + \frac{V_1 - V_3}{R_1}$

$$R_1 = 12\Omega$$




node 3  $\rightarrow$

$$5 = \frac{V_3 - V_2}{R_2} + \frac{V_3 - V_1}{R_1}$$

$$R_2 = 1\Omega$$

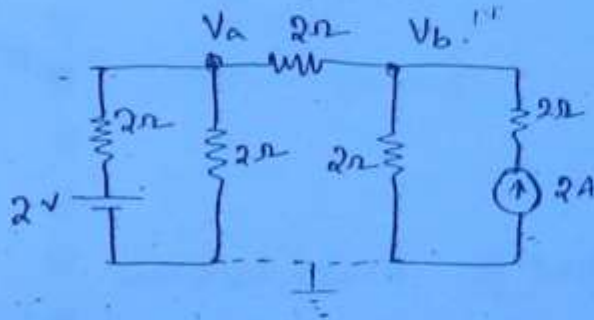(6)

Q. Find  $V_a$  &  $V_b$  of the circuit shown. [DRDO]



$$\frac{V_a - 2}{2} + \frac{V_a}{2} + \frac{V_a - V_b}{2} = 0$$

$$-\frac{V_b}{2} + \frac{V_b - V_a}{2} = 2$$

$$V_a = 8/5 \text{ V}$$

$$V_b = 14/5 \text{ V}$$


$$\frac{V_a - 2}{2} + \frac{V_a}{2} + \frac{V_a - V_b}{2} = 0$$

$$V_a + V_a - V_b - 1 = 0$$

$$2V_a - V_b = 1$$

$$3V_a - 4 - \frac{V_b}{2} - 2 + \frac{V_b - V_a}{2} = 0$$
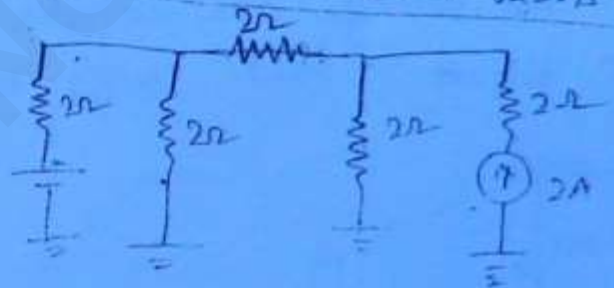
$$6V_a - 4 - V_b = 4 \Rightarrow 5V_a = 8 \Rightarrow V_a = 8/5$$




$$V_b - \frac{V_a}{2} = ?$$


$$2V_b - V_a = 4$$

$$V_b = \frac{4 + V_a}{2}$$

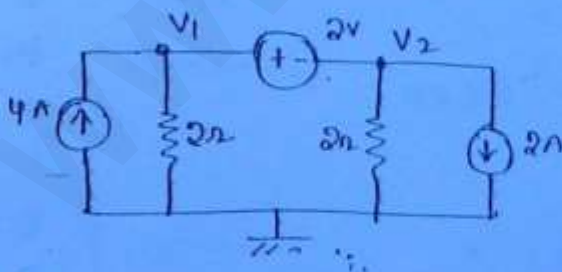Q. Find  $V_1$  &  $V_2$  of the circuit shown.



$$-4 + \frac{V_1}{2} = 2$$

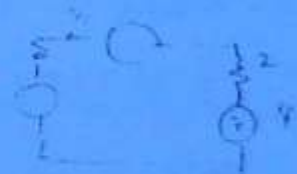

Note :-

when ideal voltage source is connected b/n two non reference nodes, it is possible to find solution by using super node technique.

$$4 = \frac{V_1}{2} + \frac{V_2}{2} + 2 \rightarrow \text{KCL}$$

$$V_1 - V_2 = 2 \rightarrow \text{KVL}$$

$$V_1 = 3V, \quad V_2 = 1V$$

$$V_1 + V_2 = 4$$

$$V_1 - V_2 = 2$$

$$2V_1 = 6$$


(42)

nodal  $\rightarrow$  KCL + Ohm's law

Super node  $\rightarrow$  KVL + KCL + Ohm's law.

A fully charged mobile phone is good for 10 min talk time. During talk time, battery delivers a constant current.

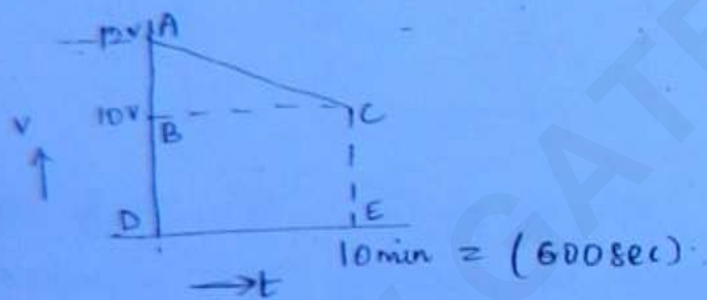2A. The voltage characteristic of battery is as shown in the figure. Find energy of the battery during talk time.




$$Vt = \Delta ABC + \square BCED$$

$$= \frac{1}{2} \times 2 \times 600 + 600 \times 10 = 6600$$

$$W = Vt$$

$$\text{eg. } = 6600 \times 2A = 13.2 \text{ kJ} = W$$

which bulb gives more brightness.

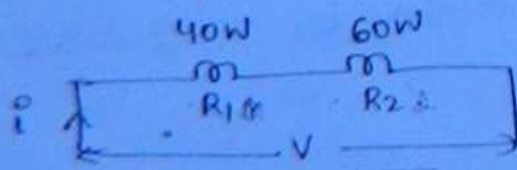

$$P \propto \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R}$$

$$P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R}$$


$$P_1 = i^2 R_1 ; P_2 = i^2 R_2$$

$$P_1 > P_2$$

B1.

(V3)

ii,

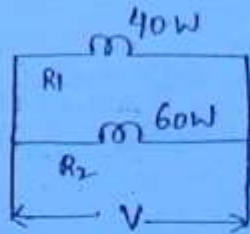

$$R_1 > R_2$$

$$P_1 = \frac{V^2}{R_1}$$

$$P_2 = \frac{V^2}{R_2}$$

$$P_1 < P_2$$

B2

Steady state ★ ★ ★



1) Bi-directional

2) Linear

3) Passive



1. Non linear

2. Uni-directional

3. Passive

Bi direc —

shud be identical  
in 1st & 3rd  
quad. else  
uni-direc.

passive —  $\frac{V}{I}$  shud be


→ +ve in 1st & 3rd quad  
else active



1. non linear

2. Bi-direc


3. Passive

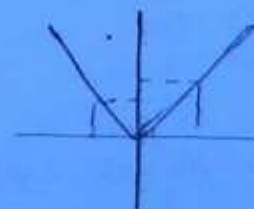

1. Uni-direc.

2. non-lin

3. active

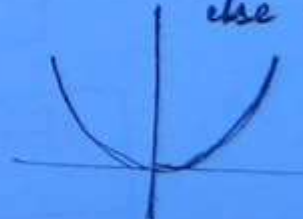

1. uni direc.

2. non lin.

3. active



# Steady state A.C. Circuits.


## Advantages of sine wave.

(L4)

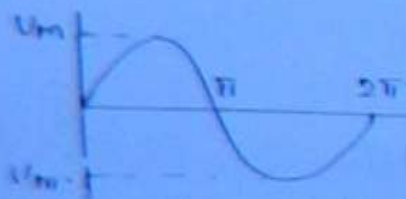1. It is easy to handle mathematically. (differential and integral of the sine func. can be re-written in terms of sine function)
2. The natural phenomena like the motion of the simple pendulum & response of undamped system, shows sinusoidal character.

Any periodic waveform can be expressed in terms of sine function by using fourier analysis. &

It is easy to generate in the laboratory.



$$V(t) = V_m \sin \omega t$$


$V_m$  = peak (or) max. value

$\omega$  = Angular frequency  $\rightarrow$  rad/sec.


$\omega t$  = argument  $\rightarrow$  rad.

$$\omega T = 2\pi \Rightarrow \boxed{T = \frac{2\pi}{\omega}} \text{ sec.}$$

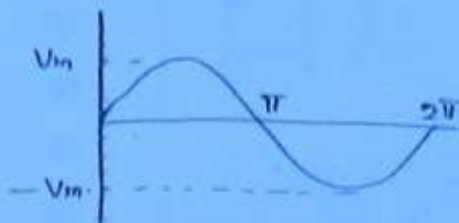
$$f = \frac{1}{T} \Rightarrow \boxed{f = \frac{\omega}{2\pi}} \text{ Hz (or) cycles/sec.}$$



$$(1) \quad V(t) = V_m \sin(\omega t)$$

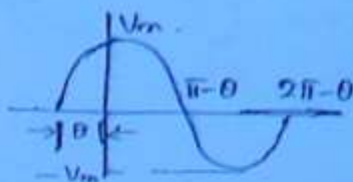

$$V(t) = V_m \sin(\omega t + \theta)$$

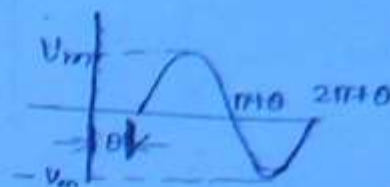

$$V(t) = V_m \sin(\omega t - \theta)$$

→ wrt 1st waveform, 2nd waveform is leading by an angle  $\theta$ .

→ wrt 1st waveform, 3rd waveform is lagging by an angle  $\theta$ .


→ wrt second waveform, 3rd waveform is lagging by an angle  $2\theta$ .

23/6/11
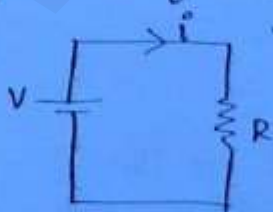
### RMS Value

→ RMS value is defined based on heating effect of the waveform.


→ The voltage at which heat dissipation in AC circuit is equal to heat dissipation in DC circuit is called as  $V_{rms}$ , provided both ac & dc circuit have equal value of resistance and operated for same time



$$P = i^2 R$$

$$W = i^2 R t$$

heat ← D.C

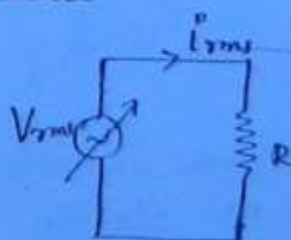

$$P = i_{rms}^2 R$$

$$W = i_{rms}^2 R t$$

$$W_{A.C} = W_{D.C}$$


## General Expressions

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2 d\omega t}$$


$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

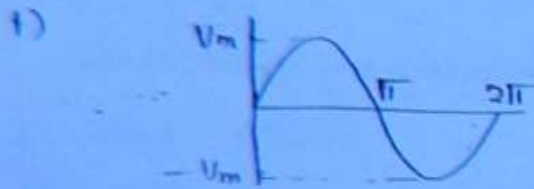(46)

Find RMS value of the following waveforms.



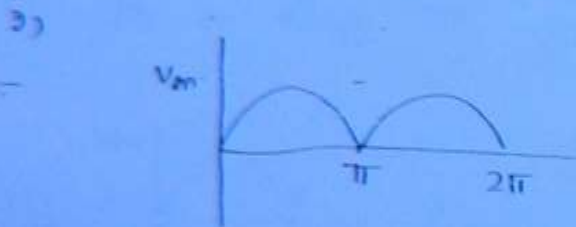
$$\begin{aligned} V_{RMS} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (1 - \cos 2\omega t) d\omega t} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t} = \boxed{\frac{V_m}{\sqrt{2}} = V_{RMS}} \end{aligned}$$



Full wave =  $\frac{V_m}{\sqrt{2}}$




1/2 wave =  $\frac{V_m}{2}$

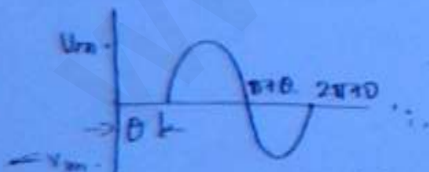

$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

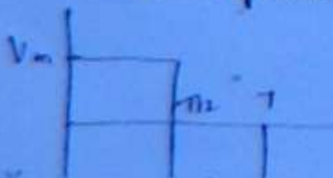
Note: RMS value is independent on the position of starting of waveform. But it depends on shape of the waveform.



$$V_{RMS} = V_m$$



(6)

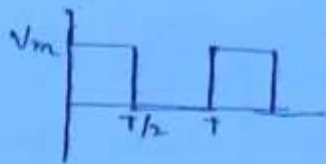

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\frac{V_m}{\sqrt{2}}$$


(7)



$$= V_m / \sqrt{3}$$


(47)

(8)

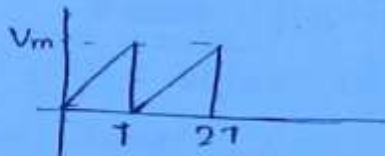

$$= V_m / \sqrt{3}$$


(9)

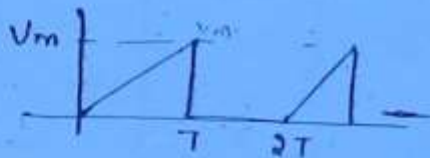

$$V_{rms} = \frac{V_m}{\sqrt{6}}$$

$$\frac{V_m}{T} \int_0^T \frac{t^2}{3} dt = \frac{V_m}{T} \times \frac{T^3}{6} = \frac{V_m^2}{6}$$

(10)

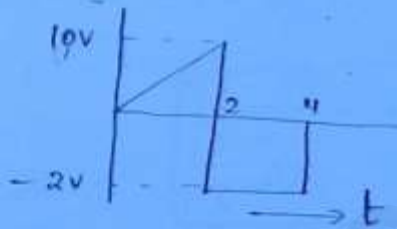

$$0 \leq t \leq 2$$

$$y = mx$$


$$m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{10 - 0}{2 - 0} = 5$$

$$V = 5t$$

$$V_{rms} = \sqrt{\frac{1}{4} \left[ \int_0^2 V^2 dt + \int_2^4 V^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} \left[ \int_0^2 (5t)^2 dt + \int_2^4 (-2)^2 dt \right]}$$

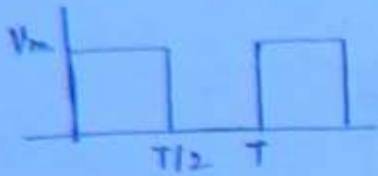★ Find power dissipation in the resistor for a given waveform.



(a)  $P_{av} = P_{peak} / 2$  (48)

(b)  $P_{av} = P_P / \sqrt{2}$

(c)  $P_{av} = P_P / \sqrt{3}$

(d)  $P_{av} = P_{peak}$

$$P_{av} = \frac{V_{rms}^2}{R}$$

$$P_{av} = \frac{(V_m / \sqrt{2})^2}{R} = \frac{V_m^2}{2R}$$

$$P_{av} = \frac{V_m^2}{2R}$$

$$P_{peak} = \frac{V_m^2}{R}$$

$$P_{av} = \frac{P_{peak}}{2}$$

$$\frac{P_{D.C.}}{P_{A.C.}} = \frac{I_{av}^2 R}{I_{RMS}^2 R}$$

$$\text{Form factor} = \frac{V_{RMS}}{V_{avg}}$$

Find RMS value of the following function

$$V(t) = 3 + \sin t + \sin 3t + \cos t$$

$$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2 + \dots + V_{rmsn}^2}$$

$$= \sqrt{3^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2}$$

$$V_{rms} = \sqrt{9\frac{1}{2}}$$


∴ RMS value is independent on frequency of the waveform.

## Average Value

→ Average value is defined based on charge transfer in the circuit.

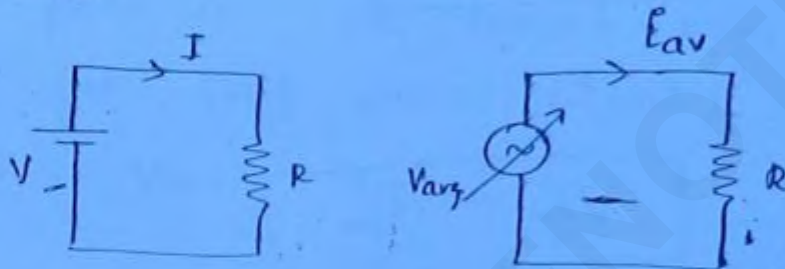(44)

→ The voltage at which the charge transfer in A.C. circuit is equal to charge transfer in D.C. circuit is called, as  $V_{avg}$ , provided both A.C. & D.C. circuits consist of equal value of resistance and operated for same time.



$$I = V/R$$

$$I = Q/t$$

$$Q = It$$

D.C.

$$I = V/R$$

$$I = Q/t$$

$$Q = It$$


A.C.

$$Q_{A.C.} = Q_{D.C.}$$

→ Avg. value of complete cycle of symmetrical wave = 0.


→ For analysis while finding avg. value of symmetrical wave only the  $1/2$  cycle is considered.

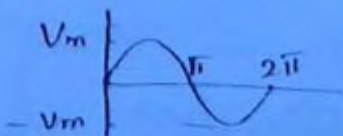→ while finding avg. value of unsymmetrical wave angle made by complete cycle is considered.



Symmetrical wave
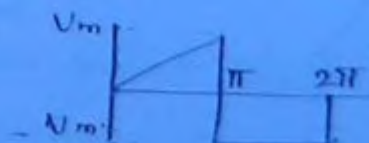
$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V \, d\omega t$$




Unsymmetrical wave

$$V_{av} = \frac{1}{2\pi} \left( \int_0^{\pi} V \, d\omega t + \int_{\pi}^{2\pi} V \, d\omega t \right)$$



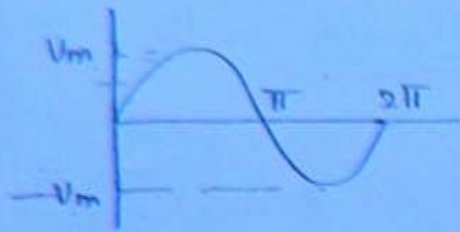Find avg value of the following waveforms:



$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V \, d\omega t \quad (50)$$


$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t$$

$$V_{av} = \frac{2V_m}{\pi}$$


Handwritten notes on the right margin:  
 $\frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t$   
 $= \frac{V_m}{\pi} [-\cos \omega t]_0^{\pi}$   
 $= \frac{V_m}{\pi} [-(-1) - (-1)]$   
 $= \frac{V_m}{\pi} [1 + 1]$   
 $= \frac{2V_m}{\pi}$




$$V_{av} = \frac{2V_m}{\pi}$$

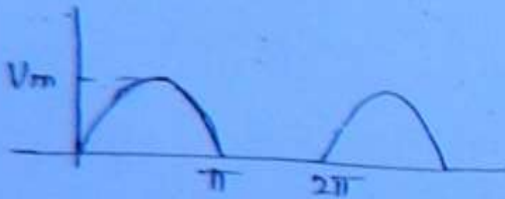

$$V_{av} = \frac{V_m}{\pi}$$

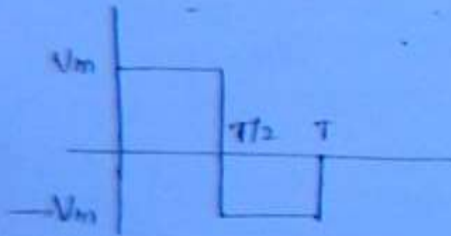


$$V_{av} = V_{rms} = V_m$$

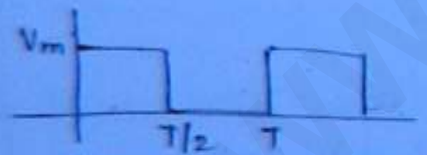


$$V_{av} = V_m/2$$


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

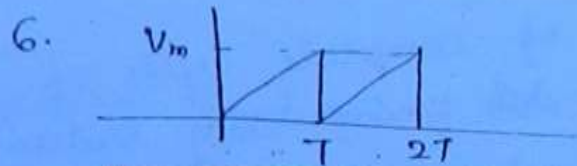

$$V_{av} = V_m/2$$

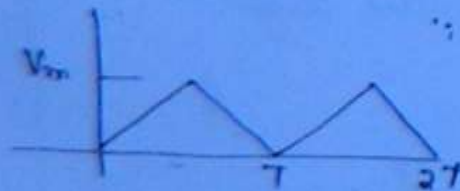


$$V_{av} = V_m/2$$

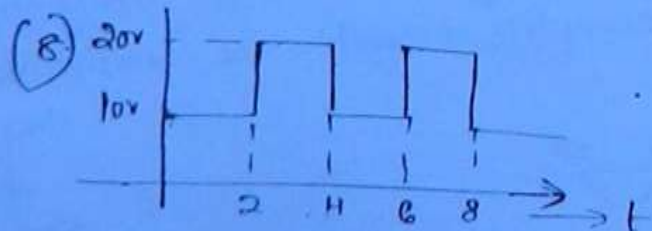

$$V_{avg} = \frac{1}{4} \left[ \int_0^4 10 \, dt + \int_4^8 20 \, dt \right]$$

$$V_{avg} = 15$$

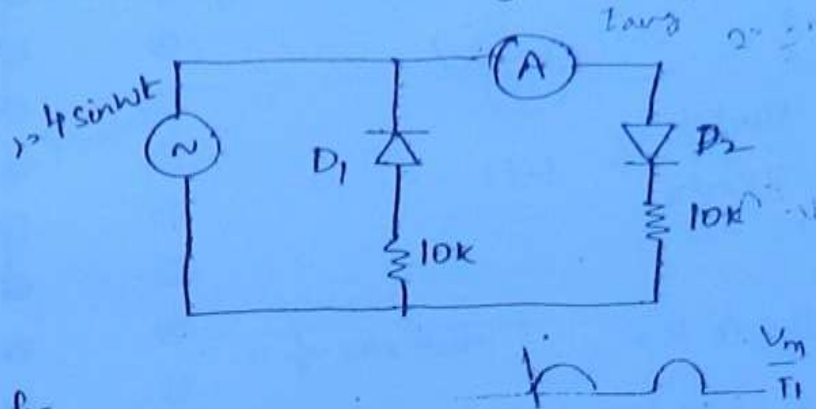When circuit is having ideal diodes and average value of indicating ammeter. Find the value of ammeter.



- (a)  $\frac{0.4}{\pi} \text{ mA}$  (57)  
 (b)  $\frac{0.8}{\pi} \text{ mA}$   
 (c)  $\frac{0.2}{\pi} \text{ mA}$   
 (d)  $\frac{1.6}{\pi} \text{ mA}$

Current flows in  $D_2$  branch only for +ve  $\frac{1}{2}$  cycle.

$\therefore$  we get half wave output.

$$O/P = V_{av} = \frac{V_m}{\pi} = \frac{4}{\pi}$$

$$I_{av} = \frac{V_{av}}{R} = \frac{4/\pi}{10k} = \frac{0.4}{\pi} \text{ mA}$$

### FORM FACTOR

Form factor is the ratio of RMS value of the waveform to average value of the waveform.

$$\text{form factor} = \frac{V_{RMS}}{V_{avg}}$$

### PEAK FACTOR

Peak factor is the ratio of max. value of the waveform to RMS value of the waveform.

$$\text{Peak factor} = \frac{V_m}{V_{RMS}}$$



To justify abt shape of the waveform, form factor and peak factor are introduced.

(52)

For sine wave, form factor =  $\frac{V_m/\sqrt{2}}{2V_m/\pi} = 1.11$





Power System,

11 kV, 33 kV, 66 kV, 132 kV, 220 kV. } multiples of 11.

These power systems are chosen based on the form factor = 1.11.

∴ which of the following waveforms have form factor equal to peak factor.

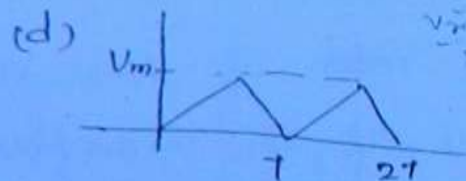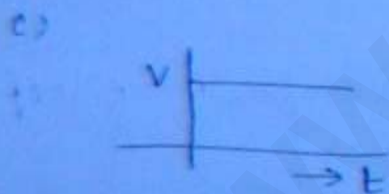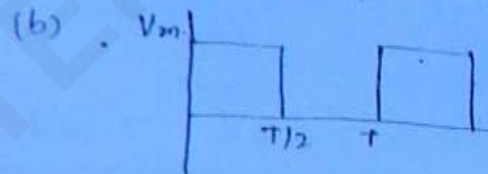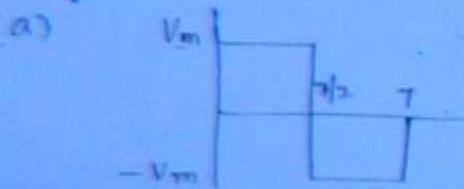$\frac{V_m}{V_{avg}} = \frac{V_m}{V_{rms}}$



✓  $V_{rms} = V_{avg} = V_m$

form factor = 1

peak factor = 1

✓ (c)  $V_{rms} = V_{avg} = V$

form factor = peak factor = 1

✓  $V_{rms} = \frac{V_m}{\sqrt{2}}, V_{avg} = \frac{V_m}{2}$

form factor =  $\frac{V_{rms}}{V_{avg}} = \sqrt{2}$

peak factor =  $\frac{V_m}{V_{rms}} = \sqrt{2}$

✗ (d)  $V_{rms} = V_m/\sqrt{3}$


$V_{avg} = V_m/2$

form factor =  $2/\sqrt{3}$

peak factor =  $\frac{V_m}{V_{rms}} = \sqrt{3}$



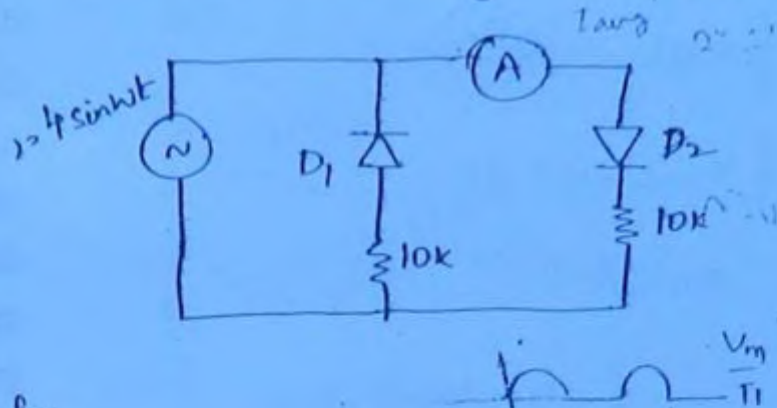When circuit is having ideal diodes and average value of indicating ammeter. Find the value of ammeter.



- (a)  $\frac{0.4}{\pi} \text{ mA}$  (S3)  
 (b)  $\frac{0.8}{\pi} \text{ mA}$   
 (c)  $\frac{0.2}{\pi} \text{ mA}$   
 (d)  $\frac{1.6}{\pi} \text{ mA}$

current flows in  $D_2$  branch only for +ve  $\frac{1}{2}$  cycle.  
 $\therefore$  we get half wave output.

$$o/p = V_{av} = \frac{V_m}{\pi} = \frac{4}{\pi}$$

$$I_{av} = \frac{V_{av}}{R} = \frac{4/\pi}{10k} = \frac{0.4}{\pi} \text{ mA}$$

### FORM FACTOR

Form factor is the ratio of RMS value of the waveform to average value of the waveform.


$$\text{form factor} = \frac{V_{RMS}}{V_{avg}}$$

### PEAK FACTOR

Peak factor is the ratio of max. value of the waveform to RMS value of the waveform.

$$\text{Peak factor} = \frac{V_m}{V_{RMS}}$$

## AC source across inductor -

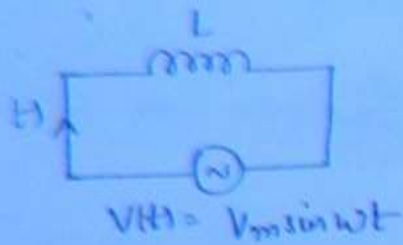

$$i_L = \frac{1}{L} \int v dt \quad (54)$$

$$i_L = \frac{1}{L} \int V_m \sin \omega t dt$$

$$i_L = -\frac{V_m}{\omega L} \cos \omega t$$

$$i_L = \frac{V_m}{\omega L} \sin(\omega t - 90^\circ)$$

$$(X_L = \omega L)$$

$$i_L = I_m \sin(\omega t - 90^\circ)$$


$$\therefore X_L = \omega L; I = \frac{V}{X_L}$$

$$p = v(t) i(t)$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t - 90^\circ)$$

$$p = \frac{1}{8\pi} \int_0^{2\pi} p(t) d\omega t$$

$$P_{avg} = 0$$

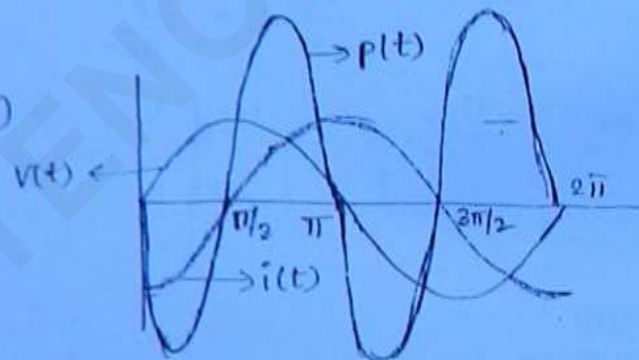

$p(t)$  freq = double  $v(t)$


∴

During the  $\frac{1}{2}$  cycle of the power, inductor takes energy from the source & in  $-ve$   $\frac{1}{2}$  cycle of the power, inductor delivers energy to the source.


hence, net power taken from the source = 0.

$$f = 50\text{Hz} \quad \{ \quad f_p = 100\text{Hz}$$

vector diagram :

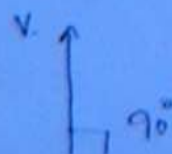


(or)

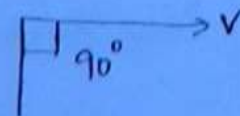



## -AC source across resistance-

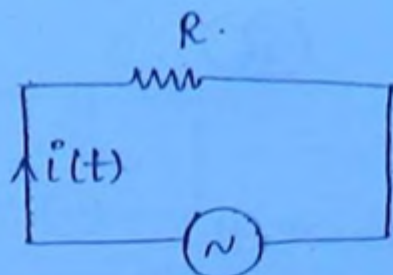

$$v(t) = V_m \sin \omega t$$

(5)

$$i(t) = v(t)/R$$

$$i(t) = \frac{V_m \sin \omega t}{R}$$


$$i(t) = I_m \sin \omega t$$

$$P(t) = v(t) i(t)$$

$$= (V_m \sin \omega t) (I_m \sin \omega t)$$

$$P(t) = \frac{V_m I_m}{2} [1 - \cos 2\omega t]$$
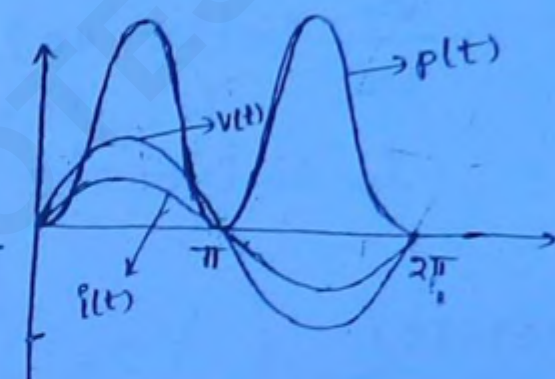
$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P(t) d\omega t$$




$$P_{avg} = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms}$$

$$f = 50\text{Hz} \Rightarrow f_p \text{ (power frequency)} = 100\text{Hz}$$

\therefore When voltage completes one cycle from 0-2\pi, power completes 2 cycles \therefore it has double the freq. of voltage.



## AC source across inductor -

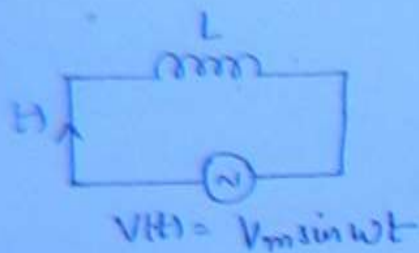

$$i_L = \frac{1}{L} \int v dt \quad (56)$$

$$i_L = \frac{1}{L} \int V_m \sin \omega t dt$$

$$i_L = -\frac{V_m}{\omega L} \cos \omega t$$

$$= \frac{V_m}{\omega L} \sin(\omega t - 90^\circ)$$

$$(X_L = \omega L)$$

$$i_L = I_m \sin(\omega t - 90^\circ)$$


$$\therefore X_L = \omega L; I = \frac{V}{X_L}$$

$$p = v(t) i(t)$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t - 90^\circ)$$

$$P = \frac{1}{2\pi} \int_0^{2\pi} p(t) d\omega t$$

$$P_{avg} = 0$$

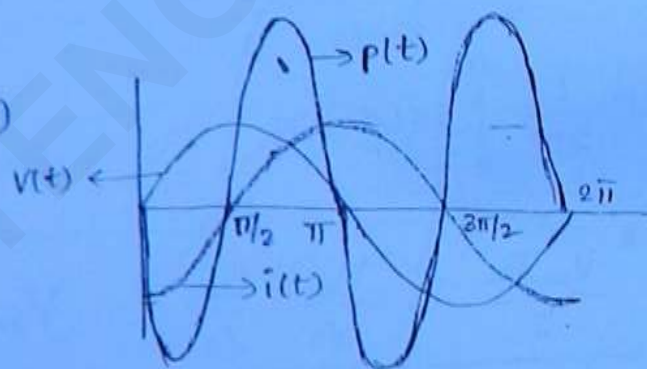

$p(t)$  freq = double  $v(t)$


∴

During the  $\frac{1}{2}$  cycle of the power, inductor takes energy from the source & in  $-\frac{1}{2}$  cycle of the power, inductor delivers energy to the source.


∴ hence, net power taken from the source = 0.

$$f = 50 \text{ Hz} \quad \{ \quad f_p = 100 \text{ Hz}$$


vector diagram ∴

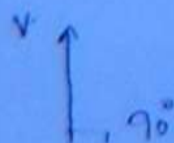

(00)

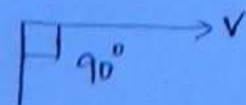

# AC source across Capacitor

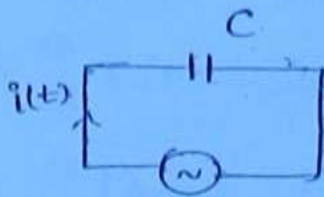

$$v(t) = V_m \sin \omega t$$

$$i = C \frac{dv}{dt}$$

$$= C \frac{d}{dt} (V_m \sin \omega t)$$

$$i = \omega C V_m \cos \omega t$$

$$i(t) = \omega C V_m \cos \omega t$$

$$i(t) = \frac{V_m}{1/\omega C} \sin(\omega t + 90^\circ)$$

$$i(t) = I_m \sin(\omega t + 90^\circ)$$

$$p(t) = v(t) i(t)$$

$$p(t) = V_m \sin \omega t \cdot I_m \cos \omega t$$

$$p(t) = \frac{V_m I_m}{2} \sin 2\omega t$$


$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} p(t) d\omega t$$

$$P_{avg} = 0$$

phasor diagram :


(60)

$$X_c = 1/\omega C$$

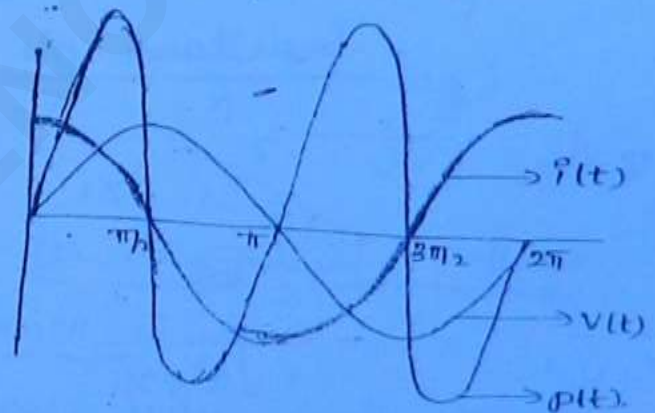

$f = 50\text{Hz}$  — voltage

$f_p = 100\text{Hz}$  — power


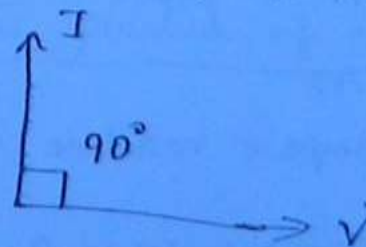




# R-L Series Circuit

58

phasor

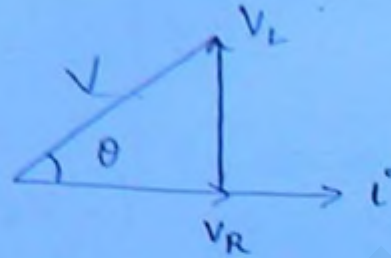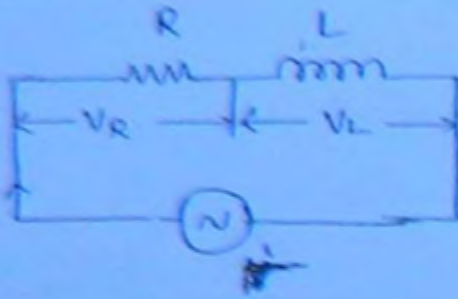


By KVL,  $V = V_R \angle 0^\circ + V_L \angle 90^\circ$

$$IZ = IR \angle 0^\circ + IX_L \angle 90^\circ$$

$$IZ = I(R + jX_L) \Rightarrow \boxed{Z = R + jX_L}$$


By  $\Delta$ le.

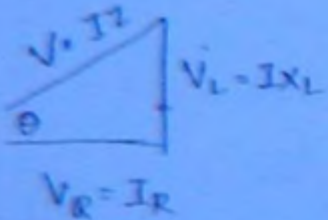

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\theta = \tan^{-1} \left( \frac{V_L}{V_R} \right)$$


Impedance  $\Delta$ le.

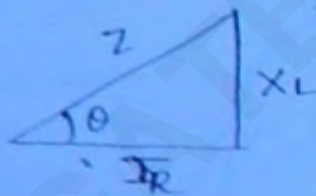

$$Z = \sqrt{R^2 + X_L^2}$$

$$\theta = \tan^{-1} \left( \frac{X_L}{R} \right)$$

power  $\Delta$ le.

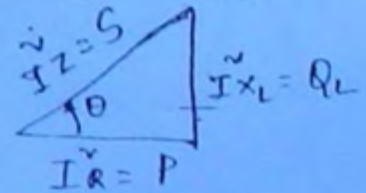

$$S = \sqrt{P^2 + Q_L^2}$$

$$\theta = \tan^{-1} \left( \frac{Q_L}{P} \right)$$

$Q_L \rightarrow$  Inductive reactive power

$Q_L \rightarrow$  unit  $\rightarrow$  VAR

(volt ampere reactive)  $\leftarrow$

$S \rightarrow$  Apparent power (or) Complex power.

$S \rightarrow$  VA (volt ampere).

$\Rightarrow P \rightarrow$  active power (or) (W). True " (or)

real "

avg. "

effective power



## Power Expressions:

$$P(t) = v(t) i(t)$$

(59)

$$P(t) = I_m \sin \omega t \cdot V_m \sin (\omega t + \theta)$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P(t) d\omega t$$

$V_m, I_m$

$$P_{avg} = \frac{V_m I_m}{2} \cos \theta$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \theta = \underline{\underline{V I \cos \theta}}$$

$V$  &  $I$  are  
Rms values  
in any ac ckt.

$$\text{power factor} = \underline{\cos \theta} = \frac{V_R}{V_T} = \frac{R}{Z} = \frac{P}{S} \quad (\text{lag})$$

wrt  $V$  i lag

→ While defining power factor for any circuit, voltage phasor is taken as a reference. Since,

- i) In the real time systems, only independent voltage source exists. (source voltage constant)
- ii) In the real time system, loads are connected in parallel (voltage is constant).

⇒ Power factor angle indicates position of current phasor wrt voltage phasor.

$$\sin(\omega t + \theta) = \sin \omega t \cos \theta + \cos \omega t \sin \theta$$



$$I_m \cos \theta = I_m \cos \theta$$

$$I_m \cos \theta$$

# C Series Circuit

(60)

Bq phasor

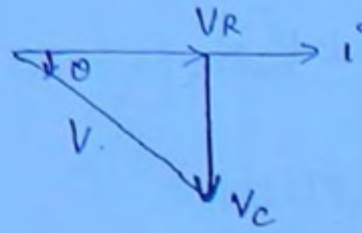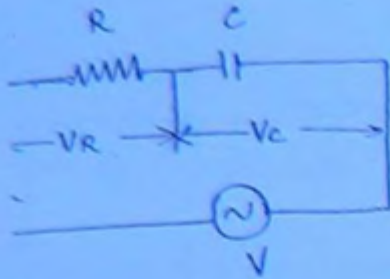


KVL,

$$V = V_R + V_C \angle -90^\circ$$

$$Z = IR \angle 0^\circ + IX_C \angle -90^\circ$$

$$IZ = I(R - jX_C) \Rightarrow \boxed{Z = R - jX_C}$$

Voltage Δ/c

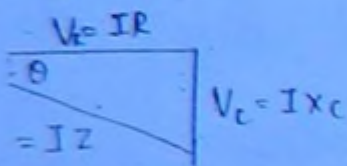


$$\sqrt{V_R^2 + V_C^2}$$

$$\tan^{-1} \left( \frac{-V_C}{V_R} \right)$$

ve  $\therefore$  CW


Impedance Δ/c

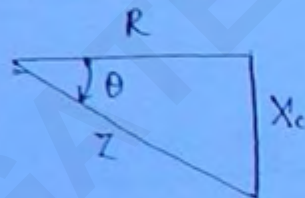

$$Z = \sqrt{R^2 + X_C^2}$$

$$\theta = \tan^{-1} \left( \frac{-X_C}{R} \right)$$

Power Δ/c

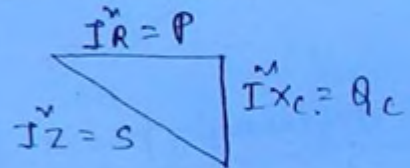


$$S = \sqrt{P^2 + Q_C^2}$$

$$\theta = \tan^{-1} \left( \frac{-Q_C}{P} \right)$$


$$\text{Power factor} = \cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S} \text{ (lead) (wrt V)}$$



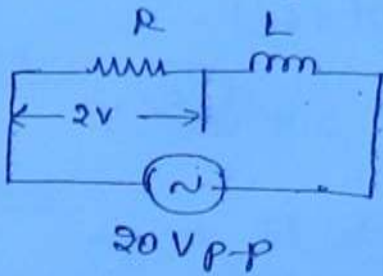Q. Find voltage across the inductor of the ckt shown:



(61)

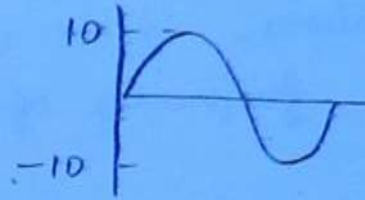

$$\frac{10 \text{ V}}{12 \text{ ms}} = \text{rms}$$

$$V_m = 10$$

$$V_{\text{rms}} = 10/\sqrt{2} = V$$

$$V = \sqrt{V_R^2 + V_L^2} \Rightarrow$$


$$V_L = \sqrt{V^2 - V_R^2}$$

$$V_L = \sqrt{46}$$

24/6/2011

Q. Find the circuit elements for a given current and voltage eqn
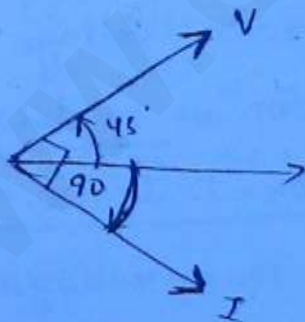
$$V(t) = 9\sin(t + 45^\circ) \quad i(t) = 3\sin(t - 45^\circ)$$



wrt I, V is leading by 90°

∴ it is an inductor

$$X_L = \frac{V}{I}$$

$$= \frac{9/\sqrt{2}}{3/\sqrt{2}} = 3$$

$$X_L = 3 \Rightarrow \omega L = 3$$

$$\omega = 1$$

$$L = 3 \text{ H}$$



1. Find circuit elements for a given voltage and current eqns.



$$v(t) = 9 \sin(t + 30^\circ) \quad i(t) = 3 \sin(2t + 60^\circ)$$

(2)

Note :-

For the above equations, it is not possible to design the circuit. Since, frequency of voltage and current are unequal.

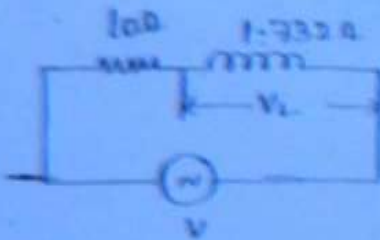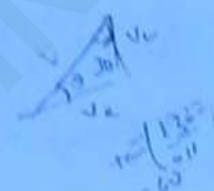
2. Find angle made by source voltage wrt  $V_L$ .



- (a) 30, (b) 60  
 ✓ (c) -30, (d) -60

$$\theta = \tan^{-1} \left( \frac{X_L}{R} \right) = \tan^{-1} \left( \frac{1.732}{10} \right) = \tan^{-1}(\sqrt{3})$$


$$\theta = 60^\circ$$

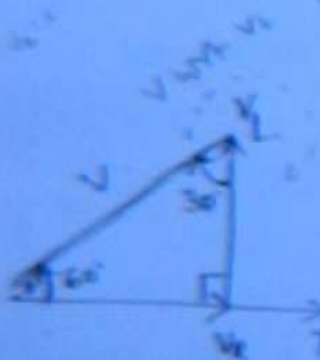

made by  
 wrt.  $V_L$  angle of source voltage is  $30^\circ$ . The angle vector is rotating in clockwise direction.  $\therefore$  it is -ve

Thus the angle made by source voltage wrt to  $V_L$  is  $-30^\circ$

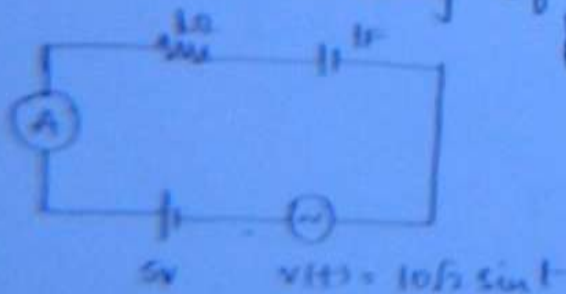Find ammeter reading of the circuit shown.



$$5 + 10 = 15$$

$$15 \sin t$$

Apply Superposition theorem.

D.C.

$$C \rightarrow \text{D.C.} \quad \therefore i_{DC} = 0$$

(3)

A.C.

$$X_C = \frac{1}{\omega C} = 1$$


$$Z = \sqrt{R^2 + X_C^2} = \sqrt{1+1} = \sqrt{2}$$

$$I_{AC} = \frac{V}{Z} = \frac{10}{\sqrt{2}}$$

$$V = V_{rms} = \frac{10\sqrt{2}}{\sqrt{2}} \\ V = 10$$

$$\text{Ammeter reading: } \frac{10}{\sqrt{2}} + 0 = \frac{10}{\sqrt{2}} \text{ A}$$

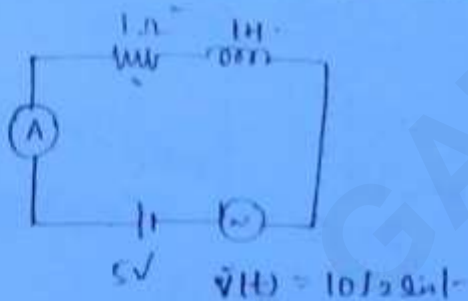Q. Find the ammeter reading of the circuit shown.



Sol.

$$I_{DC} = \frac{5}{1} = 5 \text{ A}$$

$L \rightarrow \text{S.C.}$

Superposition

$$X_L = \omega L = 1 \Omega$$



$$Z = \sqrt{R^2 + X_L^2} = \sqrt{1+1} = \sqrt{2}$$

$$I_{AC} = \frac{V}{Z} = \frac{10}{\sqrt{2}}$$

$\therefore$  Two different frequencies are present we cannot add  $i_{DC}$  &  $i_{AC}$  for total current.

$$i = \frac{5}{1} + \frac{10}{\sqrt{2}} \sin 2t$$

# RLC Series Circuit

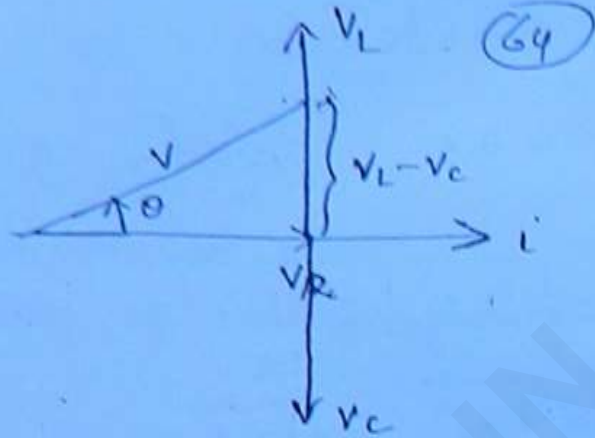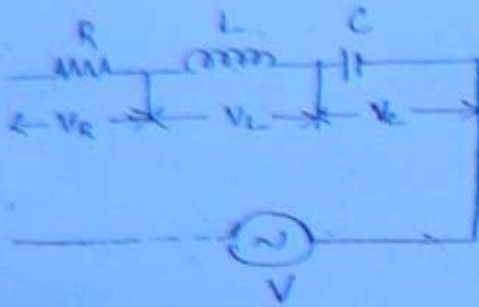


By KVL:

$$V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$$

$$IZ = I[R + j(X_L - X_C)]$$

$$Z = R + j(X_L - X_C)$$


Impedance Δ

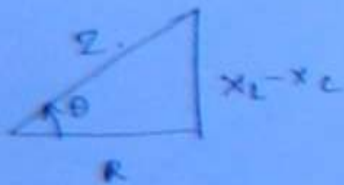

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$


Voltage Δ

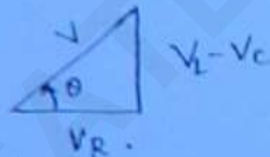

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\theta = \tan^{-1}\left(\frac{V_L - V_C}{V_R}\right)$$


Power Δ

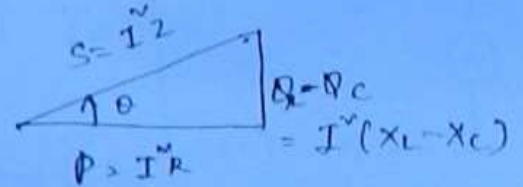

$$S = \sqrt{P^2 + (Q_L - Q_C)^2}$$

$$\theta = \tan^{-1}\left(\frac{Q_L - Q_C}{P}\right)$$

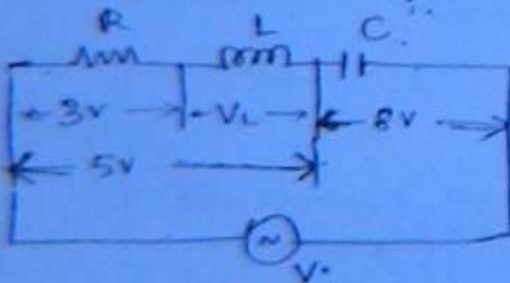Find  $V_L$  &  $V$  of the circuit shown.





$$5 = \sqrt{V_L^2 + 3^2} \Rightarrow V_L = 4$$


$$V = \sqrt{3^2 + V_L^2 + 5^2} = \sqrt{3}$$

(63)

$$V = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{3^2 + (4 - 8)^2}$$

$$V = 5V$$

Q. Find voltage across capacitor.

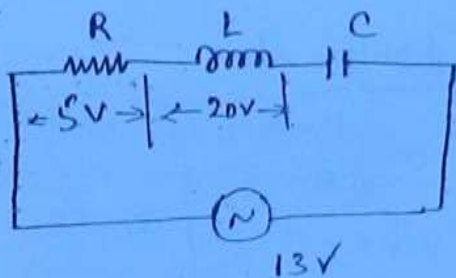

- (a) 8V (b) 32V  
 ✓ (c) 8 or 32V (d) 10V

$$13 = 5 + (20 - V_C)$$

$$12 = 20 - V_C$$

$$V^2 = V_R^2 + (V_L - V_C)^2$$

$$(V_L - V_C)^2 = V^2 - V_R^2$$

$$(20 - V_C)^2 = 13^2 - 5^2$$

$$20 - V_C = \pm 12$$

for

$$20 - V_C = 12$$

$$V_C = 8V$$



or

$$20 - V_C = -12$$

$$32 = V_C$$

$$V_C = 8 \text{ (or) } 32V$$

RL parallel circuit

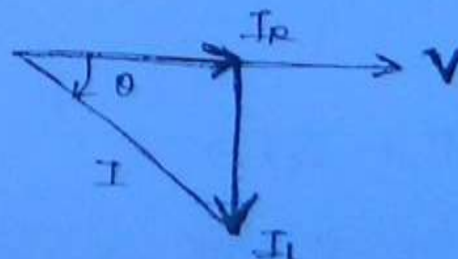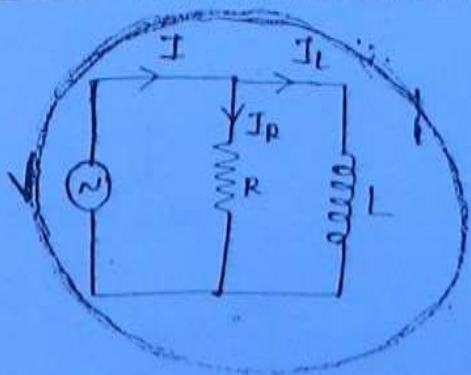

By kel

$$I = I_R \angle 0^\circ + I_L \angle -90^\circ$$

$$\frac{V}{Z} = \frac{V}{R} \angle 0^\circ + \frac{V}{X_L} \angle -90^\circ$$

$$VY = VG - jVB_L$$


$\Rightarrow$

$$Y = G - jB_L$$

$V$   
mho (or) S.

mho (or) S


Current Δe.

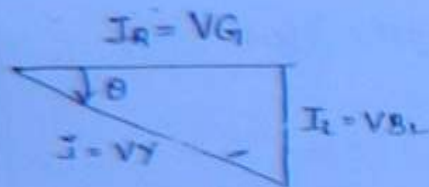

$$I = \sqrt{I_R^2 + I_L^2}$$

$$\theta = \tan^{-1} \left( \frac{-I_L}{I_R} \right)$$


admittance Δe

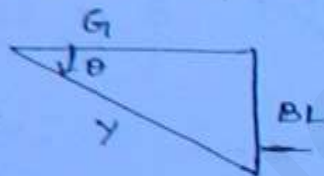

$$Y = \sqrt{G^2 + B_L^2}$$

$$\theta = \tan^{-1} \left( \frac{-B_L}{G} \right)$$


power Δe.

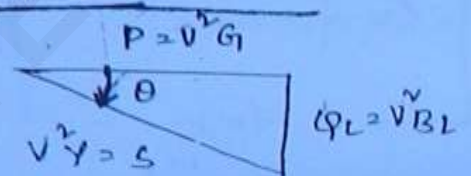


$$S = \sqrt{P^2 + Q_L^2}$$

$$\theta = \tan^{-1} \left( \frac{-Q_L}{P} \right)$$

RC - parallel circuit

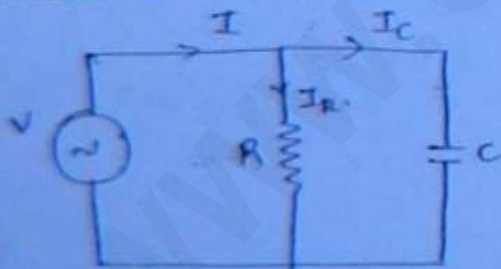

$\frac{I_R}{I} = \cos \theta$

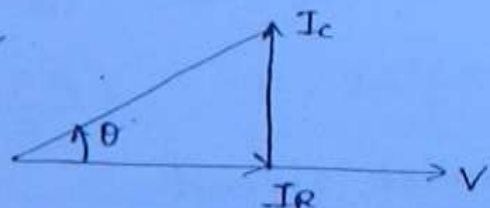

By kel,

$$I = I_R \angle 0^\circ + I_C \angle 90^\circ$$


$$\frac{V}{Z} = \frac{V}{R} \angle 0^\circ + \frac{V}{X_C} \angle 90^\circ$$

$$VY = VG + jVB_C$$

current  $\Delta$ le.


admittance  $\Delta$ le.

Power  $\Delta$ le

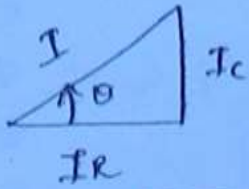

$$I = \sqrt{I_R^2 + I_L^2}$$

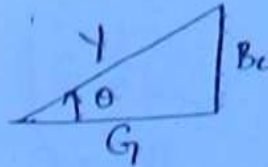
$$\theta = \tan^{-1} \left( \frac{I_L}{I_R} \right)$$



$$Y = \sqrt{G^2 + B_L^2}$$

$$\theta = \tan^{-1} \left( \frac{B_L}{G} \right)$$



(67)

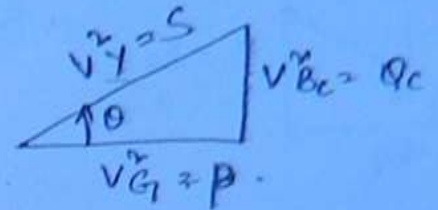

$$S = \sqrt{P^2 + Q_L^2}$$

$$\theta = \tan^{-1} \left( \frac{Q_L}{P} \right)$$

## R L C parallel Circuit

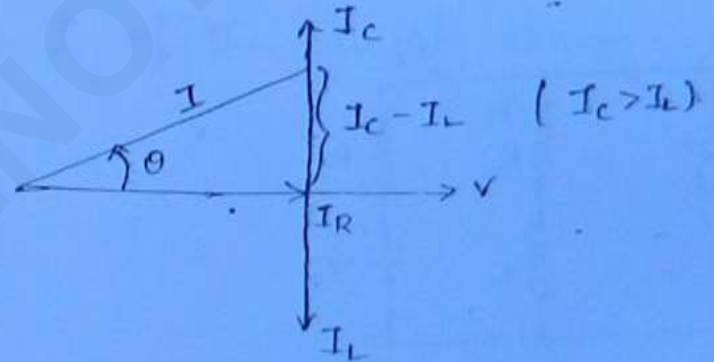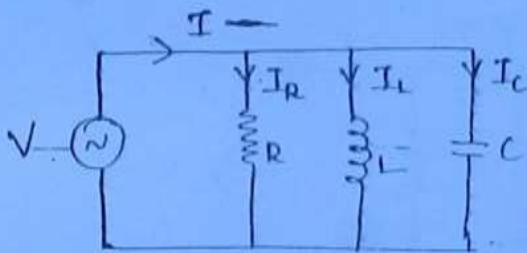

By KCL

$$I = I_R \angle 0^\circ + I_L \angle -90^\circ + I_C \angle 90^\circ$$

$$\frac{V}{Z} = \frac{V}{R} \angle 0^\circ + \frac{V}{X_L} \angle -90^\circ + \frac{V}{X_C} \angle 90^\circ$$

$$V Y = -V G + j V B_L + j V B_C$$

$$Y = G + j (B_C - B_L) \Rightarrow$$

Current  $\Delta$ le.



$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$



$$\theta = \tan^{-1} \left( \frac{I_C - I_L}{I_R} \right)$$



admittance  $\Delta e$ .

power  $\Delta e$ .

(68)

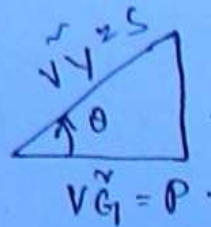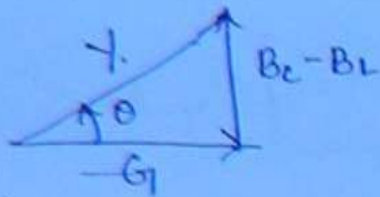

$$V(B_c - B_L) = Q = Q_c - Q_L$$


$$Y = \sqrt{G_1^2 + (B_c - B_L)^2}$$

$$S = \sqrt{P^2 + Q^2}$$

$$\theta = \tan^{-1} \left( \frac{B_c - B_L}{G_1} \right)$$

$$\theta = \tan^{-1} \left( \frac{Q}{P} \right)$$

RC parallel.

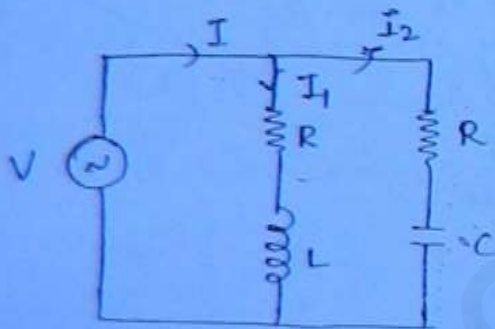

$$I_1 = \frac{V}{R_1 + jX_L} \times \frac{R_2 - jX_L}{R_2^2 + X_L^2}$$

$$\frac{V}{Z_1} = V \left[ \frac{R_1}{R_1^2 + X_L^2} - \frac{jX_L}{R_1^2 + X_L^2} \right]$$

$$VY_1 = V [G_1 - jB_L]$$

$$Y_1 = G_1 - jB_L$$

$$I_2 = \frac{V}{R_2 - jX_C} \cdot \frac{R_2 + jX_C}{R_2^2 + X_C^2}$$

$$\frac{V}{Z_2} = V \left[ \frac{R_2}{R_2^2 + X_c^2} + j \frac{X_c}{R_2^2 + X_c^2} \right]$$

$$V Y_2 = V (G_2 + j B_c)$$

(69)


$$Y_2 = G_2 + j B_c$$

$$I = I_1 + I_2$$

$$V Y_{eq} = V Y_1 + V Y_2$$

$$Y_{eq} = Y_1 + Y_2$$

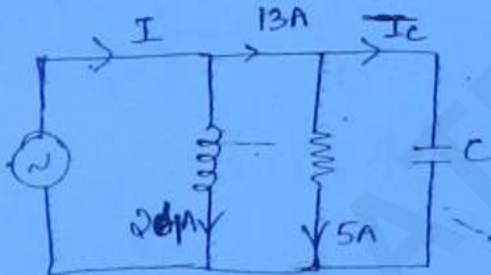Q. Find the value of  $I_c$  &  $I$  of the circuit shown.



Soln.


$$13 = \sqrt{I_R^2 + I_c^2} = \sqrt{5^2 + I_c^2}$$

$$I_c = 12A$$

$$\Rightarrow I = \sqrt{I_R^2 + (I_c - I_R)^2} = \sqrt{5^2 + (24 - 12)^2}$$

$$I = 13A$$

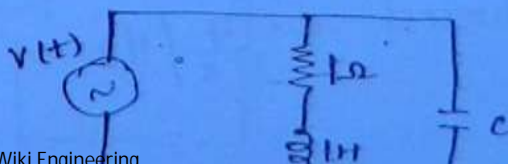Q. Find the value of  $C$  when power factor of the ckt is 0.8 lag.



$$X_L = \omega L$$

$$X_L = 1$$

(70)

$$\tan \theta = \frac{B_C - B_L}{G}$$

$$G_1 = \frac{R_1}{R_1^2 + X_L^2} = \frac{1}{1^2 + 1^2} = 1/2$$

$$B_L = \frac{X_L}{R_1^2 + X_L^2} = \frac{1}{1^2 + 1^2} = 1/2$$

$$Y_1 = G_1 - j B_L$$


$$Y_1 = 1/2 - j 1/2$$

$$Y_2 = j B_C = j \omega C = j C$$

$$Y_2 = j C$$


$$Y_{eq} = Y_1 + Y_2 \Rightarrow Y_{eq} = \frac{1}{2} + j \left( C - \frac{1}{2} \right)$$
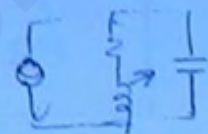
$$\Rightarrow \cos \theta = \frac{G}{\sqrt{G^2 + (B_C - B_L)^2}}$$



$$I = I_1 + j I_2$$

$$Y_{eq} = Y_1 + Y_2$$

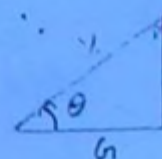

$$0.8 = \frac{1/2}{\sqrt{\left(\frac{1}{2}\right)^2 + \left(C - \frac{1}{2}\right)^2}} \Rightarrow C = \frac{7}{8}, \frac{1}{8}$$

But power factor is 0.8 LAG. Which means the ckt is inductive in nature.  $\therefore B_L > B_C$

$$B_L = 1/2 \therefore \text{for } C = 1/8 \text{ satisfies } B_L > B_C$$

$$\text{if } 0.8 \text{ lead} \Rightarrow C = 7/8$$

$$\text{if neither lead nor lag is mentioned } C = 7/8, 1/8$$




# Locus Diagram

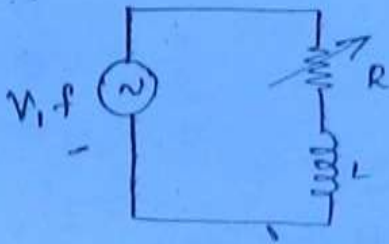(71)

- Locus diagrams are useful for analysis and designing of the circuits. Ex. filters.
- The path traced by terminals of the current vectors by varying any one of the circuit elements (or) by varying frequency is called as current locus.

Q. Draw the current locus of the circuit shown.



$$R = 0$$

$$Z = X_L$$

$$I = V/X_L$$

$$\theta = 90^\circ$$

$$R \uparrow$$


$$Z \uparrow$$

$$I \downarrow$$

$$\theta = \tan^{-1} \left( \frac{X_L}{R} \right) \downarrow$$

$$R = \infty$$


$$I = 0$$

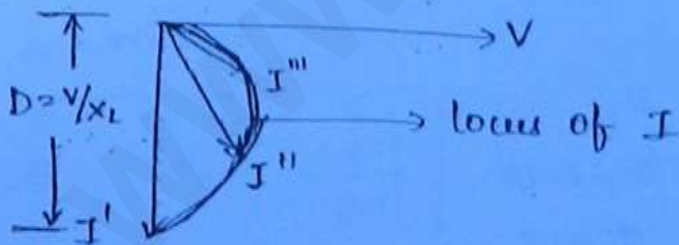

$D \rightarrow$  diameter of locus.

$$\text{radius } r = \frac{V}{2X_L}$$

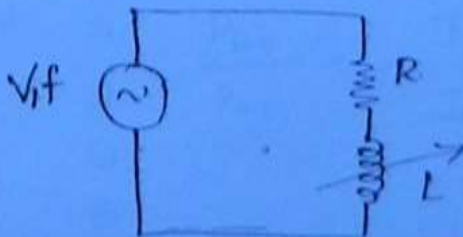Q. Draw the current locus of the ckt shown.



$$X_L = 2\pi fL$$

$$X_L = 0$$

$$Z = R$$

$$I = \frac{V}{R}$$

$$\theta = 0$$

$$X_L \uparrow$$

$$Z \uparrow$$


$$I \downarrow$$

$$\theta = \tan^{-1}\left(\frac{X_L}{R}\right) \uparrow$$

$$X_L = \infty$$


$$I = 0$$

(72)

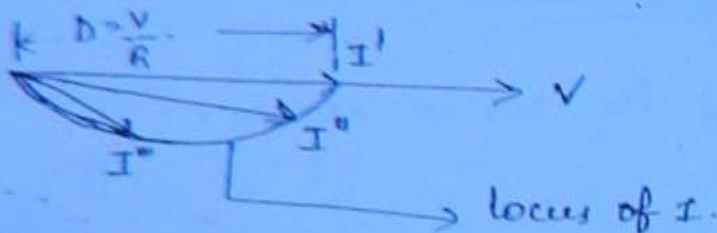

For the above ckt if  $R$  &  $L$  are kept constant & freq  $f$  is varied, then also the locus is the same.

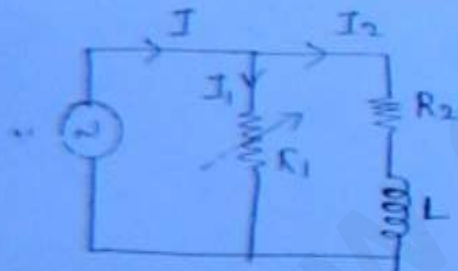2) Draw the current locus of  $i_1$  and  $i$  of the ckt shown.



$$I_2 = \frac{V}{R_2 + jX_L} = \text{const.}$$

let  $R = 0.1 \Omega$

$$R_1 \uparrow$$

$$R_1 = \infty$$

$$I_1 = \frac{V}{R_1}$$

$$I_1 \downarrow$$

$$I_1 = 0$$

$$I = I_2$$


$$\theta_1 = 0$$

$$\theta_1 = 0$$


$$I = I_1 + I_2$$

$$\therefore I_2 = \text{const.}$$

$$I \downarrow$$

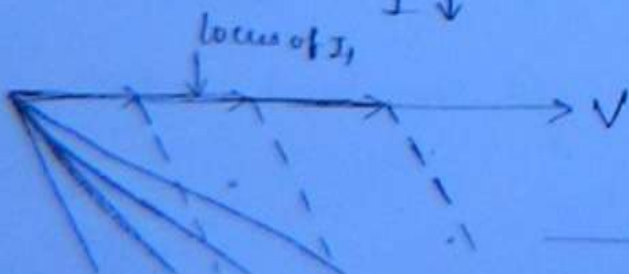

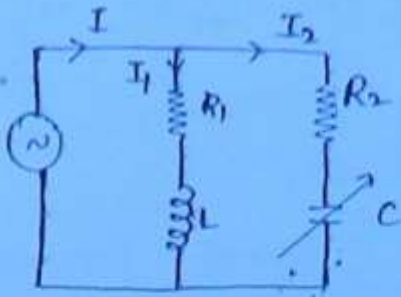
Q. Draw the current locus of  $I_2$  &  $I$  of the ckt shown.



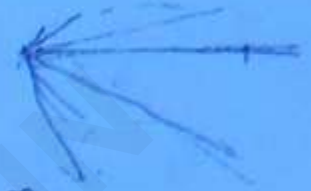(73)

$$I_1 = \frac{V}{R_1 + jX_L}$$

$$I_2 = \frac{V}{R_2 + jX_C} \tan^{-1}\left(\frac{X_C}{R_2}\right)$$



$$X_C = \frac{1}{2\pi fC}$$

$X_C \uparrow$

$X_C \rightarrow \infty$

$I_2 \downarrow$

$I_2 \rightarrow 0$

$$\theta = \tan^{-1}\left(\frac{X_C}{R_2}\right)$$

$I = I_1$

$X_C \approx 0$


$I_1 = \text{constant}$

$$I_2 = \frac{V}{R_2}$$

$\theta_2 \approx 0$

$I \downarrow$

$$I = I_1 + I_2$$

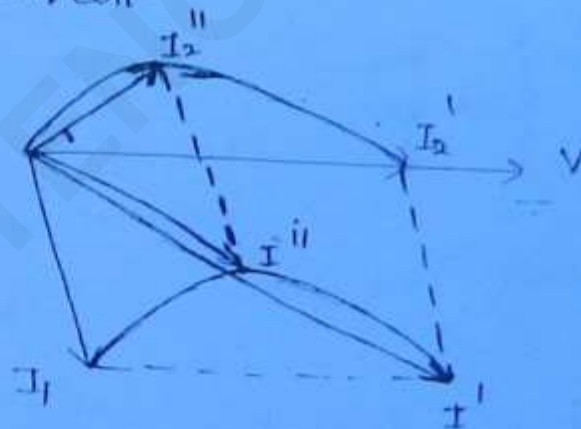

6/2011

Work book

$$1. \quad \text{Var} = \frac{1}{2\pi} \left[ \int_0^{2\pi} V \sin(\omega t + \phi) d\omega t + \int_0^{2\pi} 0 d\omega t \right] V$$

$$= \frac{V}{\pi} \cos \phi$$

2.

$$\frac{P_{D.C.}}{P_{A.C.}} = \frac{I_{av}^2 R}{I_{rms}^2 R} = \frac{(2I_m/\pi)^2}{(I_m/\sqrt{2})^2} = \frac{8}{\pi^2}$$



5.  $X_L = 20$   
 $X_C = 20$

$R = 10$ ,  $V = 200$ .

(74)


$Z = R + j(X_L - X_C) = 10$ .

$I = \frac{V}{Z} = \frac{200}{10} = 20 \text{ A}$ .

$V_C = -jIX_C = (20)(20) \angle -90 = 400 \angle -90^\circ \text{ V}$ .

$I = \sqrt{I_R^2 + I_L^2}$

$V_1 = 40 \text{ V}$ .

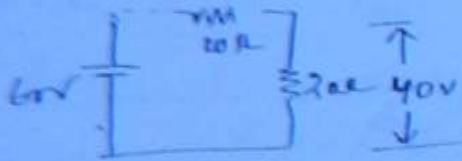

So, the current source has no effect on  $20\Omega$  across  $60\text{V}$ .


Whatever be the value of  $R$ , The voltage across  $20\Omega = 40\text{V}$ .  $\therefore I_R = 0 \Rightarrow V_1 = V_2 = 40\text{V}$ .

6. Current mag. is const.

Voltage doubles for double resistor

$I = e^{at} + e^{bt} \Rightarrow V = L \frac{di}{dt} \Rightarrow V = ae^{at} + be^{bt}$


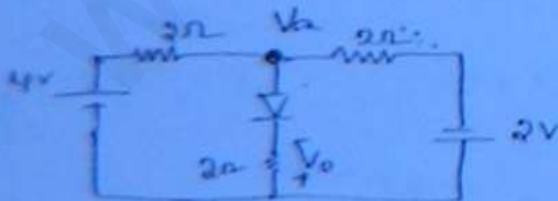
$10 + 5 + E + 1 + 0 = 0 \Rightarrow E = -16\text{V}$ .




$\Rightarrow \frac{V_a - 4}{2} + \frac{V_a}{2} + \frac{V_a + 2}{2} = 0$

$V_a = 2/3$ .

$V_0 = -V_a = -2/3$ .

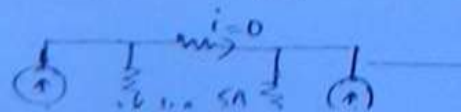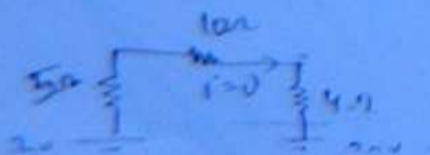

22.

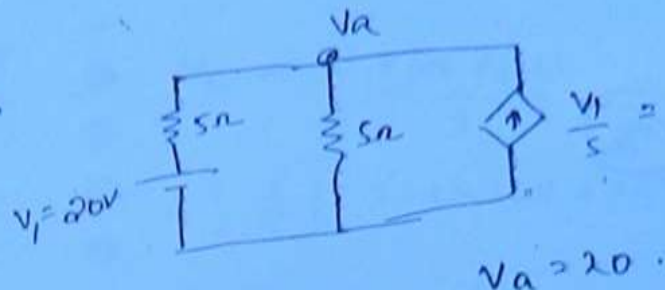


$$\frac{V_1}{5} = \frac{20}{5} = 4 \quad \frac{V_a - 20}{5} + \frac{V_a}{5} = 4$$

$$V_a = 20$$

(75)

Current source  $\Rightarrow 20 \times 4 = 80W$  deliver.

24.

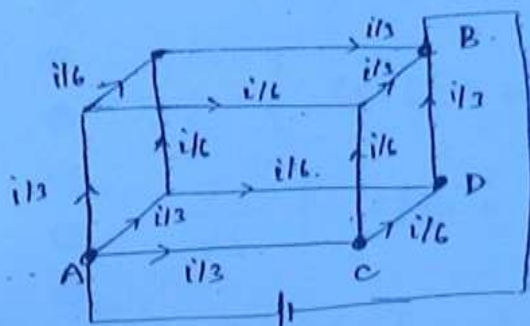

Considers equal resistors of value = R.

Loop ACDB.

$$V = \frac{I}{3}R + \frac{I}{6}R + \frac{I}{3}R$$

$$\frac{V}{I} = \frac{5}{6}R = R_{AB}$$

For resistors,  $R_{AB} = \frac{5}{6}R$ .

inductors  $L_{AB} = \frac{5}{6}L$ .


capacitors  $C_{AB} = \frac{6}{5}C$ .

25.

variable angle  $\rightarrow$  semicircle  
const.  $\rightarrow$  st. line.

28.

consider,

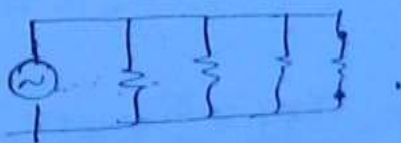


29.

$$I = VY = (3 - 2j + 6j) \sin 2t = 5 \sin(2t + 53.1^\circ)$$

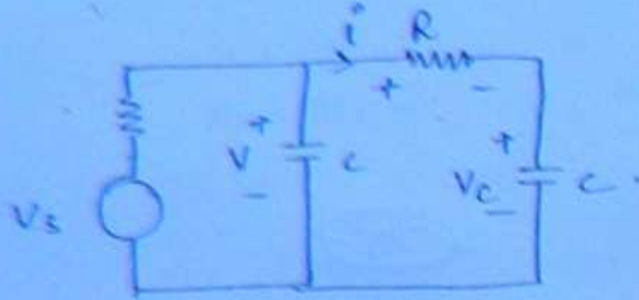30.


$$V_o = \frac{V_i \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{V_i}{1 + jRC\omega}$$

$$\omega = 10^3 \text{ rad/s}, RC = 10^{-3} \Rightarrow \frac{V_i}{1 + j} = \frac{\sqrt{2} \sin 10^3 t}{1 + j}$$



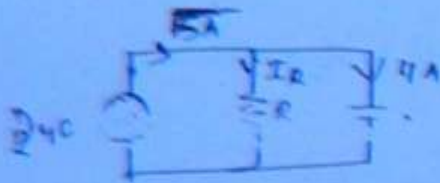
(76)

$$V = iR + V_c \Rightarrow V = C \frac{dv_c}{dt} + V_c$$



$$I_R = \sqrt{5^2 - 4^2} = 3A$$


$$R = \frac{240V}{3A} = 80\Omega$$

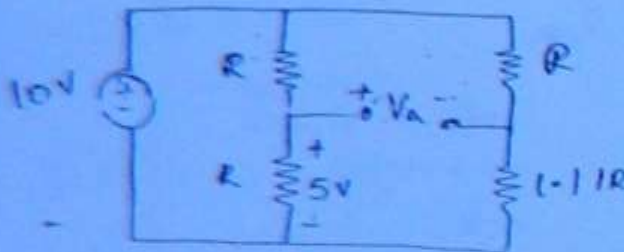

$$V_1 = \frac{10 \times 1.1R}{1.1R + R}$$


$$V_1 = 5.238V$$

$$V_a = 5 - 5.238 = -0.238V$$

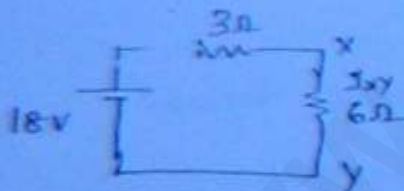

$$I_{xy} = \frac{18}{9} = 2A$$

$$V_{xy} = 2 \times 6 = 12V$$

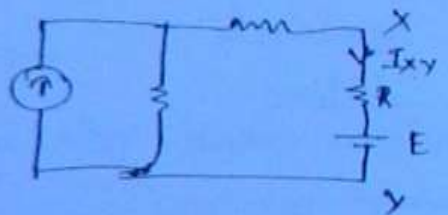

$$V_{xy} = RI_{xy} + E$$

$$12 = R_2 + E$$

Substitute the given set of values and check.


For eq. ckt, load current should be equal.  
equal load current  $\Rightarrow$  equal load voltage.



$h(t) = \sin(t)$

NG-12-10-17

77

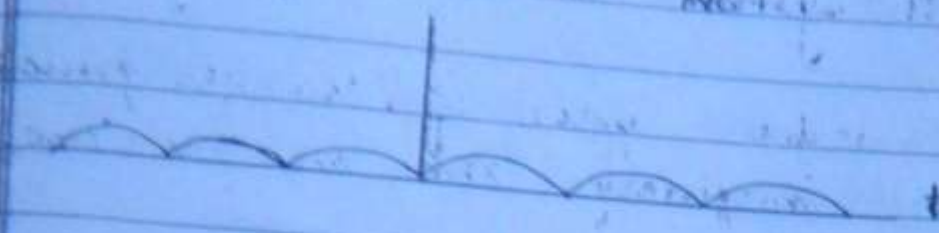



Condition for LTI system to be stable:

$$\int_{-\infty}^{\infty} |h(t)| dt < \infty$$

ie impulse response should be absolutely integrable.

If impulse response of system is represented by an energy signal then system will be stable.

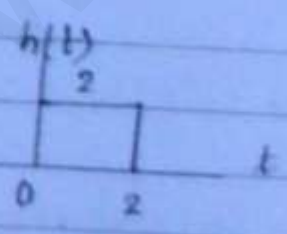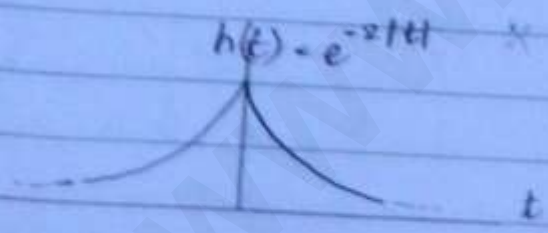Impulse response & transfer function terms are used only for LTI systems.



$h(t) = \text{Sa}(t)$

The bridge is unbalanced becoz, the angles  $j$  &  $-j$  are different for inductor & capacitor.

∴ Go for  $\Delta \rightarrow Y$  transformation.



(78)

$$\omega = 1$$

$$X_L = \omega L = 1$$

$$X_C = \frac{1}{\omega C} = 1$$
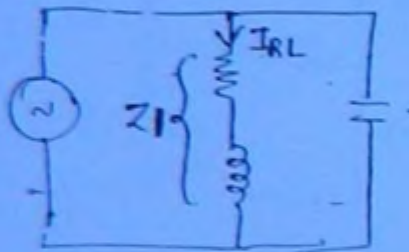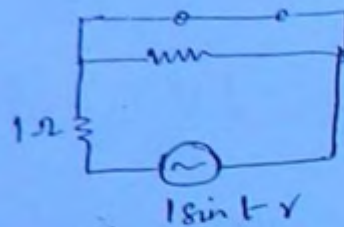
$$\Rightarrow j(X_L - X_C) = 0 \rightarrow \text{S.C.}$$



$$Z_1 = \frac{V_s}{I_{RL}}$$

$$Z_1 = \frac{1 \angle 0^\circ}{\sqrt{2} \angle -45^\circ} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$Z_1 = \frac{\cos 45^\circ}{\sqrt{2}} + j \frac{\sin 45^\circ}{\sqrt{2}} = \frac{1}{2} + j \frac{1}{2} = R + jX_L$$

$$R = 1/2 \Rightarrow P = I_{RMS}^2 R = (\sqrt{2})^2 (1/2) = 1 \text{ W}$$

phasor sum is done with rms values.

$$I_s = I_{RL} + I_C \quad \} \rightarrow \text{phasor sum} \rightarrow \text{RMS}$$

$$I_{RMS} = \sqrt{2} \text{ — by default}$$

$I_C$


Note: In real time systems, the voltage or the current values are given in rms values.

∴ if nothing is specified, by default we take it as rms value.

## Conventional Ques.

79

1.

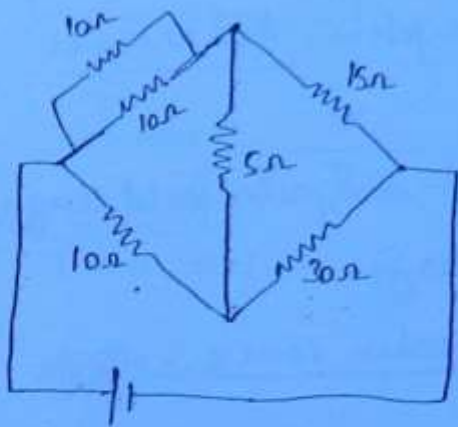


Balanced bridge.

$$5 \times 30 = 10 \times 15$$

$$150 = 150 \text{ V}$$

$$\therefore I_{5\Omega} = 0$$

2.

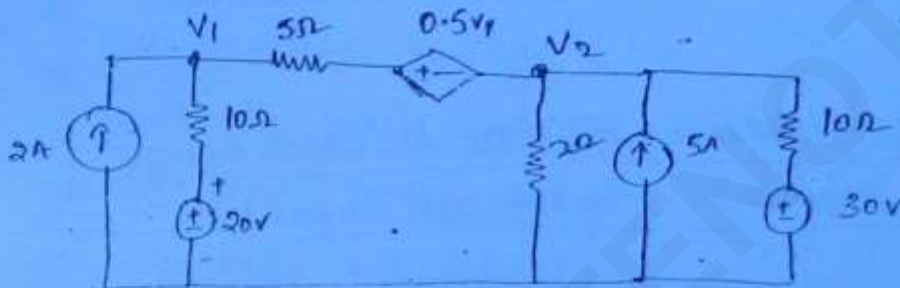

IES 2009

By KCL, at node 1

$$2 = \frac{V_1 - 20}{10} + \frac{V_1 - 0.5V_1 - V_2}{5} \rightarrow (1)$$

at node 2.

$$5 = \frac{V_2}{20} + \frac{V_2 - 30}{10} + \frac{V_2 + 0.5V_1 - V_1}{5} \rightarrow (2)$$

$$2 = 0.1V_1 - 2 + 0.1V_1 - 0.2V_2$$

$$4 = 0.2V_1 - 0.2V_2 \Rightarrow V_1 - V_2 = 20$$

$$5 = 0.5V_2 + 0.1V_2 - 3 + 0.2V_2 + 0.1V_1$$

$$8 = 0.8V_2 - 0.1V_1 \Rightarrow 8V_2 - V_1 = 80$$

$$8V_2 - 20 + V_2 = 80$$

or



# Resonance

(80)

For occurrence of resonance in any system, two energies are required.



In RLC circuit, inductor consists of magnetic field energy, and capacitor consists of electric field energy.

The circuit is said to be resonant, when source voltage and source current are in phase.

The frequency at which  $X_L = X_C$  is called as resonant frequency.

The resonant frequency indicates the rate at which energy transformation is done between inductor and capacitor.

Series resonance

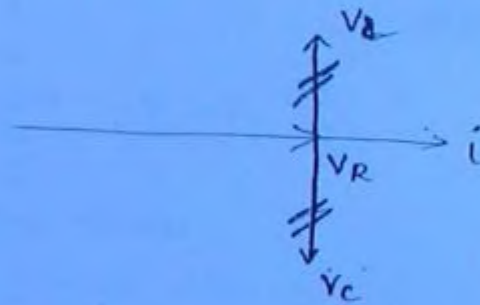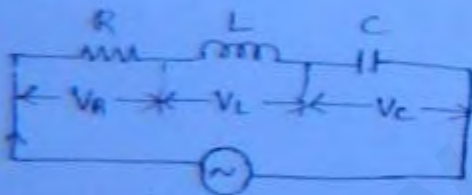

$$V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$$

for resonance,

$$V_L = V_C$$

$$I X_L = I X_C$$

$$\omega L = \frac{1}{\omega C} \Rightarrow$$

resonant freq,  $f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

1.  $Z = R + j(X_L - X_C)$

$$Z_{\min} = R$$

(81)


2.  $I_{\max} = \frac{V}{Z_{\min}} = \frac{V}{R}$

3.  $\cos \theta = 1$

(power factor = 1 in phase)

4.  $V_R = V$

(active component of the voltage)

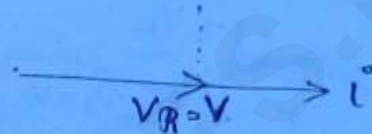


5. Net reactive voltage = 0

6. Voltage across inductor and voltage across capacitor greater than source voltage. This phenomenon is called as voltage magnification.

### Applications

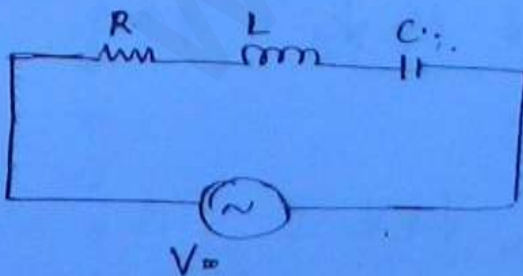1. Oscillators
2. Filters (Band pass & Band elimination filter)
3. Tuning circuits.
4. Induction heating.



$$V_C = I X_C$$

$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

\* The graph of derivation for L & C are in next P




let  $f > 0$  &  $f$  is varied (increased).

$$X_L = 0 \quad |X_L - X_C| = \infty \Rightarrow |X|$$

$$X_C = \infty \Rightarrow Z = \infty, I = 0.$$
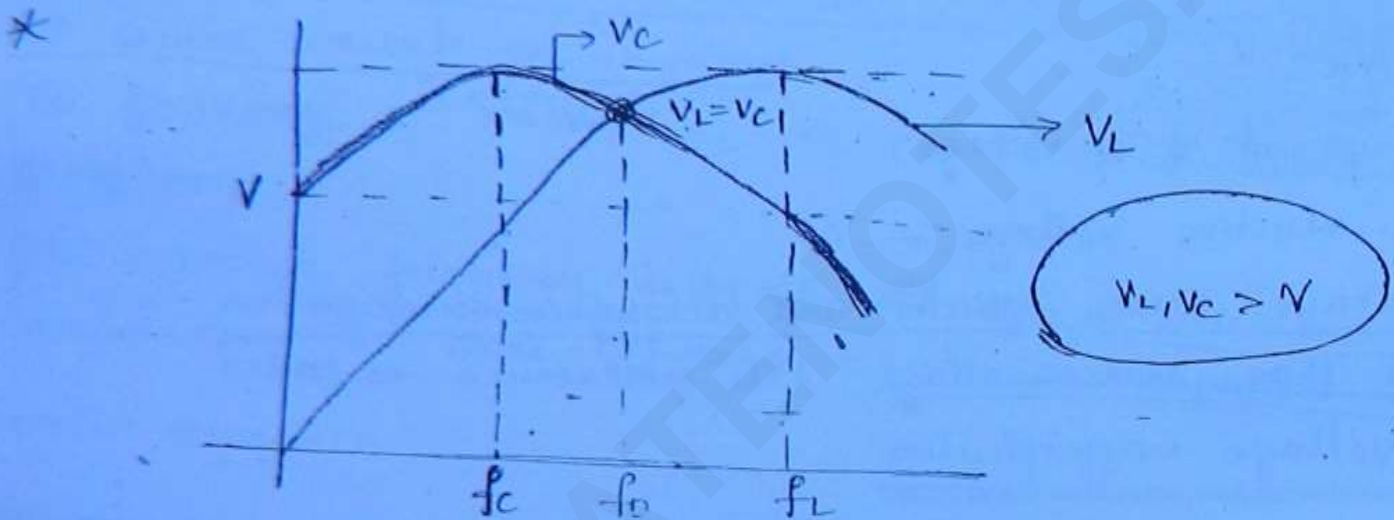
$$\therefore \boxed{V_C = V} \text{ at } f = 0.$$



$$f \uparrow \quad X_L \uparrow \quad X_C \downarrow \quad |X| = |X_L - X_C| \downarrow \downarrow$$

(100  $\Omega$ ) (100  $\Omega$ ) 90  $\Omega$

$$Z \downarrow \downarrow \Rightarrow$$

$$\uparrow \uparrow I = \frac{V}{Z \downarrow \downarrow} \Rightarrow V_C \uparrow$$

higher frequencies,

$$f \uparrow \uparrow \quad X_L \uparrow \uparrow \quad X_C \downarrow \downarrow$$

(-very low)

$$Z \uparrow \uparrow \quad I \downarrow \downarrow \quad V_C \downarrow$$

$$V_C = I X_C$$

$\approx$

$$V_C = \frac{V X_C}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$\Rightarrow$

$$V_C = \frac{V \cdot 1/\omega C}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \rightarrow \textcircled{c}$$



differentiate eq (1) wrt  $\omega$ . & equate it to zero.

we obtain,

series resonance

$$f_c = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \left(\frac{R^2 C}{2L}\right)}$$

(83)

for  $V_L$ :

$$\frac{1}{2\pi f_c} \sqrt{1 - \frac{R^2 C}{2L}}$$

$$V_L = I X_L$$

$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

for  $f = 0$ ;

$$X_L = 0$$

$$X_C = \infty$$

$$|X| = |X_L - X_C| = \infty$$

$$Z = \infty, I = 0$$

$$\rightarrow \therefore V_L = 0$$

at  $f = 0$ .

for low freq.

$$f \uparrow, X_L \uparrow, X_C \downarrow, |X| = |X_L - X_C| \downarrow \downarrow$$

(10  $\Omega$ )      (100  $\Omega$ )      90  $\Omega$

$$Z \downarrow \downarrow \rightarrow I \uparrow = \frac{V}{Z \downarrow \downarrow} \Rightarrow V_L \uparrow$$

for high freq.

$$f \uparrow \uparrow, X_L \uparrow \uparrow, X_C \downarrow \downarrow, Z = R + j(X_L - X_C) \uparrow \uparrow \uparrow$$

(very low)

$$\therefore I \downarrow \downarrow \downarrow \text{ \& } V_L \downarrow$$

$$V_L = I X_L$$

$$V_L = \frac{V X_L}{\sqrt{R^2 + (X_L - X_C)^2}}$$

(84)

$$V_L = \frac{V \omega L}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \rightarrow (2)$$

differentiate (2) wrt  $\omega$  & equating it to zero, we

get

$$\frac{P}{f_L} = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{1}{1 - (R^2 C^2 / 2L)}}$$

Quality factor - Q-factor

$$Q = 2\pi \frac{\text{Max. energy stored in the ckt}}{\text{power dissipation per cycle}}$$

$$i(t) = I_m \sin \omega t$$

$$V_C = \frac{1}{C} \int i(t) dt = \frac{1}{C} \int I_m \sin \omega t dt$$

$$V_C(t) = \frac{1}{\omega C} I_m \cos \omega t$$

$$\omega = \frac{1}{LC} \Rightarrow L = \frac{1}{\omega^2 C}$$

$$\frac{I_m \cos \omega t}{\omega C}$$

$$W_g = \frac{1}{2} L i^2 + \frac{1}{2} C v_c^2$$

(83)

$$W_g = \frac{1}{2} L (I_m \sin \omega t)^2 + \frac{1}{2} C \left( -\frac{1}{\omega C} I_m \cos \omega t \right)^2$$

$$W_g = \frac{1}{2} L I_{max}^2 \sin^2 \omega t + \frac{1}{2} \cancel{C} \cdot \frac{1}{\omega^2 \cancel{C}} I_m^2 \cos^2 \omega t$$

$$W_g = \frac{1}{2} L I_{max}^2 \sin^2 \omega t + \frac{1}{2} L I_{max}^2 \cos^2 \omega t \quad \because \frac{1}{\omega^2 C} = L$$

$$\boxed{W_g = \frac{1}{2} L I_{max}^2}$$

$$\boxed{W_g = \frac{1}{2} C V_{cmax}^2}$$

where

$$\boxed{V_{cmax} = \frac{I_{max}}{\omega C}}$$

$$Q = 2\pi \frac{\frac{1}{2} L I_{max}^2}{\left( \frac{I_{max}}{\sqrt{2}} \right)^2 R \cdot 1/f}$$

$$Q = \frac{2\pi f L}{R} = \frac{\omega L}{R}$$

$$Q = \frac{\omega L}{R} \quad \left( \omega = \frac{1}{\sqrt{LC}} \right)$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{X_L}{R} = \frac{X_C}{R}$$

$$\therefore X_L = \omega L$$

$$Q = \frac{X_L}{R} = \frac{I X_L}{I R} = \frac{V_L}{V_R} = \frac{V_L}{V}$$

But  $V_L = V_C$

$$Q = \frac{V_C}{V} = \frac{I X_C}{I V_0} = \frac{I X_C}{I V_0} = \frac{X_C}{V_0} = \frac{1}{\omega C V_0}$$



$$Q = \frac{I^2 X_L}{I^2 R} = \frac{Q_L}{P}$$

(86)

6/11

## Band width


$\frac{I_L}{P}$

> when the curve is drawn between current <sup>vs</sup> frequency, then the curve is called as resonance curve.

Band-width is a range of frequencies on either side of the resonant frequency where the current falls from maximum value to 70.7% of the max. value. It is given by,

$$BW = f_2 - f_1 \rightarrow \text{lower cut off}$$

↓  
upper cut off

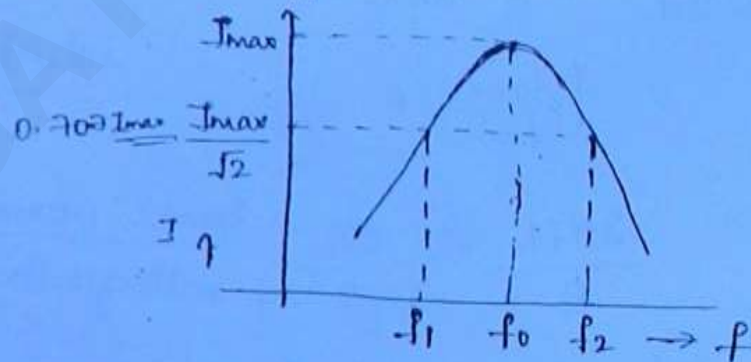

$$f_0 \rightarrow \begin{cases} I_{max} \\ Z = R \end{cases}$$

$$f_1, f_2 \rightarrow \begin{cases} \frac{I_{max}}{\sqrt{2}} \\ Z = \sqrt{2} R \end{cases}$$

$$f_0 \rightarrow \cos \theta = 1$$

$$Z = \sqrt{R^2 + X^2} = \sqrt{2} R$$

$$\Rightarrow \underline{X = R}$$

$$f_1, f_2 \rightarrow Z = R \pm jX$$

from the curve,

$$X = X_L - X_C$$

$$X_L = 2\pi fL, \quad X_C = \frac{1}{2\pi fC}$$

(87)

$$f_1 \rightarrow X_C > X_L \Rightarrow X \rightarrow -ve.$$

$$f_2 \rightarrow X_L > X_C \Rightarrow X \rightarrow +ve.$$

For  $f_1$ :

$$f_1 \rightarrow Z = R - jX, \quad X = R.$$

$$\text{Impedance angle} = \tan^{-1}\left(-\frac{X}{R}\right) = -45^\circ$$

$$I = \frac{V \angle 0}{Z \angle -45^\circ} = \frac{V}{Z} \angle +45^\circ$$

$$\text{P.f. angle} = +45^\circ$$

$$\cos 45^\circ = \frac{1}{\sqrt{2}} \text{ lead}$$


For  $f_2$ :

$$f_2 \rightarrow Z = R + jX, \quad X = R.$$

$$\text{Impedance angle}, \tan^{-1}\left(\frac{X}{R}\right) = 45^\circ$$

$$\text{P.f. angle} = -45^\circ$$
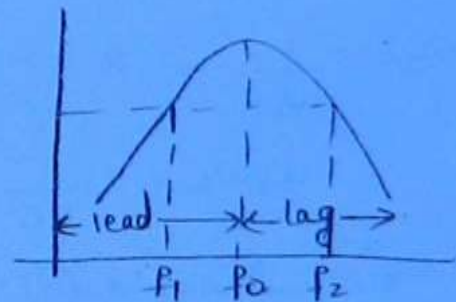
$$\cos(-45^\circ) = \frac{1}{\sqrt{2}} \text{ lag}$$



Note: Impedance angle & P.f. angle always have same magnitude but have opposite sign.

$$f_0 \leftrightarrow I_{\max}, \quad P = I_{\max}^2 R$$

$$f_1, f_2 \rightarrow \frac{I_{\max}}{\sqrt{2}}, \quad P' = \left( \frac{I_{\max}}{\sqrt{2}} \right)^2 R. \quad (88)$$

$$\therefore P' = \frac{I_{\max}^2 R}{2} = \frac{P}{2}$$

$$\boxed{P' = \frac{P}{2}}$$

$\therefore$  Power at  $f_1, f_2 = \frac{1}{2}$  power of  $f_0$ .

$\therefore f_1, f_2 \rightarrow$  half power frequencies

$$f_1: X_C > X_L, \quad X = R.$$

$$\frac{1}{\omega_1 C} - \omega_1 L = R \quad \text{--- (1)}$$

$$f_2 \rightarrow X_L > X_C, \quad X = R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R \quad \rightarrow (2)$$

$$(1) = (2) \quad \omega_1 \omega_2 = \frac{1}{LC} \quad \rightarrow (3)$$

$$\omega_0^2 = \frac{1}{LC} \quad \rightarrow (4)$$

$$(4) = (3)$$

$$\omega_0^2 = \omega_1 \omega_2$$

$$\boxed{\omega_0 = \sqrt{\omega_1 \omega_2}} \quad **$$

$$\boxed{f_0 = \sqrt{f_1 f_2}} \quad **$$

add eqn (1) & (2)

$$\frac{1}{C} \left[ \frac{1}{\omega_1} - \frac{1}{\omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$



$$\frac{1}{C} \left[ \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$L (\omega_2 - \omega_1) + L (\omega_2 - \omega_1) = 2R$$

Q9

$$\left( \begin{array}{l} \omega_1 \omega_2 = \frac{1}{LC} \\ L = \frac{1}{\omega_1 \omega_2 C} \end{array} \right)$$

\*\*

$$\begin{array}{l} B.W = \omega_2 - \omega_1 = \frac{R}{L} \text{ rad/s} \\ B.W = f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz} \end{array}$$

$R/L$   
 $f_2 - f_1$

5.)

$$Q = \frac{\omega_0 L}{R}$$

\*\*

$$= \frac{\omega_0}{(R/L)} \Rightarrow \begin{array}{l} Q = \frac{\omega_0}{\omega_2 - \omega_1} \\ Q = \frac{f_0}{f_2 - f_1} \end{array}$$

Objectives

1.  $R \uparrow$   $B.W \uparrow$   $f_1 \downarrow$   $f_2 \uparrow$ ,  $f_0 = \text{const.}$


2.  $Q = \frac{\omega L}{R} = \frac{X_L}{R} = \frac{V_L}{V}$ ,  $Q > 1$ ,  $X_L > R$ ,  $X_C > R$

\* In series resonance, always  $V_L > V \Rightarrow X_L > R$  &  $X_C > R$ .  
 $\therefore X_L = X_C$  at  $f_0$

$$f_1 = \frac{1}{2\pi LC} \left[ \sqrt{1 - \frac{R^2}{2L}} \right]$$

$$f_2 = \frac{1}{2\pi LC} \left[ \sqrt{1 + \frac{R^2}{2L}} \right]$$

By KVL,

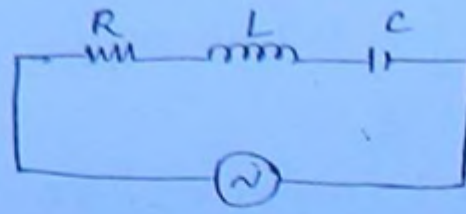

$$V = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

diff. wrt  $t$ .

(90)

$$V' = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C}$$

$\frac{1}{L}$

$$\boxed{\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{V'}{L}}$$

$\omega_2 - \omega_1$

$\omega_0^2 = 1/LC$

If a given diff. eqn is of the above form, then we can obtain BW &  $\omega_0$

coeff of  $\frac{di}{dt} = \omega_2 - \omega_1 = \frac{R}{L} = BW$

coeff of  $i = \frac{1}{LC} = \omega_0^2$

$\Rightarrow$

$$Q = \frac{\omega_0}{\omega_2 - \omega_1}$$

$$\left( D^2 + \frac{R}{L} D + \frac{1}{LC} \right) i = 0$$

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$\left. \begin{array}{l} \frac{d}{dt} = D \end{array} \right\}$$

$$\Rightarrow \omega_n^2 = \frac{1}{LC}$$

$\Rightarrow$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$2\zeta\omega_n = \frac{R}{L}$$

$$\frac{R}{2\omega_n L} = \frac{1}{2Q}$$

$$\text{Damping ratio} = \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$Q = \frac{1}{2\zeta} \sqrt{\frac{L}{C}}$$

But

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$


$\Rightarrow$  \*\*\*

$$\xi_1 = \frac{1}{2Q}$$

(211)

$$\frac{R}{2} \sqrt{\frac{C}{L}} = \frac{1}{2Q}$$

Q.

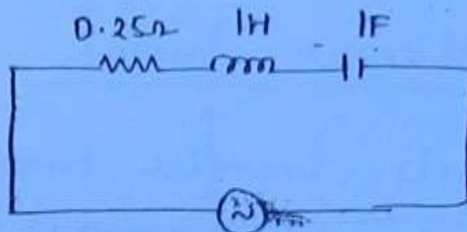

$$V(t) = 10 \sin \omega t$$

find

$$(i) f_0 = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{1 \times 1}} = \frac{1}{2\pi}$$

$$(ii) Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{0.25} \sqrt{\frac{1}{1}} = 4$$

$$(iii) BW = \frac{f_2 - f_1}{f_0} = \frac{1}{8\pi}$$

$$(iv) \xi_1 = \frac{1}{2Q} = \frac{1}{8}$$

$$(v) f_2 - f_1 = \frac{1}{8\pi} \quad \& \quad f_0^2 = f_1 f_2$$

$$\Rightarrow f_1 f_2 = \frac{1}{4\pi^2}$$

$$(f_1 + f_2)^2 - (f_2 - f_1)^2 = 4 f_1 f_2$$

$$(f_1 + f_2)^2 = \frac{1}{\pi^2} + \frac{1}{64\pi^2}$$

$f_1$




$$6. \quad I = \frac{V}{Z} = \frac{V}{R}$$

$$I = \frac{10/\sqrt{2}}{0.25} = 20\sqrt{2}$$


(92)

## Parallel Resonance.

Ques 1.

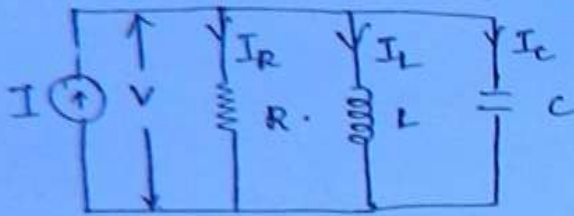
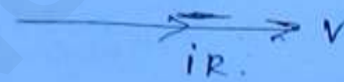
$$I = I_R \angle 0^\circ + I_L \angle -90^\circ + I_C \angle 90^\circ$$



$$I_L = I_C$$

$$\frac{V}{X_L} = \frac{V}{X_C} \Rightarrow$$

$$B_L = B_C$$

$$\frac{1}{\omega L} = \omega C \Rightarrow$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$\omega_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$$Y = G + j(B_C - B_L)$$

$$Y_{\min} = G$$

$$Z_{\max} = \frac{1}{Y_{\min}}$$

$$I_{\min} = \frac{V}{Z_{\max}}$$

5.  $I_R = I$

(active component of the current).

(93)



6. Net reactive current = 0.

7. Current flowing through inductor and capacitor greater than total current. This phenomena is called as current magnification.

8. Parallel resonant circuit is also called as Anti-resonant circuit.

9. In the parallel circuit at resonance if  $G=0$ , circuit behaves as Open circuit.

Case 2 :

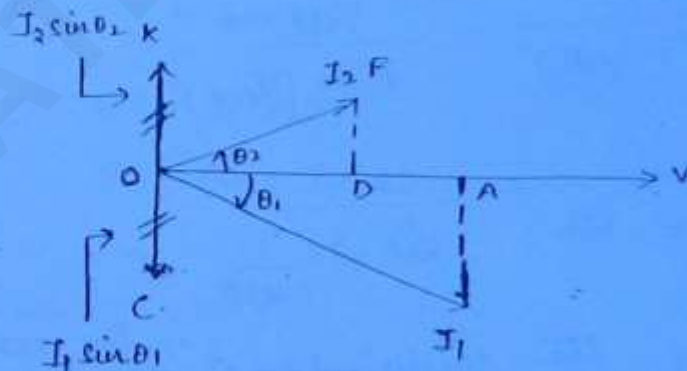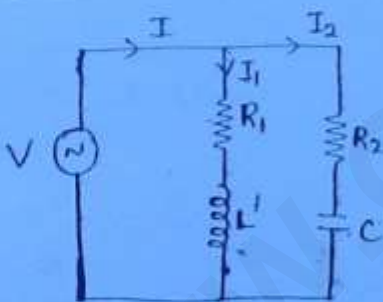

$I = I_1 \cos \theta_1 + I_2 \cos \theta_2$

$OA = I_1 \cos \theta_1$

$OC = AB = I_1 \sin \theta_1$

$OD = I_2 \cos \theta_2$

$OK = DF = I_2 \sin \theta_2$

$$B_L = B_C$$

$$\frac{X_L}{R^2 + X_L^2} = \frac{X_C}{R^2 + X_C^2}$$

(94)

$$\frac{\omega L}{R^2 + (\omega L)^2} = \frac{1/\omega C}{R^2 + (1/\omega C)^2}$$

→ ①

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_1^2 - L/C}{R_2^2 - L/C}}$$

$$\frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_1^2 - L/C}{R_2^2 - L/C}}$$

Resonance Condition for all frequencies

from eqn ① above.

$$\frac{\omega L}{R^2 + (\omega L)^2} = \frac{1/\omega C}{R^2 + (1/\omega C)^2}$$

$$\frac{1}{\frac{R_1^2}{\omega L} + \omega L} = \frac{1}{R_2^2 C \omega + \frac{1}{\omega C}}$$

Comparing the coefficients, ( $\because$  for resonance condition in the above eqn  $\forall f \Rightarrow$  it should be independent of  $\omega$ )

$$\omega \rightarrow L = R_2^2 C \Rightarrow R_2 = \sqrt{\frac{L}{C}}$$

$$\frac{1}{\omega} \rightarrow \frac{R_1^2}{L} = \frac{1}{C} \Rightarrow R_1 = \sqrt{\frac{L}{C}}$$

$$R_1 = R_2 = \sqrt{\frac{L}{C}}$$



$$Y = (G_1 + G_2) + j(B_c - B_L)$$



(95)

$$Y = \frac{R_1}{R_1^2 + X_L^2} + \frac{R_2}{R_2^2 + X_C^2}$$

$$I = VY$$

$$I = V \left[ \frac{R_1}{R_1^2 + X_L^2} + \frac{R_2}{R_2^2 + X_C^2} \right]$$


Case 3: TANK Ckt

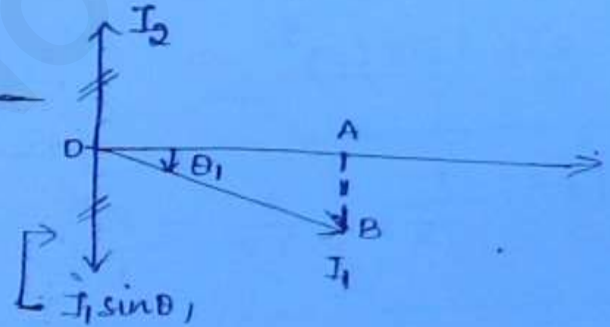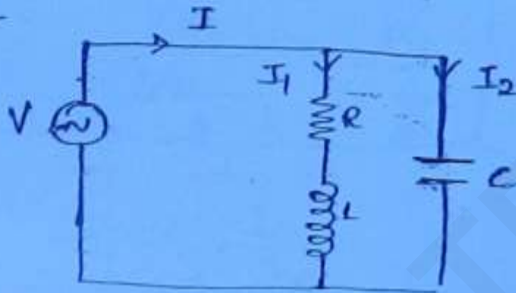

$$I = I_1 \cos \theta$$

$$OA = I_1 \cos \theta_1$$

$$OC = AB = I_2 \sin \theta_1$$

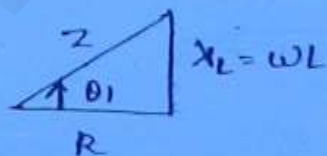

$$\sin \theta_1 = \frac{X_L}{Z_1}$$

$$\cos \theta_1 = \frac{R}{Z_1}$$

$$I_2 = I_1 \sin \theta_1$$

$$\frac{V}{X_C} = \frac{V}{Z_1} \frac{X_L}{Z_1}$$

$$Z_1^2 = X_L X_C = \frac{\omega L}{\omega C} = L/C$$

$$* * \left[ Z_1 = \sqrt{\frac{L}{C}} \right] \Omega$$

$$I = I_1 \cos \theta_1$$

$$I = \frac{V}{Z_1} \frac{R}{Z_1}$$

(96)

$$I = \frac{VR}{L/c}$$

$$I = \frac{V}{(L/Rc)}$$

$$Z_{DY} = \frac{L}{Rc} \Omega$$


Dynamic impedance.

$$Z_1^2 = R^2 + X_L^2$$

$$\frac{L}{C} = R^2 + (2\pi f_L)^2$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$
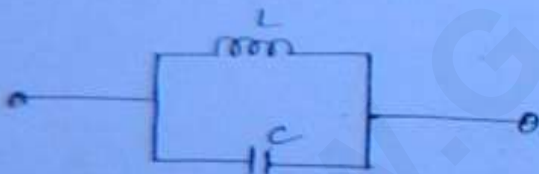
$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$



$$Z_{DY} = \frac{L}{Rc} = \infty$$

Ideal Tank ckt i.e.  $R=0$

Q-factor

$$Q = \frac{V_L \text{ (or)} V_C}{V}$$

for series.

for parallel resonant ckt

$$Q = \frac{I_L \text{ (or)} I_C}{I}$$

\*\*

$$Q = \frac{I_L}{I} = \frac{I_L}{I_R} = \frac{\text{Reactive component of current}}{\text{Active component of current.}}$$

$$Q = \frac{I_L}{R} = \frac{V/X_L}{V/R} = \frac{R}{X_L} = \frac{R}{\omega L}$$

for series

(97)

// resonance

$$\omega = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{R}{\omega L} = \frac{R}{\frac{1}{\sqrt{LC}} L} = \frac{R}{\frac{L}{\sqrt{LC}}} = \frac{R \sqrt{LC}}{L}$$

$$Q = \frac{1/X_L}{1/R} = \frac{B_L}{G}$$


$$\rightarrow Q = \frac{I_C}{I} = \frac{I_C}{I_R}$$

$$\rightarrow Q = \frac{V/X_C}{V/R} = \frac{R}{X_C} = \underline{\underline{R\omega C}}$$

For tank ckt:

$$Q = \frac{I_2}{I_1}$$
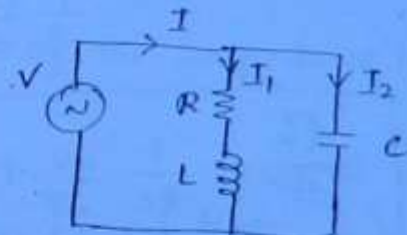
$$Q = \frac{V/X_C}{V/(L/RC)} = \frac{1/(\omega C)}{1/(L/RC)} = \frac{L/RC}{\omega L} = \frac{1}{\omega RC}$$



\*\*

$$Q = \frac{\omega L}{R}$$


for tank circuit - series




Series

(98)


Parallel

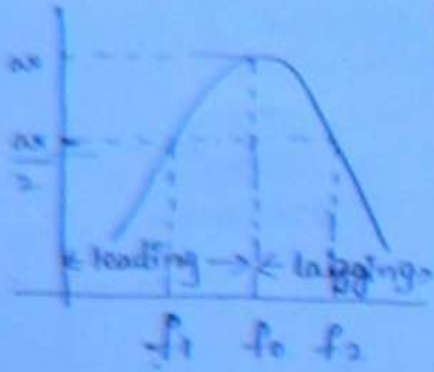

$$BW = f_2 - f_1$$

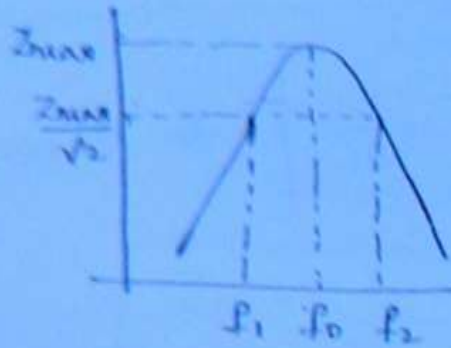

$$BW = f_2 - f_1$$

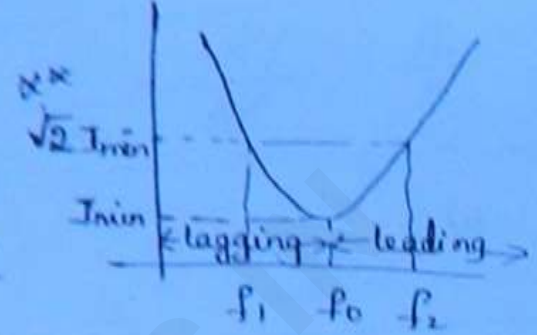


BW of C.F.

$$B_L = \frac{1}{2\pi f L}$$

$$B_C = 2\pi f C$$

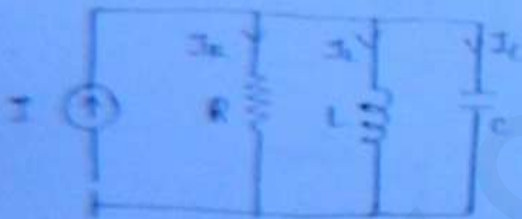Relation between damping factor and Q-factor



$$I = \frac{V}{R} + C \frac{dv}{dt} + \frac{1}{L} \int v dt$$

differentiate wrt t

$$I' = \frac{1}{R} \frac{dv}{dt} + C \frac{d^2v}{dt^2} + \frac{v}{L}$$

$\frac{1}{C}$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = \frac{I'}{C}$$

$$\omega_2 - \omega_1 = \frac{1}{RC}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$Q = \frac{\omega_0}{\omega_2 - \omega_1}$$

$$\frac{1}{RC} = \frac{\omega_0}{Q}$$

$$\left( D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V = 0 \quad \left\{ \begin{array}{l} \frac{d}{dt} = D \\ s^2 + 2\xi\omega_n s + \omega_n^2 = 0 \end{array} \right. \quad (99)$$


$$** \left[ \text{damping ratio} = \xi = \frac{1}{2R} \sqrt{\frac{L}{C}} \right] \quad \hookrightarrow \omega_n = \frac{1}{\sqrt{LC}}$$

$$** \left[ \xi = \frac{1}{2Q} \right]$$

$$\hookrightarrow 2\xi\omega_n = \frac{1}{RC}$$

where  $Q = R\sqrt{\frac{C}{L}}$  for parallel resonance

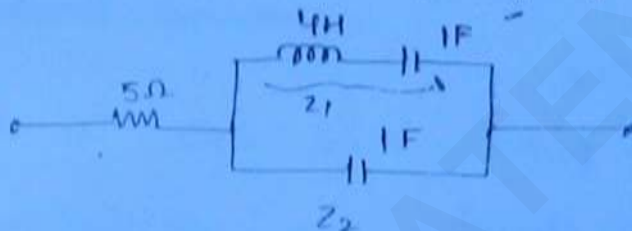Q. Find resonant frequency of the circuit shown.



(a)  $1/2 \text{ rad/s}$  (b)  $2 \text{ rad/s}$

(c)  $1 \text{ rad/s}$  (d)  $4 \text{ rad/sec}$

Sol.

Note :-

To find resonant frequency for any circuit,

→ i) find equivalent impedance

→ ii) Equate imaginary part of the impedance to zero.


$$Z_1 = j(\omega L - \frac{1}{\omega C}) = j\left(\omega L - \frac{1}{\omega C}\right) = j\left(4\omega - \frac{1}{\omega}\right)$$

$$Z_2 = \frac{-j}{\omega}$$

$$Z_1 // Z_2 \Rightarrow Z_{eq} = \frac{j\left(4\omega - \frac{1}{\omega}\right) \left(\frac{-j}{\omega}\right)}{j\left(4\omega - \frac{1}{\omega}\right) + \frac{-j}{\omega}} = \frac{\frac{1}{\omega} \left(\frac{1}{\omega} - 4\omega\right)}{\frac{1}{\omega} (4\omega^2 - 1 - 1)}$$

$$\Rightarrow \left(4\omega - \frac{1}{\omega}\right) \frac{1}{\omega} = 0 \Rightarrow \omega = 1 \text{ rad/sec}$$

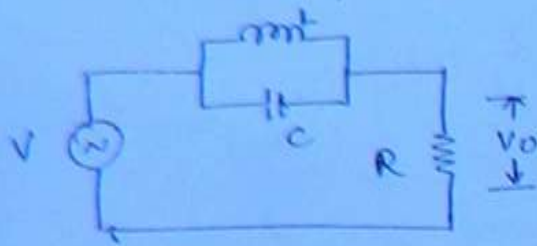Q. Find the value of  $V_0$  at resonance.




(a)  $V$  (b)  $0$

(c)  $V/2$  (d)  $\infty$

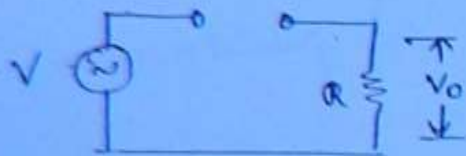(100)

sol. The given LC ckt is an ideal tank ckt.

$\therefore$  Dynamic impedance  $Z_{DY} = \infty$ .



$\Rightarrow$

current in the ckt  $= 0$

$$i = 0$$

$$\Rightarrow V_0 = 0$$

A parallel RLC circuit have.

$$BW = 1 \text{ kHz} \quad \& \quad C = 0.1 \mu\text{F}$$

Find effective resistance of the circuit.

$$BW = \omega_2 - \omega_1 = \frac{1}{RC} \text{ rad/s}$$

$$\Rightarrow f_2 - f_1 = \frac{1}{2\pi RC}$$

BW in Hz  
convert to 'f'

$$R = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 10^3} = \frac{10^4}{2\pi}$$



\* For conventional, Thevenin's & Norton are very important -

(101)


## THEOREMS.

→ when network is having several nodes, meshes & sources, the response in any element can be obtained by using theorems

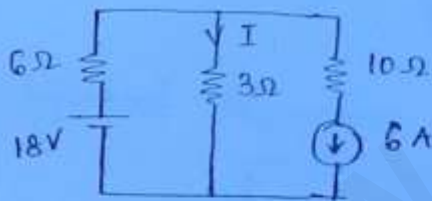
### Superposition theorem

In any linear bidirectional circuit having more number of sources the response in anyone of the elements is equal to algebraic sum of the responses caused by individual sources, while the rest of the sources are replaced by its internal resistance.

Q. Find the value of  $i$  using superposition theorem




Case i, (18V)

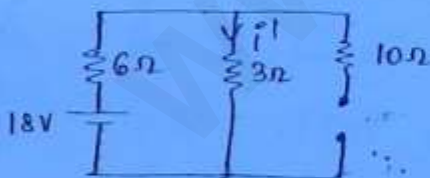

$$i' = \frac{18}{9} = 2A$$


Case ii, (6A)

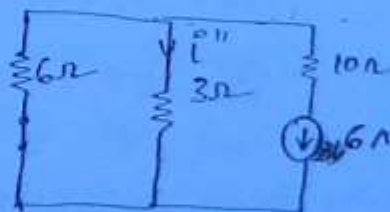

$$i'' = \frac{-6 \times 6}{9} = -4A$$

$$i^2 \quad i' + i'' = 2 - 4 = -2A$$

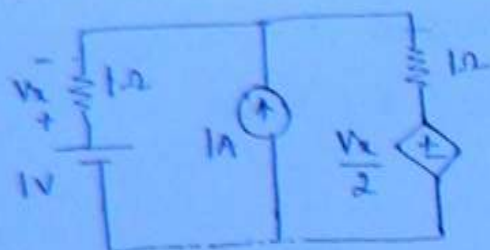
Q. Find the value of  $V_x$  by using superposition theorem.



(102)

NOTE: while applying superposition theorem, dependant source remains same as the original circuit.

Case i 1V source

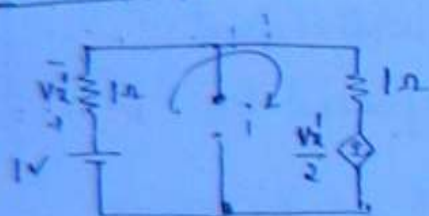


$$i = \frac{1 - V_x/2}{1+1}$$

$$2i = 1 - \frac{V_x}{2}$$

$$V_x' = 1 \times 1 = 1$$

$$V_x = 2/5 \text{ V}$$

Case ii

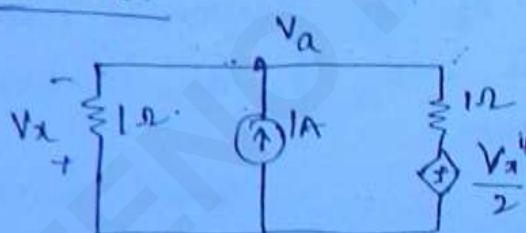

$$V_a + V_a - \frac{V_x''}{2} = 1$$


$$V_a = -V_x''$$

$$V_x'' = -2/5 \text{ V}$$

$$V_x = V_x' + V_x''$$

$$V_x = 0 \text{ V}$$

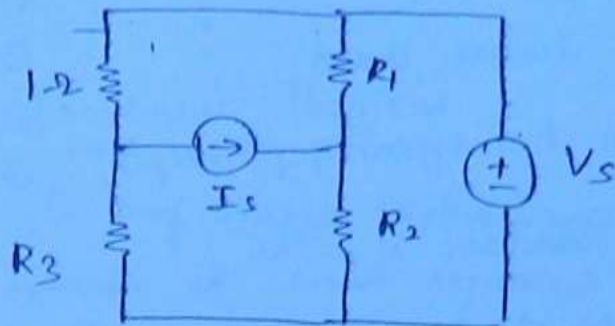In the circuit shown, power dissipation in the  $1\Omega$  resistor is  $546 \text{ W}$  when voltage source is acting alone & power dissipation in  $1\Omega$  resistor is  $1 \text{ W}$  when current source is acting alone. Find total power dissipation in  $1\Omega$  resistor.



103

Find:

$$P_1 = I_1^2 R \quad , \quad P_2 = I_2^2 R$$

$$I_1 = \sqrt{\frac{P_1}{R}} \quad I_2 = \sqrt{\frac{P_2}{R}}$$

total  $I = I_1 + I_2$  } total power dissipation =  $I^2 R$

$$R = 1 \Omega$$

$$I = \sqrt{P_1} + \sqrt{P_2}$$

$$P = (\sqrt{P_1} + \sqrt{P_2})^2 \cdot 1 \Omega = (\sqrt{576} + \sqrt{1})^2$$


$$P = 625 \text{ W}$$

General Expression for  $R = 1 \Omega$  total power dissipation

$$P = (\pm \sqrt{P_1} \pm \sqrt{P_2})^2$$

★  
Q.

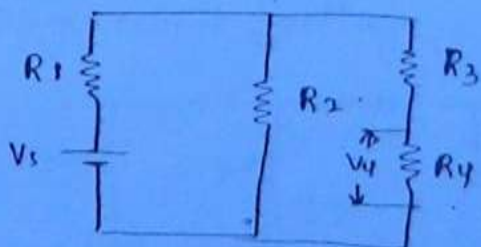In The circuit shown, if source voltage is increased by 10%. Find change in power of  $R_4$  resistor.



(a) 10% (b) 20%

(c) 21% (d) 30%

$$\frac{V_{R_4}}{R_3 + R_4} = \frac{V + 0.1V}{1.1 \times 1.21}$$



Note: When circuit is having linear and bidirectional elements, based on homogeneity principle, if excitation is multiplied with constant  $K$ , the response of each element is also multiplied with const.  $K$ .

$$P_y = \frac{V_y^2}{R_y}$$

(104)

$$P_y = \frac{(1.1 V_y)^2}{R_y}$$


$$\therefore \uparrow 10\% = 1 + 0.1 = 1.1$$

$$= 1.21 \frac{V_y^2}{R_y}$$

$$\therefore \text{increase} = 21\%$$

Find the value of  $I$  when  $V_1 = 10V$  &

$$V_2 = -4V$$

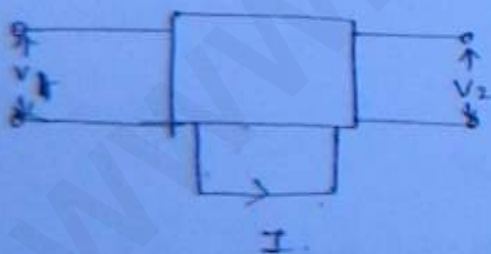

$V_1$	$V_2$	$I$
2	0	3
0	4	-2

$$V_1 = 2V$$

$$I = 3A$$

$$V_1 = 10V$$

$$I' = 3 \times 5 = 15A$$

$$= 2 \times 5$$

$$V_2 = 4$$

$$I = -2$$

$$V_2 = -4$$

$$I = 2A$$


$$I = 15 + 2 = 17A$$

## Thevenin's Theorem

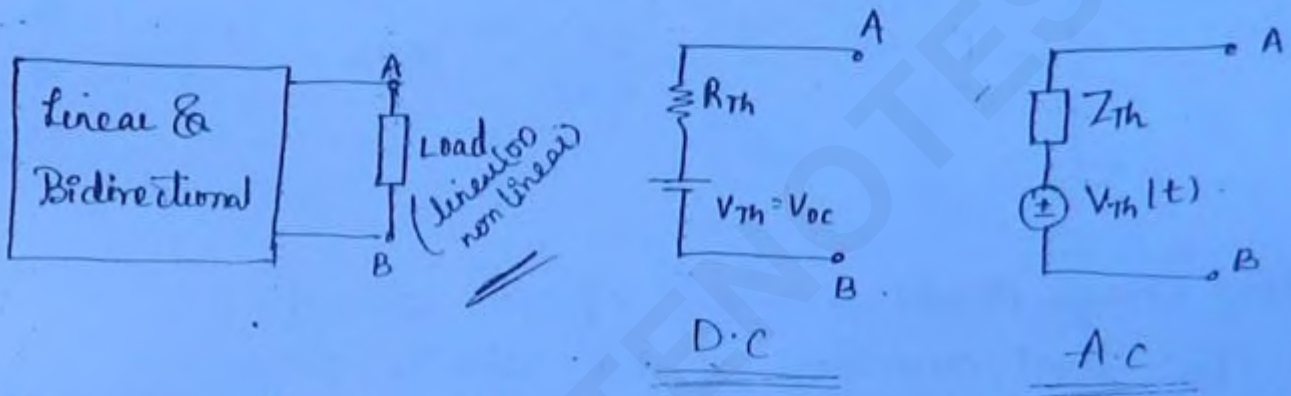
(105)

→ In any linear bidirectional circuit having more number of elements it can be replaced by single equivalent circuit consisting of equivalent voltage ( $V_{th}$ ) in series with eq. resistance ( $R_{th}$ ).


⇒ By using Thevenin's theorem load current can be calculated either in linear or non-linear load.



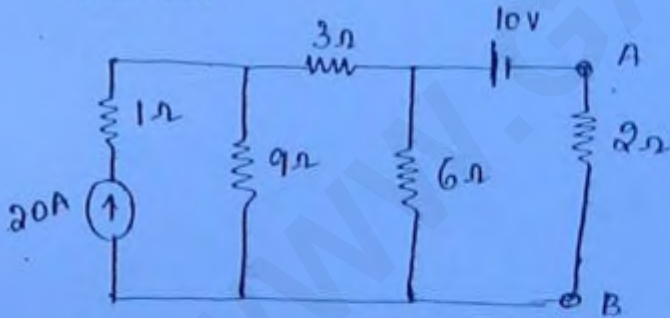Q. Find current flowing through  $2\Omega$  resistor using Thevenin's Theorem.



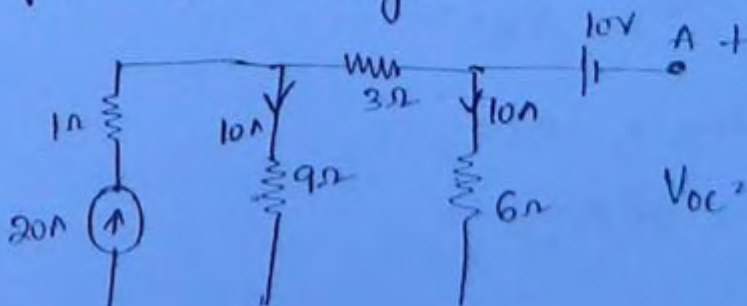Case i, ( $V_{th}$ ) ∴ disconnect the load resistor and find open circuit voltage.



KVL


$$-60 + 10 + V_{th} = 0$$

$$\underline{V_{th} = 50}$$


Case (2) ( $R_{Th}$ ).

106

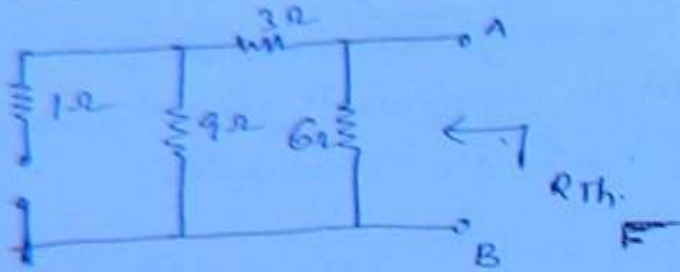Deactivate all independent sources and find equivalent resistance at load terminals.



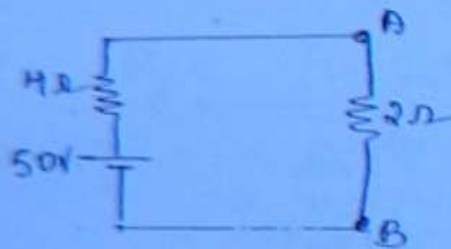
$$R_{Th} = \frac{12 \times 6}{12+6} + 3 = 4 \Omega$$




$$\Rightarrow I = \frac{50}{4+2} = 8.3 A$$

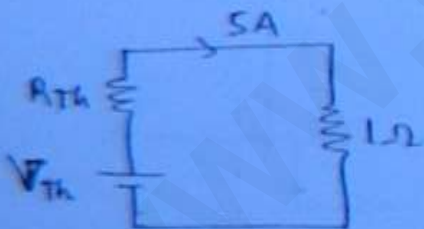A battery charger drives a current of 5A when it is connected to load resistance of  $1 \Omega$ . When the same battery charger is used for charging of ideal 2V battery at 7A rate find  $V_{Th}$  &  $R_{Th}$ .


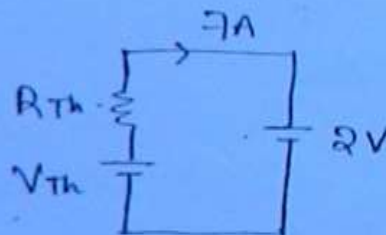
$$V_{Th} = 5(R_{Th} + 1) \rightarrow (1)$$



$$7 = \frac{V_{Th} - 2}{R_{Th}}$$

$$7R_{Th} = V_{Th} - 2$$

$$V_{Th} = 5(1.5 + 1)$$

$$V_{Th} = 12.5 V$$



$$7R_{Th} = 5R_{Th} + 5 - 2$$

$$\therefore R_{Th} = 1.5 \Omega$$




Q. A complex network of  $N$  is connected to load resistor of  $R$ . power dissipation in the resistor is  $P$  watt. When two identical complex networks are connected to load resistor. Find power dissipation in the load.

107

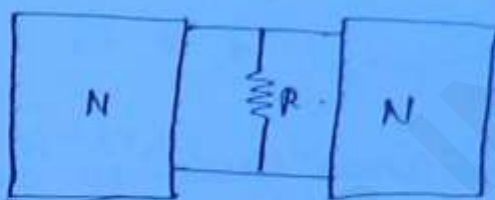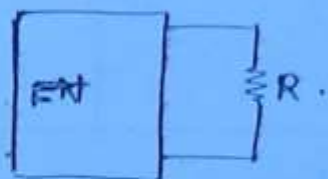

- (a)  $2P$  (b)  $4P$  (c)  $P$  to  $4P$  (d)  $3P$



Case 1

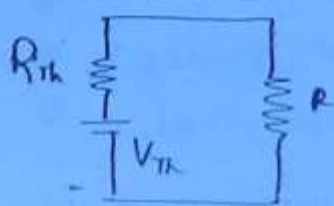



$$I = \frac{V_{th}}{R_{th} + R}$$

$$P = I^2 R$$

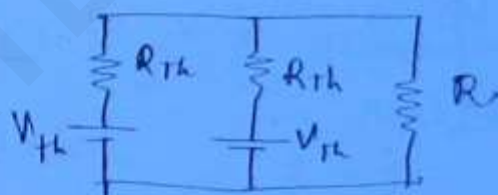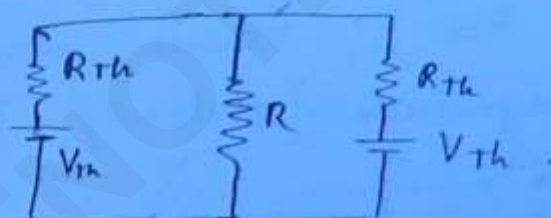
$$P = \left( \frac{V_{th}}{R_{th} + R} \right)^2 R \rightarrow (1)$$




now apply theorem

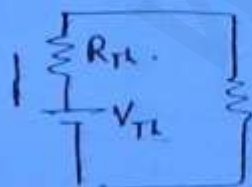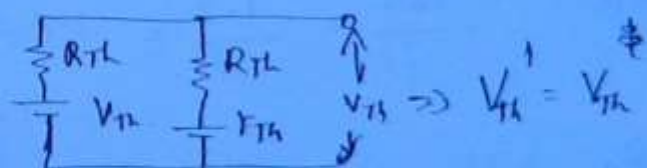

$$R_{th} = R_{th} / 2$$

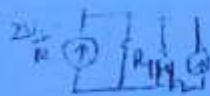
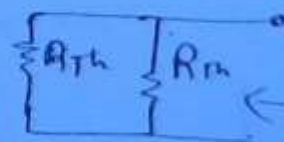
$$\frac{V_{th}}{R_{th} + R} = \frac{V_{th}}{R_{th} + R}$$




$$R_{th} = \frac{R_{th}}{2}$$

$$P = I^2 R = \left( \frac{2V_{th}}{R_{th} + 2R} \right)^2 R \rightarrow (2)$$

$$I = \frac{V_{th}}{R_{th} + R}$$


Find  $V_{Th}$  &  $R_{Th}$  wrt A & B.

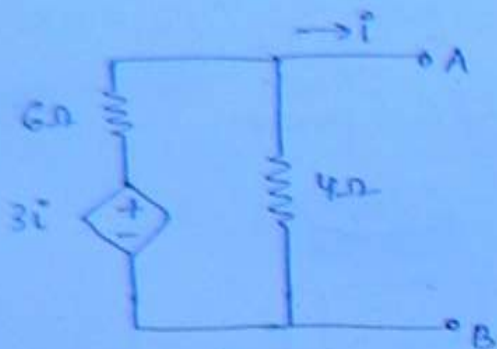

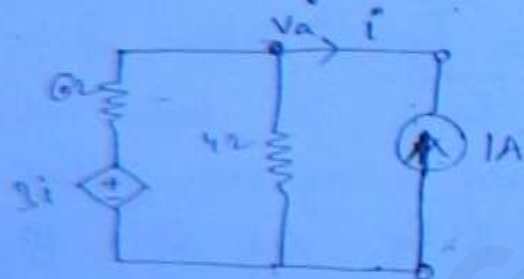(108)

Ques In the above circuit no independent source is present. Hence  $V_{Th} = 0$

or finding  $R_{Th}$ , assume either voltage/current source of any magnitude [preferably 1] across load terminals.



$$I_s = -1A$$


$$\frac{V_a - 3i}{6} + \frac{V_a}{4} = 1$$

$$V_a = 1.2V$$

$$V_{ab} = V_a = 1.2V$$


$$R_{Th} = \frac{V_{ab}}{I_s} = \frac{1.2}{1} = 1.2\Omega$$

Find  $R_{Th}$  wrt A & B.

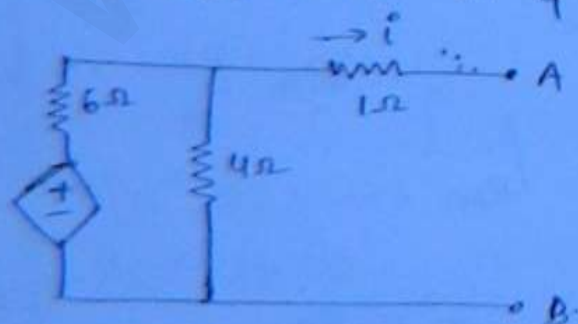

Here it is easy to solve if we connect to voltage source across terminal.

(109)

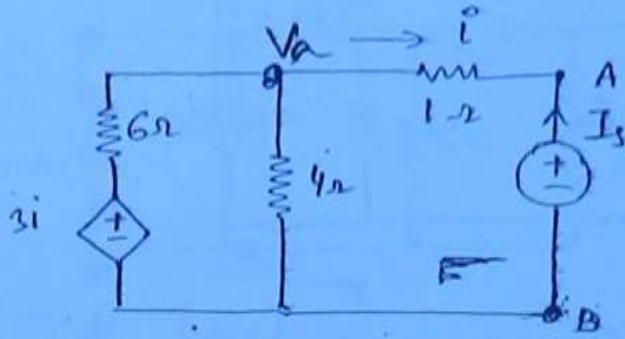

$$0 = \frac{V_1 - 3i}{6} + \frac{V_1}{4} + \frac{V_1 - 1}{1}$$

$$i = V_1 - 1$$

$$\frac{V_1 - 3V_1 + 3}{6} + \frac{V_1}{4} + \frac{V_1 - 1}{1} = 0$$


$$V_1 = 6/11 \Rightarrow i = \frac{-5}{11}$$

$I_s \rightarrow$  source current

$$I_s = -i = -\left(\frac{-5}{11}\right) = 5/11$$


$$R_{Th} = \frac{V_{ab}}{I_s} = \frac{1}{5/11} = 2.2 \Omega$$

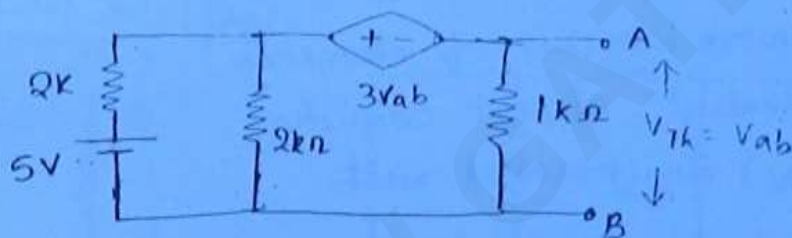Q. Find  $V_{Th}$  &  $R_{Th}$  w.r.t. A & B.



Gate, Common data ques  
linked data  
\* Thevenin &  
max power th.  
& imp.

Case i) ( $V_{Th}$ )

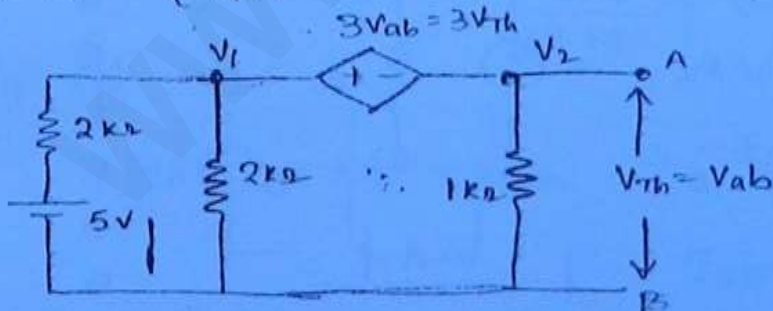



$$\frac{V_1 - 5}{2k} + \frac{V_1}{2k} + \frac{V_2}{1k} = 0 \quad \& \quad V_1 - V_2 = 3V_{Th}$$

$$\frac{1}{2} V_{Th} - 5 + \frac{1}{2} V_{Th} + V_{Th} = 0 \quad \& \quad V_2 = V_{Th}$$



102 (2) ( $R_{Th}$ )

(1/0)

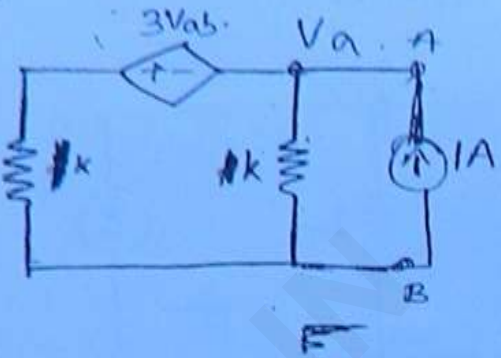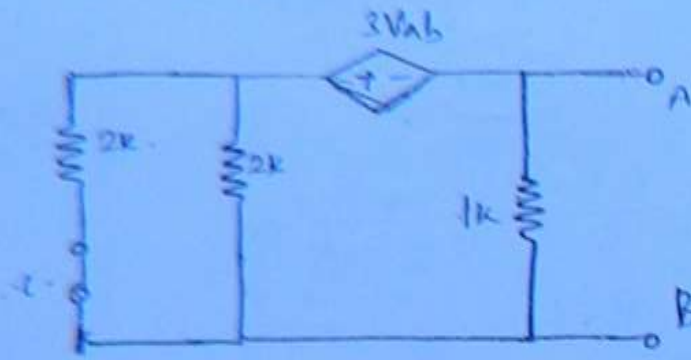

$$\frac{V_a + 3V_{ab}}{1k} + \frac{V_a}{1k} = 1$$




$$V_a = V_{ab}$$

$$V_{ab} = 200V$$


$$R_{Th} = \frac{V_{ab}}{I_s} = \frac{200}{1} = 200\Omega$$
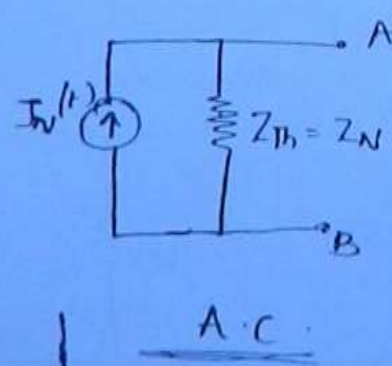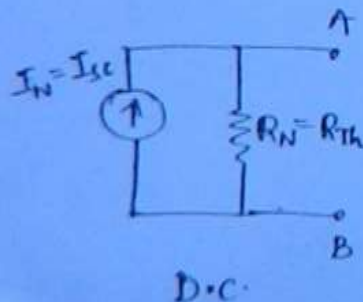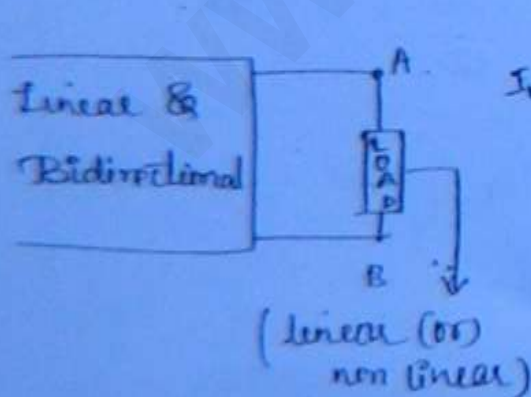
## orton's Theorem

In any complex network having more number of elements, can be replaced by single equivalent circuit consisting of equivalent current source ( $I_N$ ) in parallel with a resistance ( $R_N$ ).



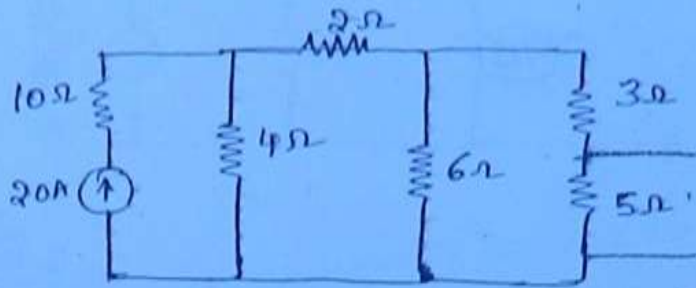
Q. Find current flowing through  $5\Omega$  resistor using Norton's theorem.



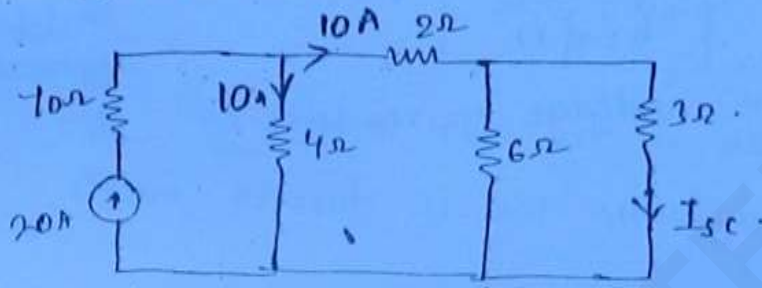(11)

Case i, ( $I_{sc}$ ).


Replace the load resistor by short circuit and find short circuit current.



$$I_{sc} = \frac{10 \cdot 6}{6+3}$$


$$I_{sc} = \frac{60}{9} = \frac{20}{3} \text{ A}$$

Case ii, ( $R_{th}$ )

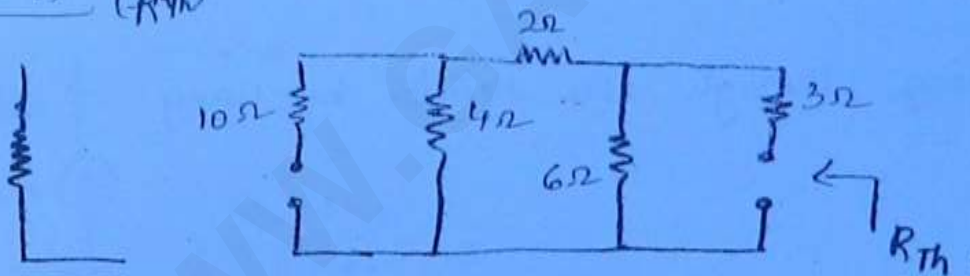

$$R_{th} = 3 + \frac{4 \times 6}{4+6} = 6\Omega$$


Eq. ckt

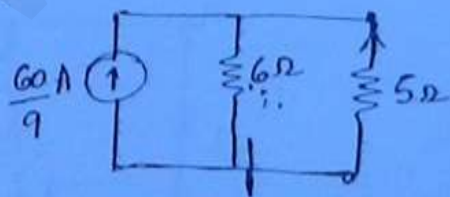


$$\Rightarrow I_{5\Omega} = \frac{60}{9} \cdot \frac{6}{6+5}$$

$$I_{5\Omega} = \frac{40}{11} \text{ A}$$

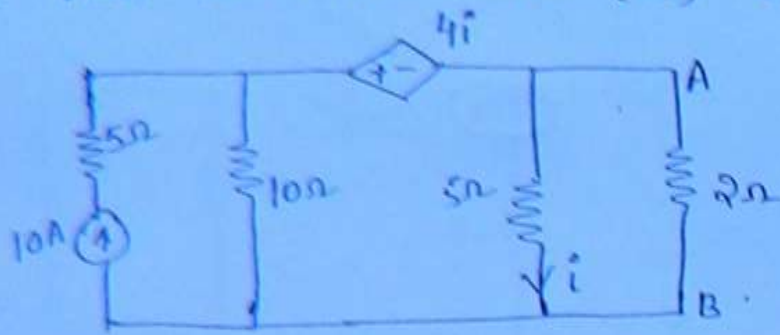Q. Find short ckt current ( $I_{sc}$ ) wrt A & B.



(112)

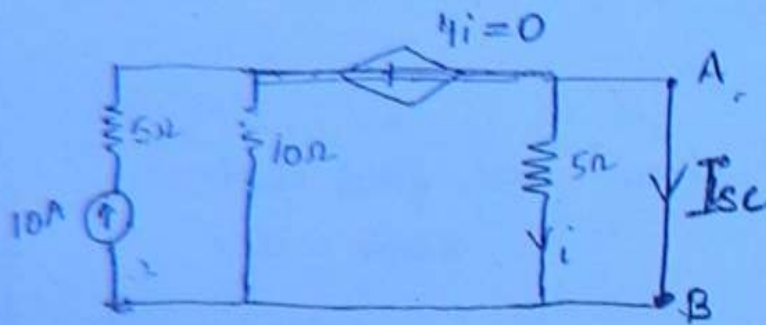


∴ AB is short ckted,

$$i = 0$$

$$4i = 0$$

⇒ voltage source is 1S.C.

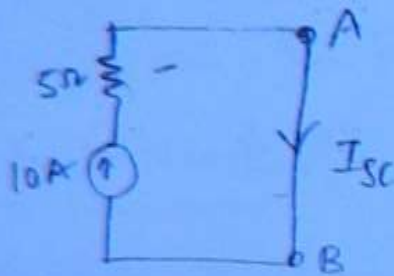

$$I_{sc} = 10A$$

Find current flowing through 4Ω resistor by using the following data.


V	0	60
I	10	0

$$I_{sc} = \frac{V_{oc}}{R_{th}}$$

$$I_{sc} = 10A$$

$$V_{oc} = 60V$$

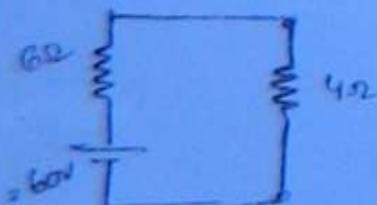
$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{60}{10} = 6\Omega$$



$$i = \frac{60}{6+4} = 6A$$



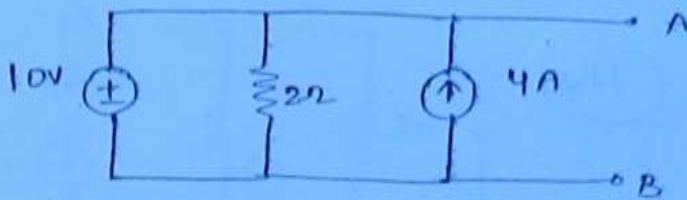Q. Obtain thevenin's & norton's eq. ckt wrt. A & B.




(113)

Soln.

$$R_{Th} = 2\Omega$$

$$V_{Th} = 10V$$


For  $I_{sc}$

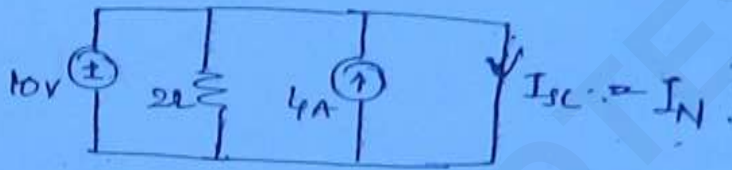


Note:

In the above ckt, it is not possible to find  $I_N$ , since above circuit is not satisfying KVL.

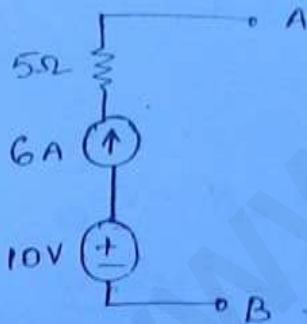
Q. Develop thevenin's & norton's eq. wrt. A & B.



Soln.

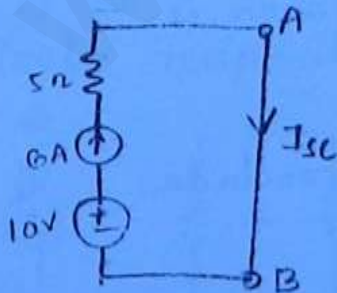


$$I_{sc} = 6A$$

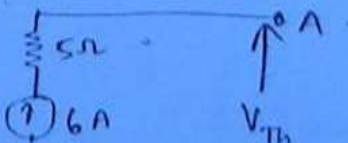

Note: For the 2<sup>nd</sup> ckt, it isn't possible to develop thevenin's eq. ckt since the ckt is not satisfying KVL.

## reciprocity theorem.

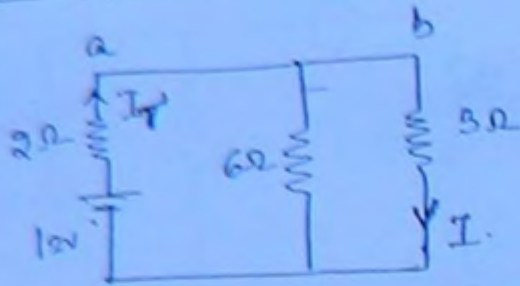


(1/4)

$$R_{eq} = 2 + \frac{6 \times 3}{1} = 4\Omega$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{12}$$

$$I_T = \frac{12}{4} = 3A$$

$$I = \frac{3 \times 6}{6+3} = 2A$$

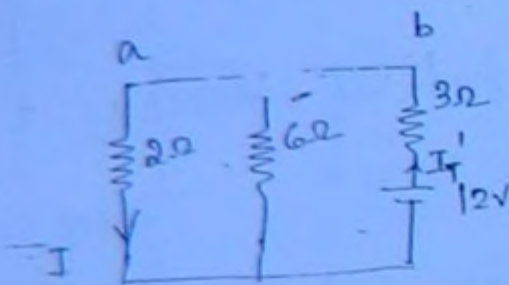

$$R_{eq}' = 3 + \frac{6 \times 2}{6+2}$$

$$I_T' = \frac{12}{R_{eq}'}$$

$$I = I_T' \frac{6}{6+2}$$


$$I = 2A$$

$$\Rightarrow \frac{\text{Response}}{\text{Excitation}} = \frac{2}{12}$$

In the above ckt after interchanging position of response and excitation, the ratio of response to excitation is const. Hence, above network satisfies reciprocity.

Using Reciprocity theorem, it is possible to conclude whether network is linear or non linear.

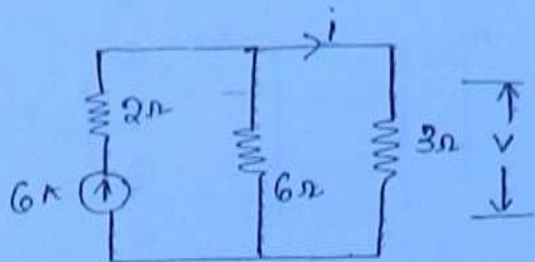Q. - Verify reciprocity th. for the circuit shown.



(115)


$$\frac{18 \times 2}{27}$$

Sol.

$$i = \frac{6 \times 6}{6+3} = 4A$$

$$V = 4 \times 3 = 12V$$
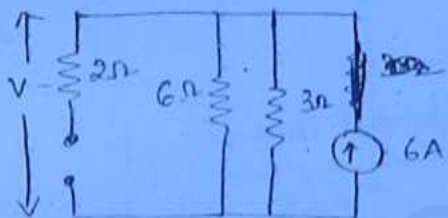
$$\frac{R_{es}}{E_{xi}} = \frac{12V}{6A} = 2$$



Current source when interchanged, should be connected in parallel.


$$i_{6\Omega} = \frac{6 \times 3}{9} = 2A$$

$$V_{6\Omega} = 2 \times 6 = 12V$$

$$V = V_{6\Omega} = 12V$$


$$\frac{R_{es}}{E_{xi}} = \frac{12}{6} = 2$$

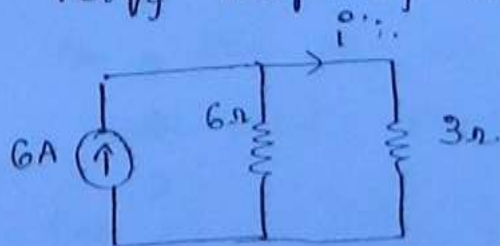Q. Verify reciprocity theorem of the circuit shown.



$$\frac{6 \times 6}{9} = 4A$$

$$i = \frac{6 \times 6}{6+3}$$

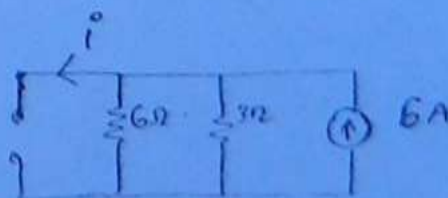



In the above 2 problems.

(116)

$$\frac{Res.}{Exc} = \frac{i}{V_s} \text{ mho}$$

$$\frac{Res}{Exc} = \frac{V}{I_s} \rightarrow \Omega$$

$$\frac{Res}{Exc} = \frac{I}{I_s}$$


$$\frac{Res}{Exc} = \frac{V}{V_s}$$

}  $\rightarrow$  No unit

To ~~apply~~ the reciprocity Theorem, unit of response excitation should be either mho ( $\infty$ )  $\Omega$ .

while applying reciprocity theorem circuit should consist of only one independent source.

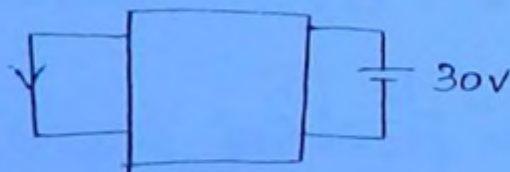
When given network satisfies reciprocity find the value of  $i$ .




$$const. = \frac{Res}{Exc} = \frac{2}{10} = \frac{I}{30}$$

$$I = 6A$$

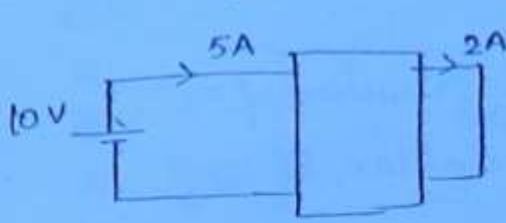
Q. When given n/w satisfies reciprocity find the value of  $i$ .



(117)

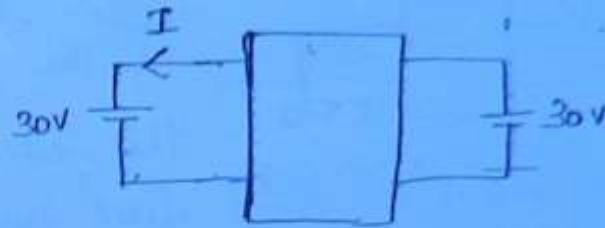

Case i) (30V)

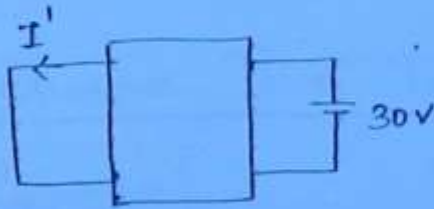

$$\frac{R_{th}}{E_{th}} = \frac{2}{10} = \frac{I'}{30}$$

$$I' = 6A$$

Case 2 (20V)




$$\frac{5}{10} = \frac{-i''}{30}$$

$$i'' = -15A$$

$$I = I' + I'' = 6 - 15 = -9A$$

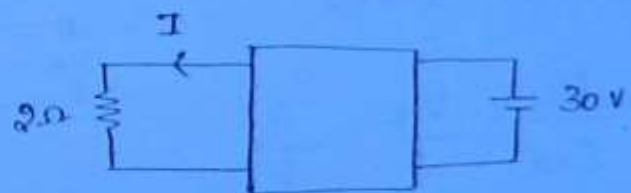Q. When given network satisfies reciprocity find the value of  $i$ .




Sol. Here we use norton eq. coz 2A branch is short ckted. Hence to find  $i$  we go for norton eq.

Case i) ( $I_{sc}$ )



$$\frac{2}{10} = \frac{I_{sc}}{30}$$

Case (2) ( $R_{Th}$ )

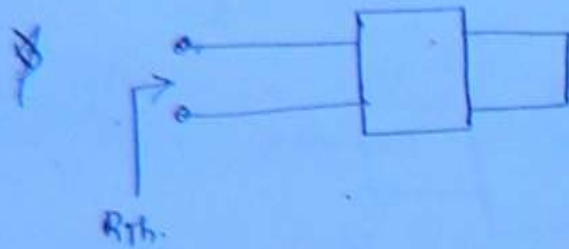


(118)

The physical connections of this circuit is similar to the first one.


$$\therefore R_{Th} = \frac{10V}{5A} = 2\Omega$$

Eq. ckt

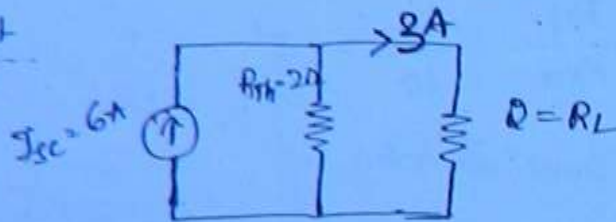

$$\therefore I_{2\Omega} = 3A$$

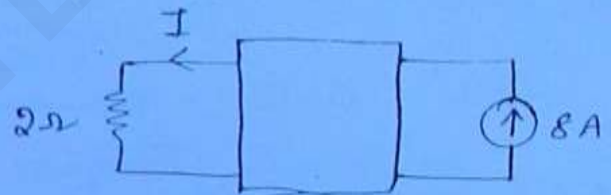when given network satisfies the reciprocity, find the value of  $i$ .




Case (1) ( $V_{Th}$ )


$$\frac{5}{4} = \frac{8}{V}$$

$$\frac{R_{es}}{E_{xc}} = \frac{V_{Th}}{8} = \frac{4}{5}$$

$$V_{Th} = \frac{32}{5}V$$

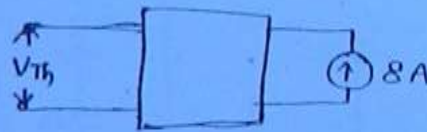


Case (2) ( $R_{Th}$ )

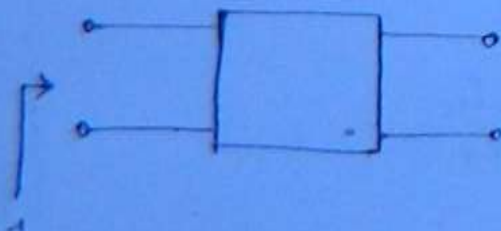

$$R_{Th} = \frac{10}{5} = 2\Omega$$




Ex.

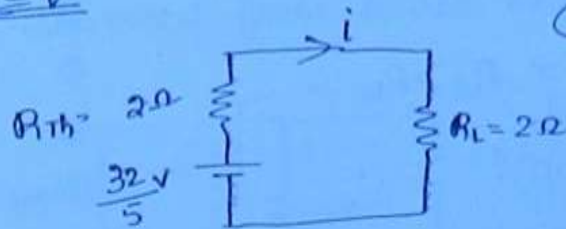

$$I = \frac{32/5}{2+2}$$

$$i = \frac{8}{5} \text{ A} = 1.6 \text{ A}$$

## Maximum Power Transfer theorem.

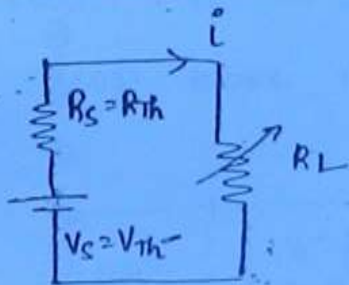

$$I = \frac{V_S}{R_S + R_L}$$

$$P_L = I^2 R_L$$

$$= \left( \frac{V_S}{R_S + R_L} \right)^2 \cdot R_L \rightarrow (1)$$

differentiate eqn (1) wrt  $R_L$  & equate it to zero.

$$\Rightarrow R_L = R_S$$

$$P_{\max} = \frac{V_S^2}{(R_S + R_L)^2} \cdot R_L$$


\*\*

$$P_{\max} = \frac{V_S^2}{4R_L}$$

$$\eta = \frac{O/P}{I/P} \times 100 \Rightarrow \frac{I^2 R_L}{I^2 (R_L + R_S)} \times 100$$

\*\*
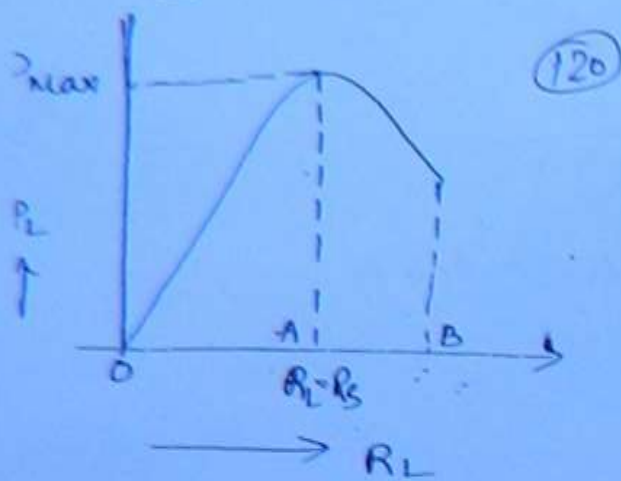
$$\eta = \frac{R_L}{R_L + R_L} \times 100 = 50\%$$






1)  $OA \rightarrow R_S > R_L$   
 $\eta < 50\%$

2)  $A \rightarrow R_L = R_S$   
 $\eta = 50\%$

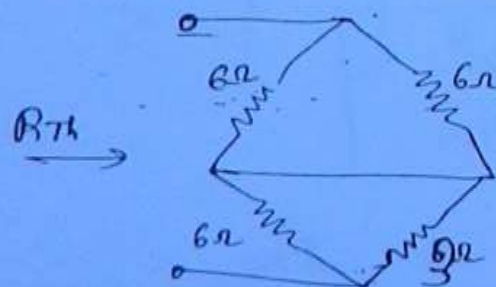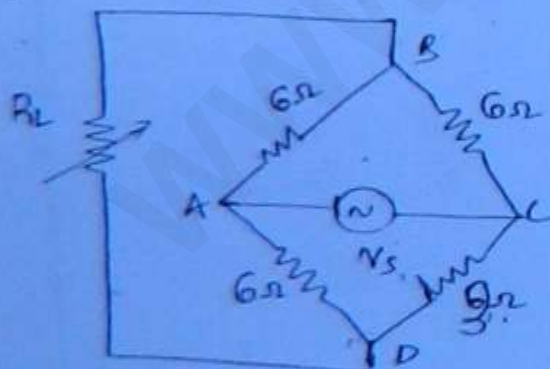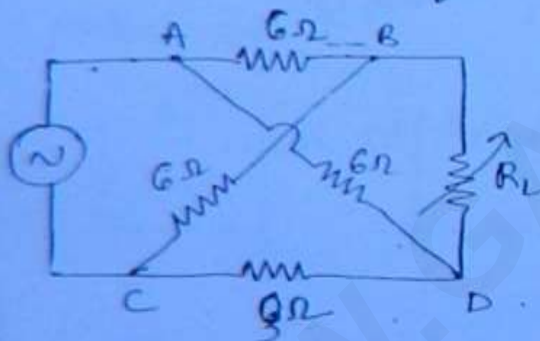3)  $AB \rightarrow R_L > R_S$   
 $\eta > 50\%$


In the circuit shown, at what value of  $R_L$  power delivered from source to load is maximum?



$R_{Th} = 3 + 2 = 5\Omega$

$R_L = R_{Th} = 5\Omega$

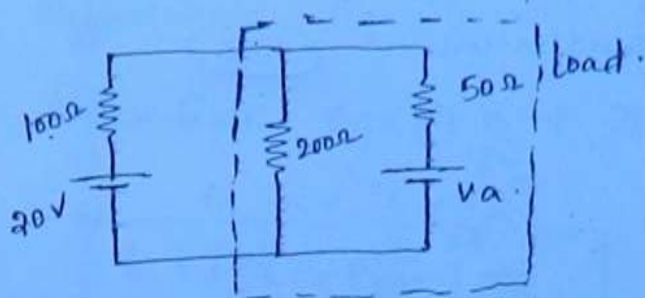
\*Q. In the circuit shown, at what value of  $V_a$ ; power delivered from source to load is maximum. (12)



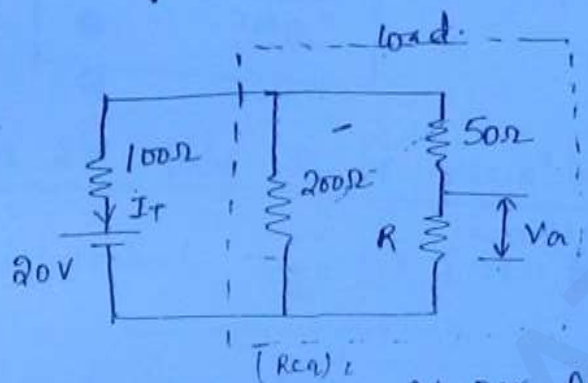- (a) 7.5V (b) 10V  
(c) 15V (d) 0V

Soln.

Here  $V_a$  is nothing but voltage drop across a resistor.



$$(Req)_L = \frac{200(50+R)}{200+50+R}$$


as per MPT  $Req = 100\Omega$

$$Req_L = R_s = 100$$

$$100 = \frac{200(50+R)}{250+R} \Rightarrow R = 150\Omega$$

$$I_T = \frac{20}{R_s + (Req)_L} = \frac{20}{100 + 100} = \frac{1}{10}$$

$$V_a = \frac{I_T}{2} \cdot R = 7.5V$$

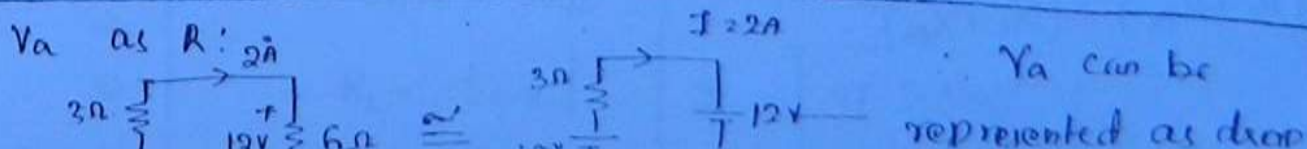


$V_a$  can be represented as drop



11

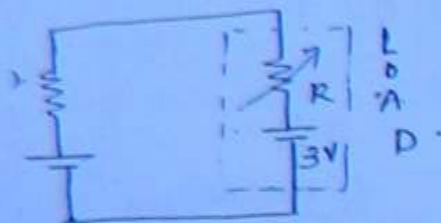In the circuit shown at what value of  $R$ , the power delivered from source to load is maximum. (122)



Handwritten calculations for problem 11:

$$I = \frac{10}{2 + 2} = 2.5 \text{ A}$$


$$I = \frac{10 - 3}{2 + R} = 2.5 \Rightarrow R = 0.8 \Omega$$

$$(R_{eq})_L = R_S = 2$$

$$I = \frac{10}{R_S + (R_{eq})_L} = \frac{10}{2 + 2} = 2.5 \text{ A}$$

$$I = \frac{10 - 3}{2 + R} = 2.5 \Rightarrow R = 0.8 \Omega$$
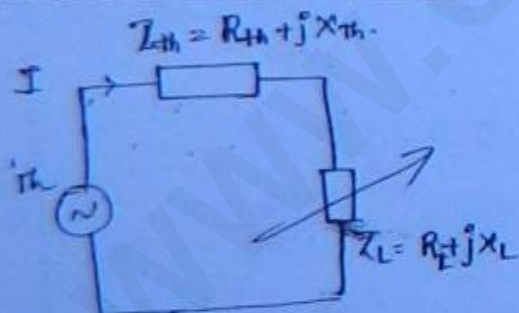
### Maximum Power Transfer Theorem (A.C.)



$$I = \frac{V_{Th}}{(R_{Th} + R_L) + j(X_{Th} + X_L)}$$

$$I = \frac{V_{Th}}{\sqrt{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}}$$

$$P_L = I^2 R_L$$

$$P_L = \frac{V_{Th}^2 R_L}{(R_L + R_{Th})^2 + (X_L + X_{Th})^2} \rightarrow \textcircled{1}$$

★ Case 1: Both  $R_L$  &  $X_L$  are variable. (123)

- Differentiate eqn ① wrt  $R_L$  and equate it to zero.
- Differentiate eqn ① wrt  $X_L$  and equate it to zero.

$$R_L + jX_L = R_{Th} - jX_{Th}$$

$$Z_L = Z_{Th}^*$$

$$P_{max} = \frac{V_{Th}^2}{4R_L}$$

$$\eta = 50\%$$

Case 2: Only  $R_L$  is variable. ( $X_L = \text{constant}$ )

- Differentiate eqn ① wrt  $R_L$  & equate it to zero

$$R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$$

$$\eta > 50\%$$

$$\text{Ex } R_L > R_{Th}$$

$$\eta = \frac{R_L}{R_L + R_{Th}} \times 100 > 50\%$$

★ Case 3:  $R_L$  is variable ( $X_L = 0$ )

$$P_L = \frac{V_{Th}^2 R_L}{(R_L + R_{Th})^2 + X_{Th}^2} \rightarrow \textcircled{2}$$


- differentiate eqn ② wrt  $R_L$  and equate it to zero.

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2}$$

$$R_L = |Z_{Th}|$$


$$\eta > 50\%$$

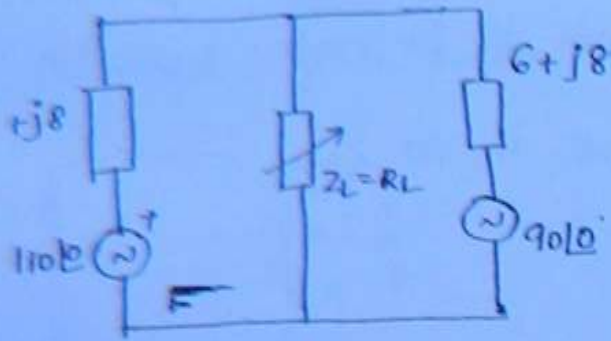Find max. power dissipation in the load impedance.



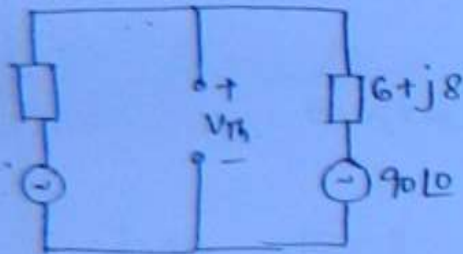(124)

= First find thevenin eq. [Case 3, Prob.]




$$\frac{V_{Th} - 100\angle 0^\circ}{6+j8} + \frac{V_{Th} - 90\angle 0^\circ}{6+j8} = 0$$

$$2V_{Th} = 200\angle 0^\circ$$

$$V_{Th} = 100\angle 0^\circ$$

$$Z_{Th} = \frac{(6+j8)(6+j8)}{2} = \frac{36 - 64 + j96}{2} = 3 + j4$$

$Z_{Th} = 3 + j4$

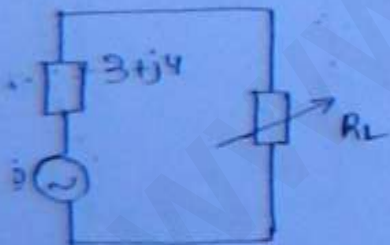

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2}$$

$$R_L = \sqrt{3^2 + 4^2} = 5\Omega$$

$$R_L = 5\Omega$$

$$I = \frac{100\angle 0^\circ}{(3+5) + j4} = \frac{100\angle 0^\circ}{8 + j4} = \frac{100\angle 0^\circ}{\sqrt{8^2 + 4^2}}$$


$$P = I^2 R_L = \frac{100^2}{(8^2 + 4^2)} \times 5$$

Ans: 625 W




Q. At what value of  $Z_L$ , power delivered from source load is max.

(125)

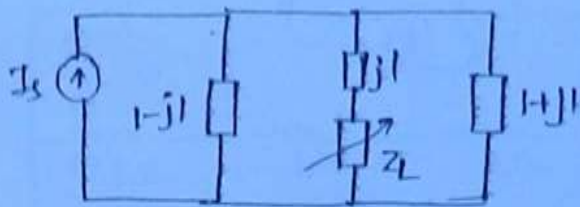

$Z_{Th}$

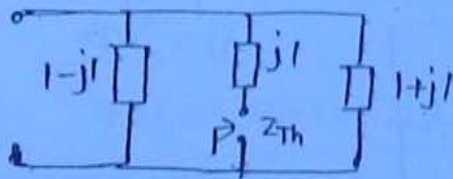

$$Z_{Th} = \frac{(1+j1)(1-j1)}{1+j1+1-j1} + j1$$



$$Z_{Th} = 1+j1$$

Case (i) from

$$\therefore Z_L = Z_{Th}^* = 1-j1$$

$$Z_L = 1-j1$$

Millman's Theorem

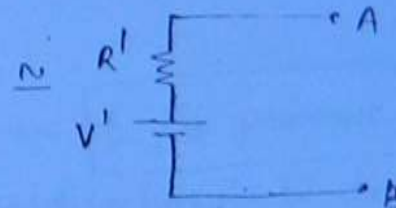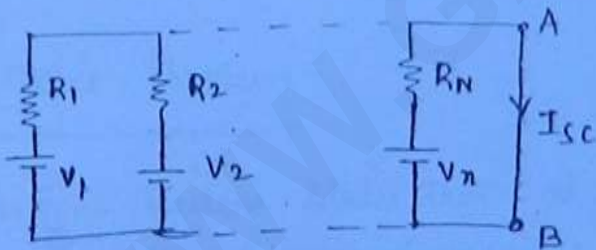

$$R' = R_{Th}$$

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

$$** \quad R' = \frac{1}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)} = \frac{1}{G_1 + G_2 + \dots + G_n}$$

$$V_{oc} = I_{sc} R_{th}$$



$$V' = I' R'$$

126

$$V' = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

$$V' = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

$$V' = V_{th}$$

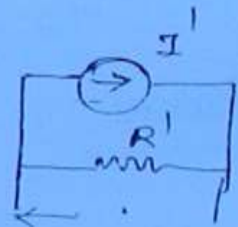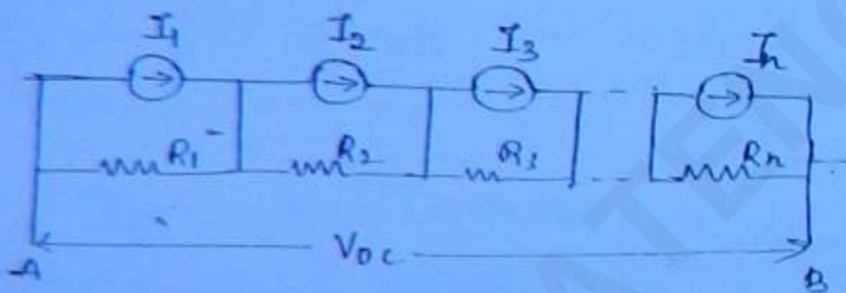

$$R' = R_{th}$$


$$R' = R_1 + R_2 + \dots + R_n$$

$$I_{sc} = \frac{V_{oc}}{R_{th}}$$

$$I' = \frac{V'}{R'}$$

$$I' = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

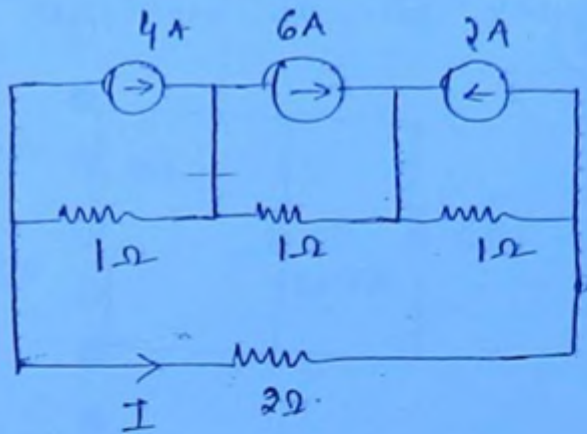Find the value of  $I$  in the ckt shown.




127

$$I' = \frac{4 \times 1 + 6 \times 1 - 2 \times 1}{1 + 1 + 1} = \frac{8}{3} \text{ A}$$

$$R' = 1 + 1 + 1 = 3 \Omega$$

$$I = - \frac{8/3 \cdot 3}{3 + 2}$$

$$I = - \frac{8}{5} \text{ A}$$

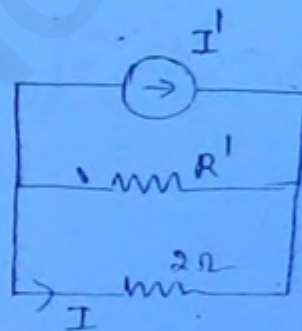


## Tellegen's Theorem

→ Tellegen's theorem states that algebraic sum of the powers in any circuit (linear, non-linear, unidirectional, bi-directional, time variant and invariant elements) at any instant = 0.

And it is given by,

$$\sum_{k=1}^n V_k i_k = 0$$



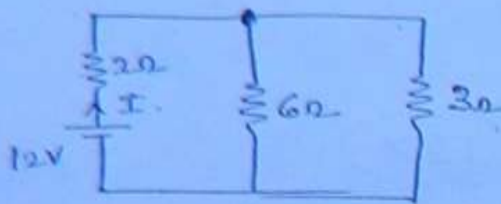

(128)

$$R_{eq} = 2 + \frac{6 \times 3}{9} = 4\Omega$$

$$I_T = \frac{12}{4} = 3A$$

$$I_{6\Omega} = \frac{2 \times 3}{9} = 1A \quad \Rightarrow \quad I_{3\Omega} = 2A$$


$$V_2 = 2 \times 3 = 6V, \quad V_3 = V_6 = 3 \times 2 = 6V$$

$$\begin{aligned} V_2 I + V_6 I_6 + V_3 I_3 - V_s I &= 6 \times 3 + 6 \times 1 + 6 \times 2 - 12 \times 3 \\ &= 18 + 6 + 12 - 36 \\ &= 0 \end{aligned}$$

For verification of Tellegen's Theorem KVL & KCL equations are used.


Tellegen's theorem works based on the principle of Law of Conservation of Energy.

### Compensation Theorem

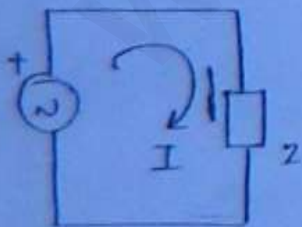


$$I = V/Z$$

$$I \Delta Z = I_T \Delta Z$$

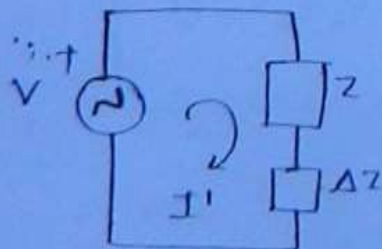


$$I' = \frac{V}{Z + \Delta Z}$$

modified circuit

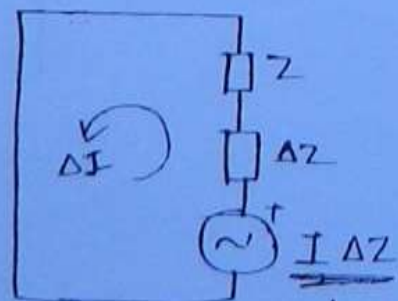


Compensation emf (or)

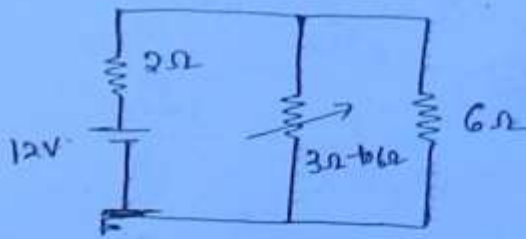Q. Find change in current in  $2\Omega$  &  $6\Omega$  resistor when resistance in the variable branch is changed from  $3\Omega$  to  $6\Omega$ .



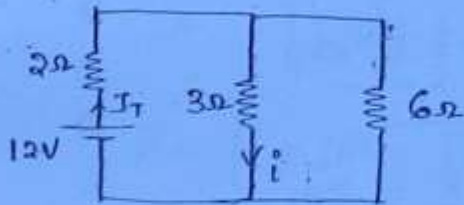(129)

Step 1: Find original current circulating in the variable branch.



$$R_{eq} = 2 + \frac{3 \times 6}{9}$$

$$= 4\Omega$$

$$I_T = 12/4 = 3A$$

$$i_{3\Omega} = 2A$$

Step 2: Find compensation emf.

$$= I \Delta Z = 2(6-3) = 6V$$

Step 3: Develop modified circuit.


while developing modified circuit, deactivate all the independent sources and connect the compensation emf in series to variable branch.

$$R_{eq} = 6 + \frac{2 \times 6}{2+6} = 22/4$$

$$I_T' = \frac{6}{R_{eq}} = \frac{8}{9} A = 0.8$$

$$\Delta I_2 = I_T' \cdot \frac{6}{6+2} = 0.6 A$$
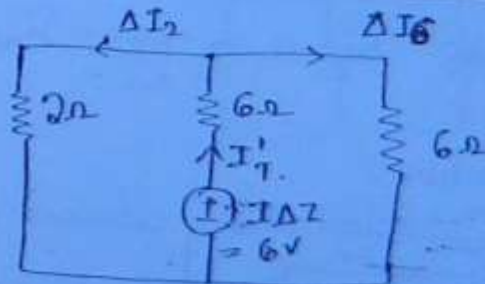
$$\Delta I_6 = I_T' - \Delta I_2 = 0.2 A$$



$$\frac{2 \times 6}{2+6} = \frac{12}{8} = 1.5$$

$$6 + 1.5 = 7.5$$

$$\frac{6}{7.5} = 0.8$$

$$0.8 \times \frac{6}{8} = 0.6$$





$$0.8 - 0.6 = 0.2$$

8-

In the Bridge circuit, to obtain null deflection in the galvanometer, compensation Theorem is used.

130

## SUBSTITUTION THEOREM

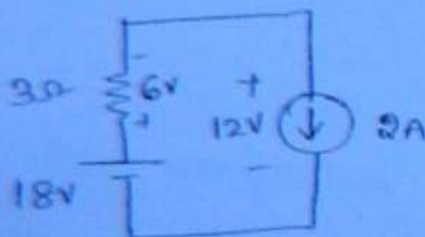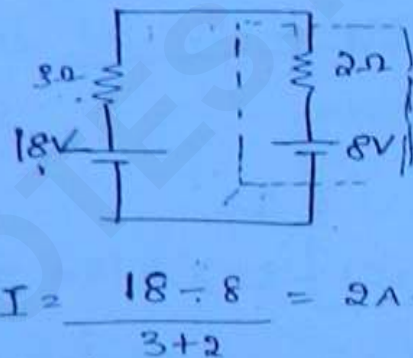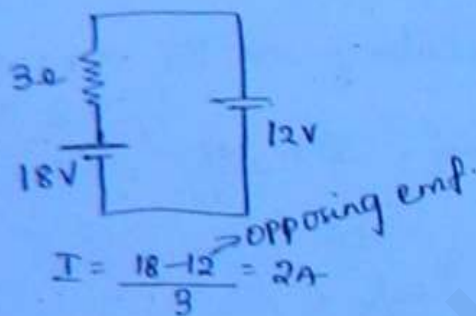
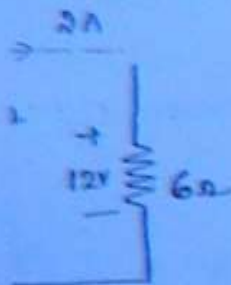


Example

Req is equal in both cases.

$$R = \frac{V}{I} = R_{eq}$$

Superposition

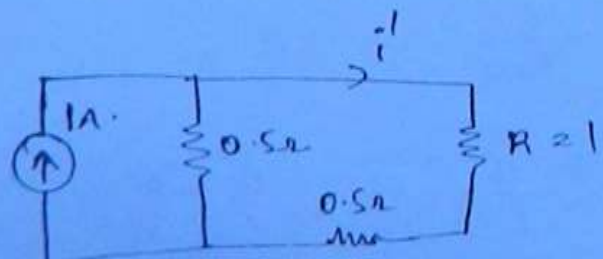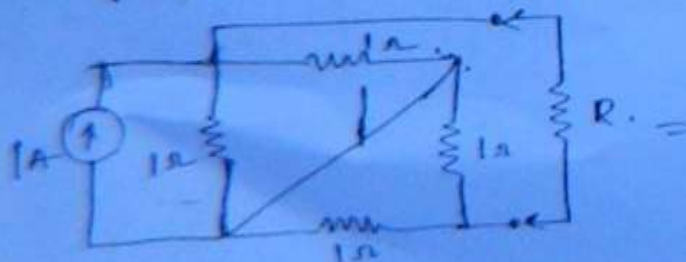

$$i' = 1 \cdot \frac{0.5}{0.5 + 0.5 + 1} = 0.25A$$

in 1A is O.C.  $\Rightarrow$  balanced bridge



$$3. \quad (R_1 + j\omega L_1) (R_4 - j/\omega C_4) = R_2 R_3 \quad (R_1 + j\omega L_1) (R_4 - j/\omega C_4) =$$

$$(R_1 + j\omega L_1) (R_4 - j/\omega C_4) = R_2 R_3$$

$$\omega L_1 R_4 - \frac{R_1}{\omega C_4} = 0 \Rightarrow \omega L_1 R_4 = \frac{R_1}{C_4}$$

$$\frac{\omega L_1}{R_1} = \frac{1}{\omega C_4 R_4}$$

$$4. \quad V_{Th} = \frac{100 \angle 0^\circ \cdot j4}{3+j4} = \frac{100 (3-j4) j4}{25} = j16 (3-j4)$$


$$5. \quad P = \left( \pm \sqrt{P^I} \pm \sqrt{P^{II}} \pm \sqrt{P^{III}} \right)^2$$

$$P_{max} = \left( \sqrt{18} + \sqrt{50} + \sqrt{98} \right)^2$$

$$P_{min} = \left( \sqrt{98} - \sqrt{50} - \sqrt{18} \right)^2$$

$$6. \quad R_{Th} = \frac{100}{5} = \frac{100}{5} = 20 \Omega$$
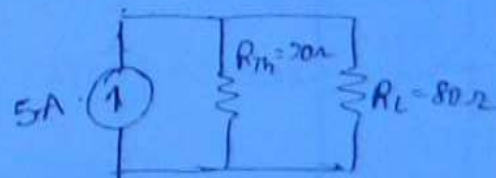
$$I_L = I_{80\Omega} = \frac{5 \times 20}{80+20} = 1A$$



7. If values are same, voltage branches can be replaced by eq. voltage source.  
In the above circuit, if freq. of sources are unequal current response can be obtained only by using superposition theorem.

$$13. \quad V_{oc} = 2 \cdot \frac{2}{2+3} = 4/5 \text{ V.}$$

$$R_{Th} = \frac{3 \times 2}{5} + \frac{4}{5} = 2 \Omega.$$

$$I_{sc} = \frac{V_{oc}}{R_{Th}} = \frac{4}{5 \times 2} = \frac{2}{5} \text{ A.}$$

$$14. \quad R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = \sqrt{10^2 + 10^2} = 10\sqrt{2} = 14.14 \Omega$$


$$15. \quad P_{max} = \frac{V_s^2}{4R_L} = \frac{12^2}{4 \times 2} = 18 \text{ W.}$$

17. millman's theorem.

$$V' = \frac{10/6 + 5/4}{1/6 + 1/4} = 7 \text{ V.}$$

$$R' = \frac{1}{\frac{1}{6} + \frac{1}{4}} = 2.4 \Omega.$$

$$18. \quad R_L = R_{Th}.$$

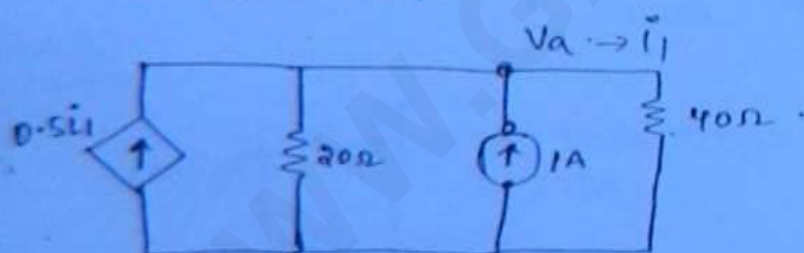

$$\frac{V_a}{20} + \frac{V_a}{40} = 0.5i_1 + 1.$$

$$i_1 = \frac{V_a}{40}.$$

$$\frac{V_a}{20} + \frac{V_a}{40} = \frac{V_a}{80} + 1.$$

$$\Rightarrow V_a = 16.$$

$$R_{Th} = \frac{V_a}{I_s} = \frac{16}{1} = 16 \Omega$$


$$19. \quad I_{4\Omega} = \frac{3}{4} \text{ A}$$

$$I_{2\Omega} = \frac{3}{4} + 0.25 = 1 \text{ A}$$

20.

$$I_{sc} = 3A$$

(133)

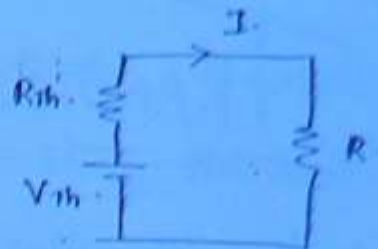

$$I = \frac{V_{Th}}{R + R_{Th}}$$

$$3 = \frac{V_{Th}}{R_{Th} + 0} \rightarrow (1) \quad R = 0$$

$$1.5 = \frac{V_{Th}}{R_{Th} + 2} \rightarrow (2) \quad R = 2$$

$$V_{Th} = 6, \quad R_{Th} = 2$$

$$R = 1 \Rightarrow I = \frac{V_{Th}}{R_{Th} + 1} = 2A$$

$$1.5 \times 2$$

$$= 3V$$

$$\frac{3}{1.5}$$

$$= 2$$

$$\frac{3 \times 2}{2} = 3A$$

21.

$I_1$	$I_2$	$V$
8A	12A	80
-8A	4A	0
10A	10A	?

Same network,  
network constants are same.

$$8k_1 + 12k_2 = 80$$

$$-8k_1 + 4k_2 = 0 \Rightarrow k_1 =$$

$$k_2 =$$

$$V = 10k_1 + 10k_2$$

$$\frac{80}{12} = \frac{80 + 100}{22}$$

$$k_1 = \frac{80}{12}$$

22. equal currents  $\Rightarrow$  equal resistance

23.

$$Z_{Th} = 1 + j1$$


$$Z_L = Z_{Th}^* = 1 - j1$$



2/11

# TRANSIENTS

134

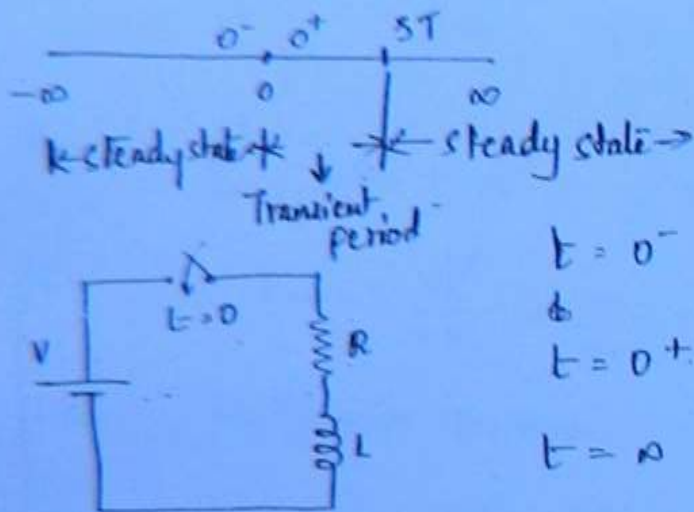

$$t = 0^-$$

$$i = 0$$

$$t = 0^+$$

$$i = 0 \quad (\text{O.C.})$$

$$t = \infty$$


$$V_L = L \frac{di}{dt} = 0 \quad (\text{S.C.})$$

Transients are present in the circuit when the circuit is subjected to any changes either by changing source magnitude or while changing any circuit elements, provided circuit consists of any energy storage elements. Since,

Inductor doesn't allow sudden change of current. and it stores energy in the form of magnetic field.

Capacitor doesn't allow sudden change of voltage. and it stores energy in the form of electric field.

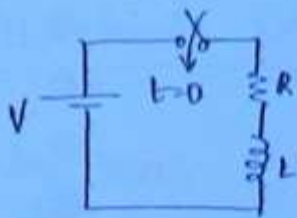When circuit is having only resistive elements, no transients are present in the circuit. Since resistor allows sudden change of current and voltage. and it doesn't store any energy.




$t=0^-$  indicates immediately

before operating the switch.

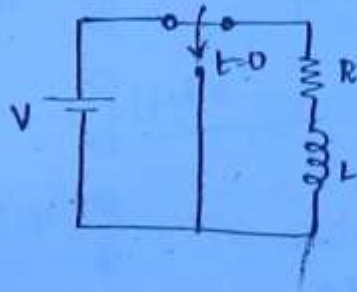(135)

$t=0^+$ , indicates immediately after operating switch.


$t=\infty$  indicates steady state condition.



$$t=0^- \quad i = I_0$$

$$t=0^+ \quad i = I_0 \text{ (current source)}$$


$$t=\infty \quad i = 0$$

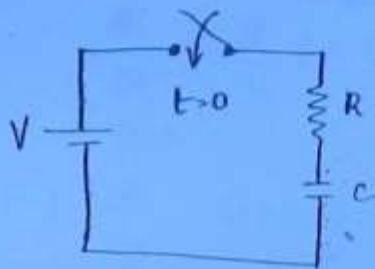

$$t=0^- \quad V_c = 0$$

$$t=0^+ \quad V_c = 0 \text{ (S.C.)}$$
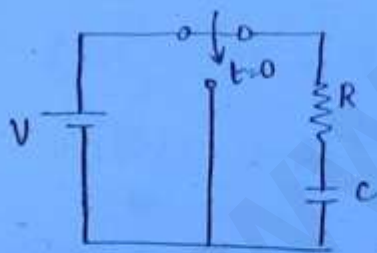
$$t=\infty \quad V_c = V, \quad i = 0 \text{ (O.C.)}$$




$$t=0^- \quad V_c = V_0 \quad (V_0 = V)$$

$$t=0^+ \quad V_c = V_0 \text{ (voltage source)}$$

$$t=\infty \quad V_c = 0$$

### Source Free RL circuit

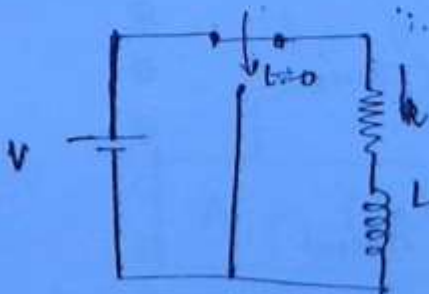

$$t=0^- \quad i = I_0$$

$$t=0^+ \quad i = I_0$$

$$t > 0$$



$$iR + L \frac{di}{dt} = 0$$

$$iR = -L \frac{di}{dt}$$




$$\int_0^t -\frac{R}{L} dt = \int_{I_0}^{i(t)} \frac{di}{i} = \log \frac{i(t)}{I_0} \Rightarrow I_0 e^{-Rt/L} = i(t)$$

$$V_L = L \frac{di}{dt}$$



$$V_L = L \frac{d}{dt} (I_0 e^{-Rt/L}) = -I_0 R e^{-Rt/L}$$

$$V = iR$$

$$V = I_0 R e^{-Rt/L}$$

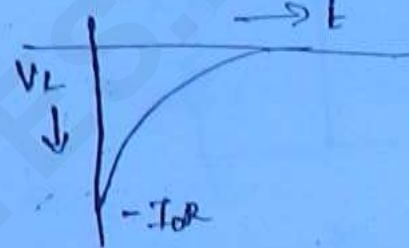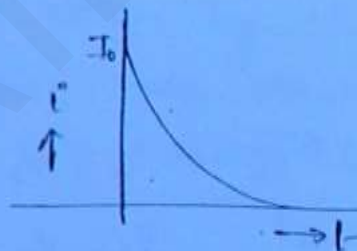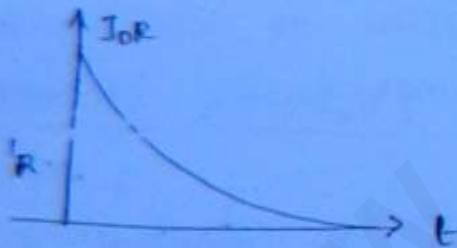

$$i(t) = I_0 e^{-Rt/L}$$

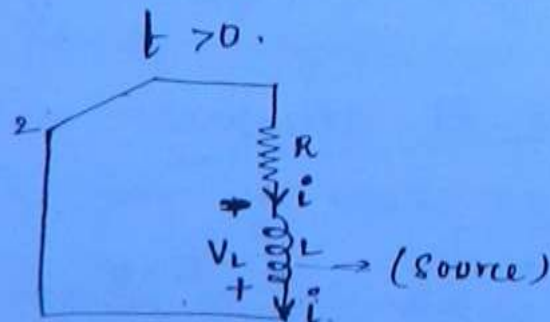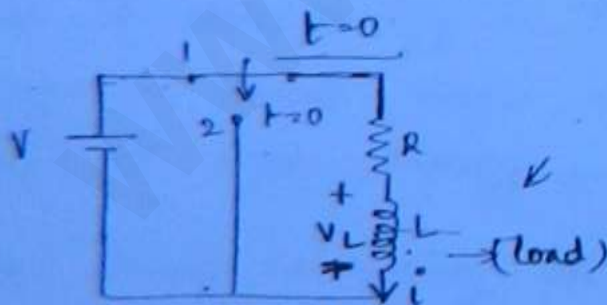

In the discharging inductor current direction doesn't change but voltage polarities are reversed




## RL circuit with Source

By KVL,

$$V = iR + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L}$$

$$i(t) = C.F + P.I$$

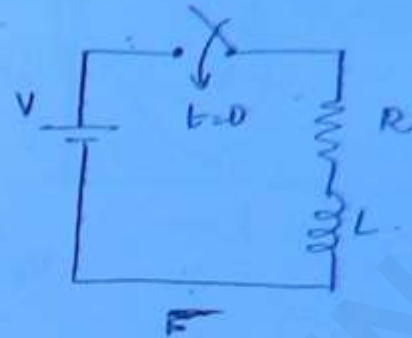

C.F  $\Rightarrow$  complementary func.

P.I - particular integral.

C.F  $\rightarrow$  Transient response (or) Source free response.

$$\frac{di}{dt} + \frac{R}{L} i = 0 \quad \Rightarrow \quad i(t) = A e^{-Rt/L}$$

P.I  $\rightarrow$  Steady state response / Final value.  $\rightarrow$  S.C.  
 $i = V/R$

$$i(t) = C.F + P.I$$

$$i(t) = A e^{-Rt/L} + V/R$$

$$t = 0^- \quad i = 0$$

$$t = 0^+ \quad i = 0$$

$$0 = A + \frac{V}{R} \quad \Rightarrow \quad A = 0 - \frac{V}{R}$$

$$* \quad \boxed{A = i(0^+) - i(\infty)}$$

Note:

$\therefore$  This formula is only applied


$$* \quad \boxed{i(t) = \left[ i(0^+) - i(\infty) \right] e^{-Rt/L} + i(\infty)}$$

$$i(t) = \left[ \underset{\substack{\downarrow \\ J.V.}}{i(0^+)} - \underset{\substack{\downarrow \\ F.V.}}{i(\infty)} \right] e^{-\frac{R}{L}t} + \underset{\substack{\downarrow \\ F.V.}}{-i(\infty)}$$


(138)

$$v = iR$$

$$v = V(1 - e^{-Rt/L})$$

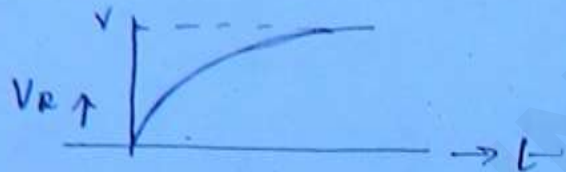

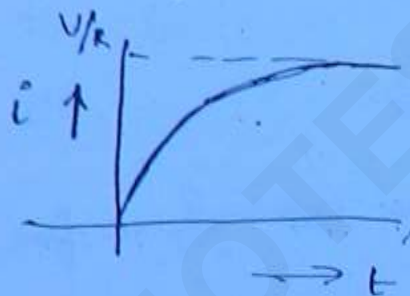
$$i(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$




$$v = L \frac{di}{dt} = L \left\{ \frac{d}{dt} \left[ \frac{V}{R} (1 - e^{-Rt/L}) \right] \right\}$$

$$v_L = V e^{-Rt/L}$$

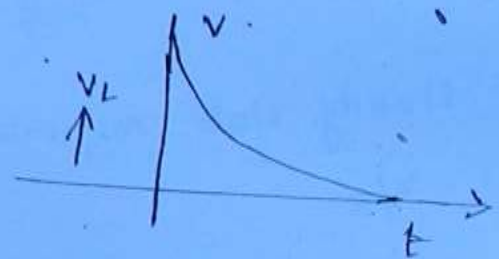


Source Free RC ckt.

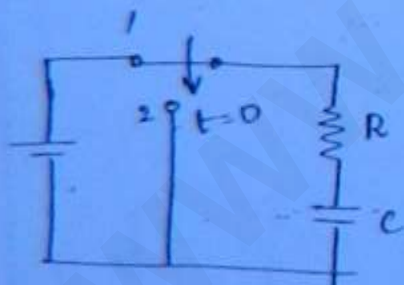

$$t=0^-, V_C = V_0$$

$$t=0^+, V_C = V_0$$

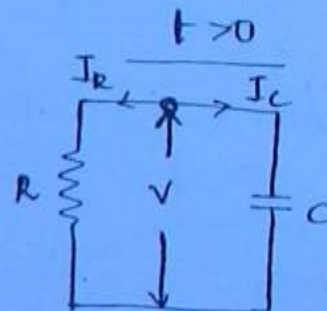

Assume a  
virtual  
voltage source  
 $v$


$$I_R + I_C = 0$$

$$\frac{V}{R} + C \frac{dv}{dt} = 0 \Rightarrow \frac{V}{R} = -C \frac{dv}{dt}$$

$$- \frac{1}{RC} dt = \frac{dv}{v}$$


$$\int_0^t \frac{-1}{RC} dt = \int_{V_0}^{V(t)} \frac{dv}{v}$$

$$V(t) = V_0 e^{-t/RC}$$

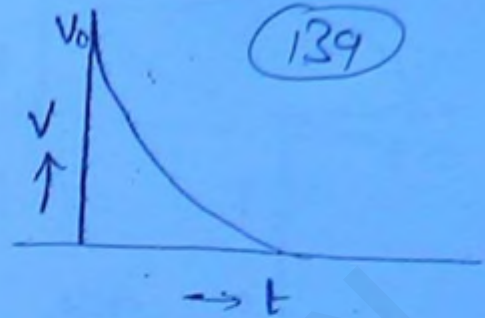




$$I_R = \frac{V}{R}$$

$$I_R = \frac{V_0}{R} e^{-t/RC}$$

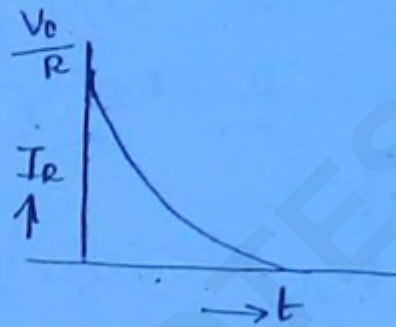

$$I_C = C \frac{dv}{dt}$$
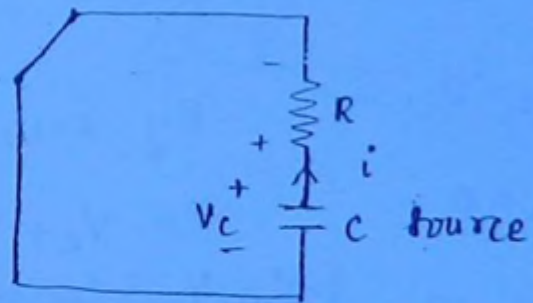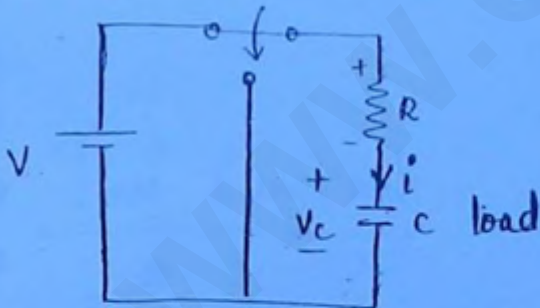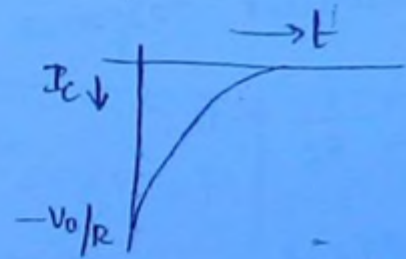
$$I_C = C \frac{d}{dt} (V_0 e^{-t/RC}) = -\frac{V_0}{R} e^{-t/RC}$$




Note

In the discharging capacitor voltage across capacitor polarities do not change. But current direction of the capacitor is reversed.



## RC circuit with source.

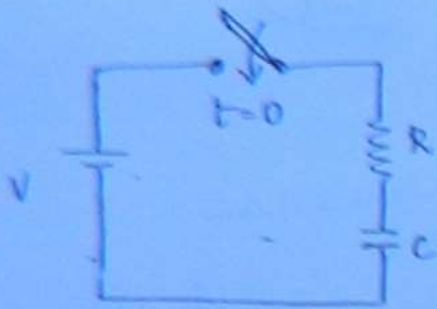

By KVL,

$$V = iR + \frac{1}{C} \int i dt$$

diff. wrt

$$0 = R \frac{di}{dt} + \frac{i}{C}$$

$$\boxed{\frac{di}{dt} + \frac{i}{RC} = 0}$$

$$i(t) = CF + PI$$

CF = Transient response,

$$\frac{di}{dt} + \frac{i}{RC} = 0 \Rightarrow i(t) = A e^{-t/RC}$$

PI  $\rightarrow$  Steady state :

$$C \rightarrow \infty \Rightarrow i = 0 \Rightarrow i(\infty) = 0$$

$$t = 0^-, V_C = 0$$

By KVL,

$$t = 0^+, V_C = 0$$

$$V = V_R + V_C$$

$$t = 0^+, V = IR + 0 \Rightarrow V(0^+) = V/R$$

$$i(t) = CF + PI$$

$$i(t) = A e^{-t/RC} + 0$$


$$A = i(0^+) - i(\infty)$$

$$A = V/R - 0$$

$$i(t) = \frac{V}{R} e^{-t/RC}$$


$$A = V/R$$

$$i(t) = \frac{V}{R} e^{-t/RC}$$

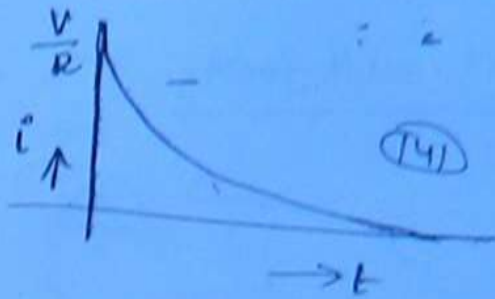

$$V_R = iR$$

$$V_R = V e^{-t/RC}$$

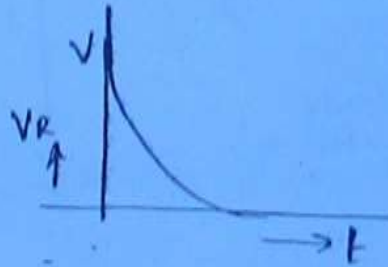


$$V_C = \frac{1}{C} \int_0^t i dt = \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$

$$V_C(t) = -V e^{-t/RC} + V$$

$$* V_C(t) = \left[ V_C(0^+) - V_C(\infty) \right] e^{-t/RC} + V_C(\infty)$$

$$V_C(t) = V (1 - e^{-t/RC})$$

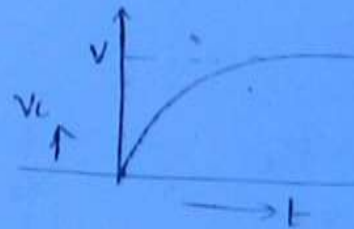

## Time Constant


→ Time constant is the time taken for response to rise 63.2% of the max. value & is given by,

$$\left. \begin{aligned} \tau &= \frac{L}{R} \quad - RL \\ \tau &= RC \quad - RC \end{aligned} \right\} \text{unit - sec.}$$


$$t = \tau$$

$$i(t) = \frac{V}{R} (1 - e^{-1}) = 0.63 V/R$$

## R-L with source

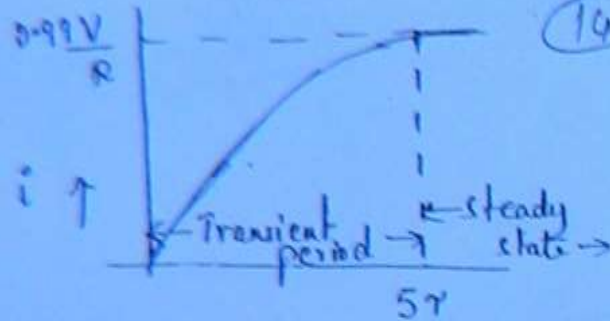

## RC with source

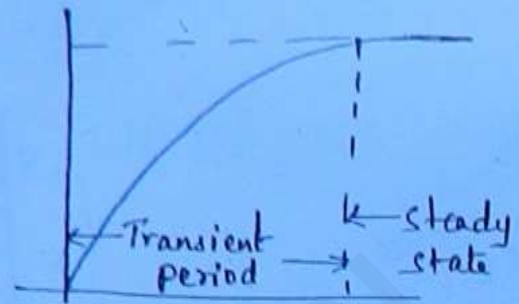

$$i(t) = \frac{V}{R} (1 - e^{-\frac{Rt}{L}})$$




$$V_c = V (1 - e^{-t/RC})$$

$$i(t) = \frac{V}{R} (1 - e^{-t/\tau})$$

Find response of  $V_c$ ,  $i_c$ , and  $V_x$  when initial value of the capacitor is 3V. i.e.  $V_0 = 3V$

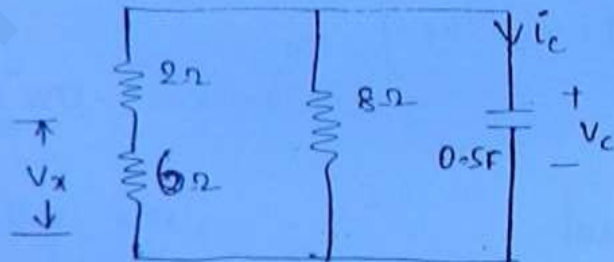First find out the equivalent resistance & capacitance.



$$V_c = V_0 e^{-t/RC}$$

$$V_c = 3 e^{-t/2}$$

Source free

$$V_x = V_c \cdot \frac{6}{6+2} = V_c \cdot \frac{6}{8}$$

$$V_x = 3 e^{-t/2} \cdot \frac{6}{8}$$

$\Rightarrow$

$$V_x = \frac{9}{4} e^{-t/2}$$



$$i_c = C \cdot \frac{dv_c}{dt} \Rightarrow i_c = C \cdot \frac{d}{dt} (3e^{-t/2})$$


$$i_c = \frac{1}{2} \cdot \frac{-3}{2} \cdot e^{-t/2} \Rightarrow \boxed{i_c = -\frac{3}{4} e^{-t/2}}$$

(143)

Q. Find the rate of rise of voltage across capacitor at  $t=0^+$ .

(a)  $RC$     ☒ (b)  $1/RC$

(c)  $0$     (d)  $V$

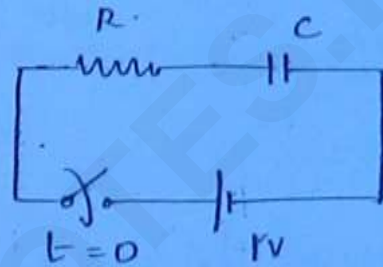

$v_c = V(1 - e^{-t/RC})$

Soln:-

$$V_c = -Ve^{-t/RC} + V$$


$$\frac{dv_c}{dt} = \frac{+V}{RC} e^{-t/RC} + 0$$

$$\left. \frac{dv_c}{dt} \right|_{t=0^+} = \frac{V}{RC} = \frac{1}{RC}$$

$$\therefore V = 1V$$

Q.


Find  $\frac{di_L}{dt}$  at  $t=0^+$

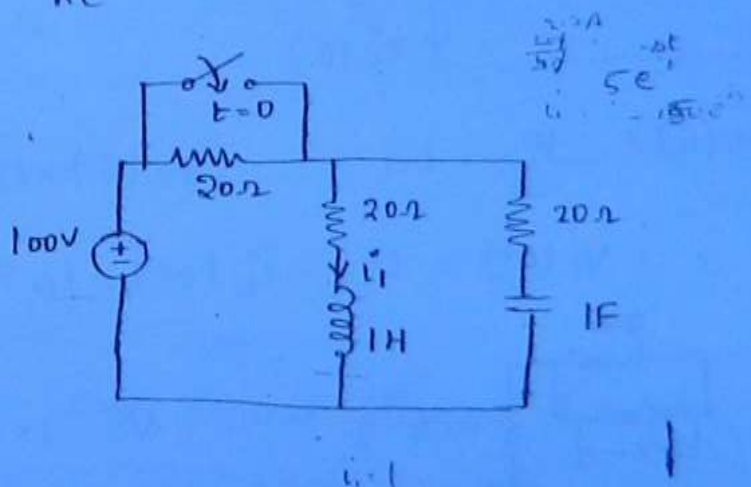

Soln


first find ckt at  $t=0^-$   
to calculate initial values

$t=0^-$

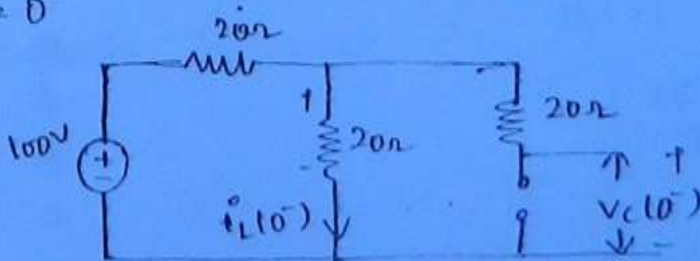

$$i_L(0^-) = \frac{100}{20+20} = 2.5A$$

$$V_C(0^-) = 2.5 \times 20 = 50V$$

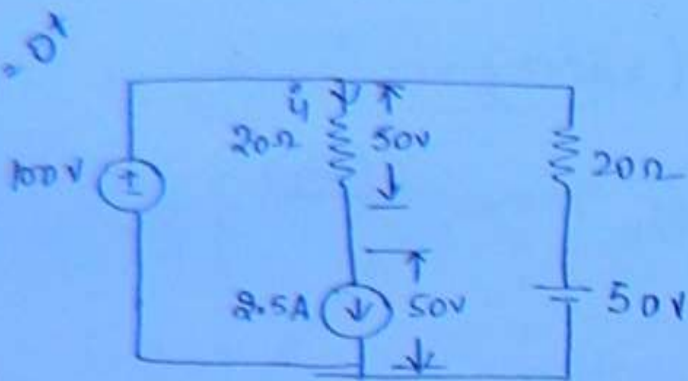

144

$$i_L(0^+) = i_L(0^-) = 2.5A$$

$$V_C(0^-) = V_C(0^+) = 50V$$



$$V_L = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{V_L}{L}$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = 50 A/s$$


Find voltage across the switch at  $t=0^+$

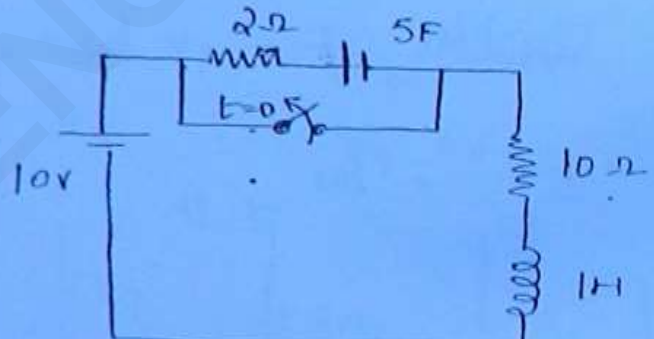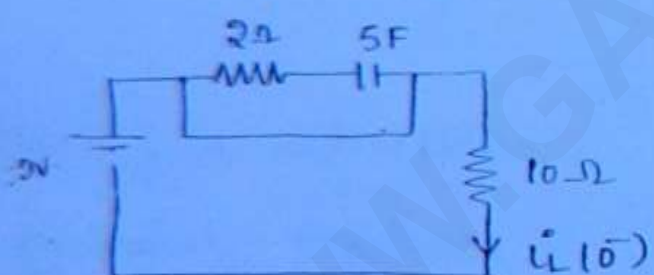- (a) 5V      (b) 10V  
(c) 0      (d) none




$$i_L(0^-) = \frac{10}{10} = 1A, \quad V_C(0^-) = 0$$
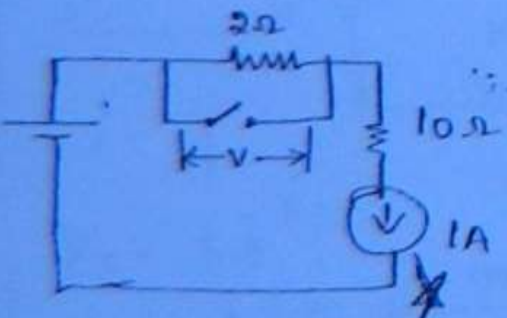
$$t=0^+, \quad V_L(0^+) = 0, \quad i_L(0^+) = 1A$$



$$V = 1 \times 2\Omega$$

$$V = 2V$$

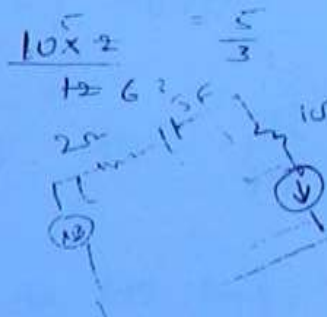

Q. Find  $i_L(t^+)$ ,  $V_L(t^+)$ ,  $w_C(\infty)$ ,  $w_L(\infty)$

at  $t=0^-$ , (145)

$$V_C(0^-) = 0, \quad I_L(0^-) = 0.$$



$t=0^+$

$$V_C(0^+) = 0, \quad I_L(0^+) = 0.$$

$$i_C(0^+) = \frac{10}{3+2} = \frac{2A}{2} = 1A$$

$$i_C(0^+) = 1A$$
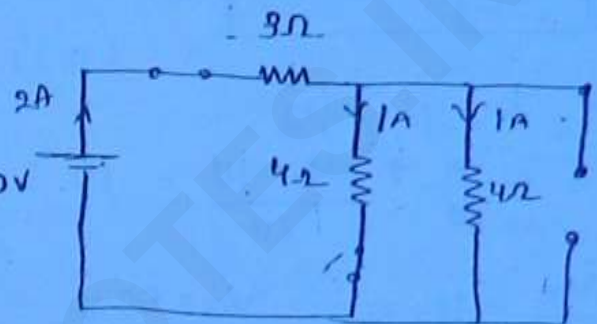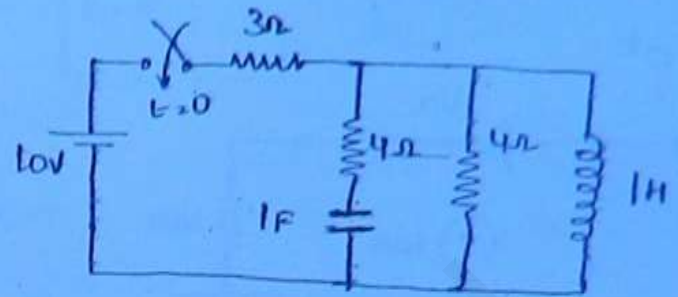
$$V_L(0^+) = \frac{10 \times 2}{2+3} = 4V$$



$$\Rightarrow V_L(0^+) = 4V$$

at  $t=\infty$


$$i_L(\infty) = 10/3 A$$

$$w_L(\infty) = \frac{1}{2} L i_L^2(\infty)$$


$$= \frac{1}{2} \times 1 \times \left(\frac{10}{3}\right)^2 = \frac{50}{3}$$

$$V_C(\infty) = 0$$
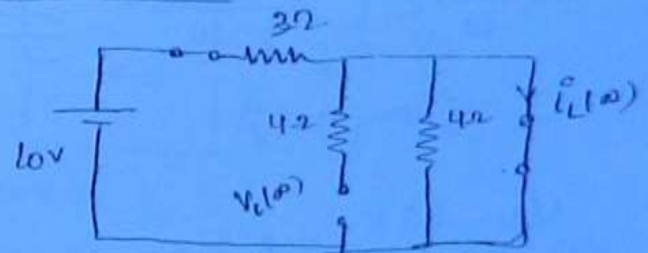
$$w_C(\infty) = \frac{1}{2} C V_C^2(\infty) = 0$$



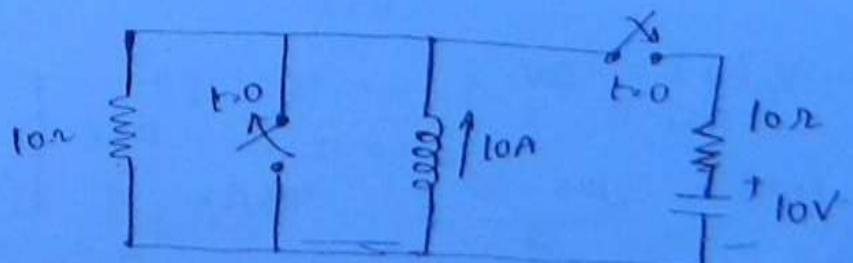Q. Find Voltage across inductor and current flowing through capacitor at  $t=0^+$






$$i_L(0^+) = i_L(0^-) = 10 \text{ A}, \quad V_L(0^-) = V_C(0^-) = 10 \text{ V}.$$

at  $t = 0^+$

(146)

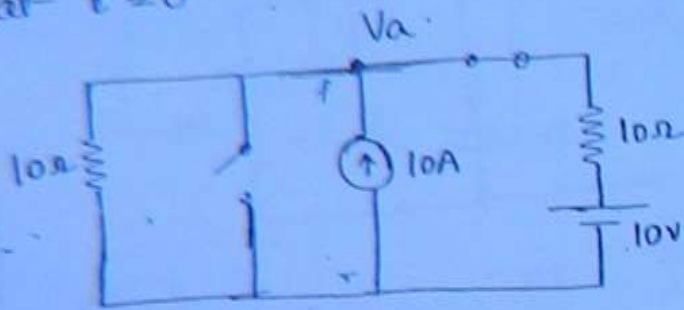

g kel,

$$\frac{V_A}{10} + \frac{V_A - 10}{10} = 10$$

$$\frac{V_A}{5} = 11 \Rightarrow \underline{V_A = 55 \text{ V}}$$

$$i_C = \frac{V_A - 10}{10} = \frac{55 - 10}{10} = \frac{45}{10} = 4.5 \text{ A}$$

$$i_C = 4.5 \text{ A}$$

$$V_L = V_A = 55 \text{ V}$$

Find  $i_C(0^+)$ ,  $i_C(1 \text{ s})$ .



$V_C(0^+)$ ,  $V_C(\infty)$

then  $Q_0 = 10 \text{ C}$

$$V_0 = \frac{Q_0}{C} = \frac{10}{0.5} = 20 \text{ V}$$

$$V_C(0^+) = V_C(0^-) = 20 \text{ V}$$
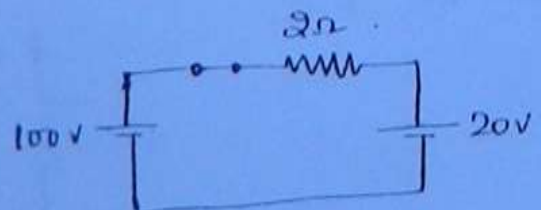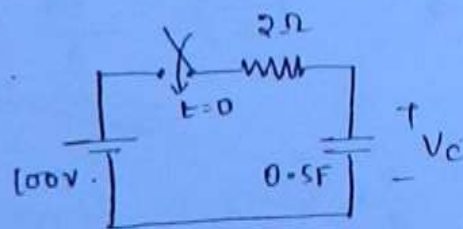
$$i_C(0^+) = \frac{100 - 20}{2} = 40 \text{ A}$$




$t \rightarrow \infty$

$V_c(\infty) = 100V$  (147)

$W_c(\infty) = \frac{1}{2} C \cdot V_c^2(\infty)$

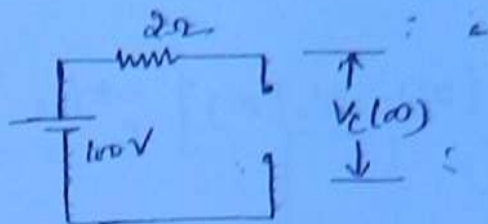$= \frac{1}{2} \cdot 0.5 \times 100^2 = 2500 J$



$i(\infty) = 0$

$i(t) = [i(0^+) - i(\infty)] e^{-t/RC} + i(\infty)$

$i(t) = 40 e^{-t}$

$RC = 1$

$i(1\text{sec}) = 40 e^{-1} = 14.7 A$


Q. Find response of  $v_o$  for the circuit shown.

(a)  $22 e^{-3.75t} + 8$

(b)  $22 e^{-t/3.75} + 8$

(c)  $22 e^{-1.2t} + 8$

(d)  $22 e^{-t/1.2} + 8$

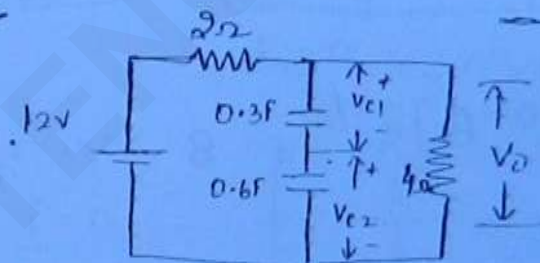


$V_{c1}(0) = 20V$

$V_{c2}(0) = 10V$

Handwritten calculations for the second problem, including time constant  $\tau = 0.2$  and final value  $8$ .

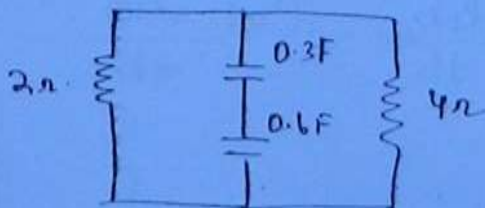Soln. Deactivate all the independent sources to find the independent sources. time const.



$R_{eq} = \frac{2 \times 4}{2 + 4} = 6\Omega$

$C_{eq} = \frac{0.3 \times 0.6}{0.3 + 0.6} = 0.2F$

$\tau = R_{eq} C_{eq}$

$-t/\tau$

$$V_o(t) = [V_o(0^+) - V_o(\infty)] e^{-t/RC} + V_o(\infty) \rightarrow (1)$$

$$V_o = V_{C1} + V_{C2}$$


148

at  $t = 0^+$

$$V_o(0^+) = V_{C1}(0^+) + V_{C2}(0^+)$$





$$V_o(0^+) = 20 + 10 = 30V$$

$t = \infty$

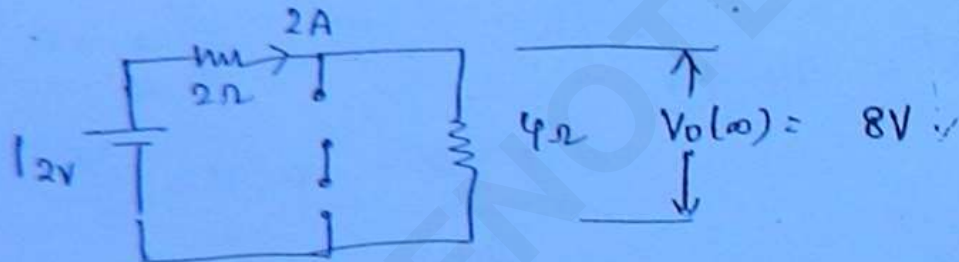

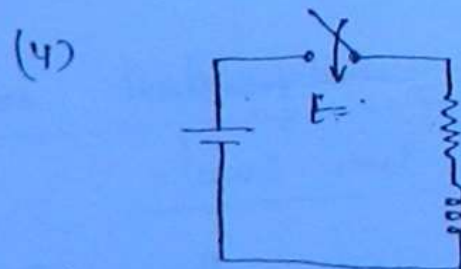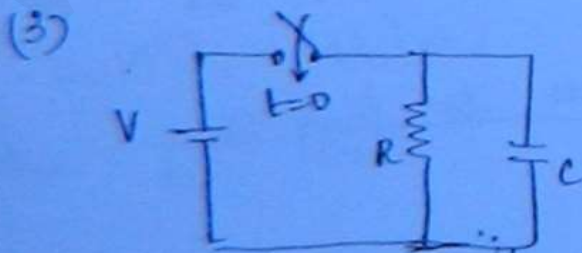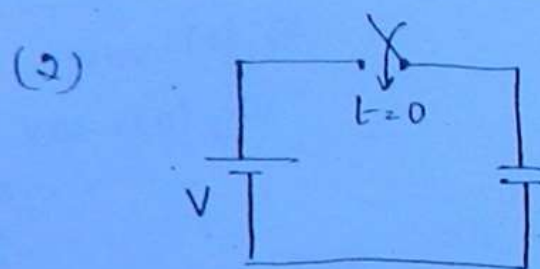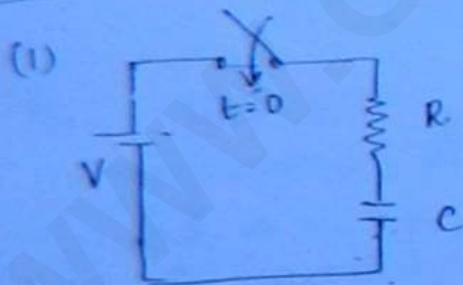
(1)

$$V_o(t) = [30 - 8] e^{-t/RC} + 8 = 22 e^{-3.75t} + 8$$





1.

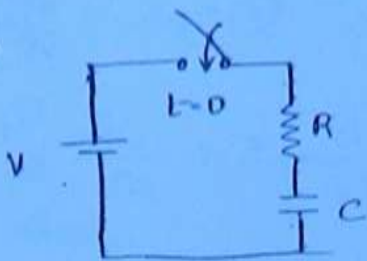

$$t = 0^-, V_C = 0$$


$$t = 0^+, V_C = 0$$



$$\tau = RC$$


(149)

2. \*\*

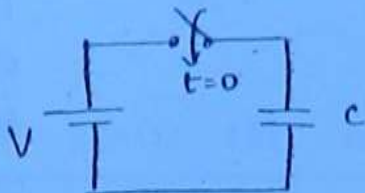


$$t = 0^-, V_C = 0$$

$$t = 0^+, V_C = V$$

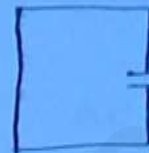


$$\tau = RC = 0$$

3. \*\*

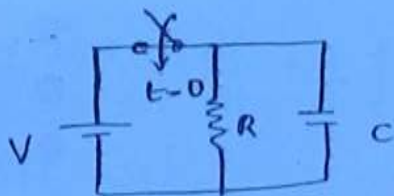


$$t = 0^-, V_C = 0$$

$$t = 0^+, V_C = V$$

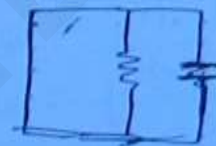

$$R_{eq} = 0 \Rightarrow \tau = RC = 0$$

4.

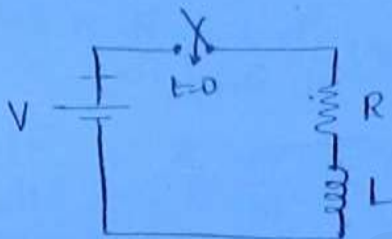


$$t = 0^-, i = 0$$

$$t = 0^+, i = 0$$



$$\tau = L/R$$

5. \*

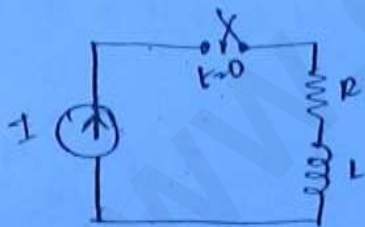

$$t = 0^-, i = 0$$


$$t = 0^+, i = I$$



$$\tau = \frac{L}{R_{eq}} = \frac{L}{\infty} = 0$$

Q.

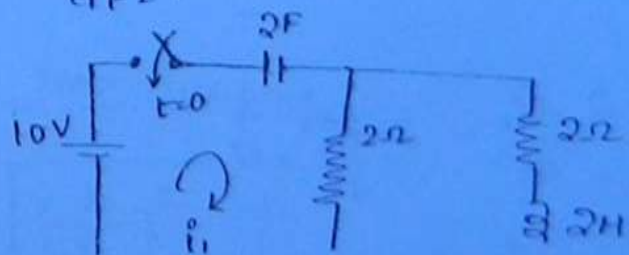Find  $i_1(0^+)$ ,  $i_2(0^+)$ ,  $V_C(0^+)$ ,  $\frac{di_1}{dt}(0^+)$ ,  $\frac{di_2}{dt}(0^+)$ ,  $\frac{d^2i_1}{dt^2}(0^+)$ ,  $\frac{d^2i_2}{dt^2}(0^+)$



at  $t = 0^-$ ,

$$i_1(0^-) = 0$$

$$i_2(0^-) = 0$$

$$V_c(0^-) = 0$$

150

at  $t = 0^+$ ,

$$V_c(0^+) = i_2(0^+) = 0$$

$$i_1(0^+) = \frac{10}{2} = 5A$$

KVL in loop 2:

$$4i_2 + 2 \frac{di_2}{dt} - 2i_1 = 0$$

①

at  $t = 0^+$

$$4 \times 0 + 2 \frac{di_2}{dt} - 2(5) = 0 \Rightarrow \frac{di_2}{dt}(0^+) = 5A/sec$$

KVL in loop 1

$$10 = \frac{1}{C} \int i_1 dt + 2(i_1 - i_2)$$

diff wrt

$$\frac{i_1}{2} + 2 \frac{di_1}{dt} - 2 \frac{di_2}{dt} = 0$$

at  $t = 0^+$

$$\frac{5}{2} + 2 \left. \frac{di_1}{dt} \right|_{0^+} - 2 \times 5 = 0$$

$$\left. \frac{di_1}{dt} \right|_{0^+} = 3.75 A/sec$$

$$2 \times \frac{5}{2} = 5$$
$$5 - 10 = -5$$
$$-5 = -2.5$$

if ① wrt

$$4 \frac{di_2}{dt} + 2 \frac{d^2 i_2}{dt^2} - 2 \frac{di_1}{dt} = 0$$

at  $t = 0^+$

$$\frac{di_2}{dt}$$

- diff eq. (2) wrt -

157

$$\frac{1}{2} \frac{di_1^o}{dt} + 3 \left[ \frac{d\tilde{i}_1}{dt^2} - \frac{d\tilde{i}_2}{dt^2} \right] = 0$$

$$\frac{d\tilde{i}_1}{dt^2} =$$

▮

RLC series ckt with DC excitation

$$V = iR + L \frac{di^o}{dt} + \frac{1}{C} \int i dt$$

diff wrt

$$0 = R \frac{di^o}{dt} + L \frac{d^2 i^o}{dt^2} + \frac{i^o}{C}$$

$$\frac{d^2 i^o}{dt^2} + \frac{R}{L} \frac{di^o}{dt} + \frac{i^o}{LC} = 0$$

$$\left( D^2 + \frac{R}{L} D + \frac{1}{LC} \right) i = 0 \quad \frac{d}{dt} = D$$


$$D_1, D_2 = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$D_1, D_2 = \frac{-\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}{1}$$

Case 1:

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC} \quad \text{over damping}$$
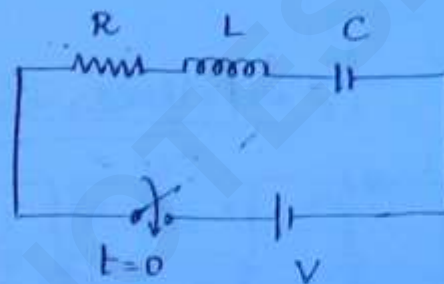
$$\alpha = \frac{R}{2L}, \quad \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$





$$i(t) = c_1 e^{(\alpha - \beta)t} + c_2 e^{(\alpha + \beta)t}$$

152

Case 2:

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC} \quad \text{critical damping.}$$

$$i(t) = (c_1 + c_2 t) e^{\alpha t}$$

Case 3:

$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC} \quad \text{under damping}$$

$$\alpha = -R/2L, \quad \beta = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$\Rightarrow i(t) = (c_1 \cos \beta t + c_2 \sin \beta t) e^{\alpha t}$$

$$\text{Damping coefficient} = \frac{R}{2L}$$

$$\text{Time constant} = \frac{1}{\text{damping coeff.}} = \frac{2L}{R}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\omega_d = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{R^2 C}{4L}}$$

$$\omega_d = \omega_0 \sqrt{1 - \xi^2}$$

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\frac{1}{2\xi} = \frac{1}{2\xi}$$

Case 4:

153

$$R = 0$$

undamping.

$$\alpha = 0$$

$$\beta = \frac{1}{\sqrt{LC}}$$


$$i(t) = c_1 \cos \beta t + c_2 \sin \beta t$$

RLC parallel circuit with DC excitation

$$I = \frac{V}{R} + C \frac{dv}{dt} + \frac{1}{L} \int V dt$$

diff wrt.
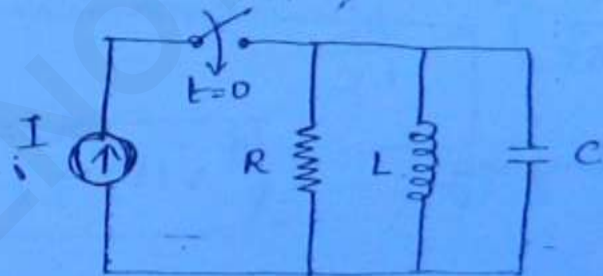
$$0 = \frac{1}{R} \frac{dv}{dt} + C \frac{d^2 v}{dt^2} + \frac{V}{L}$$



$$\left[ \frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{V}{LC} = 0 \right]$$

$$\left( D^2 + \frac{D}{RC} + \frac{V}{LC} \right) V = 0$$

$$D_1, D_2 = \frac{-1/RC \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$$

$$D_1, D_2 = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

ex 1:

$$\left(\frac{1}{2RC}\right)^2 > \frac{1}{LC}$$

overdamping

$$\alpha = -1/2RC$$

154

$$\beta = \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$V(t) = c_1 e^{(\alpha - \beta)t} + c_2 e^{(\alpha + \beta)t}$$

ex 2

$$\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC}$$

critical damping

$$V(t) = (c_1 + c_2 t) e^{\alpha t}$$

ex 3:

$$\left(\frac{1}{2RC}\right)^2 < \frac{1}{LC}$$

underdamping

$$\alpha = -\frac{1}{2RC}$$

$$\beta = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

$$V(t) = (c_1 \cos \beta t + c_2 \sin \beta t) e^{\alpha t}$$

→ Damping coefficient =  $\frac{1}{2RC}$

Time const. =  $\frac{1}{\text{damping coeff.}} = 2RC$

$$\omega_d = \frac{1}{\sqrt{LC}}$$
$$= \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$$\omega_d = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

$$\omega_d = \frac{1}{2R} \sqrt{\frac{L}{C} - \frac{1}{R^2}}$$



case 4:

$$G = 0$$

$$\frac{1}{R} = 0$$

$$R = \infty$$

undamping


(155)

$$\beta = \frac{1}{\sqrt{LC}}$$

$$V(t) = \xi \cos \beta t + c_2 \sin \beta t$$

\*\*  
\*Q.

Find current response for  $t > 0$

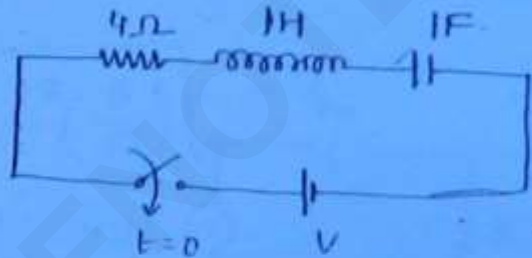

$t \geq 0$

Note:

1. Steady state current response of RLC series circuit with DC excitation = 0.

2.

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$\xi > 1 \Rightarrow$  over damped

$\xi = 1$  critically damped

$\xi < 1$  under damped

$\xi = 0$  undamped.

$$V = LC \frac{d^2 i}{dt^2} + L \frac{di}{dt} + i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$




$$-\frac{1}{LC} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$\frac{1}{LC} \left( \left( \frac{R}{2L} \right)^2 - \frac{1}{LC} \right)$$

$$\frac{R}{2L} \Rightarrow \xi = \frac{R}{2L} \sqrt{\frac{C}{L}}$$

3.

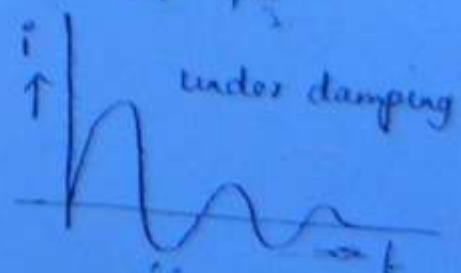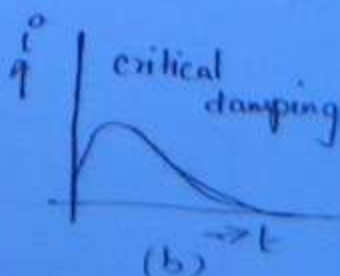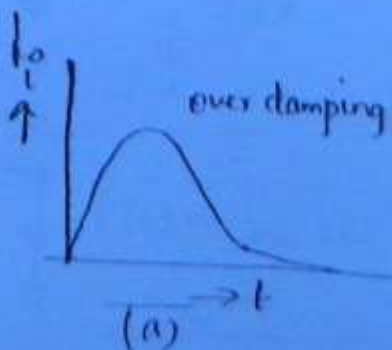

⇒ In over & critical damping no oscillations are present.

$$\Rightarrow \xi \geq 1 \Rightarrow \frac{R}{2} \sqrt{\frac{C}{L}} \geq 1 \quad (\text{for series ckt})$$

For under damping systems more than one oscillation is present. ( $\xi < 1$ ).

When response is asked,

$$i(t) = c_1 e^{(\alpha-\beta)t} + c_2 e^{(\alpha+\beta)t}$$

$$\alpha = -\frac{R}{2L}$$

$$\beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

WWW.GATEWAYNOTES.COM

# AC TRANSIENTS

(157)

- Intensity of the DC Transients are more than intensity of the AC Transients.
- In the AC circuit, based on selection of circuit elements, operating frequency and switching operation it is possible to obtain TRANSIENT FREE RESPONSE. But in the DC ckt, it is not possible to obtain transient free response.

$$V = iR + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L}$$

$$i(t) = CF + PI$$


CF  $\rightarrow$  Transient response

$$\frac{di}{dt} + \frac{R}{L} i = 0 \Rightarrow i(t) = A e^{-Rt/L}$$

P.I  $\rightarrow$  steady state response

$$i = \frac{V}{Z \angle \alpha}$$

$$i = \frac{V \angle -\alpha}{Z}$$

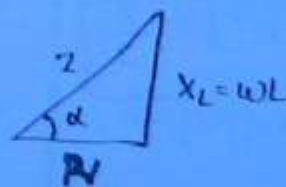

$$\alpha = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$i(t) = \frac{V_m \sin(\omega t + \theta - \alpha)}{Z}$$



$$i(t) = C.F + P.I$$

$$i(t) = A e^{-R/L t} + \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$

$$t = 0^-, \quad i = 0$$

$$t = 0^+, \quad i = 0$$

$$0 = A + \frac{V_m}{Z} \sin(\theta - \alpha)$$

$$A = -\frac{V_m}{Z} \sin(\theta - \alpha)$$

$$i(t) = \underbrace{-\frac{V_m}{Z} \sin(\theta - \alpha) e^{-\frac{R}{L} t}}_{T.R.} + \underbrace{\frac{V_m}{Z} \sin(\omega t + \theta - \alpha)}_{S.R.}$$

use 1:

$$v(t) = V_m \sin(\omega t + \theta), \quad t = 0$$

$$\theta - \alpha = 0$$

$$\theta = \alpha$$

\*\*

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Condition for transient  
free response


use 2:

$$v(t) = V_m \sin(\omega t + \theta), \quad t = 0$$

\*\*

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}$$

use 3:

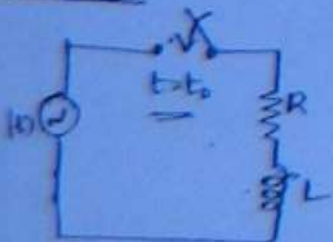

$$i(t) = C.F + P.I$$

$$i(t) = A e^{-\frac{R}{L}(t-t_0)} + \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$

$$t = t_0^-, \quad i = 0$$

$$t = t_0^+, \quad i = 0$$

$$\theta = A + \frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)$$

(159)

$$A = -\frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)$$

Case 3:

$$V(t) = V_m \sin(\omega t + \theta), t = t_0$$

$$\omega t_0 + \theta - \alpha = 0$$

$$\omega t_0 = \alpha - \theta$$

\*\*

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$$

Case 4:

$$V(t) = V_m \cos(\omega t + \theta), t = t_0$$

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta + \pi/2$$

→ parallel  
→ series

	RL		RC
1. $V(t) = V_m \sin(\omega t + \theta), t = 0$ $i(t) = I_m \sin(\omega t + \theta), t = 0$	$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$	$\theta = \tan^{-1}(\omega R)$	$\theta = \tan^{-1}(\omega RC)$
2. $V(t) = V_m \cos(\omega t + \theta), t = 0$	$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}$	$\theta = \tan^{-1}(\omega R) + \frac{\pi}{2}$	$\theta = \tan^{-1}(\omega RC) + \frac{\pi}{2}$
3. $V(t) = V_m \sin(\omega t + \theta), t = t_0$	$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$	$\tan^{-1}(\omega R) - \theta$	$\tan^{-1}(\omega RC) - \theta$
4. $V(t) = V_m \cos(\omega t + \theta), t = t_0$	$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta + \frac{\pi}{2}$	$\tan^{-1}(\omega R) - \theta + \frac{\pi}{2}$	$\tan^{-1}(\omega RC) - \theta + \frac{\pi}{2}$

Note

→ In RLC ckt, it is not possible to obtain transient free response since ckt is having two energy storing elements.



Ex. for underdamped <sup>RLC</sup> sys.

$$i(t) = (C_1 \cos pt + C_2 \sin pt) e^{\alpha t}$$

(163)

For transient free response,


$$C_1 \cos pt + C_2 \sin pt \text{ should be } = 0$$

But  $\cos$  &  $\sin$  term will never be equal to zero simultaneously. Hence, there will be no transient free response.

At what value of  $t_0$  transient free response is obtained?

$$\omega t_0 = \tan^{-1} \left( \frac{\omega L}{R} \right) - \theta$$

$$\theta = 0^\circ$$

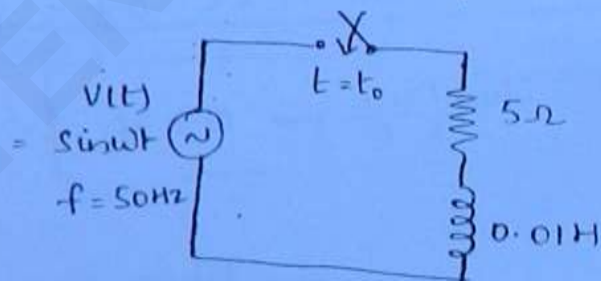

$$\omega t_0 = \tan^{-1} \left( \frac{2\pi \times 50 \times 0.01}{5} \right) = \tan^{-1} (0.2\pi)$$

$$t_0 = \frac{32.14 \times \pi}{2\pi \times 50 \times 180}$$

$$t_0 = 1.78 \text{ msec.}$$


$\tan^{-1} (0.2\pi)$  should be taken in radians.

$$\frac{32.14 \times 180}{1000 \times 180} = 1.78$$

At what value of  $t_0$ , transient free response is obtained?

$$\omega t_0 = \tan^{-1} (\omega RC) - \theta + \pi/2$$

$$\theta = 0^\circ$$

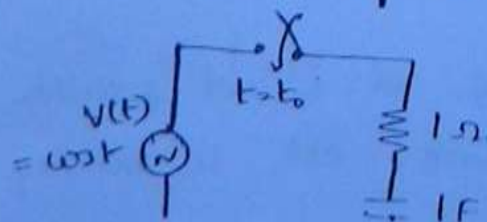



$$\omega = 1$$

$$t_0 = \tan^{-1}(1) + \pi/2$$

$$= \pi/4 + \pi/2 = \frac{3\pi}{4}$$

(16)

$$t_0 = \frac{3\pi}{4} \text{ sec.}$$

17/8/11

## Laplace Transforms

$$A \rightarrow A/s$$

$$e^{at} \rightarrow \frac{1}{s-a}$$

$$\sin \omega t \rightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\cos \omega t \rightarrow \frac{s}{s^2 + \omega^2}$$

$$e^{at} \sin \omega t \rightarrow \frac{\omega}{(s-a)^2 + \omega^2}$$

$$u(t) \rightarrow 1/s$$

$$e^{-at} \cos \omega t \rightarrow \frac{s+a}{(s+a)^2 + \omega^2}$$

$$\delta(t) \rightarrow 1$$

$$\frac{df}{dt} \rightarrow sF(s) - f(0^+)$$

$$\frac{d^2f}{dt^2} \rightarrow s^2 F(s) - sf(0^+) - f'(0^+)$$

Initial value theorem

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s) = \lim_{t \rightarrow 0} f(t)$$

$$f(0^-)$$

Find initial-value of  $F(s) = \frac{(2s+1)(s+3)}{s(s+2)(3s+4)}$ .

$$F(s) = \frac{(2+1/s)(1+3/s)}{s(1+2/s)(3+4/s)}$$

(162)

$$f(0^+) = \lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} \frac{(2+1/s)(1+3/s)}{(1+2/s)(3+4/s)}$$

$$= \frac{2 \times 1}{3} = \frac{2}{3}$$

Find initial value of the following function.

$$f(t) = 6\delta(t)$$

$$F(s) = \frac{6}{s} + 1$$

Note.

the above function initial value theorem cannot be applied. Since, to apply the initial " " denominator power would be  $>$  numerator power.

Final value theorem.

$$f(\infty) = \lim_{s \rightarrow 0} s F(s) = \lim_{t \rightarrow \infty} f(t).$$

Find final value of the following function.

$$F(s) = \frac{(s+1)(s+3)}{s(s+2)(s+6)}$$

$$(\infty) = \lim_{s \rightarrow 0} s F(s) = \frac{1 \times 3}{2 \times 6} = \frac{1}{4}$$

Q. Find final value of the following function.

$$f(t) = 3 + e^{2t}$$

$$F(s) = \frac{3}{s} + \frac{1}{s-2}$$

(63)

$$\lim_{s \rightarrow 0} \frac{3 + \frac{1}{s-2}}{s} = \frac{3}{0} = \infty$$

Note: For the above function final value theorem cannot be applied since pole is present in right  $1/2$  of the  $s$  plane. [unstable system].

Q. Find final value of the following function

$$F(s) = \frac{\omega}{s^2 + \omega^2}$$

(a) 0 (b) 1 (c)  $\infty$  (d) none

Soln

$$f(t) = \sin \omega t$$

Ans: lies b/n 1 & -1.

Note: For marginally stable system also, final value theorem cannot be applied.

Q. Current flowing through 4H inductor is given by,

$$I(s) = \frac{10}{s(s+2)}$$

Find initial voltage of the inductor.

Soln

$$V_L = L \frac{di}{dt} \Rightarrow V_L(s) = 4 [sI(s) - i(0^+)]$$

$$V(s) = 4sI(s) - 4i(0^+)$$



$$i(0^+) = \lim_{s \rightarrow \infty} s P(s) = \frac{s \cdot 10}{s(s+2)}$$

$$i(0^+) = 0$$

(164)

$$V(s) = 4s \cdot I(s) = \frac{4s \cdot 10}{s(s+2)}$$

$$= \frac{40}{(s+2)}$$

$$V(0^-) = \lim_{s \rightarrow \infty} s V(s) = \lim_{s \rightarrow \infty} \frac{s \cdot 40}{s[1+2/s]} = 40$$

$$V(0^+) = 40 \text{ V}$$

Exceptional case in inductor

$$i_L = \frac{1}{L} \int_{-\infty}^t v dt$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^{0^-} v dt + \frac{1}{L} \int_{0^-}^t v dt$$

$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_{0^-}^t v dt$$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v dt$$

is  $i_L(0^+) = i_L(0^-) + 0$   $\rightarrow$  Inductor doesn't allow sudden current change  $\therefore 0$

$$i(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v dt$$

then  $V \rightarrow \delta(t)$

$$i_L(0^+) = i_L(0^-) + \left[ \frac{1}{L} \int_{0^-}^{0^+} \delta(t) dt \right] \rightarrow \text{area} = 1. \quad (165)$$

$$\boxed{i_L(0^+) = \frac{1}{L}} \rightarrow \textcircled{1} \quad i_L(0^-) = 0.$$

$$W(0^+) = \frac{1}{2} L i_L^2(0^+) = \frac{1}{2} \cdot L \left( \frac{1}{L} \right)^2$$

$$\boxed{W(0^+) = \frac{1}{2L}}$$

Note:-

From above relation it is concluded that inductor doesn't allow instantaneous change for given i/p.

→ from above relations it is concluded that inductor allows instantaneous changes for voltage impulse function.  $(\textcircled{2})$

In case of capacitor

$$V_C = \frac{1}{C} \int_{-\infty}^t i dt$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^{0^-} i dt + \frac{1}{C} \int_{0^-}^t i dt$$

$$V_C(t) = V_C(0^-) + \frac{1}{C} \int_{0^-}^t i dt$$

$$t=0^+, \quad V_C(0^+) = V_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i dt$$

note:-  $V_C(0^+) = V_C(0^-) + 0$

From the above relation, it is concluded that capacitor

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i dt$$

when  $i \rightarrow \delta(t)$

$$V_c(0^+) = V_c(0^-) + \left( \frac{1}{C} \int_{0^-}^{0^+} \delta(t) dt \right)$$

166

area = 1


$$V_c(0^+) = 1/C$$

$$W_c(0^+) = \frac{1}{2} C V_c^2(0^+) = \frac{1}{2} C \left[ \frac{1}{C} \right]^2$$

$$W_c(0^+) = \frac{1}{2C}$$


note: from the above relation it is concluded that capacitor ~~does not~~ allow instantaneous <sup>voltage</sup> change for a given ~~type~~ current impulse function.

splane domain

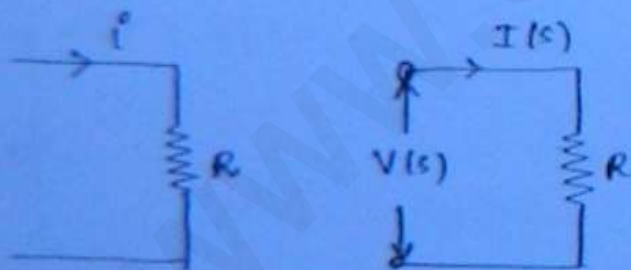


$$V(t) = R i(t)$$

$$V(s) = R I(s)$$

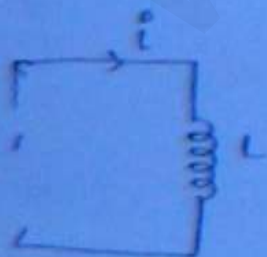

$$V = L \frac{di}{dt}$$

$$V(s) = L [s I(s) - i(0^+)]$$

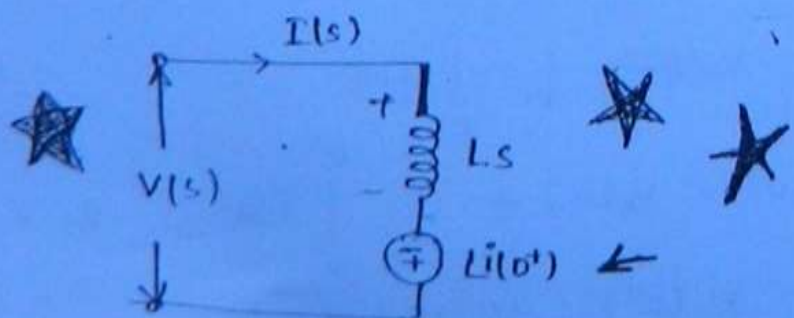


$$Z(s) = \frac{V(s)}{I(s)} = L(s) - L i(0^+)$$




$$L s I(s) = V(s) + L i(0^+)$$

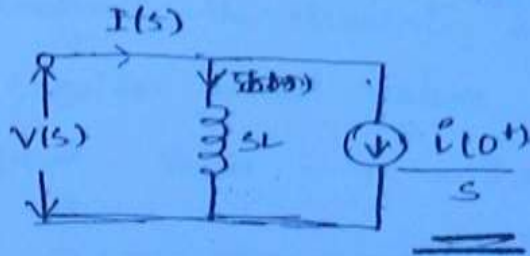
$$I(s) = \frac{V(s)}{Ls} + \frac{L i(0^+)}{Ls} \rightarrow (kcl)$$



$$i(0^+) = 0$$

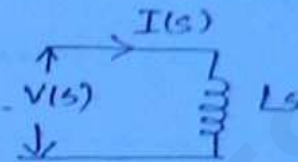

Capacitor

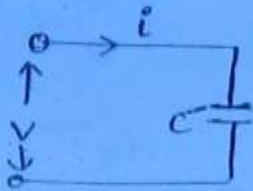


$$i = C \frac{dv}{dt}$$

$$I(s) = C [sV(s) - V(0^+)]$$

$$I(s) = \frac{V(s)}{1/Cs} - C V(0^+)$$

$\rightarrow kcl$

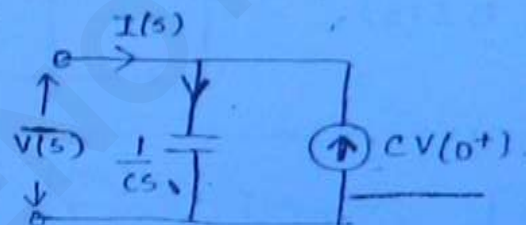


$$V(s) = \frac{I(s)}{C s}$$

$$V(s) = \frac{I(s)}{C s} + \frac{C V(0^+)}{C s}$$

$$\frac{V(s)}{1/Cs} = I(s) + C V(0^+)$$
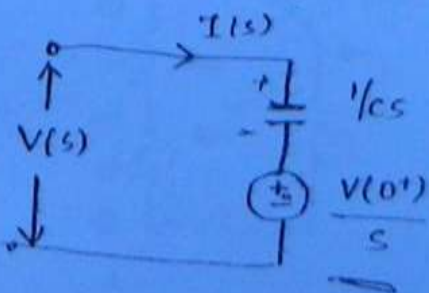
$$V(s) = \frac{1}{Cs} I(s) + \frac{C V(0^+)}{Cs} \rightarrow KVL$$






$$Z(s) = \frac{V(s)}{I(s)} = \frac{1}{Cs} + \frac{V(0^+)}{s I(s)}$$

$$V(0^+) = 0$$



transformation of dependant sources from time domain to s-domain

168

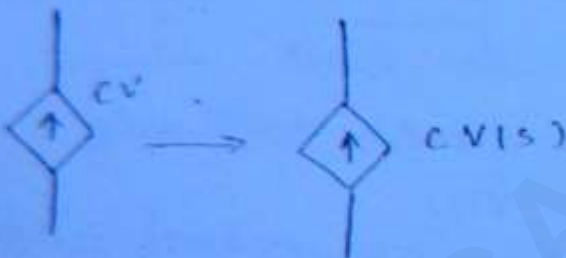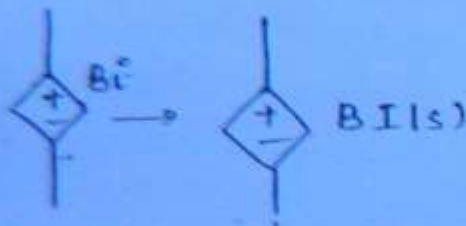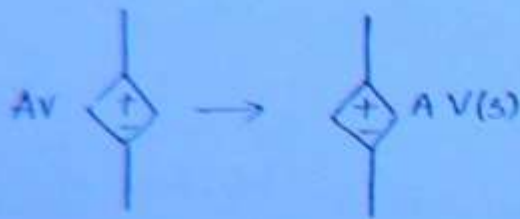


$$V(s) = R i(s) + L \frac{di}{dt}$$

$$V(s) = R i(s) + s L i(s) - L i(0^+)$$

$$V(s) = 3 i(s) + 5 i(s) - i(0^+)$$

$$\frac{V(s) - 1}{5s} = \frac{1}{sL} \Rightarrow \frac{1}{5L} = \frac{1}{sL}$$

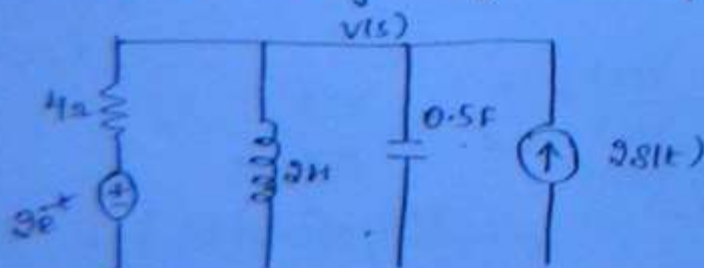Find  $V(s)$  when initial current of the inductor is 2A and initial voltage of the capacitor is 3V.



$$\frac{V(s) - 1}{5s} = \frac{1}{sL}$$

Soln


$$i_L(0^+) = 2A$$

$$V_0 = 3V$$

169

4

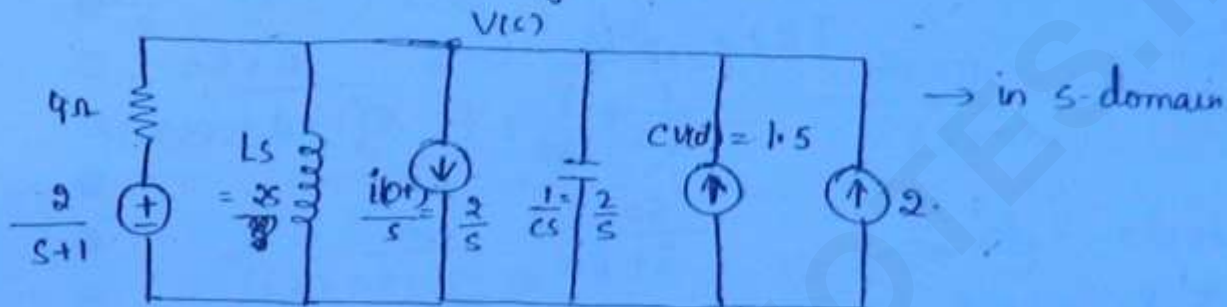
Whenever, the elements in circuit are in parallel, then consider initial values as current sources & vice versa i.e. series  $\rightarrow$  voltage sources.



$$\frac{V(s) - \frac{2}{s+1}}{4} + \frac{V(s)}{2s} + \frac{2}{s} + \frac{V(s)}{2/s} = 1.5 + 2$$


$$\frac{(s+1)V(s) - 2}{4(s+1)} + \frac{V(s)}{2s} + \frac{2}{s} + \frac{s \cdot V(s)}{2} = 3.5$$

Q. Find  $i(t)$  for  $t > 0$

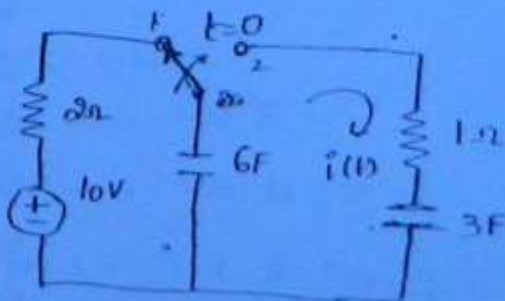




$t = 0^-$

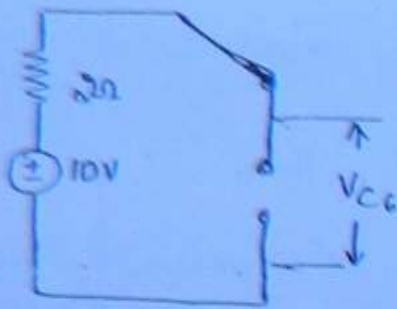

$$V_{C6}(0^-) = 10 \text{ V}$$

$$V_{C3}(0^-) = 0$$

$t > 0$

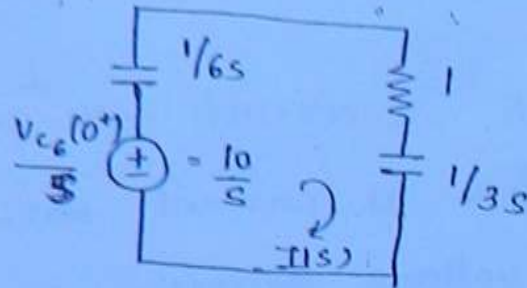

170

$$I(s) = \frac{10/s}{\frac{1}{6s} + \frac{1}{3s} + 1} = \frac{10 \times 6s}{s(1+2+6s)}$$


$$= \frac{60}{3+6s} = \frac{20}{1+2s}$$

$$= \frac{10}{s+1/2} \Rightarrow i(t) = 10e^{-t/2}$$


2 using classical method

$$i(t) = \frac{V_0}{R} e^{-t/RC}$$


$$i(t) = \frac{10}{1} e^{-t/2}$$

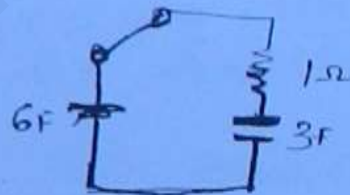

Find current response for  $t > 0$ .

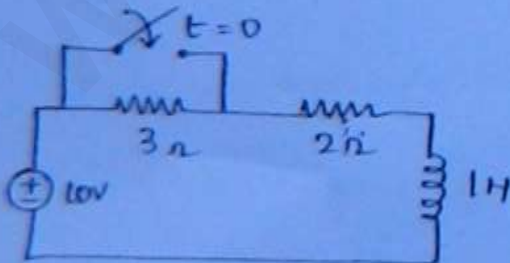

$t = 0^-$ ,

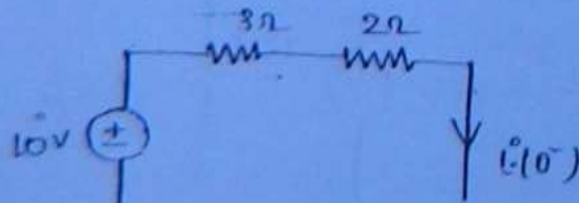


$$i(0^-) = 2 \text{ A}$$


$t > 0$

$$5 - [5 - 2] e^{-\frac{2t}{1}} = 5 - 3e^{-2t}$$

(17)

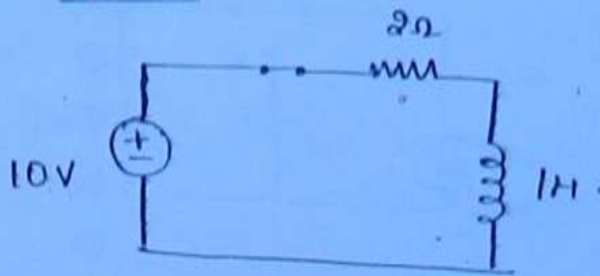

$\xrightarrow{\text{S domain}}$

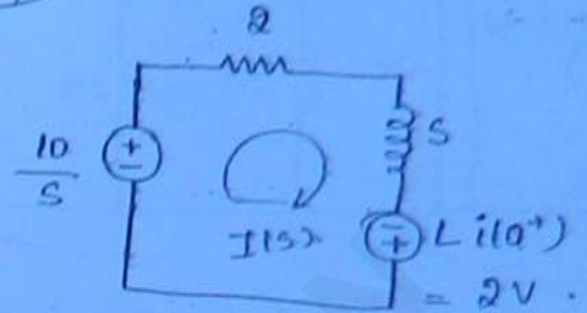

$$2 + \frac{10}{s} = (2 + s) I(s)$$

$\Rightarrow$

$$I(s) = \frac{2s + 10}{s(2 + s)}$$

$$I(s) = \frac{5}{s} - \frac{3}{s + 2}$$

$$i(t) = 5 - 3e^{-2t}$$


$\rightarrow$  obj - classical  
sub - L.T.

For obj

$$\begin{aligned} i(t) &= [i(0+) - i(\infty)] e^{-Rt/L} + i(\infty) \\ &= (2 - 5) e^{-2t} + 5 = 5 - 3e^{-2t} \end{aligned}$$



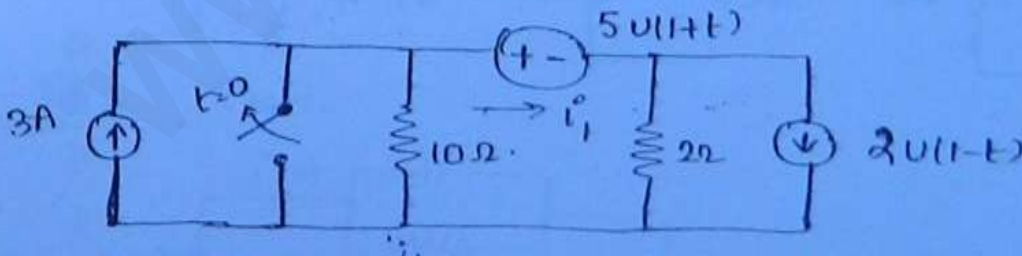Find the value of  $i_1$  at  $t = -2$  sec.



$$U(t) \rightarrow 0 \text{ to } \infty$$


$$U(-t) \rightarrow -\infty \text{ to } 0$$

$$\text{D.C.} \rightarrow -\infty \text{ to } \infty$$

$$U(1+t) \rightarrow -1 \text{ to } \infty$$

$$U(1-t) \rightarrow -1 \text{ to } \infty$$

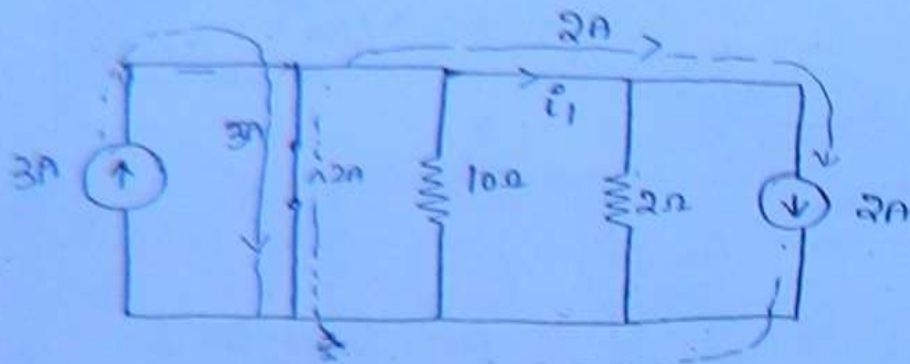
$$U(1-t) \rightarrow -\infty \text{ to } 1$$



172


$$i_1 \big|_{t=2} = 2A$$

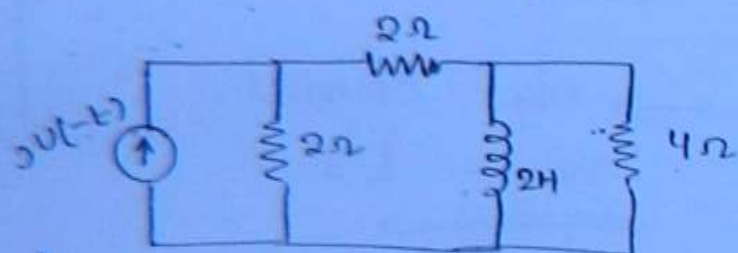Find current response in the inductor for  $t > 0$




$$\frac{-2t}{15 \times 12}$$

$t = 0^-$

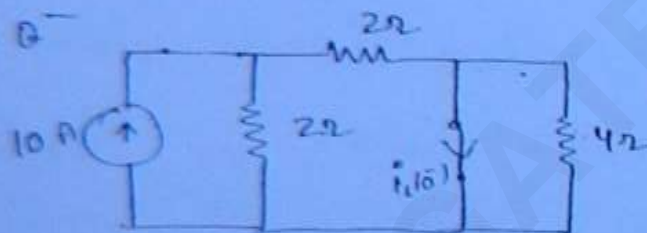

$$i_L(0^-) = 5A$$

$t > 0$

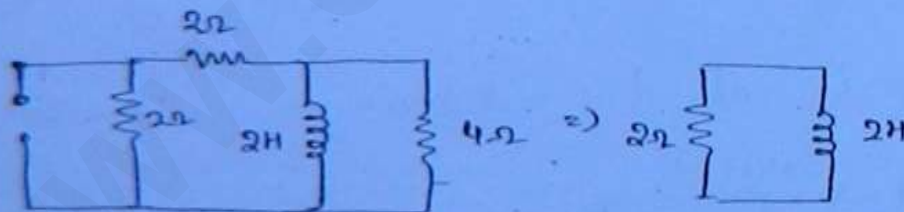


$$\tau = \frac{L}{R} = 1$$

$$i(t) = I_0 e^{-Rt/L} = 5e^{-t}$$

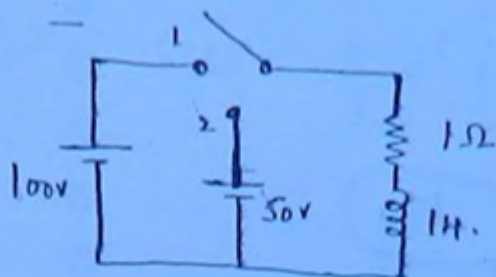In the circuit shown, at  $t = 0$  sec, the switch is connected to 1. After 1-time constant, the switch is transferred to position 2. Find the current response when the switch is at position 2.





(173)

Soln.

position - 1

$$i(t) = 100 \{ 1 - e^{-t} \}$$

$$\left[ \frac{V}{R} [1 - e^{-Rt/L}] \right]$$

position 2.

$$i(t) = [i(t_0) - i(\infty)] e^{\frac{-R(t-t_0)}{L}} + i(\infty)$$

50

$$50 - [50 - 63.2] e^{-(t-1)}$$

$$= 50 + 13.2 e^{-(t-1)}$$

at  $t = t_0 = 1s \Rightarrow 1\tau$  (one time const.)

$$i(t_0) = 100(1 - e^{-1}) = 63.2A$$

( $\therefore$  from position 1)

at position 2,

$$i(t) = [63.2 - 50] e^{-(t-1)} + 50$$


$$i(t) = 50 + 13.2 e^{-(t-1)}$$


$$f(t) = f(s)$$

$$f(t+1) = f(s) e^5$$

Pg-34

Conv.



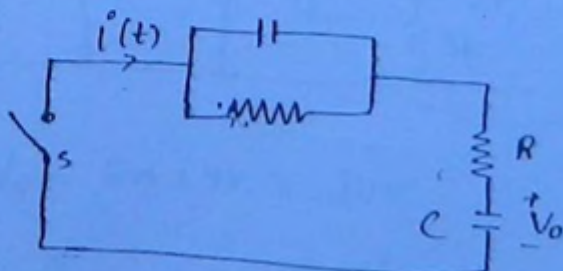


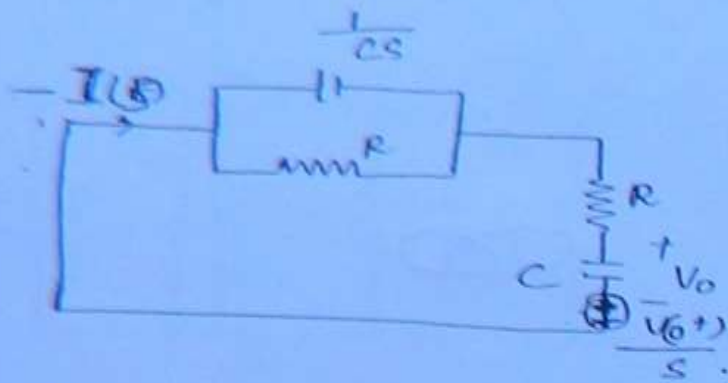

174

$$I(s) = \frac{-V(0+)/s}{R + \frac{1}{Cs} + \frac{R \cdot 1/Cs}{R + 1/Cs}}$$
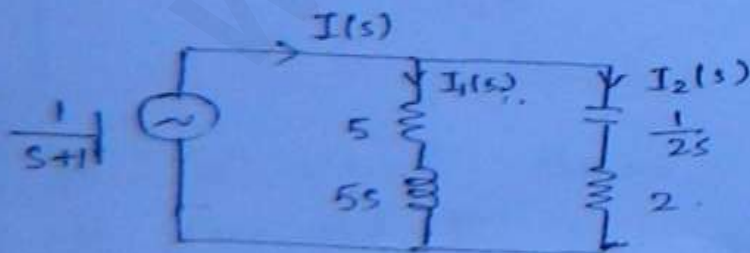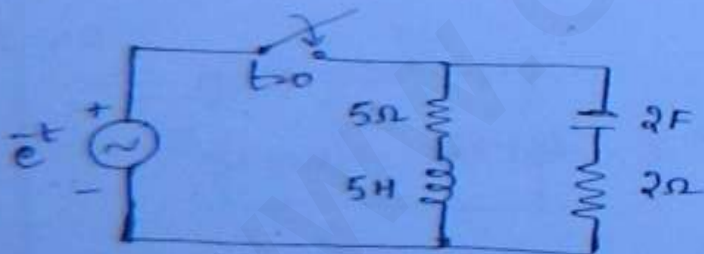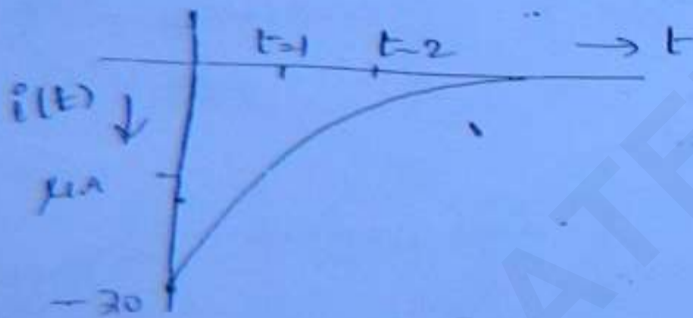
$$i(t) = -[14.46e^{-2.62t} + 5.54e^{-0.38t}] \mu A$$




$$I(s) = I_1(s) + I_2(s) = \frac{1/s+1}{5+5s} + \frac{1/s+1}{2+1/2s}$$

$$i(t) = \frac{2}{3} e^{-t} + \frac{1}{5} t e^{-t} - \frac{1}{6} e^{-t/4}$$

125

4.

$t = 0^-$

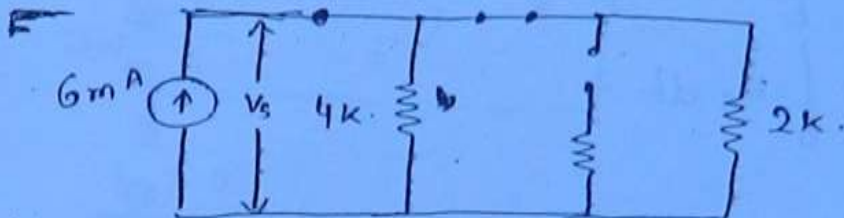


$$I_{4k} = \frac{6m \times 2k}{4k + 2k} = \frac{12}{6k}$$

$$I_{4k} = 2mA$$

$$V_{4k} = 2mA \times 4k = 8V$$

$$\Rightarrow V_C(0^-) = V_{4k} = 8V \Rightarrow V_C(0^-) = 8V$$

at  $t = 0^+$

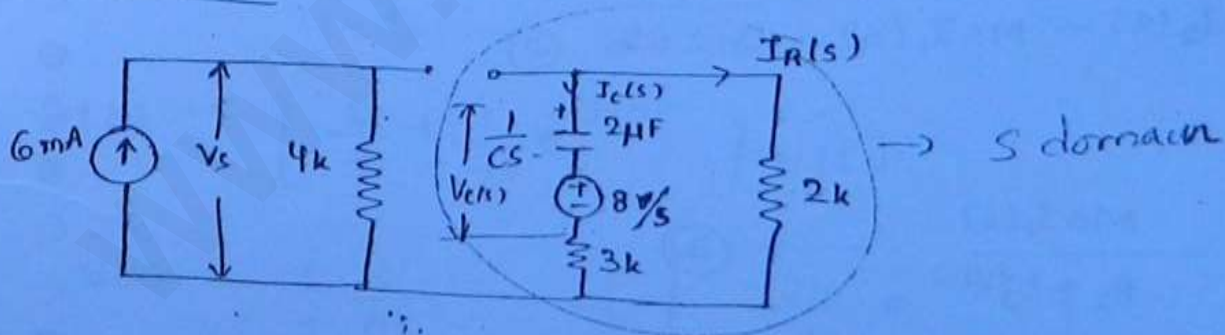

$$V_s = 6m \times 4k = 24V$$

$$I_R(s) = \frac{V(0^+)/s}{3k + 2k + 1/cs} = \frac{8/s}{5k + \frac{500k}{s}} = \frac{8m}{s}$$



$$-i_R(t) = 1.6 e^{-100t} \text{ mA}$$


$$i_c(t) = -i_R(t) = -1.6 e^{-100t} \text{ mA}$$

176

$$V_c = \frac{1}{C} \int_{-\infty}^t i_c dt$$

$$= \frac{1}{C} \int_{-\infty}^0 i_c dt + \frac{1}{C} \int_0^t i_c dt$$
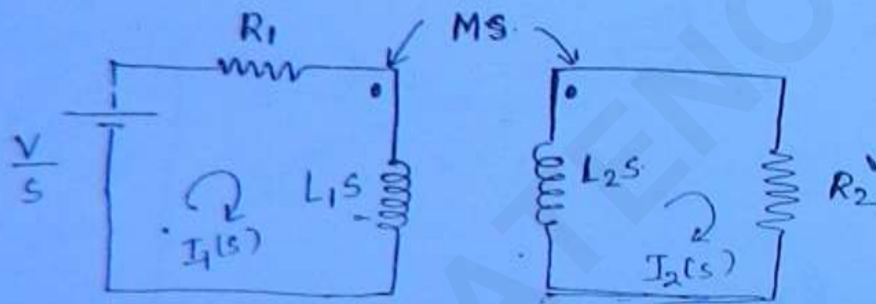
$$V_c = 8 + \frac{1}{C} \int_0^t i_c dt$$



$$-\frac{V}{s} + (R_1 + L_1 s) I_1(s) - M s I_2(s) = 0 \rightarrow (1)$$

$$(R_2 + L_2 s) I_2(s) - M s I_1(s) = 0 \rightarrow (2)$$

From eq. (2)


$$I_2(s) = \frac{M s I_1(s)}{R_2 + L_2 s} \rightarrow (3)$$

Sub eq (3) in (1)

$$i_1(t) = [5 + e^{-t/5}] u(t)$$

-6.

$t = 0^-$

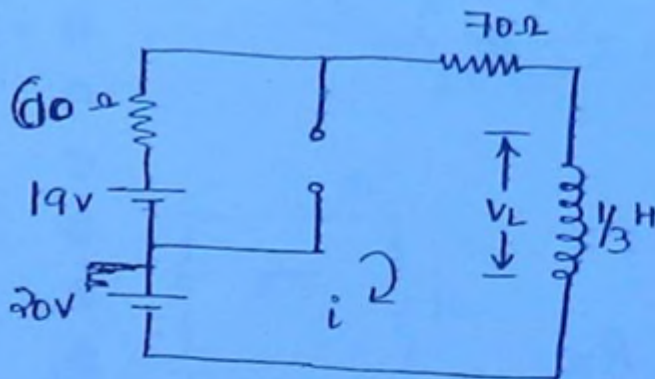


(17)

$$i(0^-) = \frac{20 + 19}{60 + 70}$$

$$i(0^-) = 0.3A$$

$t > 0$

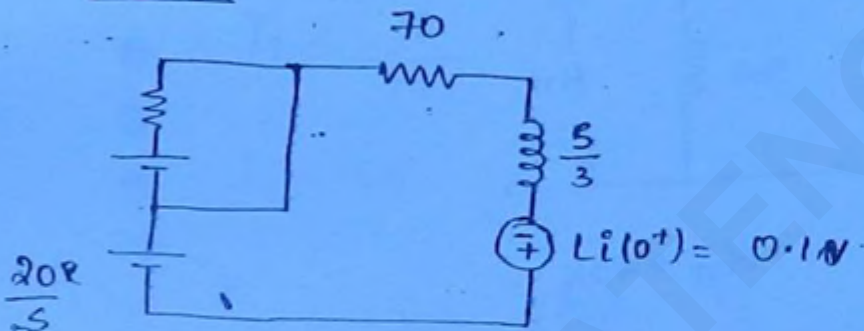


$$I(s) = \frac{\frac{20}{s} + 0.1}{70 + s/3} = \frac{3(20 + 0.1s)}{s[s + 210]}$$

$$= \frac{2/7}{s} + \frac{1/70}{s + 210}$$

$$i(t) = \left[ \frac{2}{7} + \frac{1}{70} e^{-210t} \right] u(t)$$

$$v(t) = L \frac{di}{dt} = \frac{1}{3} \left[ \frac{-210}{70} e^{-210t} \right]$$


$$v(t) = -e^{-210t}$$

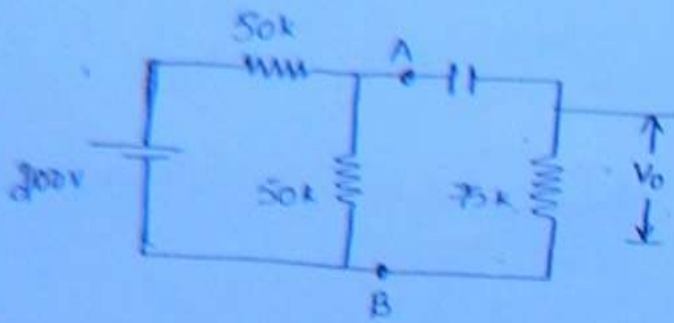


178

Thevenin eq. across AB.


Case i) ( $V_{Th}$ ).

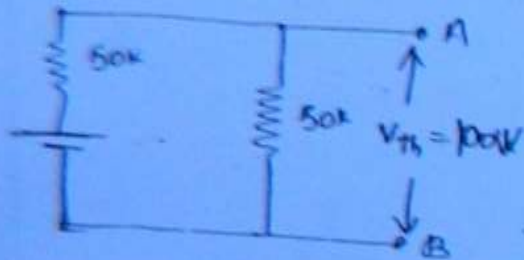


Case ii)  $R_{Th}$ .

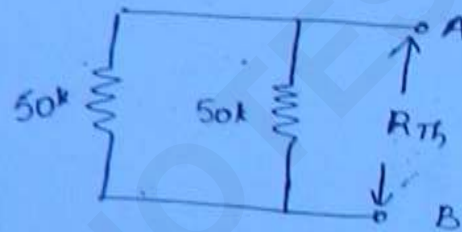

$$R_{Th} = 25k$$

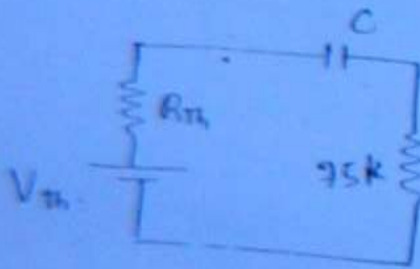

→ domain

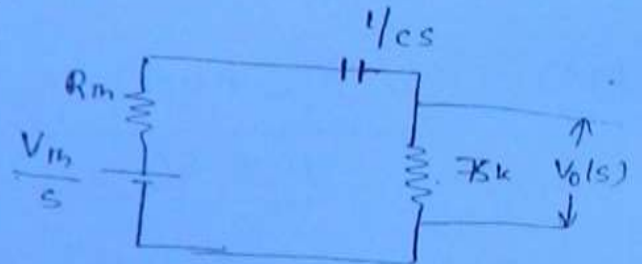

$$V_0(s) = \frac{V_{Th}}{s} \cdot \frac{75k}{75k + \frac{1}{Cs} + R_{Th}}$$

$$V_0(t) = \mathcal{L}^{-1}\{V_0(s)\}$$

at  $t = t_0$

$$V_0(t) = 75e^{-10t}$$

$$V_0(t) = 75e^{-(t-t_0)}$$

$t = t_0$

$$V_0 = 75V$$

$$t = 25 \times 10^{-3} \Rightarrow V_0(t) = e^{-10(25 \times 10^{-3} - t_0)}$$




# Theorems obj.

25.

$$i = \frac{V_1 - V_2}{1 \times 10^6} \Rightarrow R_{CRO} = \frac{V_2}{i}$$


129

28.

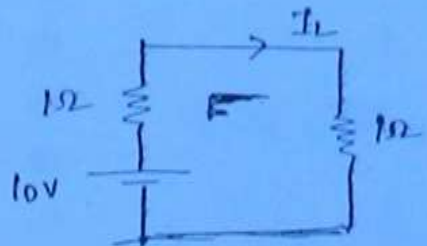

$$I_L = \frac{10}{1+1}$$

$$I_L = 5A$$

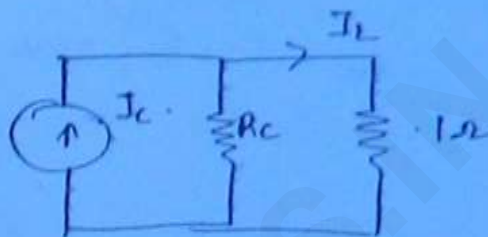

$$I_L = I_C \cdot \frac{R_C}{R_C + 1}$$

$$5 = \frac{I_C R_C}{R_C + 1}$$

ans: (b)


check the values

30.

$$P_{max} = \frac{V_s^2}{4R_L} \Rightarrow R_L = R_s = 100\Omega$$


$$P_{max} = 0.25W \quad \text{--- (c)}$$

31.

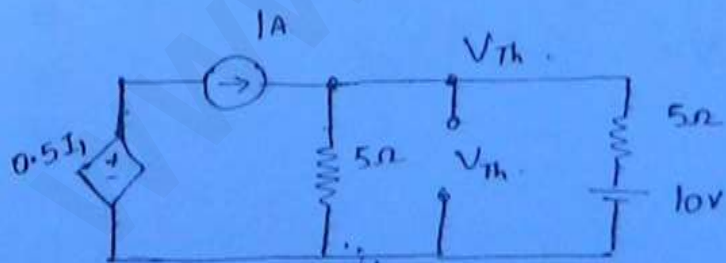

$$I = \frac{V_{Th}}{5} + \frac{V_{Th} - 10}{5} \Rightarrow V_{Th} = 7.5V$$

$$R_{Th} = 5/2 = 2.5\Omega$$

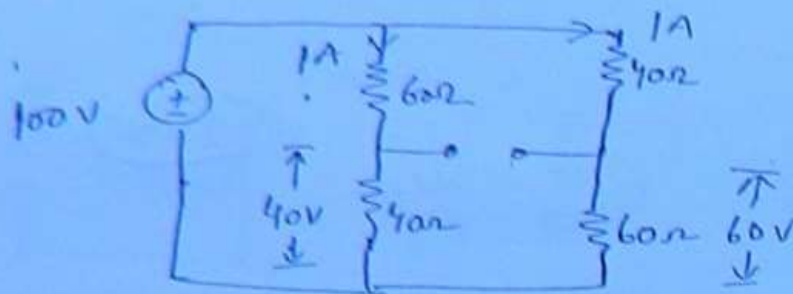

186

$$V_{Th} = 60 - 40 = 20V.$$



Ans:

In balanced bridge voltage across adjacent branches is same.

$$E = E_1, \quad I = 0, \quad V = 5 \Rightarrow V_{oc} = 5V.$$

$$E = 0, \quad I = 1, \quad V = 5 \Rightarrow R_{Th} = 5\Omega$$

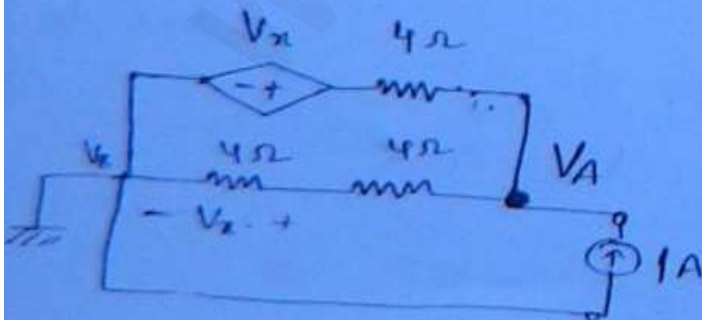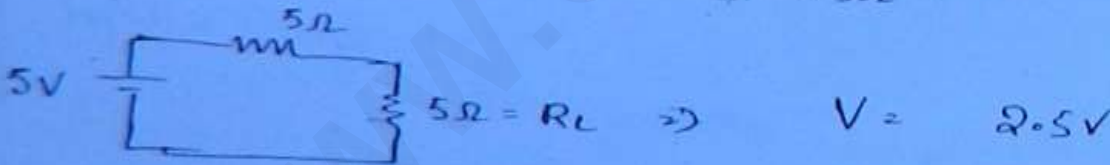
$$E = 5V, \quad I = 1, \quad V = 5 \Rightarrow R_{Th} = 5\Omega$$



$$I = \frac{V_A}{8} + \frac{V_A - V_x}{4}$$

$$V_x = V_A/2$$

39.

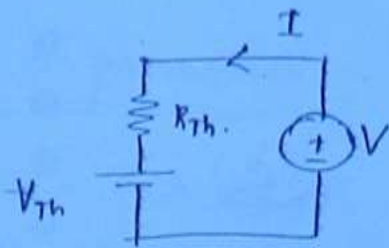

$$V - V_{Th} = IR_{Th}$$

(18)

$$V = V_{Th} + R_{Th} \cdot I \rightarrow (1)$$

$$I = \frac{V - V_{Th}}{R_{Th}}$$

$$I = 0.2V - 2$$

$$0.2V = I + 2 \rightarrow (2)$$

$$V = 5I + 10 \rightarrow (2)$$

Compare (1) & (2)


$$V_{Th} = 10V, R_{Th} = 5\Omega$$

40.

$$Z_L = Z_S^* \Rightarrow Z_L = 3 + j4$$

$$P_{max} = \frac{V_s^2}{4R_L} = \frac{240 \times 240}{4 \times 3} = 4.8 \text{ kW}$$

41.

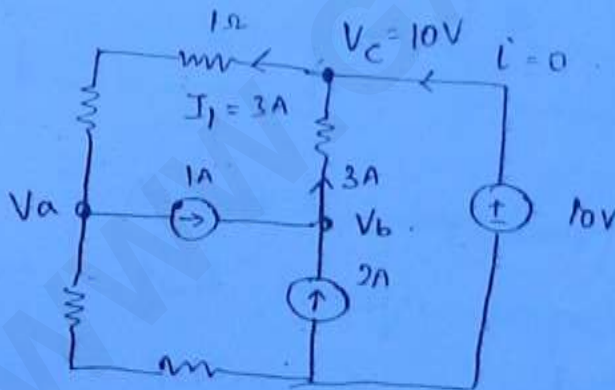

$$\frac{V_a}{2} + \frac{V_a - 10}{2} + 1 = 0$$

$$V_a = 4V$$

$$I_1 = \frac{10 - 4}{1 + 1} = 3A$$

44.

$$I_{sc} = \frac{16 \angle 0^\circ}{25 + 15 + j30}$$

$$I_{sc} = 6.4 - j4.8$$




# TWO PORT N/Ws

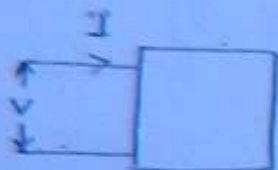
(182)

A pair of terminals at which signal may enter or leave from the network is called as port.

When n/w is having 1 pair of terminals then it is called as single port n/w.




Ex: motor

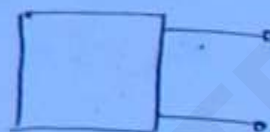

Ex: Generator

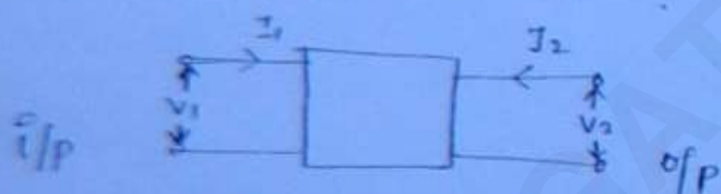When n/w is having two pair of terminals, then the n/w is called as 2 port n/w.



Ex: Transformer

## Classification of parameters

- $Z$  [ Open circuit parameters ].
- $Y$  [ Short circuit " ].
- $h$  [ Hybrid parameters ].
- $\phi$  [ Inverse hybrid parameters ].
- $ABCD$  [ Transmission line parameters ].
- $abcd$  [ Inverse " " " " ].

## Z parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow (1) \quad \text{kVL}$$

183


$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow (2) \quad \text{kVL}$$

$V_1, V_2 \} \rightarrow$  dependant variables.

$I_1, I_2 \} \rightarrow$  independent variables [source]

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

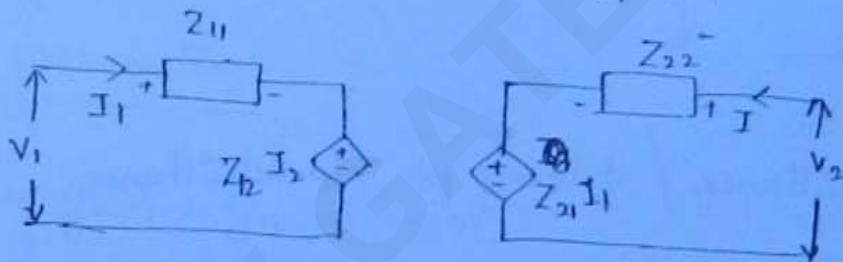

$Z_{11} \Rightarrow$  Open ckt i/p impedance / driving pt. i/p impedance

$Z_{21} \Rightarrow$  fwd transfer impedance

$Z_{12} \Rightarrow$  reverse "

$Z_{22} \Rightarrow$  O.C. o/p impedance (or) driving point o/p impedance

## Parameters ..

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (1) \quad \text{kcl}$$

(184)



$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (2) \quad \text{kcl}$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

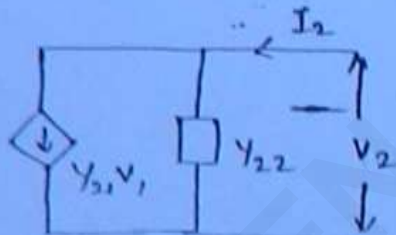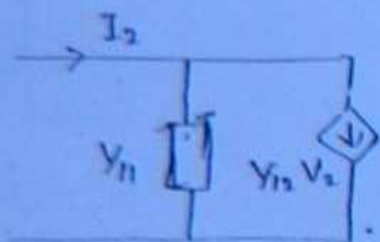

$y_{11} \rightarrow$  short ckt i/p admittance / driving pt. i/p admittance.

$y_{21} \rightarrow$  fwd transfer admittance.

$y_{12} \rightarrow$  reverse " " " "

$y_{22} \rightarrow$  short ckt o/p admittance / driving pt. o/p admittance.

## parameters

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (2)$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad \left( h_{11} \neq z_{11}, \quad h_{11} = \frac{1}{y_{11}} \right)$$





$$h_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad \left( h_{21} = \frac{Y_{21}}{Y_{11}} = \frac{I_2/V_1}{I_1/V_1} \right)$$

[no unit]

183

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad \left( h_{12} = \frac{Z_{12}}{Z_{22}} \right)$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} \quad \left( h_{22} \neq Y_{22}, \quad h_{22} = \frac{1}{Z_{22}} \right)$$

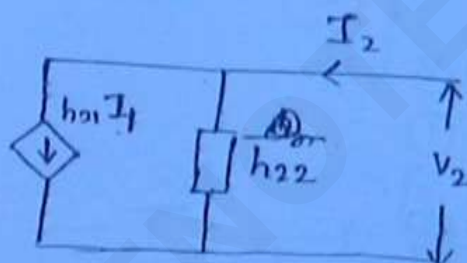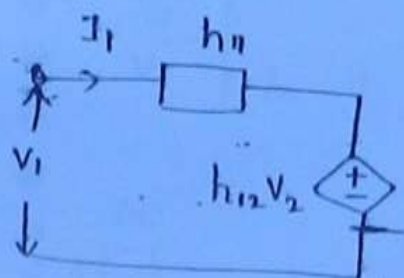

## g parameters

$$I_1 = g_{11} V_1 + g_{12} I_2 \rightarrow (1)$$

$$V_2 = g_{21} V_1 + g_{22} I_2 \rightarrow (2)$$


$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \quad \left( g_{11} \neq Y_{11}, \quad g_{11} = \frac{1}{Z_{11}} \right)$$

(mho)

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \quad \left( g_{21} = \frac{Z_{21}}{Z_{11}} \right)$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0} \quad \left( g_{12} = \frac{Y_{12}}{Y_{22}} \right)$$

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} \quad \left( g_{22} \neq Z_{22}, \quad g_{22} = \frac{1}{Y_{22}} \right)$$

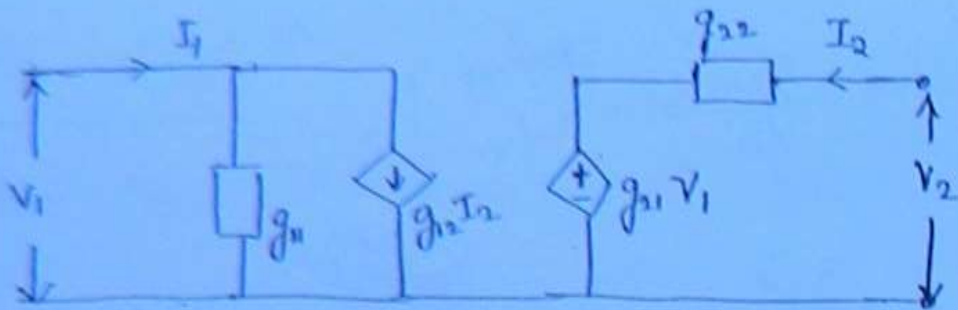

$$\begin{aligned} V_1 &= A V_2 - B I_2 \quad \text{--- (1)} \\ I_1 &= C V_2 - D I_2 \quad \text{--- (2)} \end{aligned}$$

186

### ABCD parameters

$$V_1 = A V_2 - B I_2 \quad \text{--- (1)}$$

$$I_1 = C V_2 - D I_2 \quad \text{--- (2)}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \left[ A = \frac{Z_{11}}{Z_{22}} \right]$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \left[ C = \frac{1}{Z_{21}} \right]$$

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0} \quad \left[ B = \frac{-1}{Y_{21}} \right]$$

$$D = \left. \frac{-I_1}{I_2} \right|_{V_2=0} \quad \left[ D = \frac{-Y_{11}}{Y_{21}} \right]$$

We: For ABCD parameters, it is not possible to develop equivalent circuit  $\because$  both eqn 1 & 2 are developed wrt I/p.

# abcd parameters

$$V_2 = aV_1 - bI_1$$

$$I_2 = cV_1 - dI_1$$


(187)

$$a = \left. \frac{V_2}{I_1} \right|_{I_1=0}$$


$$b = \left. -\frac{V_2}{I_1} \right|_{V_1=0}$$

$$c = \left. \frac{I_2}{V_1} \right|_{I_1=0}$$


$$d = \left. -\frac{I_2}{I_1} \right|_{V_1=0}$$

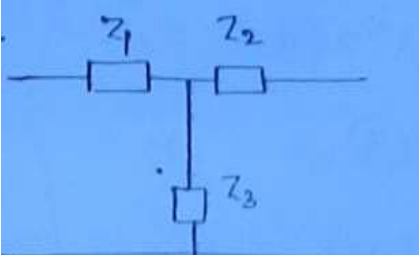


Unsymmetrical T

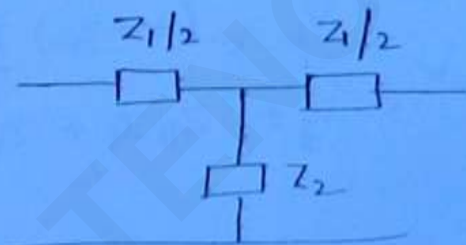


Symmetrical T

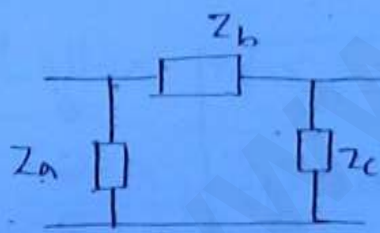

Unsymmetrical Pi

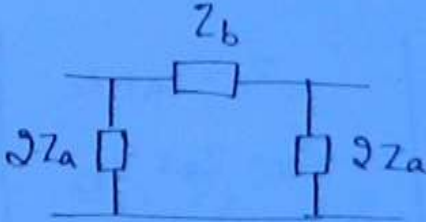

Symmetrical Pi

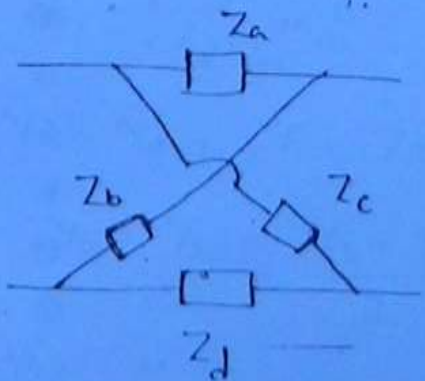

$\left. \begin{matrix} Z_a = Z_d \\ Z_b = Z_c \end{matrix} \right\} \rightarrow \text{Symmetrical lattice}$

$\left. \begin{matrix} Z_a \neq Z_d \\ Z_b \neq Z_c \end{matrix} \right\} \rightarrow \text{Unsymmetrical lattice}$



## symmetrical

$$Z_{11} = Z_{22}$$

$$Y_{11} = Y_{22}$$

$$h_{11}h_{22} - h_{21}h_{12} = 1$$

$$d = A = \bar{D}$$

## Reciprocal


$$Z_{12} = Z_{21}$$

$$Y_{12} = Y_{21}$$

$$h_{12} = -h_{21}$$

$$AD - BC = 1$$

188

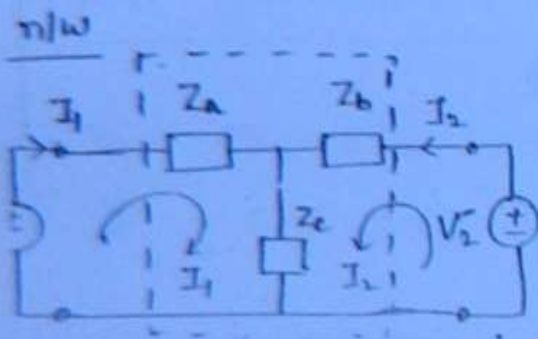

$$V_1 = (Z_a + Z_c) I_1 + Z_c I_2 \rightarrow (1)$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow (2)$$

$$V_2 = Z_c I_1 + (Z_b + Z_c) I_2 \rightarrow (3)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow (4)$$

$$Z_{11} = Z_a + Z_c$$

$$Z_{21} = Z_{12} = Z_c$$

$$Z_{22} = Z_b + Z_c$$

$$Z_{11} = Z_a + Z_c$$


$$Z_{11} = Z_a + Z_{12}$$

$$Z_a = Z_{11} - Z_{12}$$

$$Z_b = Z_{22} - Z_{12}$$

$$Z_c = Z_{12} = Z_{21}$$

II n/w

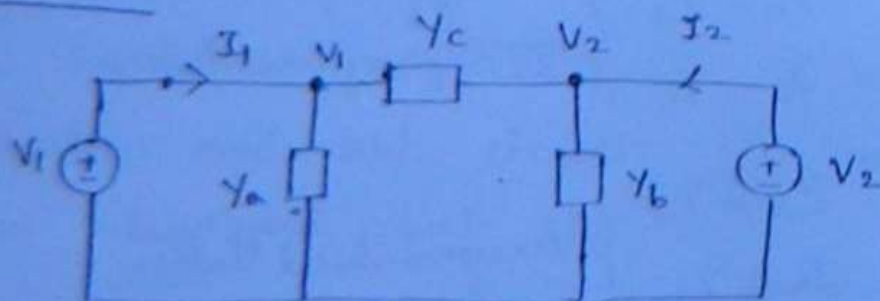

$$I_1 = V_1 Y_a + (V_1 - V_2) Y_c$$

$$I_1 = (Y_a + Y_c) V_1 - Y_c V_2 \rightarrow (1)$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (2)$$

189

$$I_2 = V_2 Y_b + (V_2 - V_1) Y_c$$

$$I_2 = -Y_c V_1 + (Y_b + Y_c) V_2 \rightarrow (3)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (4)$$


$$\begin{aligned} Y_{11} &= Y_a + Y_c \\ Y_{21} &= Y_{12} = -Y_c \\ -Y_{22} &= Y_b + Y_c \end{aligned}$$

$$\begin{aligned} Y_a &= Y_{11} + Y_{12} \\ Y_a &= Y_{22} + Y_{12} \\ Y_c &= -Y_{12} = -Y_{21} \end{aligned}$$

$$Y_{11} = Y_a + Y_c$$

$$\rightarrow Y_{11} = Y_a - Y_{12}$$

Lattice n/w

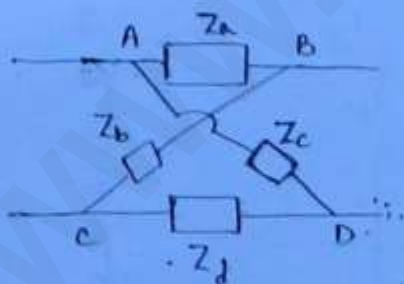

$$Z_a = Z_d, Z_b = Z_c \text{ } \} \text{ sy-lattice}$$


$$Z_{11} = Z_{22} = \frac{Z_b + Z_a}{2} \checkmark$$

$$Z_{12} = Z_{21} = \frac{Z_b - Z_a}{2}$$

$$Y_a = Y_d, Y_b = Y_c$$
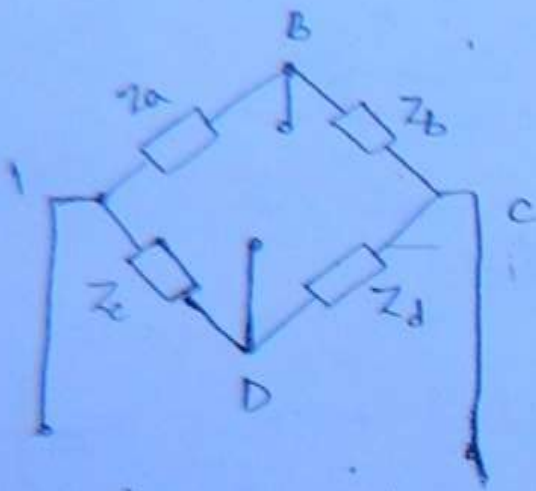
$$Y_{11} = Y_{22} = \frac{Y_b + Y_a}{2}$$






190

Bridge n/w

Equivalent Impedance parameters

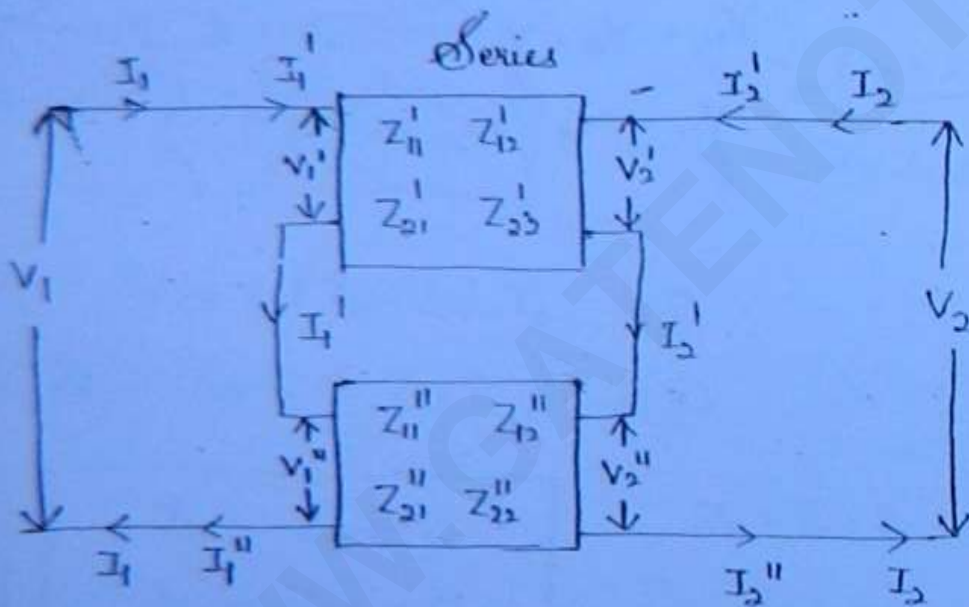

$$V_1 = V_1^I + V_1^{II}$$


$$V_2 = V_2^I + V_2^{II}$$

$$I_1 = I_1^I = I_1^{II}$$

$$I_2 = I_2^I = I_2^{II}$$
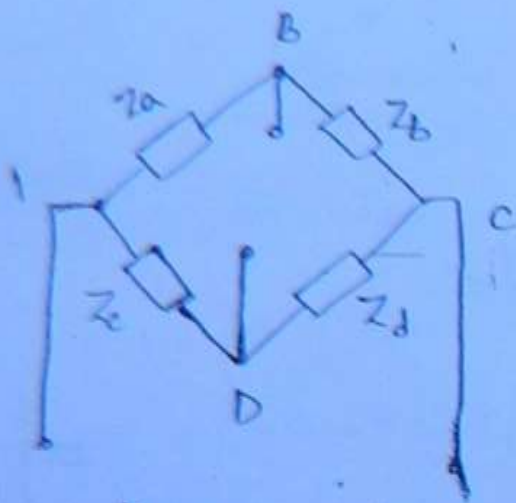
$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11}^I & Z_{12}^I \\ Z_{21}^I & Z_{22}^I \end{bmatrix} + \begin{bmatrix} Z_{11}^{II} & Z_{12}^{II} \\ Z_{21}^{II} & Z_{22}^{II} \end{bmatrix}$$






190

Bridge n/w

Equivalent Impedance parameters

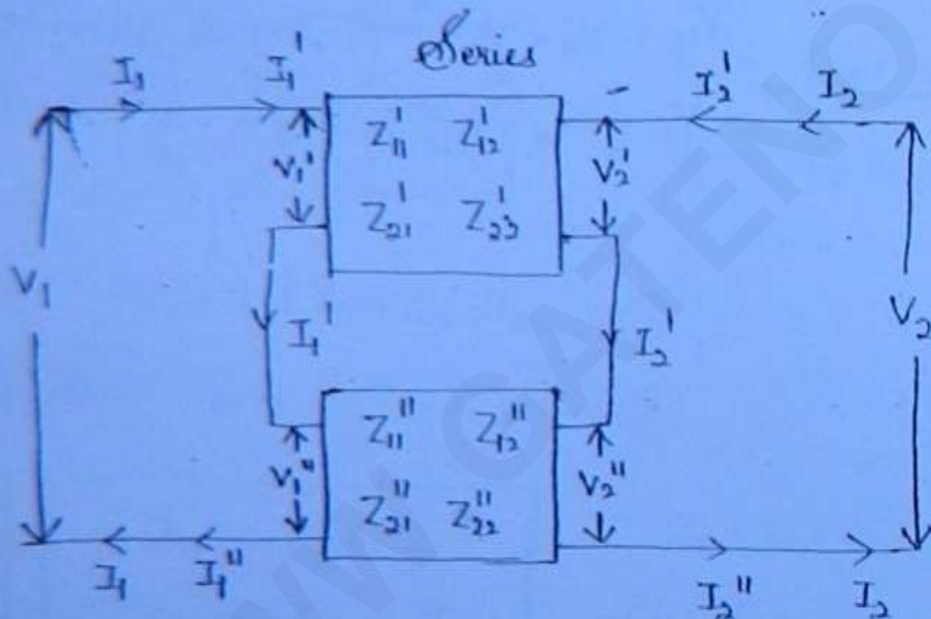

$$V_1 = V_1^I + V_1^{II}$$

$$V_2 = V_2^I + V_2^{II}$$


$$I_1 = I_1^I = I_1^{II}$$

$$I_2 = I_2^I = I_2^{II}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11}^I & Z_{12}^I \\ Z_{21}^I & Z_{22}^I \end{bmatrix} + \begin{bmatrix} Z_{11}^{II} & Z_{12}^{II} \\ Z_{21}^{II} & Z_{22}^{II} \end{bmatrix}$$

# Cascade / Tandem n/w

(192)

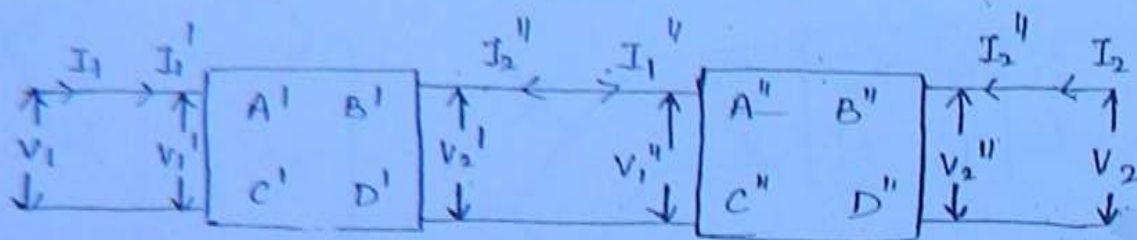

$$V_1 = V_1'$$

$$I_1 = I_1'$$

$$V_2' = V_1''$$

$$V_2 = V_2''$$


$$I_1'' = -I_2'$$

$$I_2 = I_2''$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \cdot \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix}$$

Ex 11

Find Z, Y & ABCD parameters of the n/w shown.

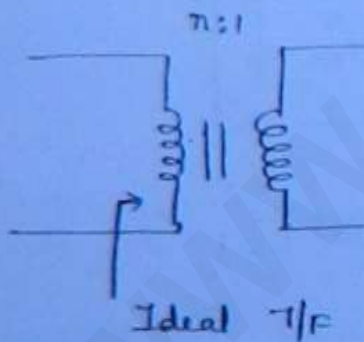

Ex 2

In the ideal T/F it is not possible to find impedance and admittance values, since self and mutual inductance of ideal T/F are  $\infty$ .

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{n}{1}$$


$$A = \frac{V_1}{V_2} = n$$

(193)

$$D = \frac{-I_1}{I_2} = \frac{+1}{n}$$

(∵ (-) sign is only for the current direction but not the parameter).

Equivalent resistance.

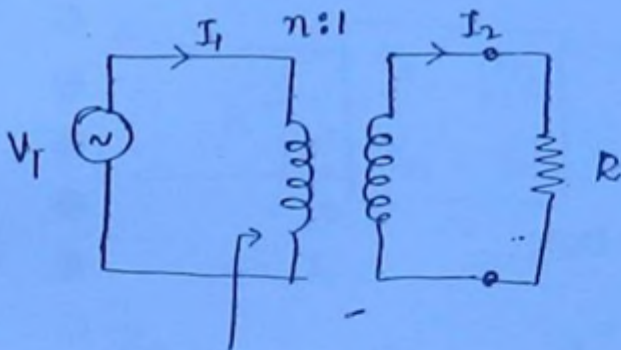

Ideal T/F

find the eq. i/p impedance resistance.

impedance

$$I_1^2 R_1 = I_2^2 R_2 \Rightarrow R_1 = \left( \frac{I_2}{I_1} \right)^2 R_2$$

$$R_1 = n^2 R$$

→ if inductor is given


$$L_1 = n^2 L$$

→ " capacitor " "

$$C_1 = \frac{C}{n^2}$$

Q. Find eq. impedance wrt

(i) 1-1'  
(ii) 2-2'

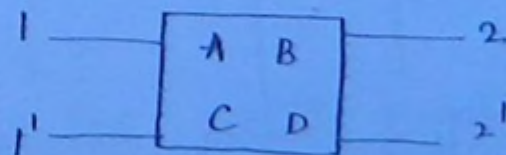



1-1'

$$Z_{eq} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2} \quad \Big|_{I_2=0}$$

194

$$Z_{eq} = \frac{A}{C} \Omega$$



2-2'

$$Z_{eq} = \frac{V_2}{I_2} \quad \Big|_{I_1=0}$$

$$I_1 = CV_2 - DI_2 \Rightarrow 0 = CV_2 - DI_2$$

$$Z_{eq} = \frac{D}{C} \Omega$$

Find eq. impedance wrt X & Y.

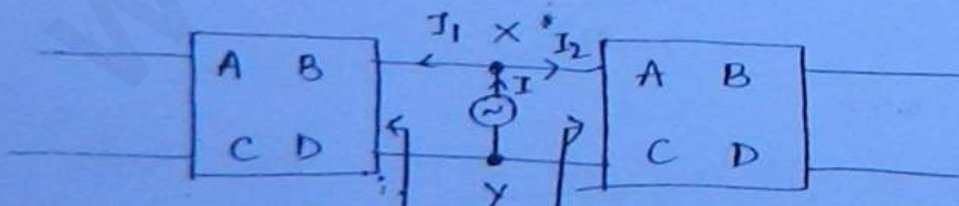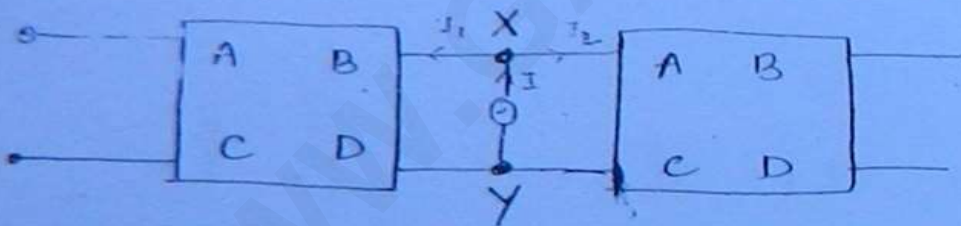

in previous prob)

$$Z_{eq1} = \frac{D}{C}$$


$$Z_{eq2} = \frac{A}{C}$$

$$Z_1 \parallel Z_2$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{AD/C^2}{(A+D)/C}$$

Q. Find eq admittance w.r.t A & B.

(195)

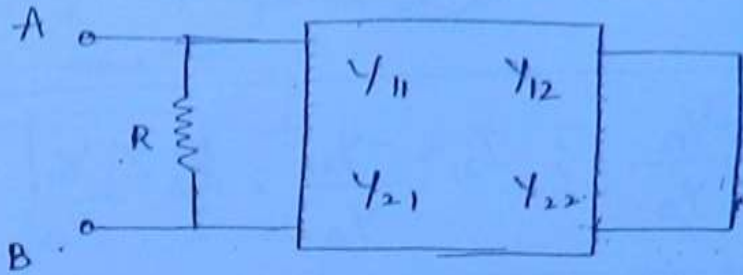


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$1/Y_{11}$

Soln.

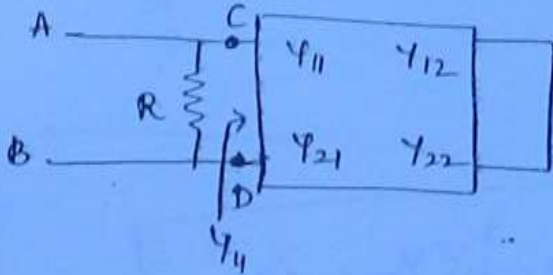

$$Y_{eq} = \frac{1}{R} + Y_{11}$$

$Y \rightleftharpoons Z$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \rightarrow (1)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{1}{Z_{11}Z_{22} - Z_{12}Z_{21}} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \rightarrow (2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \rightarrow (3)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{1}{Y_{11}Y_{22} - Y_{12}Y_{21}} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \rightarrow (4)$$

From (1) & (4)

(196)

$$Z_{11} = \frac{Y_{22}}{Y_{\Delta}} ; Z_{12} = \frac{-Y_{12}}{Y_{\Delta}} ; Z_{21} = \frac{-Y_{21}}{Y_{\Delta}} ; Z_{22} = \frac{Y_{11}}{Y_{\Delta}}$$


$$Y_{\Delta} = Y_{11}Y_{22} - Y_{12}Y_{21}$$

from (2) & (3)


$$Y_{11} = \frac{Z_{22}}{Z_{\Delta}} ; Y_{12} = \frac{-Z_{12}}{Z_{\Delta}} ; Y_{21} = \frac{-Z_{21}}{Z_{\Delta}} ; Y_{22} = \frac{Z_{11}}{Z_{\Delta}}$$

$$Z_{\Delta} = Z_{11}Z_{22} - Z_{12}Z_{21}$$

Find eq. impedance wrt A & B.

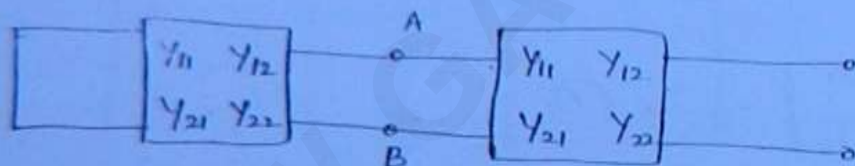

Reqd

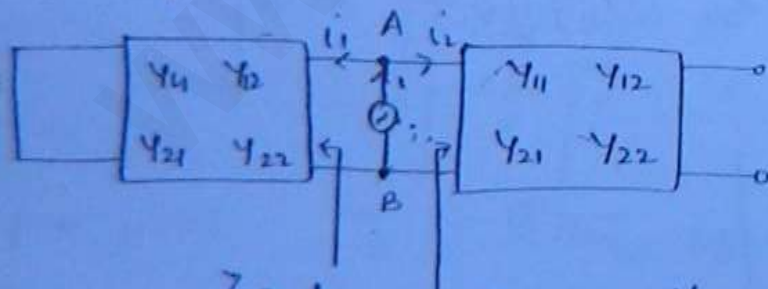

$$Z_1 = \frac{1}{Y_{22}}$$


$$Z_{11} = \frac{Y_{21}}{Y_{11}Y_{22} - Y_{12}Y_{21}}$$

$$Z_{eq} = Z_1 \cdot Z_{11}$$

$$Y_{22} / Y_{11}$$




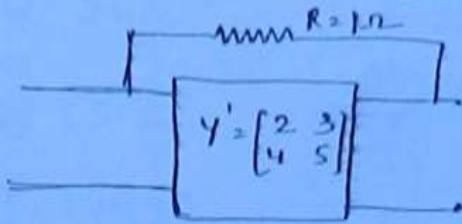Q. when two, 2port n/ws are connected in parallel, -  
find eq: Y parameters.




(197)

Soln.

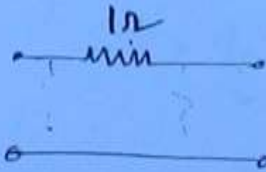

~

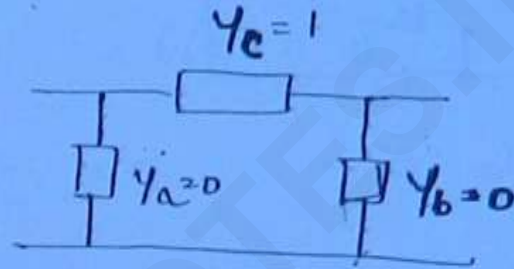

$$Y_{11}'' = Y_a + Y_c = 1$$

$$Y_{22}'' = Y_b + Y_c = 1$$


$$Y_{12}'' = Y_{21}'' = -Y_c = -1$$

$$Y'' = \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$


$$[Y] = [Y'] + [Y''] = \begin{bmatrix} 2 & 3 \\ 4 & 5 \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$

$$[Y] = \begin{bmatrix} 3 & 2 \\ 3 & 6 \end{bmatrix}$$


Q. Find B & D of the n/w shown.

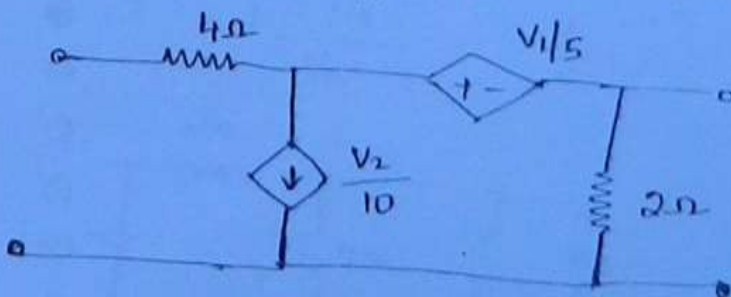

$$V_1 = 1V$$

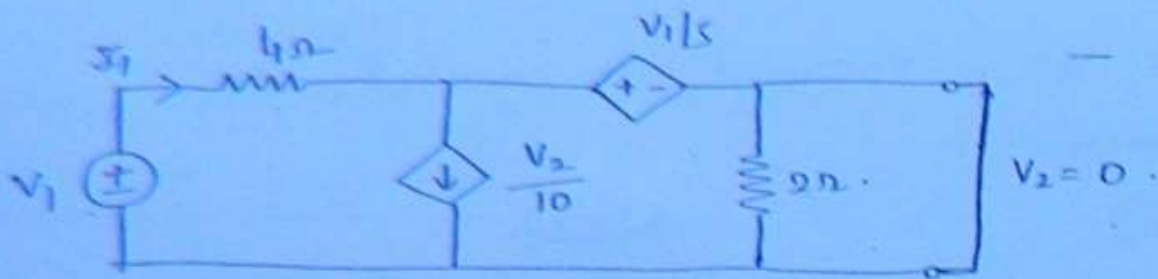

(198)

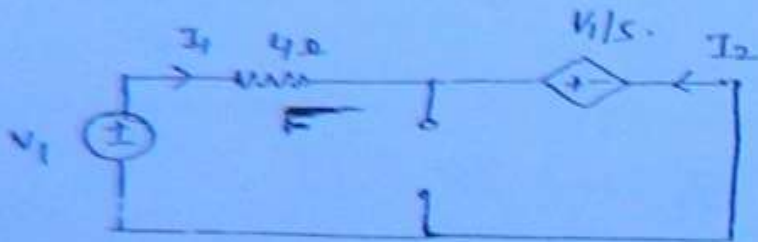

$$I_1 = -I_2 \Rightarrow$$

$$D = \frac{-I_1}{I_2} = 1$$


$$\underline{D = 1}$$

$$V_1 - 4I_1 - V_1/s = 0 \Rightarrow V_1 + 4I_2 - V_1/s = 0$$

$$\frac{4V_1}{s} = -4I_2 \Rightarrow \frac{V_1}{I_2} = -s$$

$$\underline{B = -s}$$

Transient W.B.

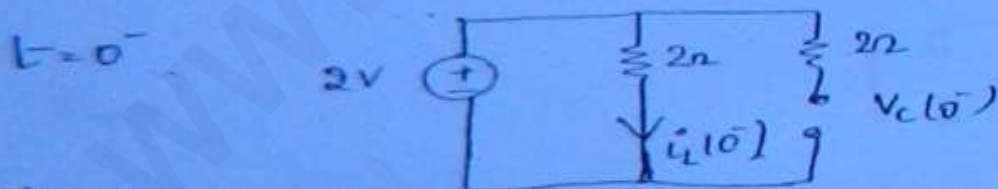

$$i_L(0^-) = \frac{2}{2} = 1A$$


$$V_C(0^-) = 2V$$

$$t > 0,$$

$$V_C(0^+) = 2V$$

$$i_L(0^+) = 1A$$

S-domain

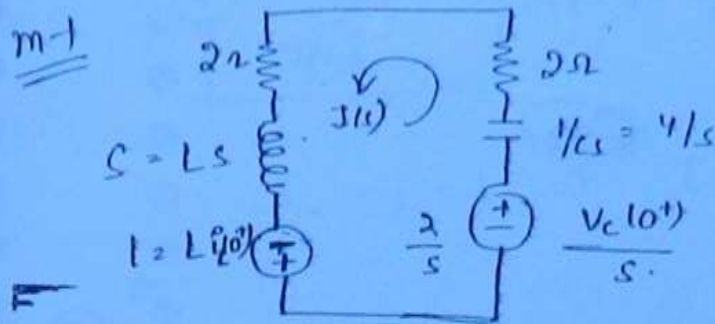

$$\gamma = 1/2 = 0.5$$

(b)

799

$$I(s) = \frac{2/s + 1}{2 + 2 + \frac{4}{s} + s}$$

$$i(t) = e^{-t/1/2}$$

$$i(t) = e^{-2t}$$

m-2

$$\text{Time const.} = \frac{2L}{R} = \frac{2 \times 1}{4} = \underline{\underline{1/2 \text{ sec}}}$$

current in inductor is decaying  $\therefore$  not oscillatory.

8. (i) In the above circuit energy transformation is continuously done b/w inductor & capacitors. Thereby output response is oscillatory.


(ii) In the above circuit no energy loss is present.  
 $\therefore$  resistance  $= 0$ .

Ans (b)

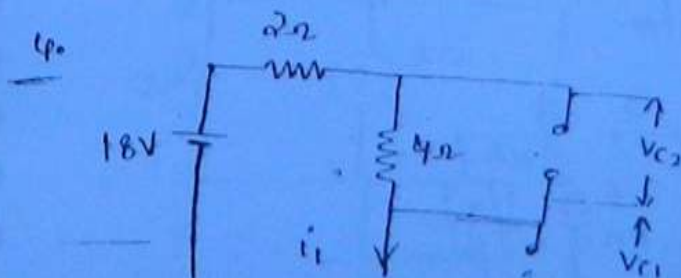2.

$$I = 1 \cdot \frac{1/8}{1/2 + 1/8} = \frac{1}{5}$$

$$V = I \cdot 1/2 = \underline{\underline{0.1V}}$$




$$i_L = \frac{18}{2+4} = 3A$$



$$-V_{C2} = 12 \cdot \frac{C}{C+2C} = 4V$$

$$V_{C1} = 12 - 4 = 8V$$

200

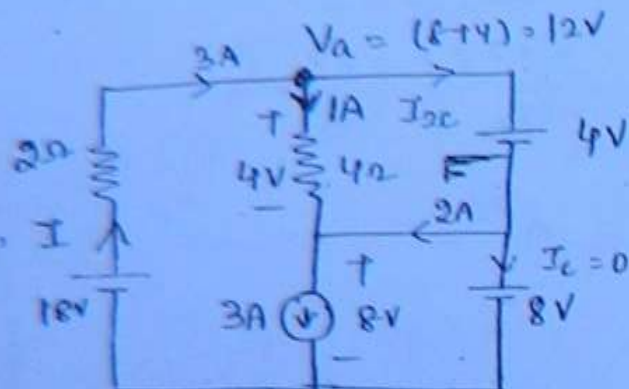

$$\beta = 1 + I_{2C}$$

$$I_2 = 2A$$

$$I = \frac{18 - 12}{2} = 3A$$

$$V = IR + L \frac{di}{dt} \Rightarrow 18 = 6 \times 1 + L(6)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} \Rightarrow V_o(s) = \frac{1}{(s-2)(s-3)} \Rightarrow L = 2H$$


Initial & final value theorems.


at  $t \rightarrow \infty$ , energy in the inductor is totally dissipated.  
 current in  $R = 0$  at  $t = \infty$

$$i(t) = I \sin(\omega t + 30^\circ)$$

current leads  $\rightarrow$   $X =$  Capacitor

$$i(0^+) = \frac{I}{2}$$

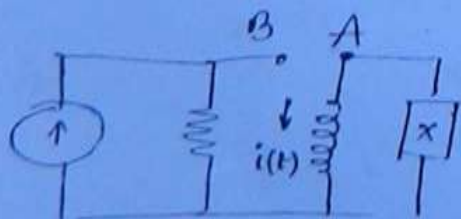


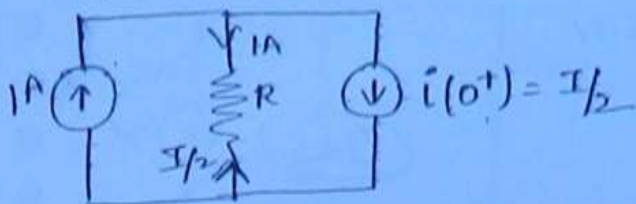

20)

$$\frac{I}{2} - 1 = 1 \Rightarrow I = 4A.$$

11)

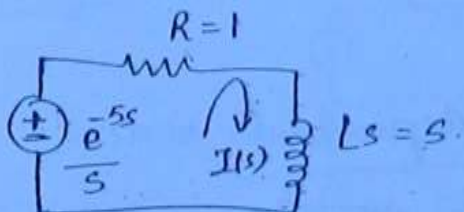

12)

$$H(s) = \frac{1}{s+1}, \quad V_i = \cos t.$$

$$H(j\omega) = \frac{1}{j\omega+1} = \frac{V_o}{V_i} \Rightarrow \frac{1}{j+1} = \frac{1}{\sqrt{2}} \angle -45^\circ = \frac{V_o}{V_i}$$

$$V_o = \frac{V_i}{\sqrt{2}} \angle -45^\circ = \frac{1}{\sqrt{2}} \cos(t - 45^\circ)$$



13)

$$V_R = V_L = V/2, \quad V_L = V/2.$$

$$V e^{-Rt/L} = V/2 \Rightarrow e^{-t/\tau} = \frac{1}{2}.$$



$$t = -\tau \ln(1/2).$$

15)

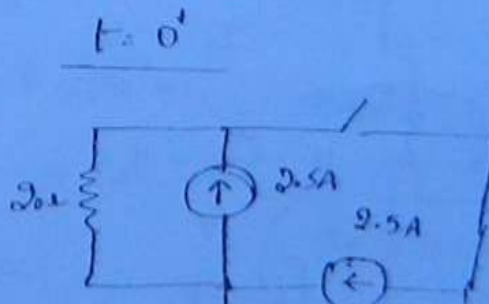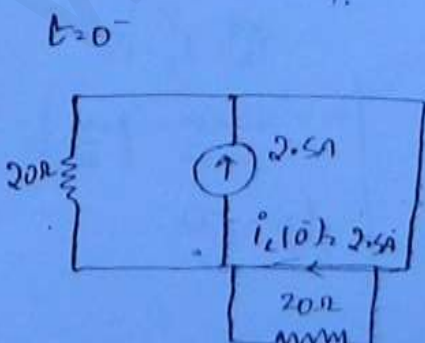

$$V_x = -(2.5) \times (20) = -50V$$

16.

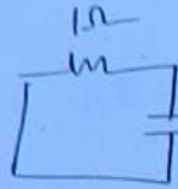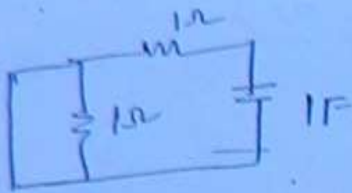

202

$$\tau = RC = 1 \text{ sec}$$

106.

while finding  $\tau$  deactivate all independent sources.  
 $\tau$  is calculated after operating the switch.

$$t = 0^+$$

$$iR + L \frac{di}{dt} + E_2 = 0$$

$$-8R + 2(1) - 4R = 0$$


$$R = 0.5 \Omega$$

$$t = \infty, L \rightarrow SC$$

$$E_2 = -i(\infty)R$$

$$E = -4R$$

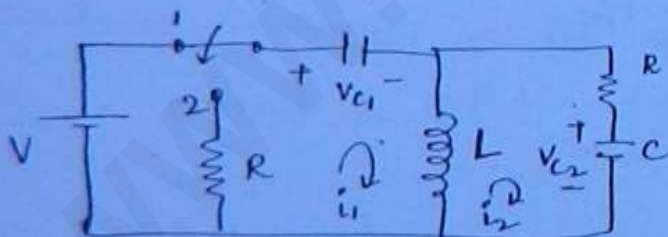
$$V(t) = (C_1 + C_2 t) e^{\alpha t} \Rightarrow \text{critically damped}$$



$$V_{C1} = V$$

$$V_{C2} = 0$$

$$i_L = 0$$

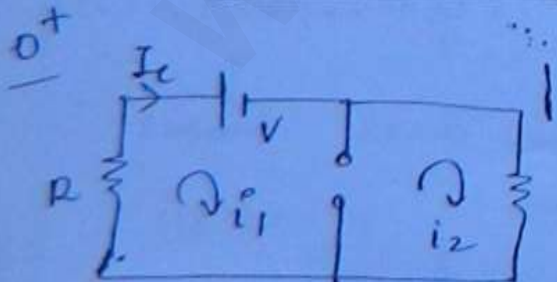

$$I_c = \frac{V}{R+R} = \frac{V}{2R}$$

$$i_1 = I_c = \frac{V}{2R}$$

$$i_2 = -V$$


$$i_L = i_1 - i_2$$

$$= \frac{V}{2R} - \left( -\frac{V}{2R} \right)$$

$$i_L = 0$$



Q3.

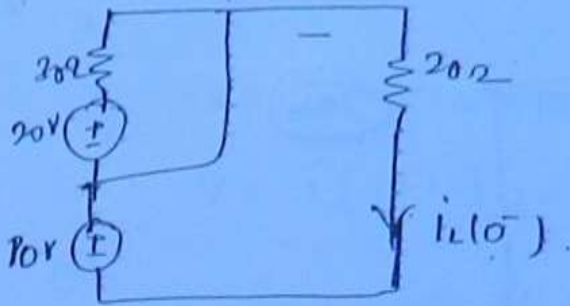


$$i_L(0^-) = 10/20$$

(20Ω)

$$i_L(0^-) = 0.5A = i_L(0^+)$$

$t = \infty$

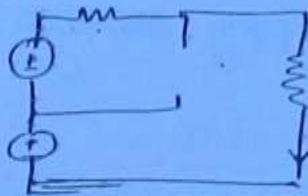


$$i(\infty) = \frac{10 + 20}{30 + 20} = 0.6$$

$$\tau = \frac{1}{50}$$

$$i(t) = 0.6 - 0.1e^{-50t}$$


Q5

$t = 0^-$

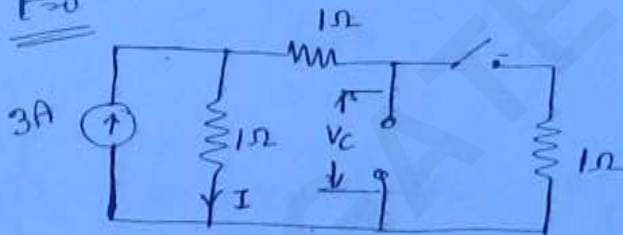

$$V_C = 3 \times 1 = 3V$$

$t = 0^+$

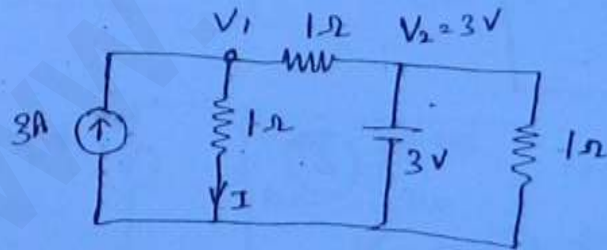

$$3 = \frac{V_1}{1} + \frac{V_1 - 3}{1}$$

$$V_1 = 3$$


$$I = \frac{V_1}{1} = \frac{3}{1} = 3A$$


Q6.

$$\tau = RC$$

$$= 10^3 \times 10^{-7} \rightarrow \tau = 10^{-4} \text{ sec}$$

$$V_2 = -3V$$

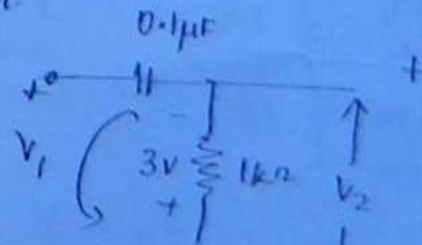


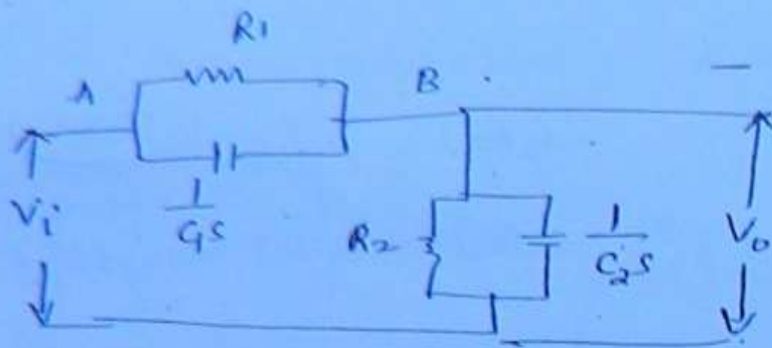

204

Transform in  $s$  domain & apply voltage division  
ans. (C)


$t=0^-$

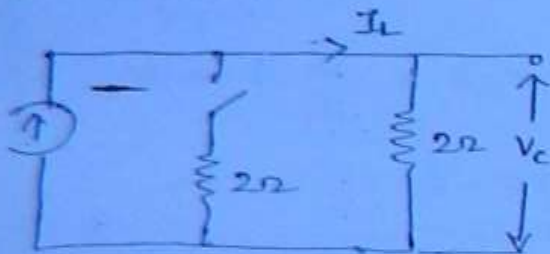

$$V_C = 2 \times 2 = 4V$$

$$I_L = 2A$$

$t=0^+$

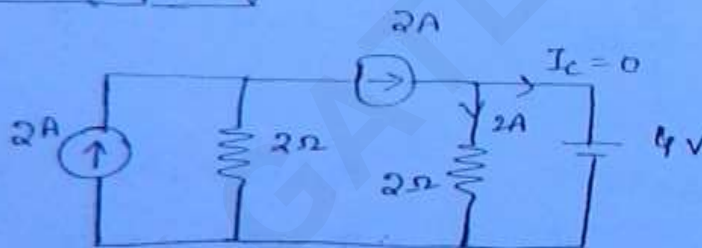

$$V(0^+) = 4V$$


$$I_C = C \frac{dv}{dt}$$

(B)

$$i(t) = [i(0^+) - i(\infty)] e^{-t/RC} + i(\infty)$$

(B)

(a) 3V

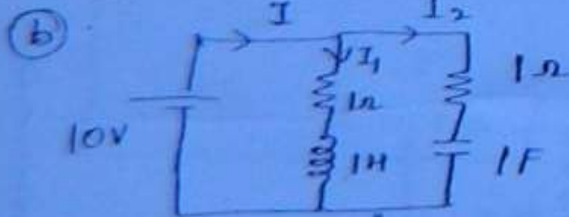

$$I = I_1 + I_2$$

$$I_1 = \frac{V}{R} (1 - e^{-Rt/L})$$


$$I_2 = \frac{V}{R} e^{-t/RC} = 10 e^{-t}$$

40. (d) -

41.

$$\frac{V}{10} = 2A \Rightarrow V = 20V$$

$$V = i[10+5] = 2[15] = 30V$$

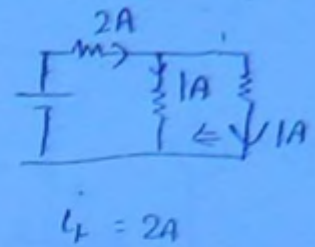

(a)

(20)

42.

(a)  $Z_{12} = 20 \Omega$

(b)  $Y_{12} = \frac{-Z_{12}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = 0.2$


(c)  $h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{Z_{12}}{Z_{22}} = \frac{20}{10} = 2.0$

(d)  $A = \frac{V_1}{V_2} \Big|_{I_2=0} \left( A = \frac{Z_{11}}{Z_{21}} \right)$


$$\begin{array}{r} 20 \\ 10 \end{array} = 2$$

43.

$t=0^-$

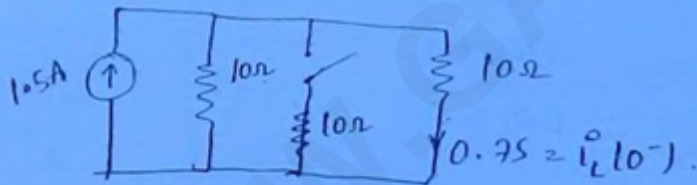


$t=0^+$

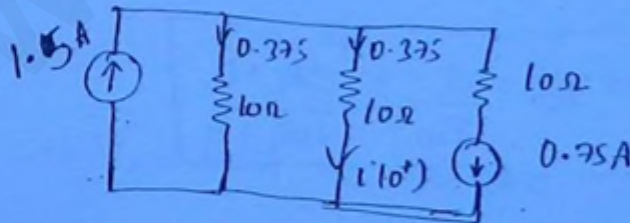

$i_L(0^+) = 0.75A$


$t=\infty$

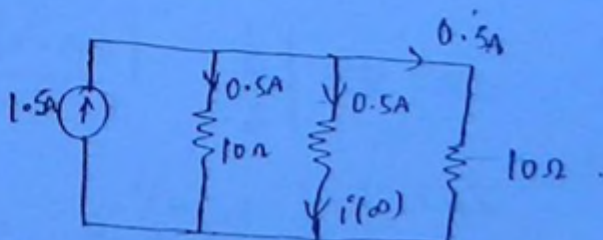

(a)



Two port W.B

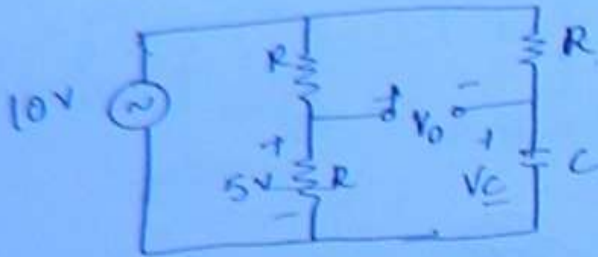

$$V_c = \frac{-jX_c}{R - jX_c}$$

206


$$-5 + V_0 + V_c = 0$$

$$V_0 = 5 - V_c$$

$$V_0 = 5 + \frac{10jX_c}{R - jX_c}$$

$$|V_0| = 5 \frac{|R + jX_c|}{|R - jX_c|}$$

$$\Rightarrow |V_0| = 5V$$

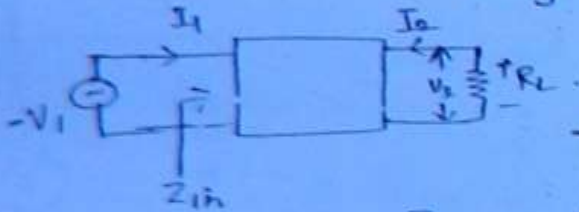

$$V_2 = -I_2 R_L$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2}$$


$$Z_{in} = \frac{A(-I_2 R_L) - B(I_2)}{C(-I_2 R_L) - D(I_2)} \Rightarrow \frac{AR_L + B}{CR_L + D}$$

$$= \frac{1 \times 10 + 2}{1 \times 10 + 3} = 12/13$$

$$Z_{in} = \frac{AR_L + B}{CR_L + D}$$

$$Y_{in} = \frac{1}{Z_{in}} = \frac{CR_L + D}{AR_L + B}$$

addition of matrices (b)

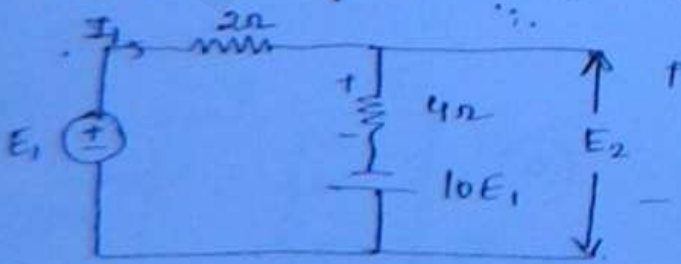

$$Z_{21} = \left. \frac{E_2}{I_1} \right|_{I_2=0}$$

$$Z_{11} = \left. \frac{E_1}{I_1} \right|_{I_2=0} = \frac{6}{11}$$


$$I_1 = \frac{E_1 + 10E_1}{2}$$

$$E_1 = \frac{6}{11} I_1$$

# 5. Π - T transform

6.  $I(s) = \frac{V(s)}{Z(s)} = \frac{1/s}{(s+2)/(s+3)} =$

207

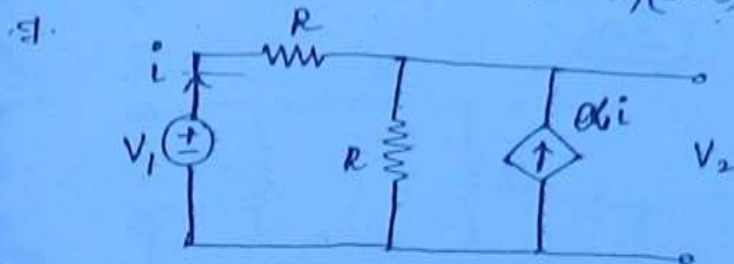


$i + \alpha i = V_2/R \rightarrow (1)$

$i = \frac{V_1 - V_2}{R} \rightarrow (2)$

(C)

11.

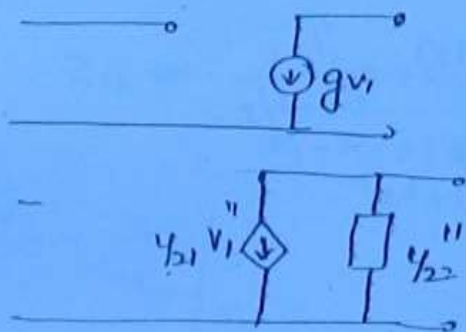

$y_{11} = y_{22} = -y_{12} = -y_{21} = Y$

$y_{21}'' = g$


$y_{21} = -Y$

$y_{21} = y_{21} + y_{21}''$

$-y_{21} = -Y + g$

(C)

12.

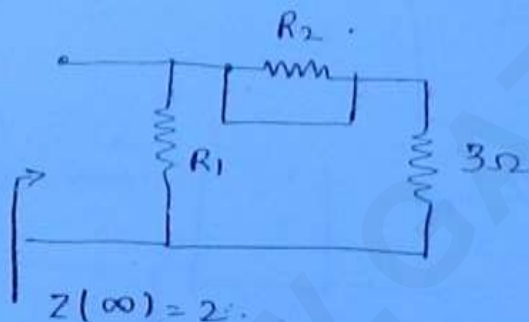

$s \rightarrow \infty$

$X_C = 1/sC = 0$

$C \rightarrow S.C.$

$2 = \frac{R_1 \cdot 3}{3 + R_1} \Rightarrow R_1 = 6\Omega$


$s \rightarrow 0 \Rightarrow X_C = \infty \Rightarrow C \rightarrow O.C$

$Z(0) = 3 \therefore$

$3 = \frac{R_1(3 + R_2)}{R_1 + R_2 + 3}$

1


$R_2 = 3\Omega$

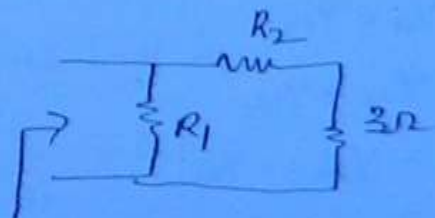

13.

$\frac{V_c}{V_i} = \frac{1/100\mu s}{10k + 10ms + 1/100\mu s}$

(D)

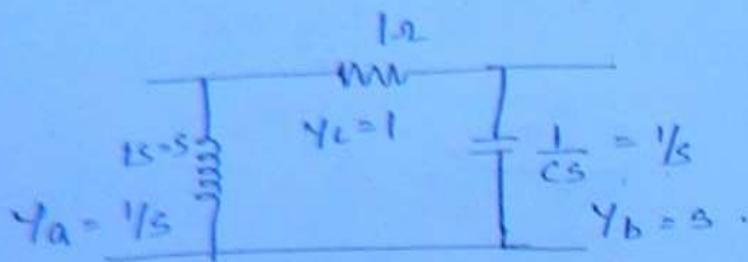


(208)

$$Y_{11} = Y_a + Y_c =$$

$$Y_{22} = Y_s + Y_c$$

$$Y_{12} = Y_{21} = -Y_c$$

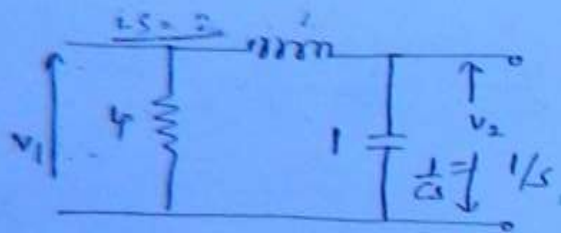


$$V_2(s) = V_1(s) \cdot \frac{1/s}{2s + 1/s} = \frac{1}{1 + 2s^2}$$

(d) is product @.

$$D = \frac{-I_1}{I_2} \bigg|_{V_2=0}$$
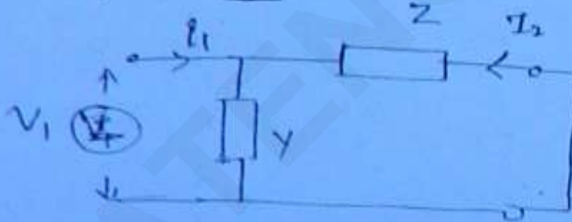
$$I_2 = \frac{-I_1 \cdot 1/Y}{Z + 1/Y} \Rightarrow D = 1 + YZ$$



$\Pi - T$



$$Y_{11} = 5, \quad Y_{12} = Y_{22} = -1, \quad Y_{22} = 1$$

$$Y_1 = Y_{11} + Y_{12}$$

$$Y_2 = Y_{22} + Y_{12}$$

$$Y_3 = -Y_{12} = -Y_{21}$$

transform to s domain

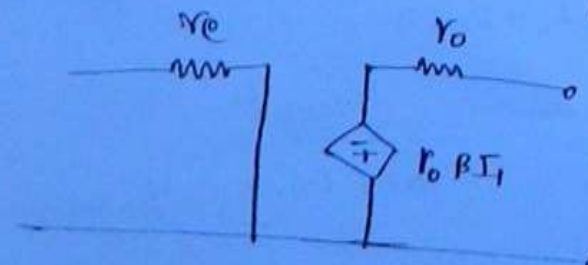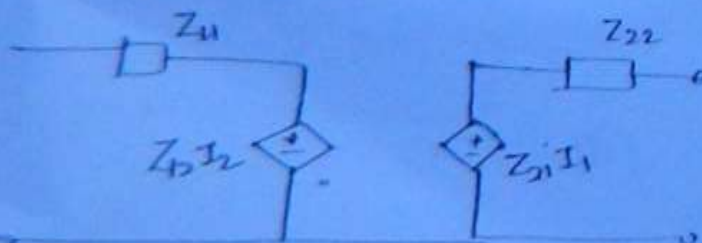



27.


$$Z_{11} = Z_{11} - Z_{12}$$

$$Z_{22} = Z_{22} - Z_{12}$$

$$Z_{12} = Z_{21} = Z_{12}$$

209

28.

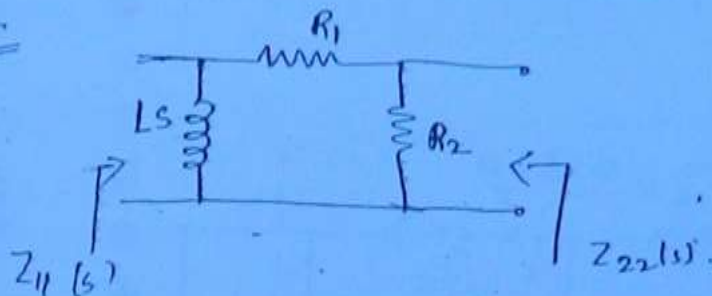


$$Z_{11} = \frac{Ls(R_1 + R_2)}{R_1 + R_2 + Ls}$$

$$Z_{22}(s) = \frac{R_2(Ls + R_1)}{R_1 + R_2 + Ls}$$



29.

$$Y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0}$$

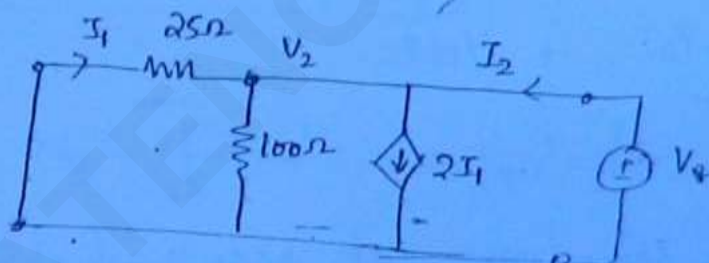


$$I_1 = \frac{-V_2}{25} \Rightarrow \frac{I_1}{V_2} = -0.04$$

30.

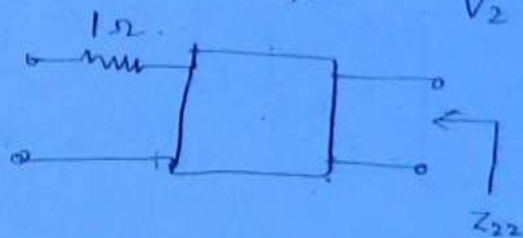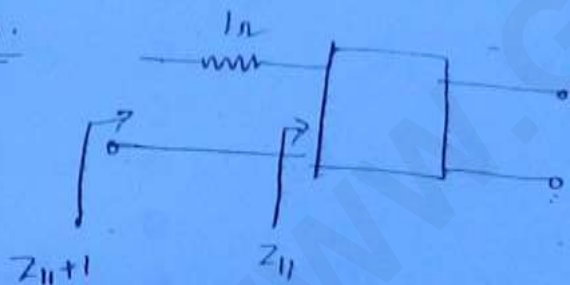


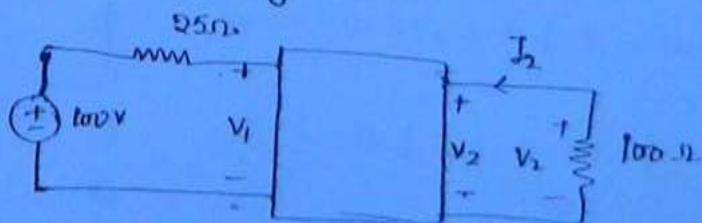whenever a linear element is added, there will be no variation in  $Z_{22} = \frac{V_2}{I_2}$  &  $Z_{21} = \frac{V_2}{I_1}$  but  $Z_{11}$  will vary.



$$V_2 = -100 I_2, \quad I_2 = -V_2 / 100$$

Conv.

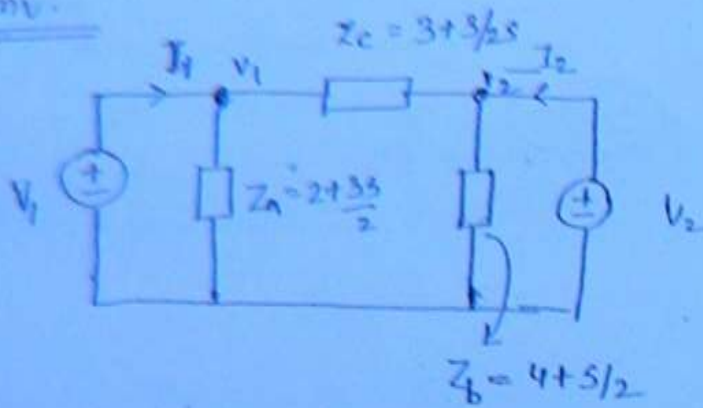

(2/0)

$$I_1 = \frac{V_1}{Z_A} + \frac{V_1 - V_2}{Z_C}$$

$$I_1 = V_1 \left[ \frac{1}{Z_A} + \frac{1}{Z_C} \right] - \frac{V_2}{Z_C}$$

$$I_1 = V_1 Y_{11} + Y_{12} V_2$$

$$Y_{11} = \frac{1}{Z_A} + \frac{1}{Z_C}, \quad Y_{12} = \frac{1}{Z_C}$$

By apply the same proc. at node 2  $V_2$ . & find  $Y_{22}, Y_{21}$



$$V_S = V_1 + I_1 R_S$$

$$V_0 = V_S - I_1 R_S$$

$$V_2 = -I_2 R_L$$

$$V_1 = V_S - I_1 R_S$$

$$V_2(s) = -I_2(s) \cdot 1$$

$$V_1(s) = \frac{1}{s} - 2 I_1(s)$$

$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} 2 \\ 1 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$

$$\begin{bmatrix} 1/s - 2 I_1(s) \\ -I_2(s) \end{bmatrix} = \begin{bmatrix} 2 \\ 1 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$


Solve the above matrix & find  $I_2(s)$ .

$$V_2(s) = -I_2(s)$$

(211)

$$V_2(t) = \mathcal{L}^{-1}\{V_2(s)\} = \left[ 0.037 + 0.0456e^{-1.9t} - 0.083e^{-7.08t} \right]$$

3.

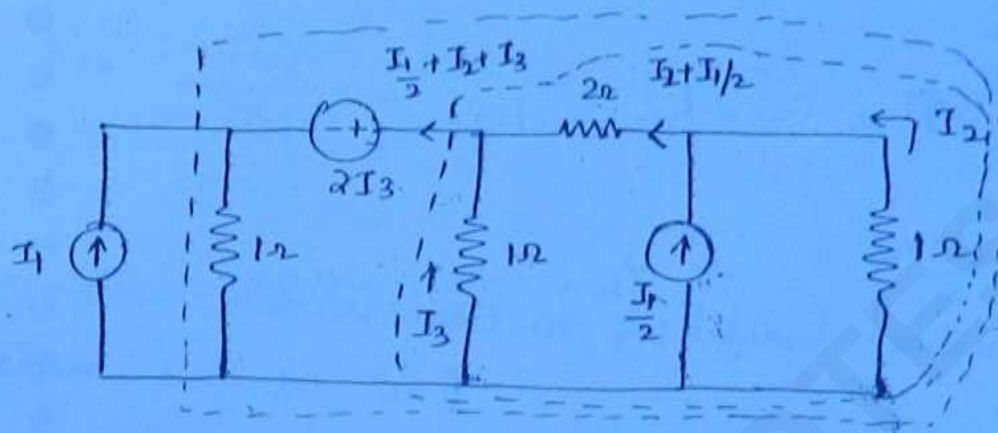

$$1 \times I_2 + 2 \left( I_2 + \frac{I_1}{2} \right) + 2I_3 + 1 \left( \frac{3I_1}{2} + I_2 + I_3 \right) = 0 \rightarrow (1)$$

$$(1 \times I_2) + 2 \left( I_2 + \frac{I_1}{2} \right) - (I_2 \times 1) = 0 \rightarrow (2)$$


from eq. (2)

$$I_3 = I_2 \times 1 + 2 \left( \frac{I_1 + I_2}{2} \right) \rightarrow (3)$$

Sub eq. (3) in (1)

$$Ans = -11/26$$

4.

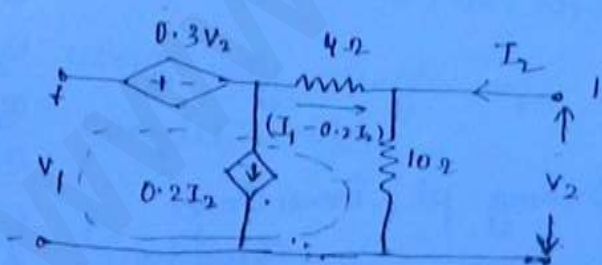

$$V_1 = 0.3V_2 + 4(I_1 - 0.2I_2) + V_2 \rightarrow (1)$$

$$V_2 = 10(I_1 + 0.8I_2) \rightarrow (2)$$

Sub (2) in (1)

$$V_1 = 21I_1 + 9.6I_2$$

$$V_1 = 17I_1 + 9.6I_2$$



$$V_2 = 10I_1 + 8I_2$$

$$8I_2 = V_2 - 10I_1 \Rightarrow I_2 = \frac{V_2}{8} - \frac{10}{8}I_1 \rightarrow (5)$$

Substitute eq. (5) in eq. (1).

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$V_1 = 5I_1 + 1.2V_2 \rightarrow (6)$$

$$h_{12} = 1.2$$

$$I_1 = \frac{V_1}{5} - \frac{1.2V_2}{5}$$

$$\Rightarrow Y_{12} = -\frac{1.2}{5} = -0.24$$


## NETWORK FUNCTIONS



$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)}$$

$$Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

} Immittance functions

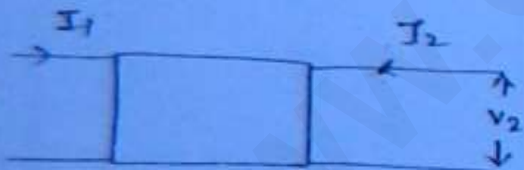

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)}, Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

Driving pt. immittance function

$$Z_{22}(s) = \frac{V_2(s)}{I_2(s)}, Y_{22}(s) = \frac{I_2(s)}{V_2(s)}$$

$$Z_{12}(s) = \frac{V_1(s)}{I_2(s)}$$

Impedance Transfer ratio

$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$$

3.  $V_{12}(s) = \frac{I_1(s)}{V_2(s)}$

(2/3)

$Y_{21}(s) = \frac{I_2(s)}{V_1(s)}$  admittance transfer ratio

4.  $G_{12} = \frac{V_1(s)}{V_2(s)}$

$G_{21} = \frac{V_2(s)}{V_1(s)}$  Voltage transfer ratio

5.  $\alpha_{12} = \frac{I_1(s)}{I_2(s)}$

$\alpha_{21} = \frac{I_2(s)}{I_1(s)}$  Current transfer ratio

→ Parameters are calculated at predefined conditions (either o.c or s.c).

$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$

$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$

→ To calculate network function, no predefined conditions are required.

→ To design the n/w simultaneously 4 parameters are required. i.e.  $Z_{11}, Z_{12}, Z_{21}, Z_{22}$ .

→ By using only single n/w function, it is possible to design complete n/w.

## Network Synthesis:

→ In the n/w synthesis for a given function, n/w is designed.

Single port →  $Z(s), Y(s)$  } immittance

Two port } i.  $Z_{11}(s), Z_{22}(s), Y_{11}(s), Y_{22}(s)$  - driving pt immittance func.

In the network synthesis, for a given function, it is possible to design the following networks.

- (274)
- Series - Foster I form
  - Parallel - Foster II form
  - Ladder -
    - Cauer-I form
    - Cauer-II form
- } Partial fraction of Expansion
- } Continued fraction of Expansion

$F(s)$  should be PRF (the real func.).

$$R \geq 0, L \geq 0, C \geq 0.$$

If  $F(s)$  is PRF,  $\frac{1}{F(s)}$  is also PRF.

If  $F_1(s)$  &  $F_2(s)$  are PRF

i)  $F(s) = F_1(s) + F_2(s) \rightarrow \text{PRF}$

ii)  $F(s) = F_1(s) - F_2(s)$

(a)  $F_1(s) > F_2(s) \rightarrow \text{PRF}$

(b)  $F_1(s) < F_2(s) \rightarrow -ve.$

All the poles of the function should be present in the left half of the plane.

Imaginary poles and zeroes should be conjugate pair.


In the partial fraction of Expansion, residue should be the real.



- Numerator and denominator polynomial should satisfy Hurwitz criteria.
- The highest powers of numerator and denominator polynomial should differ by at most UNITY. This condition prohibits multiple poles and zeros at  $\infty$ .
- The lowest powers of numerator and denominator polynomial should differ by at most UNITY. This condition prohibits multiple poles and zeros at origin.


$$Z(s) = Z_1(s) + Z_2(s)$$

$$Z_2(s) = Z(s) - Z_1(s)$$

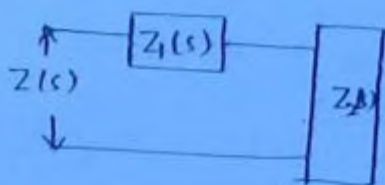

$$Z_2(s) = Z_3(s) + Z_4(s)$$

$$Z_4(s) = Z_2(s) - Z_3(s)$$

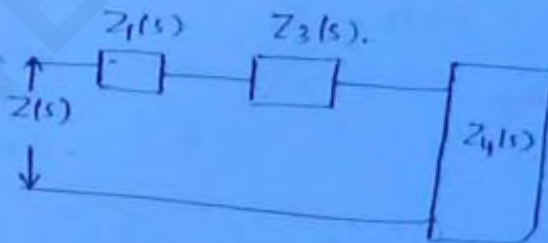

### 1. Removal of pole at $\infty$


$$Z(s) = \frac{b_{n+1}s^{n+1} + b_n s^n + \dots + b_0}{a_n s^n + a_{n-1}s^{n-1} + \dots + a_0}$$

$$Z(s) = \frac{b_{n+1}s^{n+1}}{a_n s^n} + Z_2(s)$$

$$\left( H = \frac{b_{n+1}}{a_n} \right)$$

$$Z(s) = Hs + Z_2(s)$$

$$Z_2(s) = Z(s) - H(s)$$

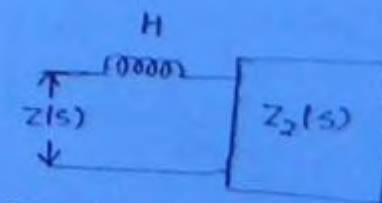


$$Y(s) = Hs + Y_2(s)$$

(2/6)

$$B_c = sC \therefore Z_c = 1/sC$$

$$Y_2(s) = Y(s) - Hs$$

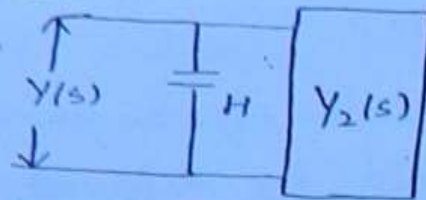

## Removal of pole at origin

$$Z(s) = \frac{b_0 + \dots + b_{n-1}s^{n-1} + b_ns^n}{s(a_0 + \dots + a_{n-1}s^{n-1} + a_ns^n)}$$

$$Z(s) = \frac{b_0}{sa_0} + Z_2(s) \quad \left( \frac{b_0}{a_0} = k_0 \right)$$


$$Z(s) = \frac{k_0}{s} + Z_2(s)$$

$$X_c = 1/sC$$

$$Z_2(s) = Z(s) - \frac{k_0}{s}$$


for admittance func.

$$B_c = 1/Ls$$

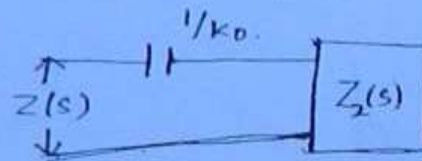

$$Y(s) = \frac{k_0}{s} + Y_2(s)$$

$$Y_2(s) = Y(s) - \frac{k_0}{s}$$

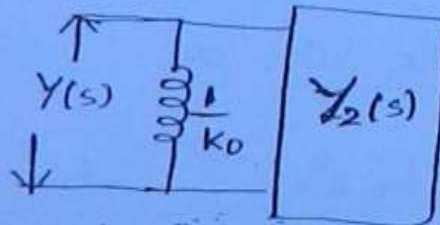

## Removal of Conjugate pair of poles

$$Z(s) = Z_1(s) + Z_2(s)$$

$$Z_2(s) = Z(s) - Z_1(s)$$

$$Z_1(s) \rightarrow \text{poles} \rightarrow \pm j\omega$$

$$Z_1(s) = \frac{k_1}{s+j\omega} + \frac{k_2}{s-j\omega} \quad (k_1 = k_2 = k)$$

$$\frac{10}{s^2 + 6s}$$


$$Z_1(s) = \frac{k}{s+j\omega} + \frac{k}{s-j\omega}$$



$$Z_1(s) = \frac{2ks}{s^2 + \omega^2}$$

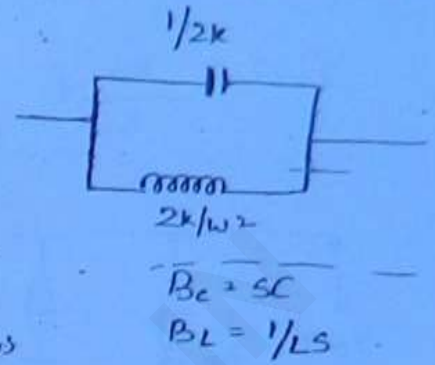
(217)

$$Z_1(s) = \frac{1}{\frac{s^2}{2ks} + \frac{\omega^2}{2ks}} = \frac{1}{Y_a + Y_b}$$



Illy with admittance function,
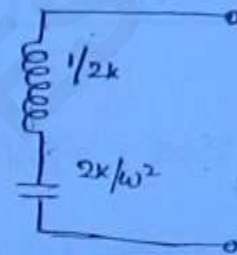
$$Y(s) = \frac{1}{\frac{s}{2k} + \frac{\omega^2}{2ks}} = \frac{1}{Z_a + Z_b}$$





#### 4. Removal of constant

$$Z(s) = k + Z_2(s)$$

$$Z_2(s) = Z(s) - k$$

$$Y(s) = k + Y_2(s)$$

$$Y_2(s) = Y(s) - k$$

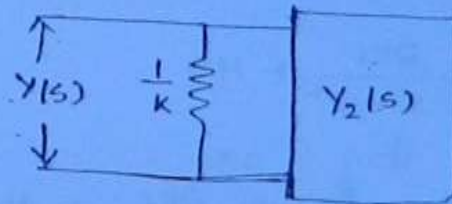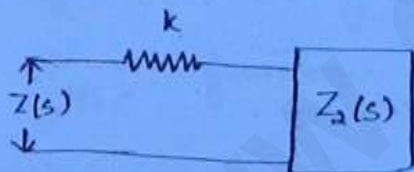


#### LC n/w. - Foster I form (Series)

$$X_c = 1/sC$$

$$X_L = Ls$$

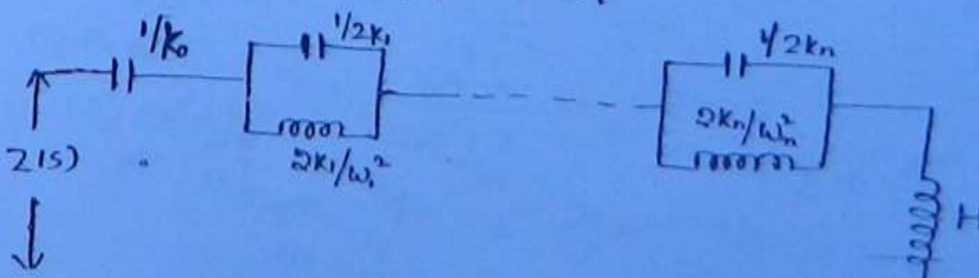
$$Z(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + Hs$$




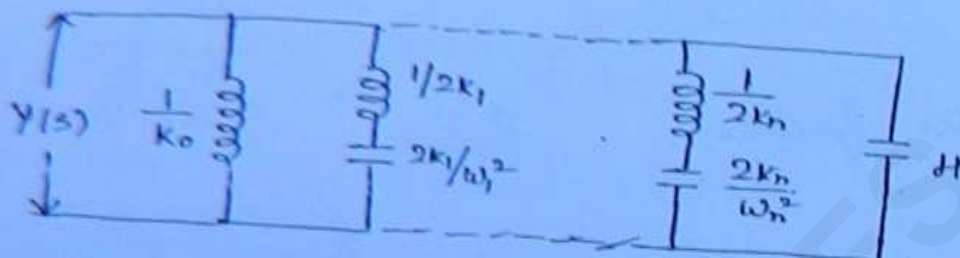
# L.C. n/w Foster-II form [Parallel]

$$Y(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + HS \quad (2/8)$$



obtain the Foster I & II form of  $Z(s)$

$$Z(s) = \frac{(s^2+2)(s^2+4)}{s(s^2+3)} \quad \frac{4}{3}$$

$P \rightarrow \infty$  ✓

$P \rightarrow$  origin ✓

$P \rightarrow$  conjugate pair ✓

$$Z(s) = \frac{k_0}{s} + \frac{2ks}{s^2 + \omega^2} + HS$$

$$\frac{(s^2+2)(s^2+4)}{s(s^2+3)} = \frac{k_0}{s} + \frac{2ks}{s^2 + \omega^2} + HS$$

$$k_0 = 8/3 \therefore$$

$$2k = 1/3$$

$$H = 1$$

$$\frac{3s^2+8}{8(s^2+3)} + 1$$

$$\frac{1}{s} + \frac{1}{s^2+3}$$

$$\frac{s^4 + 6s^2 + 8}{s^2 + 3}$$

$$\frac{s^4 + 3s^2 + 5s^2 + 8}{s^2 + 3} = \frac{s^4 + 3s^2 + 8}{s^2 + 3} + \frac{2s^2 + 8}{s^2 + 3}$$

$$Z(s) = \frac{8/3}{s} + \frac{1/3}{s^2+3} + s$$

$$Z(s) = \frac{1}{s} + \frac{1}{s^2+3} + s$$

$$\begin{aligned} k_0 &= 8/3 \\ 2k &= 1/3 \\ H &= 1 \end{aligned}$$


$$k_0 = 8/3$$

$$B_c = sC$$

$$B_L = 1/sL$$

$$\left( \frac{1}{Y_A + Y_B} \right)$$

219

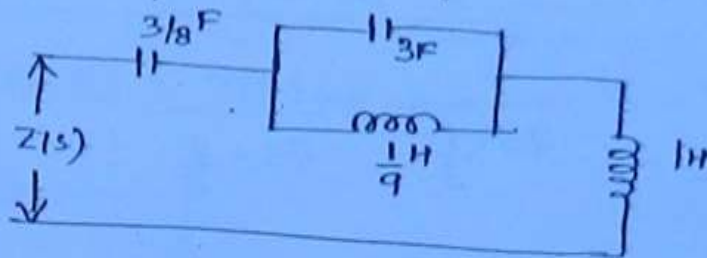

Foster-II form.

$$Z(s) = \frac{(s^2+3)(s^2+4)}{s(s^2+2)} \Rightarrow Y(s) = \frac{s(s^2+3)}{(s^2+2)(s^2+4)}$$

Note: (1) if  $F(s)$  is given, same function is utilized to obtain foster I & II<sup>nd</sup> form.

(2) If  $Z(s)$  is given, to obtain foster II<sup>nd</sup> form,  $\frac{1}{Z(s)}$  function is used.

(3) If  $Y(s)$  is given, to obtain foster I<sup>st</sup> form,  $\frac{1}{Y(s)}$  function is used.

$$\therefore Y(s) = \frac{s(s^2+3)}{(s^2+2)(s^2+4)}$$

no pole at  $\infty$   
 " " " origin  
 conjugate pair of poles = 2.

$$\therefore Y(s) = \frac{2k_1 s}{s^2 + \omega_1^2} + \frac{2k_2 s}{s^2 + \omega_2^2}$$

$$\frac{s(s^2+3)}{(s^2+2)(s^2+4)} = \frac{2k_1 s}{s^2+2} + \frac{2k_2 s}{s^2+4}$$

$$2k_1 \rightarrow 1/2, \quad 2k_2 \rightarrow 1/2$$

$$Y(s) = \frac{s/2}{s^2+2} + \frac{s/2}{s^2+4}$$


(220)

$$Y(s) = \frac{1}{\frac{s^2}{s/2} + \frac{2}{s/2}} + \frac{1}{\frac{s^2}{s/2} + \frac{4}{s/2}} \Rightarrow \frac{1}{2s + \frac{4}{s}} + \frac{1}{2s + \frac{8}{s}}$$

$$Y(s) = \frac{1}{Z_a + Z_b} + \frac{1}{Z_c + Z_d}$$

$$X_L = Ls$$

$$X_C = 1/cs$$

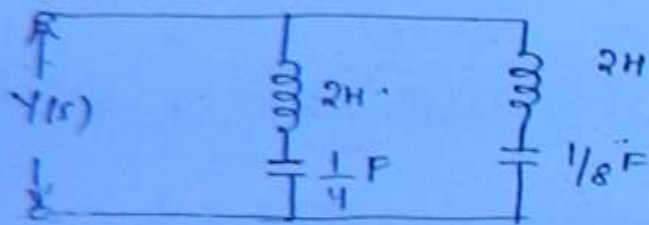

C n/w Cauer-I form. (ladder).  
(np > dp)

Removal of pole at  $\infty$ .

$$Z_2(s) = Z(s) - H_1 s$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - H_2 s$$



$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - H_3 s$$

$$Y_4 = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - H_4 s$$

$$Y_4(s) = H_4(s) + Y_5(s)$$

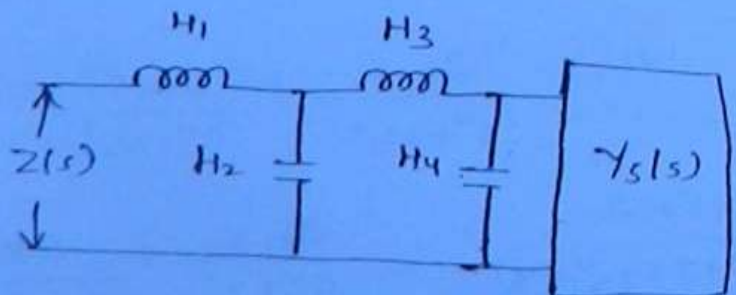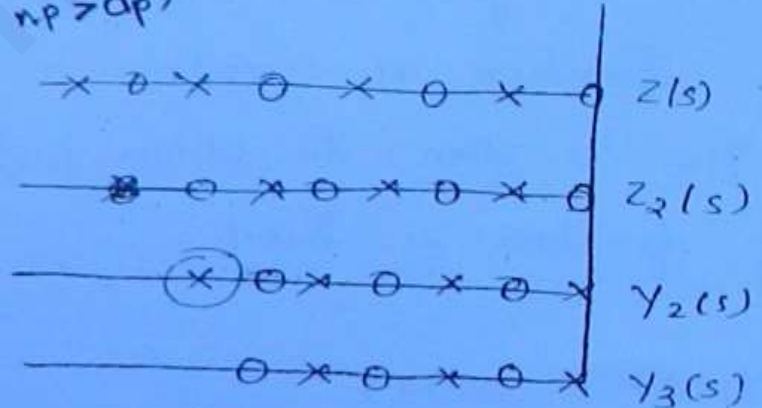



## LC n/w , Cauer-II form.

(221)

Removal of pole at origin.

$$Z_2(s) = Z(s) - \frac{k_{01}}{s}$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - \frac{k_{02}}{s}$$



$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - \frac{k_{03}}{s}$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - \frac{k_{04}}{s}$$

$$Y_4(s) = Y_5(s) + \frac{k_{04}}{s}$$

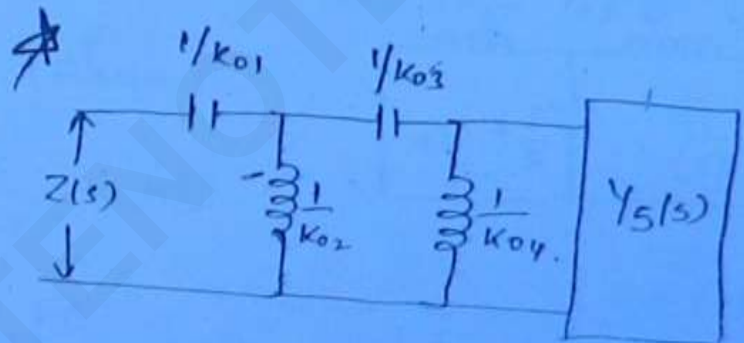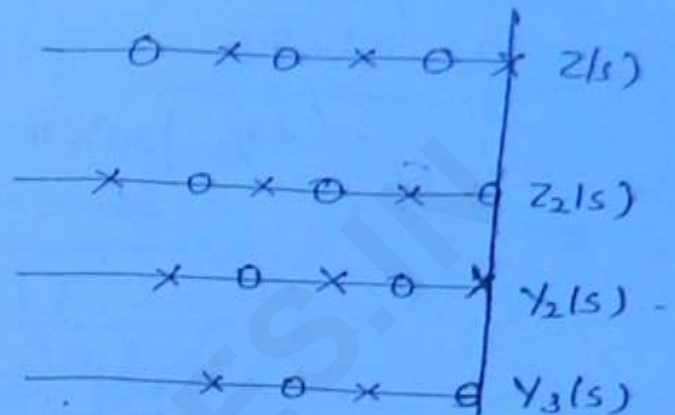

Q. obtain Cauer-I & II form.

$$Z(s) = \frac{s^3 + 2s}{s^4 + 5s^2 + 4}$$

Cauer-I

No pole at  $\infty$ ,  $\therefore$  consider  $Y(s)$


$$Y(s) = \frac{s^4 + 5s^2 + 4}{s^3 + 2s}$$

$$(s^3 + 8s) \begin{matrix} \nearrow C_1 \\ \rightarrow Y \end{matrix} \quad BC = SC \quad (222)$$

$$\frac{s^4 + 2s^2}{3s^3 + 4} \begin{matrix} \nearrow L_1 \\ \rightarrow Z \end{matrix}$$

$$\frac{2s/3}{3s^2} \begin{matrix} \nearrow C_2 \\ \rightarrow Y \end{matrix}$$
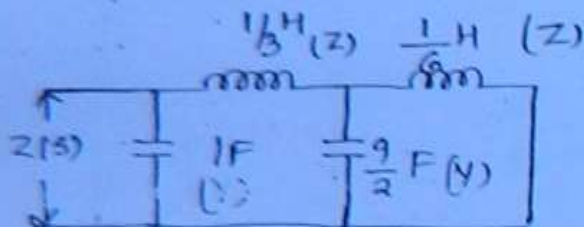
$$\frac{4}{2s/3} \begin{matrix} \nearrow L_2 \\ \rightarrow Z \end{matrix}$$



$$Z(s) = \frac{1}{s + \frac{1}{\frac{s}{3} + \frac{1}{\frac{9s}{2} + \frac{1}{s/6}}}} \Rightarrow \frac{s^3 + 2s}{s^4 + 5s^2 + 4}$$

auer-1 form.

P → origin

$$Z(s) = \frac{s^3 + 2s}{s^4 + 5s^2 + 4}$$


$$Y(s) = \frac{s^4 + 5s^2 + 4}{s^3 + 2s} \quad ; \quad Y(s) = \frac{s^4 + 5s^2 + 4}{s(s^2 + 2)}$$

$$(2s + s^3) \begin{matrix} \nearrow L_1 \\ \rightarrow Y \end{matrix} \quad \frac{4 + 5s^2 + s^4}{4 + 2s^2} \left( \frac{2}{s} \right)$$

$$\frac{3s^2 + s^4}{2s + s^3} \begin{matrix} \nearrow C_2 \\ \rightarrow Z \end{matrix} \quad \left( \frac{1}{3s} \right)$$

$$\frac{2s^3 + 2s^2 + 1}{2s^3 + 2s^2 + 1} \begin{matrix} \nearrow L_2 \\ \rightarrow Y \end{matrix}$$

$$B_L = 1/Ls \quad X_C = 1/sC$$

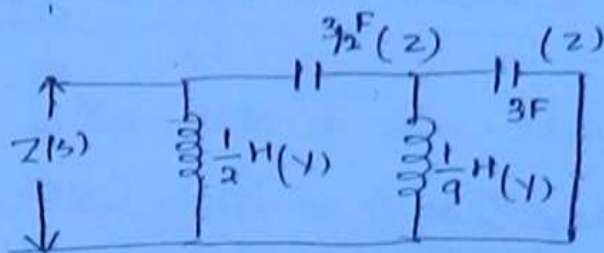


223

$$Z(s) = \frac{1}{\frac{2}{s} + \frac{1}{\frac{2}{3s} + \frac{1}{\frac{9}{s} + \frac{1}{1/3s}}}}$$


RC n/w Foster-I form (Series)

$$Z_{LC}(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + Hs$$
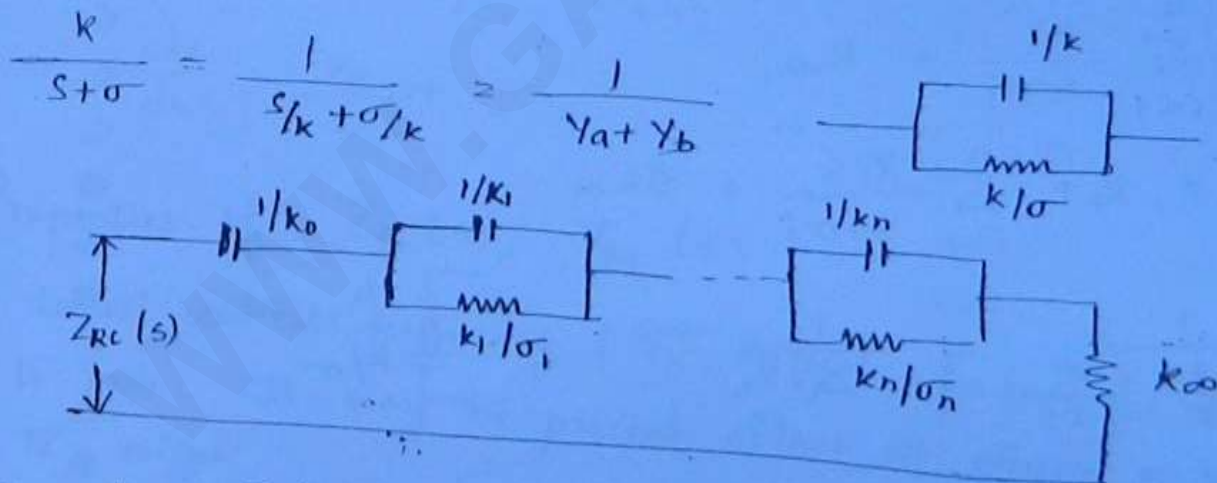
$$Z_{RC}(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \sigma_i} + k_\infty$$



RC n/w Foster II form

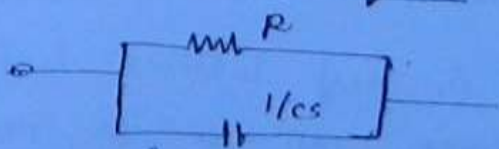


$$Z_{RC}(s) = \frac{R \cdot 1/cs}{1} = R$$



$$Z_{RC} = \frac{R}{RC \left[ s + 1/RC \right]} = \frac{1}{s + \frac{1}{RC}}$$

224

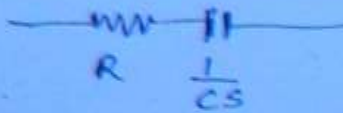

$$Y_{RC}(s) = \frac{1}{R + \frac{1}{CS}}$$

$$Y_{RC}(s) = \frac{CS}{RC \left( s + 1/RC \right)}$$



$$\Rightarrow \frac{Y_{RC}(s)}{s} = \frac{1}{R \left( s + 1/RC \right)}$$

Pole zero pattern of  $Z_{RC}(s)$  &  $\frac{Y_{RC}(s)}{s}$  are identical.

$$\frac{f(s)}{s} = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \sigma_i} + k_\infty$$

$$Y_{RC}(s) = k_0 + \sum_{i=1}^n \frac{k_i s}{s + \sigma_i} + s k_\infty$$
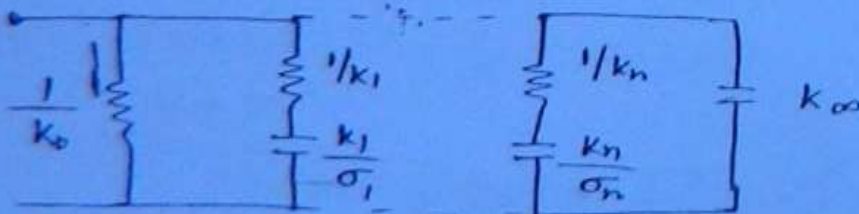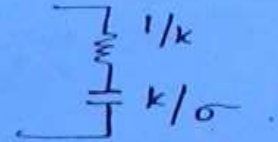
$$\frac{k_s}{s + \sigma} = \frac{1}{\frac{1}{k} + \frac{\sigma}{ks}} = \frac{1}{Z_A + Z_B} \Rightarrow$$



## Properties of LC network

225

1. Either pole or zero should be present at origin.
  2. Either pole or zero should be present at  $\infty$ .
  3. Poles and zeros are arranged alternately on  $j\omega$  axis.
- In the partial fraction of expansion, residue should be +ve real.

5. ✓  $\frac{dx}{d\omega} > 0 \Rightarrow$  slope is +ve

$$Z(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2K_i s}{s^2 + \omega_i^2} + Hs$$

$$jX = \frac{k_0}{j\omega} + \sum_{i=1}^n \frac{2K_i j\omega}{-\omega^2 + \omega_i^2} + j\omega H$$

$$Z = \int (X_L - X_C)$$

$$Z = jX$$

$$X = \frac{-k_0}{\omega} + \sum_{i=1}^n \frac{2K_i \omega}{-\omega^2 + \omega_i^2} + H\omega$$

$$\frac{dx}{d\omega} = \frac{k_0}{\omega^2} + \dots \Rightarrow \frac{dx}{d\omega} > 0$$

## Properties of $Z_{Re}(s)$ , $Y_{RL}(s)$

1. Lowest critical frequency (1st critical frequency) is due to pole. It may be present either at origin or nearer to origin.
2. Poles and zeros are arranged alternately on -ve real axis.
3. Highest critical freq. is due to zero, it may present either at  $\infty$  (or) nearer to  $\infty$ .



$$1. \quad \frac{dZ_{RC}}{ds} < 0 \quad \text{slope -ve} \quad \frac{dY_{RL}}{ds} < 0 \quad (226)$$

$$Z_{RC}(0) > Z_{RC}(\infty)$$

$$X_C = 1/sC$$

$$S=0$$

$$S=\infty$$

$$Y_{RL}(0) > Y_{RL}(\infty)$$

$$X_C(0) = \infty \quad X_C(\infty) = 0$$

Properties of  $Y_{RC}(s)$  &  $Z_{RL}(s)$ .

$$Y_{RC} = K_0 + \sum_{i=1}^n \frac{K_i s}{s + \sigma_i} + K_{\infty} s.$$

Highest critical frequency is due to pole. It may be present at  $\infty$  or near to  $\infty$ .

Poles and zeros are arranged alternately on -ve real axis.  $\times \circ \times \circ \times \circ$

Lowest critical frequency is due to zero, it may be present either at origin or near to origin.

$$\times \circ \times \circ \times \circ \mid Y_{RC} \quad \circ \times \circ \times \circ \times \circ \mid Z_{RC}$$

$$\frac{dY_{RC}}{ds} > 0 \quad \text{slope is +ve} \quad \frac{dZ_{RL}}{ds} > 0$$

$$Z_{RL}(0) < Z_{RL}(\infty)$$

$$Y_{RC}(0) < Y_{RC}(\infty)$$

$S=0$	$S=\infty$
$X_L = LS$	$X_L = \infty$
$X_L = 0$	

origin

origin



- RC n/w Cauer-II form. (ladder)

$$LC \rightarrow Z_2(s) = Z(s) - H_1(s)$$

(227)

$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - H_2 s \quad (B_c = s)$$

$$Z_3(s) = 1/Y_3(s)$$

$$Z_4(s) = Z_3(s) - k_2$$

$$Y_4(s) = 1/Z_4(s) \Rightarrow Y_5(s) = Y_4(s) - H_2 s$$

$$Y_4(s) = Y_5(s) + H_2(s)$$


RC  $\rightarrow$  step 1: Removal of constant from  $Z(s)$

$$Z_2(s) = Z(s) - k_1$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

Step 2: Removal of pole at  $\infty$  from  $Y(s)$ .

$$Y_3(s) = Y_2(s) - H_1 s$$

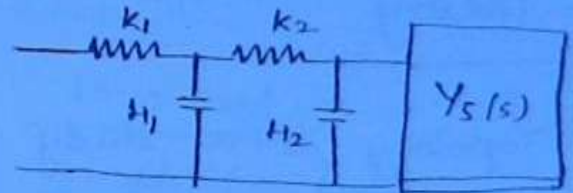

Step 1 & step 2 are alternately repeated until the total function is realized.

RC n/w Cauer-PI form.

$$LC \rightarrow Z_2(s) = Z(s) - \frac{k_{01}}{s}$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - \frac{k_{02}}{s}$$

( $B_L = \frac{1}{s}$ )

$$-Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - \frac{K_{02}}{s}$$

$$Y_4(s) = 1/Z_4(s)$$

$$Y_5(s) = Y_4(s) - K_2$$

$$Y_4(s) = Y_5(s) + K_2$$

Note :- Step 1 & step 2 are alternately repeated until the total function is realized.

(228)


RC  $\rightarrow$  Step 1: Removal of pole at origin from  $Z(s)$

$$Z_2(s) = Z(s) - \frac{K_{01}}{s}$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

Step 2: Removal of constant from  $Y(s)$

$$Y_3(s) = Y_2(s) - K_1$$

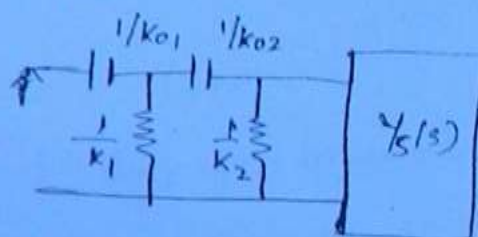


## Graph Theory

Network Topology is a study of the n/w properties by investigating interconnections b/n branches and nodes, it mainly concentrates on the geometry of the network.


In the network topology, any network is replaced by graph. To develop the graph each element is replaced by either st. line or arc of the semicircle. Voltage source is replaced by short circuit, current source is replaced by o.c. and graph retains all the nodes of the original n/w.



Ex

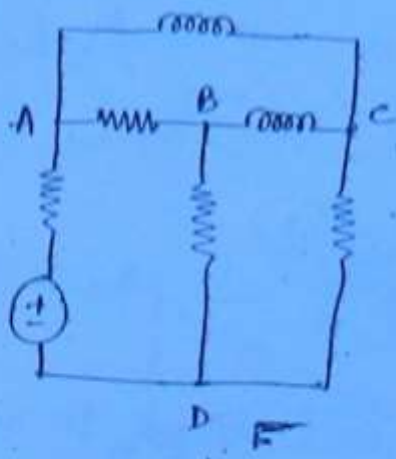

229

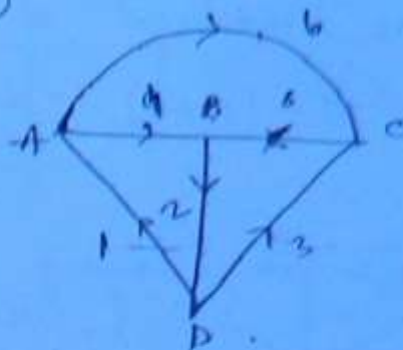

$$C = N - 1$$

$$C = M$$

No. of branches of n/w  $\geq$  no. of branches of graph

in +ve Augmented Incident matrix

	1	2	3	4	5	6
A	1			-1		-1
B		-1		+1	+1	
C			+1		-1	+1
D	-1	+1	-1			

Reduced Incident matrix


	1	2	3	4	5	6
A	1			-1		-1
B		-1		+1	+1	
C			+1		-1	+1

D is ref

→ All the information regarding the graph can be represented mathematically in concise form is called as, incidence matrix.

→ For a given graph augmented incidence matrix is unique

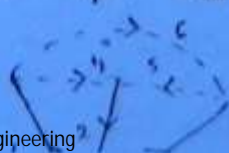→ Tree is a connected sub graph, it connects all the nodes of the n/w but it does not consist of any closed path.




Tree  $\{1, 2, 3\}$



- Total tree branches =  $N - 1 = 4 - 1 = 3$   $N = \text{no. of nodes.}$

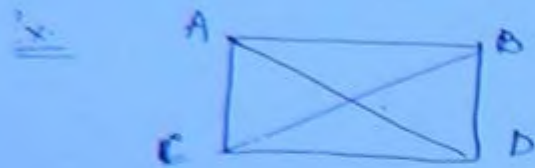Link (links) =  $b - (N - 1) = 6 - (4 - 1) = 3$   $b = \text{no. of branches}$



& Tree



The tree is invalid, because there is no interconnection between the nodes.

The set of branches which are disconnected, to form a tree is called as co-tree. (complementary tree).

A branch which forms a tree is called as tree branch (twig). Generally it is indicated by solid line (or) thick line.

Total no. of tree branches =  $N - 1$

A branch which is disconnected to form a tree is called as link. also known as chord. Generally it is indicated by dotted lines.

Total no. of links =  $l = b - (N - 1)$



For a given graph tree is not unique.

Total no. of possible trees =  $N^{N-2}$

Note:-

The above formula can be applied when connections should be present b/n all the nodes.

E.g.

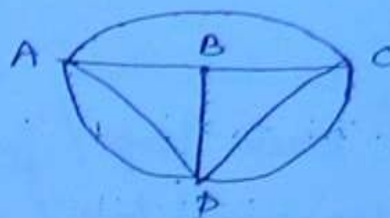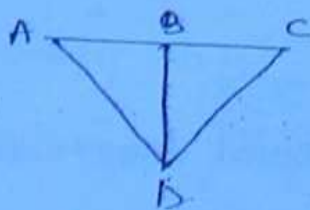

(23)

For the above two graphs the formula is not applicable.

→ Total no. of possible trees for any graph ⇒

$$= \det |AAT|, \text{ where } A = \text{reduced incidence matrix.}$$

Node Pair voltages.

$$\text{Total no. of node pair voltages} = \frac{N(N-1)}{2} = N C_2$$

$$= \frac{4(4-1)}{2} = 6$$



$$\rightarrow \text{Total no. of edges} = \frac{N(N-1)}{2}$$

⇒ edge = branch

[8/11]


Develop a graph for the network shown.

Step 1

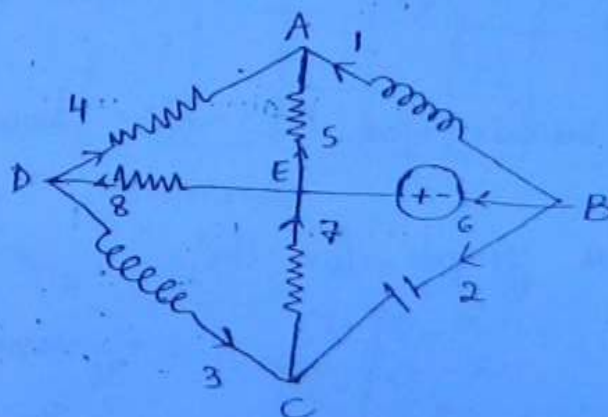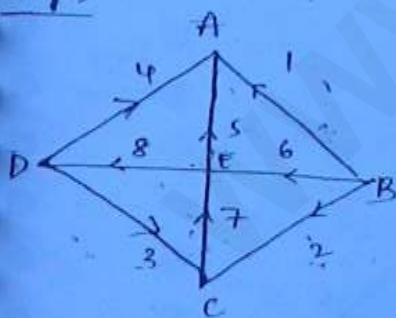

Step 2

Develop a tree for the graph.

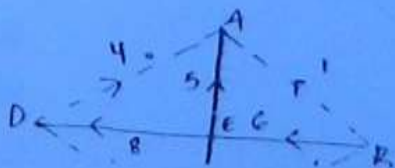



Step 3:

Identify total no. of basic loops / fundamental loops. (or)  
Independent loops / f-loops.

Basic loop should consist of only one link.

Total no. of basic loops = total no. of links.


$$L = b - (N - 1)$$

Basic loop direction is same as the link current direction.

Tie set matrix  $[C]$

	$V_1$	$V_2$	$V_3$	$V_4$	$V_5$	$V_6$	$V_7$	$V_8$
$I_1$	+1				-1	-1		
$I_2$		+1				-1	+1	
$I_3$			+1				+1	+1
$I_4$				+1	-1			+1

$$[C] = [U : C_b] \text{ voltages}$$

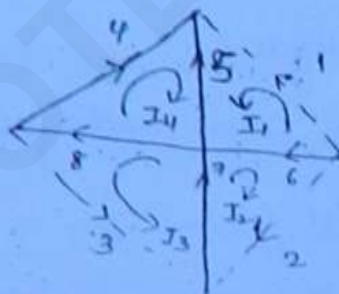

KVL

$$V_1 - V_5 - V_6 = 0$$

$$V_2 - V_6 + V_7 = 0$$

$$V_3 + V_7 + V_8 = 0$$

$$V_4 - V_5 + V_8 = 0$$



Cut-set matrix

Develop cut-set matrix for the n/w shown.

Step 1: Develop a graph for the given n/w.



Step 2: Develop a tree for a graph.

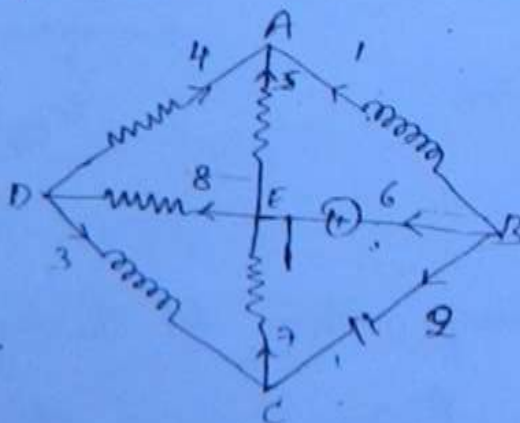
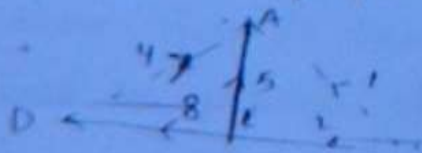




3. i. Identify total no. of basic cut sets / fundamental cut sets / f-cut sets

(233)

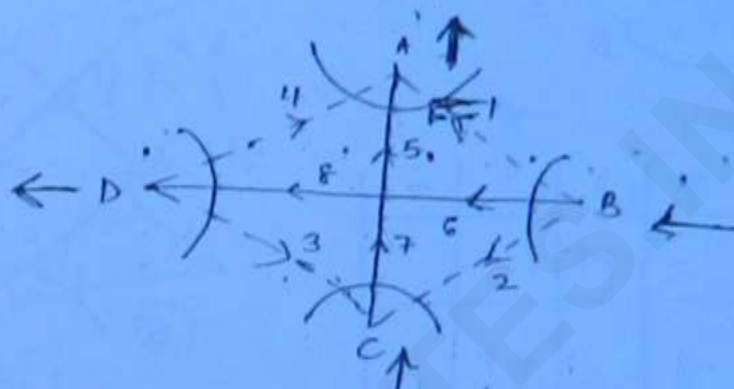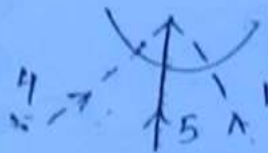ii. Basic cut set should consist of only one tree branch.



iii. Total no. of basic cut sets = total no. of tree branches

iv. Basic cut set direction is same as the tree branch current direction.

cut-set matrix

$[B]$

	$i_1$	$i_2$	$i_3$	$i_4$	$i_5$	$i_6$	$i_7$	$i_8$
A	+1			+1	+1			
B	+1	+1				+1		
C		-1	-1				+1	
D			-1	-1				+1

ket

$$i_1 + i_4 + i_5 = 0$$

$$i_1 + i_2 + i_6 = 0$$

$$-i_2 - i_3 + i_7 = 0$$

$$-i_3 - i_4 + i_8 = 0$$


currents

$$[B] = [B_1 : U]$$

7. Develop cut set matrix for the graph shown.




Assume 4, 5, 6 as free branches.

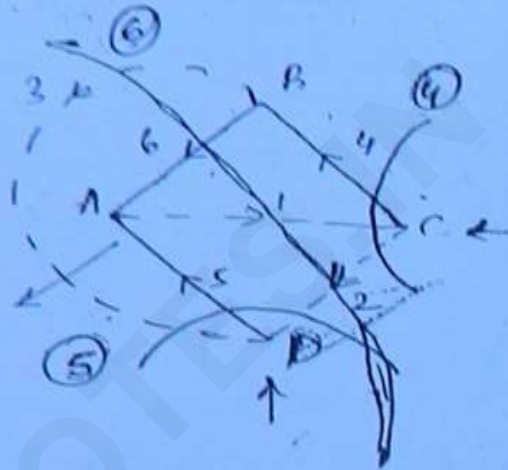

	1	2	3	4	5	6
4	-1	+1		+1		
5		-1	-1		+1	
6	-1	+1	+1			+1

Identify total no. of cut sets of the graph shown.

- (a) 3 (b) 4  
(c) 5 (d) 6

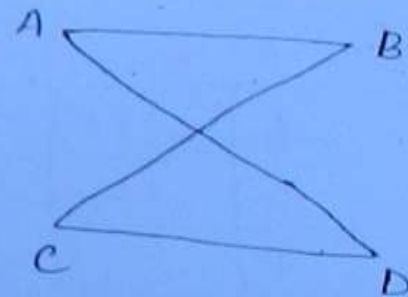

Conclusions

Total no. of possible trees =  $N^{N-2}$

The set matrix is not unique, total no. of possible tree set matrices =  $N^{N-2}$ .

3. Cut set matrix is not unique. Total no. of possible cut set matrices =  $N^{N-2}$

(235)

4.  $[C] \xrightarrow{\text{Tie set}} [U : C_b]$

$[B] \xrightarrow{\text{Cut set}} [B_1 : U]$

$B_1 = -[C_b]^T$

$[B_1] = -[C_b]^T$

$[C_b] = -[B_1]^T$

5. The rank of the tie set matrix = total no. of links.  
Rank =  $l = b - (N - 1)$

6. Rank of the cut set matrix = total no. of tree branches

=  $(N - 1)$   
7. Rank of the incidence matrix =  $N - 1$

## Duality

$R \longleftrightarrow G$

$L \longleftrightarrow C$

$V \longleftrightarrow I$

$KVL \longleftrightarrow KCL$

loop  $\longleftrightarrow$  node  
(mesh)

$\frac{dv}{dt} \longleftrightarrow \frac{di}{dt}$

series  $\longleftrightarrow$  parallel

D.C  $\longleftrightarrow$  S.C

Tie set  $\longleftrightarrow$  Cut set



Theremin's  $\longleftrightarrow$  Norton's

Foster I form  $\longleftrightarrow$  Foster II form



Duality doesn't mean equivalence. But it means, mathematical representation of both the networks are identical.

(236)


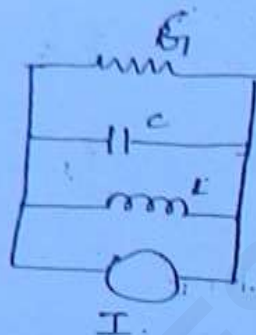
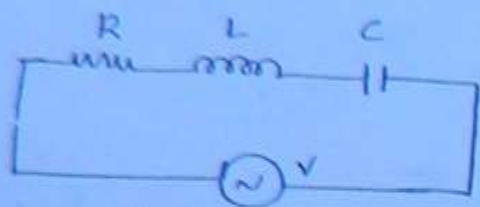


$$V = IR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

→ KVL

$$I = VG + C \frac{dv}{dt} + \frac{1}{L} \int v dt \rightarrow KCL$$

Draw the dual of the n/w shown.

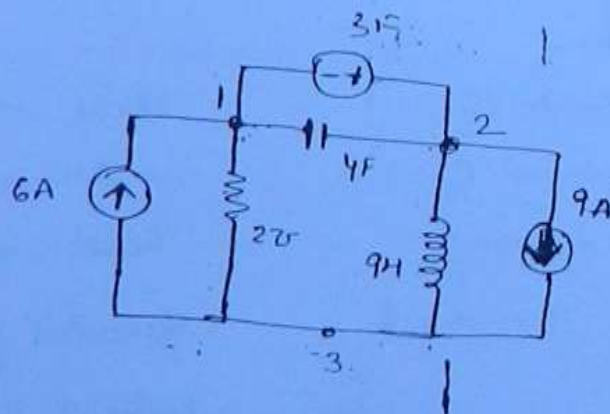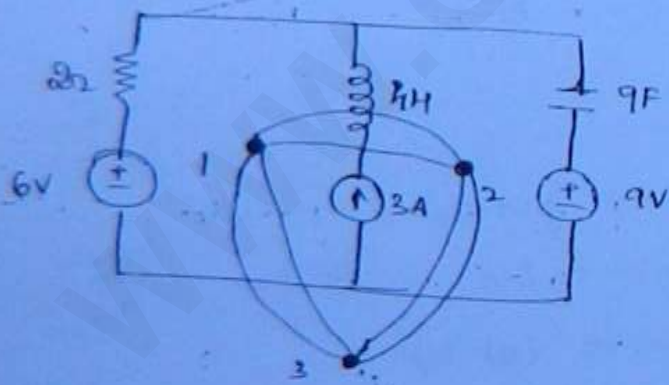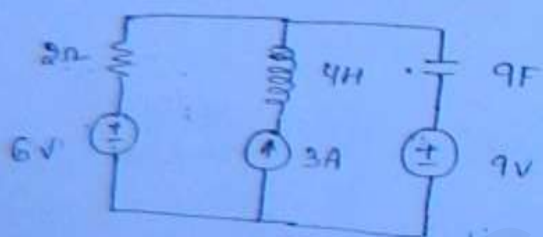

Ex:

When voltage source drives a current in CW direction arrow mark of the current source is indicated towards respective node.

when current source drives a current in ccw direction  
+ve sign is assigned to respective node.

(237)

W.B.


①  $f \text{ loops} = l = b - (N - 1) = 6 - (4 - 1) = \underline{3}$

②  $\frac{N(N-1)}{2} = \frac{10(10-1)}{2} = 45$

③

④

⑤

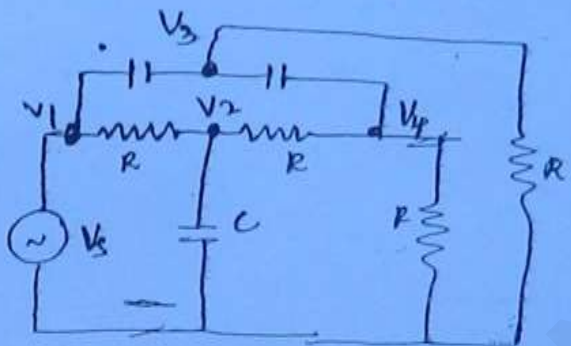

$e = m = 4$

$e = N - 1 = 5 - 1 = 4$

$\underline{\underline{\min = 3}}$  ( $V_5 = V_1$  not considered)

⑥  $f\text{-cutset} = N - 1 = 8 - 1 = 7$

⑦  $N^{N-2} = 4^{4-2} = 16$

⑧  $f \text{ loops} = l = b - (N - 1) \Rightarrow 3 = b - (4 - 1)$   
 $b = 6$

Conv.

1. Develop graph & then develop Tie-set matrix.

# Network Synthesis W.B.

$$TF = \frac{1}{RCs + 1} = \frac{1}{RC[s + 1/RC]}$$

(d) 238

$$Y(s) = \frac{s^2 + 2.5s + 1}{s^2 + 4s + 3} = \frac{(s + 0.5)(s + 2)}{(s + 1)(s + 3)}$$


1. lowest critical freq  $\rightarrow$  pole  $= x$   $\rightarrow 0.5 \Rightarrow$  zero

2. alternate pole zero  $\checkmark$

x 3.

$$4. Y(0) = \frac{0.5 \times 3}{2 \times 1} = 1/3$$
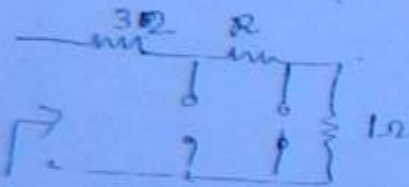
$$s=0, \quad X_c = \frac{1}{sC} = \infty, \quad C \rightarrow 0C$$



$$Z(0) = \frac{3 \times 8}{3} = 4 + j$$

$$\Rightarrow 8 = 4 + R \Rightarrow R = 4\Omega$$

for C value, find  $Z(s) \big|_{s=1}$

$$Y(s) = \frac{I(s)}{V(s)} = \frac{1/s}{1/s + 1/s + 1/4} = \frac{1s + 1}{2Ts + 1}$$

$$= \frac{1s + 1/2 + 1/2}{2Ts + 1} = \frac{Ts + 1/2}{2Ts + 1} + \frac{1/2}{2Ts + 1}$$

$\downarrow$  2  
 $R_1$

$\downarrow$   $\left( \frac{1}{2s + 2b} \right)$   $R_2$

$$Z(s) = s + 2 + \frac{3}{s}$$

$\downarrow$   $L=1$   $\downarrow$   $R=2$   $\downarrow$   $L$   $\downarrow$   $C=1/3$

$Z(s)$  is PRP



10.  $Z(j\omega) = \frac{j\omega + \alpha}{j\omega + \beta} = \frac{[\tan^{-1}(\omega/\alpha)]}{[\tan^{-1}(\omega/\beta)]} = \tan^{-1}\left(\frac{\omega}{\alpha}\right) - \tan^{-1}\left(\frac{\omega}{\beta}\right)$

$\phi(\text{line}) = \alpha < \beta$

239

11. 
$$\frac{(s^2 + s + 1)(s^2 + 2s + 2)}{s^2 + s + 1} \rightarrow Z, R$$

$$\frac{(s + 1)(s^2 + s + 1)}{s^2 + s} \rightarrow C, Y$$

$$\frac{1(s + 1)(s)}{s} \rightarrow Z$$

$$\frac{1(1)(1)}{Q.P.} \rightarrow R$$

(d)

12.  $Z(s) = \frac{k(s+3)}{(s+1+j)(s+1-j)} = \frac{k(s+1)}{(s^2 + 2s + 2)}$

13.  $Z(s) = \frac{k(s^2 + 20s)(s^2 + 60s)}{s(s^2 + 40s^2)}$


Note - Imaginary poles & zeros should be conjugate pair.

Only for LC n/w imaginary poles and zeros are present.

$P \rightarrow \infty \rightarrow H.S.$

$P \rightarrow \text{origin} \rightarrow \frac{K_0}{s}$

$P \rightarrow \text{conjugate pair}$

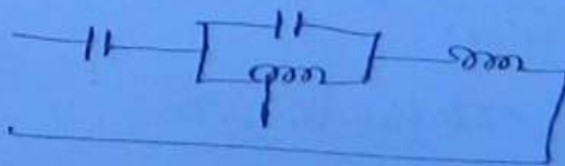

$Z(s) = \frac{(s+1)}{(s+s_2)(s+\frac{1}{s_2})}$

$\Rightarrow Z(j\omega) = \frac{j\omega + 1}{j\omega + \frac{1}{j\omega}}$

$$[10] = \sin t \Rightarrow \omega = 1$$

(240)

$$Z(j) = \frac{1+j}{(\sqrt{2}+j)(\frac{1}{\sqrt{2}}+j)}$$

$$V = 1/2$$

$$|Z| = \frac{\sqrt{2}}{(\sqrt{3})(\sqrt{3}/2)} = 2/3$$

$$|V| = |Z| = 2/3$$

3.  $Z_{re}$
- lowest  $\rightarrow$  pole
  - alternate

(3) - high  $\rightarrow$  zero

In the continued fraction expansion, if all the quotients have the sign then it satisfies Hurwitz.

$$\begin{array}{r|rrrr} 5 & 1 & 3 & 1 & \\ 1 & 5 & 9 & 1 & \\ 3 & 4/5 & 4/5 & & \end{array}$$

$$Q(s) = s^5 + 3s^3 + s$$

$$Q'(s) = 5s^4 + 9s^2 + 1$$

$$\psi(s) = \frac{Q(s)}{Q'(s)} = (5s^4 + 9s^2 + 1) \frac{s^5 + 3s^3 + s}{\dots}$$

$Q$  satisfies Hurwitz

$$F(s) = \frac{P(s)}{Q(s)} = \frac{m_1(s) + n_1(s)}{m_2(s) + n_2(s)}$$

$$F(s) = \frac{m_1 + n_1}{m_2 - n_2}$$

$$F(s) = \frac{m_1 m_2 - n_1 n_2}{m_2^2 - n_2^2} + \frac{n_1 m_2 - m_1 n_2}{m_2^2 - n_2^2}$$

(24)

$$= \text{Even } F(s) + \text{Odd } F(s)$$

$$= \text{Real } F(s) + \text{Im } F(s)$$

$$s^{\text{even}} \cdot s^{\text{even}} = s^{\text{even}}$$

$$s^{\text{odd}} \cdot s^{\text{odd}} = s^{\text{odd}}$$

$$s^{\text{even}} \cdot s^{\text{odd}} = s^{\text{odd}}$$

also  $F(s) = \text{PRF}$

$$s^{\text{even}} = (j\omega)^4 = \omega^4 \angle 0^\circ$$

$$s^{\text{odd}} = (j\omega)^2 = -\omega^2 \angle 180^\circ$$

$$\frac{m_1 m_2 - n_1 n_2}{m_2^2 - n_2^2} \geq 0$$

$$m_1 m_2 - n_1 n_2 \geq 0$$

KK

$$\frac{m_1 (\text{even})}{n_2 (\text{odd})} = \frac{n_1 (\text{odd})}{m_2 (\text{even})}$$

23

$$(s^3 + 4s) \quad 2s^4 + \dots \quad (2s + \dots)$$



24

$$Z_{11} = \frac{(R_2 + Ls) R_1}{R_1 + R_2 + Ls}$$

$$Z_{22} = \frac{R_2 (R_2 + Ls)}{R_1 + R_2 + Ls}$$

equal denominators.

$$Z_2(s) = \text{PRF}$$

$$|\text{Re } Z(\omega)| > \text{Rug}$$

30

$$Z(s) = \frac{2s+1}{s(s+1)} = \frac{A}{s} + \frac{B}{s+1} = \frac{1}{s} + \frac{1}{s+1}$$



$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow A = \frac{Z_{11}}{Z_{21}}$$

$$B = -\frac{V_1}{V_2}$$



$$\therefore B = - \left( \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} \right) = \textcircled{242}$$

$$D = \left. \frac{-I_1}{I_2} \right|_{V_2=0}, \quad D = \frac{-Y_{11}}{Y_{21}} = \left( \frac{Z_{22}/Z_{\Delta}}{Z_{21}/Z_{\Delta}} \right) = \frac{Z_{22}}{Z_{21}}$$

Conv:

$$1. \quad Z(s) = \frac{s^2+1}{s(s^2+2^2)}$$

$P \rightarrow \infty$  X

$P \rightarrow \text{origin}$  ✓

$P \rightarrow \text{conjugate pair}$  ✓

$$Z(s) = \frac{k_0}{s} + \frac{2ks}{s^2+\omega^2}$$


$$\frac{s^2+1}{s^2(s^2+4)} = \frac{k_0}{s} + \frac{2ks}{s^2+4}$$

$$k_0 \rightarrow 1/4$$

$$2k \rightarrow 3/4$$

$$Z(s) = \frac{1/4}{s} + \frac{3s/4}{s^2+4}$$
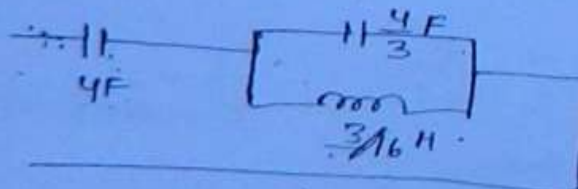
$$Z(s) = \frac{1}{4s} + \frac{1}{4s/3 + 16/3s}$$



1. (b)

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)} = \frac{A}{s} + \frac{B}{s+2} + C \quad (243)$$

2.

$$Z_D(s) = \frac{K(s+2)(s+6)}{s(s+4)(s+8)}$$

$$Z_D(s) \Big|_{s=-3} = +1 \Rightarrow K=5.$$

$$Z_D(s) = \frac{1.875}{s} + \frac{1.25}{s+4} + \frac{1.875}{s+8}$$


Resonance

$$1. \quad Q = \frac{\omega L}{R} = \frac{X_L}{R} = \frac{1000}{0.1} = 10^4$$

$$BW = \frac{f_0}{Q} = \frac{10 \times 10^6}{10^4} = 1 \text{ kHz}$$

2. Find  $Z_{th}$ .

~~Req~~

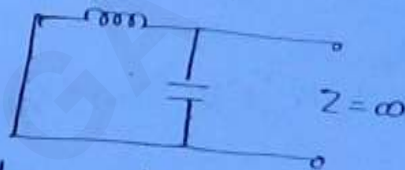

$Z = \infty$  for ideal current source


$$\omega_0 = \frac{1}{\sqrt{LC}} = 4 \text{ rad/sec} \Rightarrow \text{Resonant condition}$$

\* Q. In the ckt shown, at what value of  $R_1, R_2$  circuit resonant, for all frequencies.

$$B_L = B_C$$

$$\frac{X_L}{R_1^2 + X_L^2} = \frac{X_C}{R_2^2 + X_C^2}$$
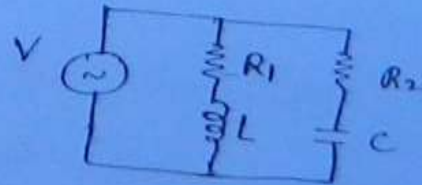
$$\frac{\omega L}{R_1^2 + (\omega L)^2} = \frac{1/\omega C}{R_2^2 + 1/\omega^2 C^2}$$



$$\frac{1}{\frac{R_1 + j\omega L}{j\omega L}} = \frac{1}{R_2 j\omega C + \frac{1}{j\omega C}}$$

(244)

$$\omega \rightarrow -L = R_2^m C \Rightarrow R_2 = \sqrt{\frac{L}{C}}$$

$$\frac{1}{\omega} \rightarrow \frac{R_1^2}{L} = \frac{1}{C} \Rightarrow R_1 = \sqrt{\frac{L}{C}}$$

$$R_1 = R_2 = \sqrt{\frac{L}{C}}$$

$$Y(s) = \frac{s^m + 0.5s + 100}{5s} = \frac{s}{5} + 0.1 + \frac{20}{s}$$

$$L = \frac{1}{20} \text{ H}, \quad G = 0.1, \quad C = 1/5$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$15 = \sqrt{V_R^2 + 9^2} \Rightarrow V_R = 12 \text{ V}$$

$$20 = \sqrt{V_R^2 + V_L^2} \Rightarrow 20^2 = 12^2 + V_L^2 \Rightarrow V_L = 16 \text{ V}$$

$$V_L - V_C = 9$$


$$V_C = 7$$


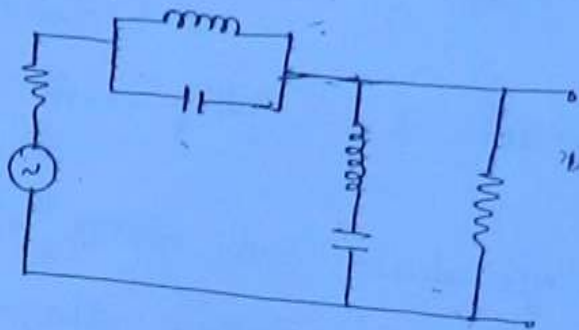
# Low pass filter

245


Q. Identify type of n/w for the n/w shown



at  $f=0$ ,

$$X_C = \infty \rightarrow C \rightarrow O.C.$$

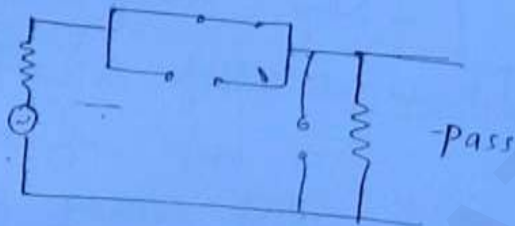
$$X_L = 0 \rightarrow L \rightarrow S.C.$$




at  $f = \infty$ ,

$$X_C = 0 \rightarrow C \rightarrow S.C.$$
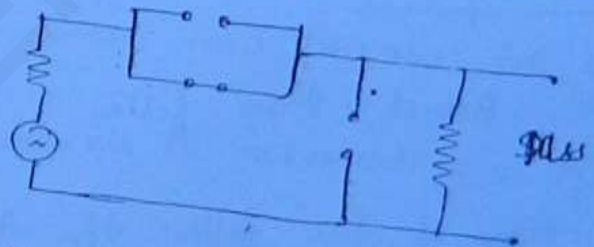
$$X_L = \infty \rightarrow L \rightarrow O.C.$$



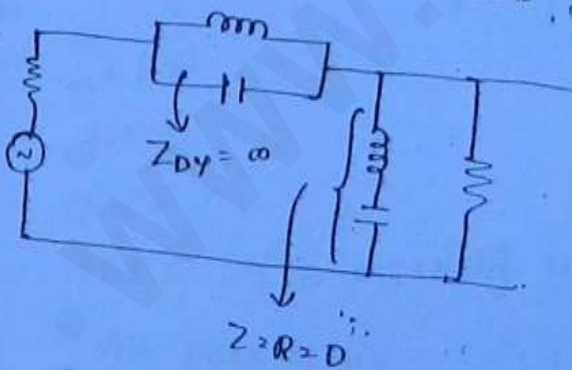
to verify whether BEF or all pass filter we have to check resonant freq.



at  $f = f_0$




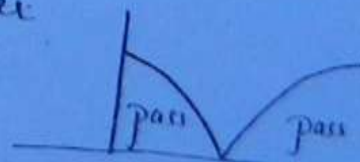When BEF eliminates only few frequencies, then it is also called as notch filter



Identify type of the n/w for the n/w shown.

246


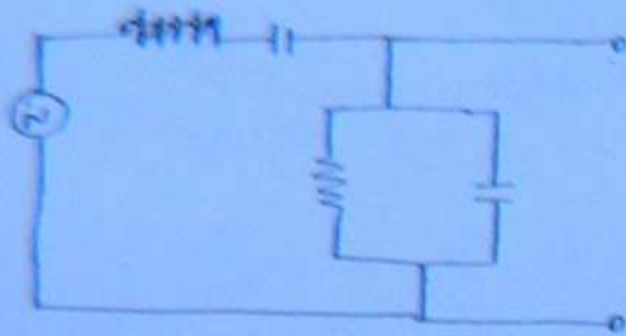


at  $f=0$ ,

$$X_C \rightarrow \infty \Rightarrow \text{c.o.c.}$$


at  $f=\infty$ ,
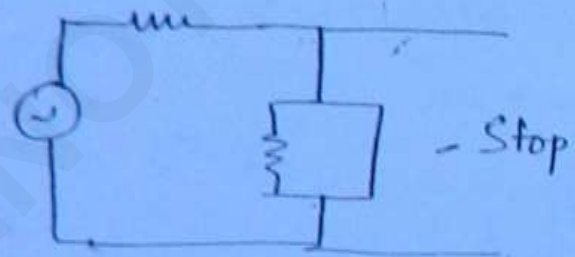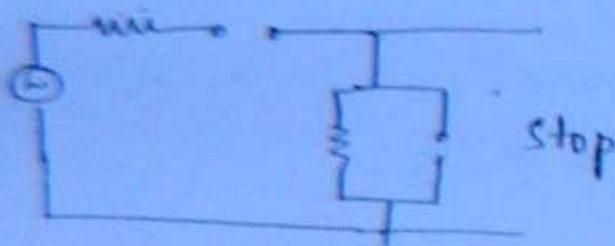
$$X_C \rightarrow 0, \text{ s.c.} \rightarrow \text{c.}$$



$\Rightarrow$  Band Pass filter

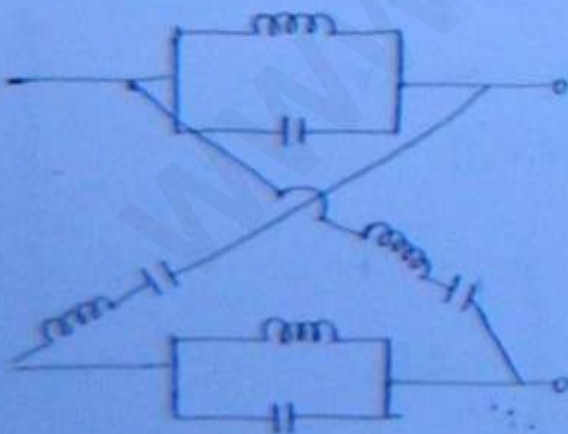Identify type of the filter of the n/w shown



- (a) LPF
- (b) BPF
- (c) BEF
- ✓ (d) all pass filter



# FILTERS

(247)

Based on components present in the filter, filters are classified as

1. Active filter
2. Passive filter.


- Active filters are made up of op-amp & capacitor.
- Generally inductor is not used in the active filter, since size of the inductor is bulky & cost is high.
- In the active filter, it is possible to increase gain of the system.
- Passive filter is made up of series and parallel LC sections. (reactive n/w)
- In passive filter it is not possible to increase gain of the system.
- Based on frequency of operation, filters are classified

as

1. LPF
2. HPF
3. BPF
4. BEF (BSF)
5. All pass filter.

LPF

First order


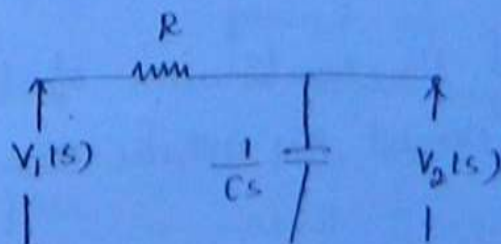




$$V_2(s) = V_1(s) \frac{1/cs}{R + 1/cs} = \frac{-V_1}{1 + RCS}$$


248

## Second order

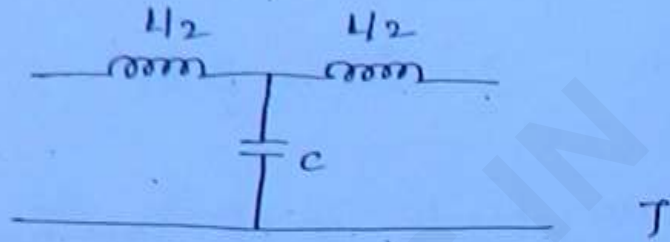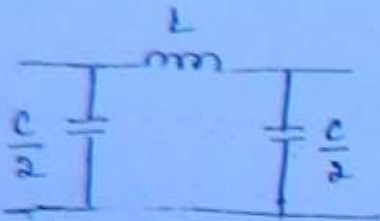


$$X_C = \frac{1}{2\pi f C}$$

$$X_L = 2\pi f L$$

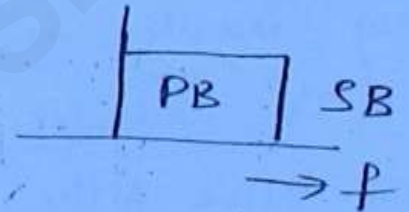

## 1PF



### First order

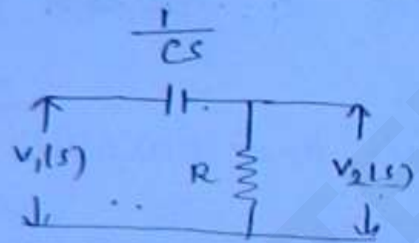

$$V_2(s) = V_1(s) \frac{R}{R + 1/cs}$$


$$\frac{V_2(s)}{V_1(s)} = \frac{Rcs}{1 + RCS}$$

### cond order

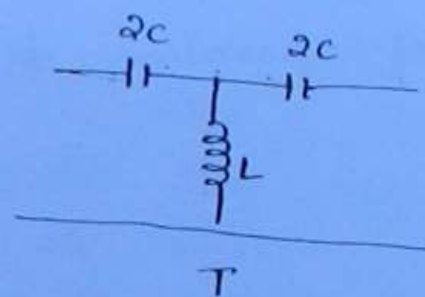
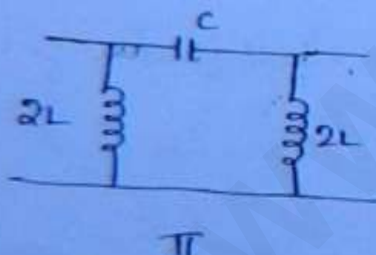


$$X_C = \frac{1}{2\pi f C}$$



$$X_L = 2\pi f L$$

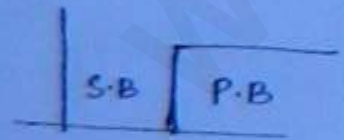

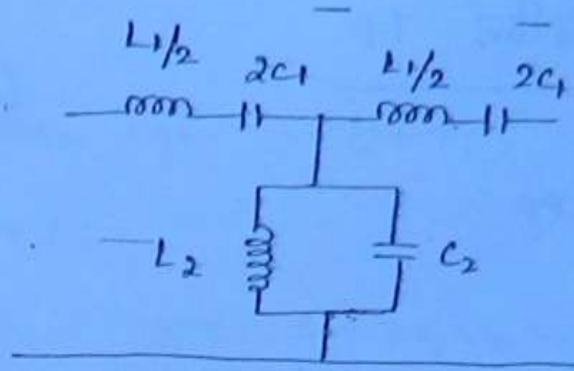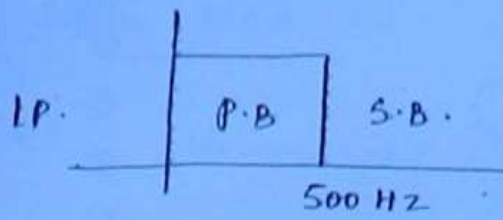PF can be obtained with the combination of LPF & HPF  
cut off freq. of LPF should be greater than, cut off  
freq. of HPF.






249

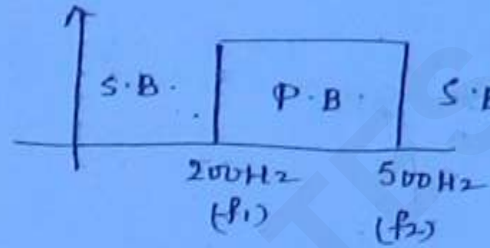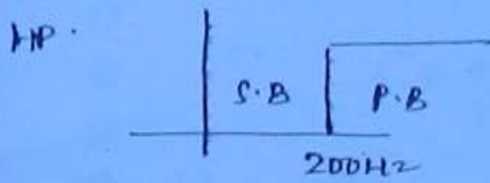
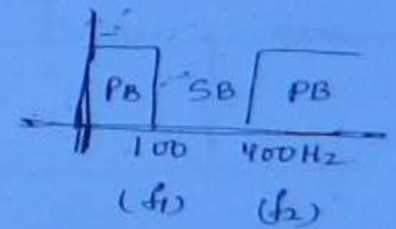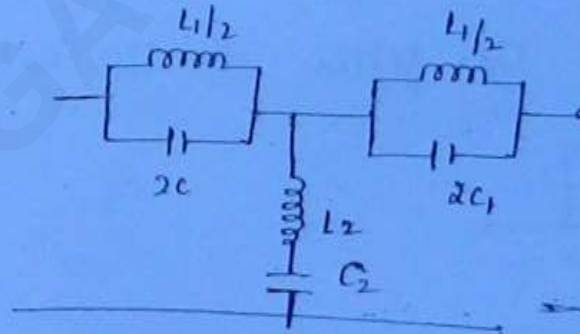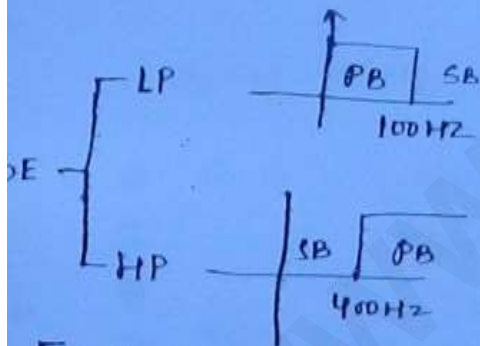
### BEF/BSF

BEF can be obtained by connecting LPF & HPF in parallel and cut off frequency of the HPF should be greater than cut off freq. of LPF.



### First Order filter T.F

$$\frac{1}{1 + \tau_c s} \rightarrow \text{LPF}$$

$$\frac{\tau_c s}{1 + \tau_c s} \rightarrow \text{HPF} \quad \tau_c = RC$$

$$\frac{1 - \tau_c s}{1 + \tau_c s} \rightarrow \text{All pass}$$

### Note :-

1. In All pass filter poles are present in LHP & zeros are present in right half plane.
2. Poles and zeros are in symmetric about jw axis.

## Second Order filters T.P

(256)

$$\frac{P}{s^2 + as + b} \rightarrow \text{LPF}$$


$$\frac{Ps^2}{s^2 + as + b} \rightarrow \text{HPF}$$

$$\frac{Ps}{s^2 + as + b} \rightarrow \text{BPF}$$

$$\frac{Ps^2 + q}{s^2 + as + b} \rightarrow \text{BEF}$$

$$\frac{s^2 - ps + q}{s^2 + as + b} \rightarrow \text{All-pass filter.}$$

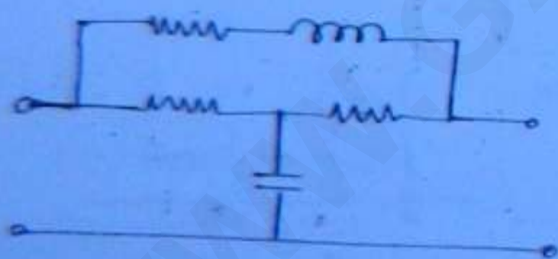
Identify type of the filter for the network shown.



$$f = 0,$$

$$X_C = \frac{1}{2\pi fC} = \infty \Rightarrow C \rightarrow \text{o.c.}$$

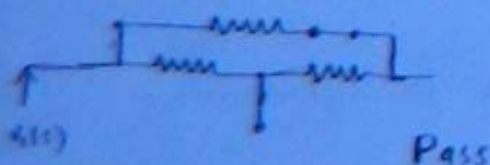
$$X_L = 2\pi fL = 0 \Rightarrow L \rightarrow \text{s.c.}$$



$$\text{at } f = \infty,$$

$$X_C = 0 \Rightarrow C \rightarrow \text{s.c.}$$
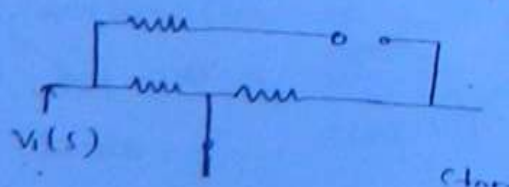
$$X_L = \infty \Rightarrow L \rightarrow \text{o.c.}$$





## Filter WB

(25/)

① denominator - charac. eqn.  $= (1 + \gamma s)^2$

$$= \gamma^2 s^2 + 2\gamma s + 1$$

$$\Rightarrow s^2 + \frac{2}{\gamma} s + \frac{1}{\gamma^2} = s^2 + 2\zeta\omega_n s + \omega_n^2$$

$$\omega_n = 1/\gamma$$

$$2\zeta \cdot \frac{1}{\gamma} = \frac{2}{\gamma} \Rightarrow \zeta = 1 \rightarrow \text{critically damped.}$$

9.  $B_1 = R/L_1$

$$B_2 = R/L_2 = \frac{R}{L_1/4} = \frac{4R}{L_1} \Rightarrow \frac{B_1}{B_2} = 1/4$$

## Resonance WB cont.

10.  $\left( D^2 + \frac{R}{L} D + \frac{1}{LC} \right) = 0 \quad s^2 + 20s + 10^6 = 0$

$$\omega_2 - \omega_1 = BW = \frac{R}{L} = 20, \quad \omega_0 = 10^6$$


$$Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{10^6}{20} = 50$$

11.  $V_L = 2V_C$

$$IX_L = 2IX_C \Rightarrow X_C = \frac{X_L}{2}$$

$$\cos\theta = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}} \Rightarrow \cos 45^\circ = \frac{20}{\sqrt{20^2 + \left(X_L - \frac{X_L}{2}\right)^2}}$$

$$\Rightarrow X_L = 40\Omega$$

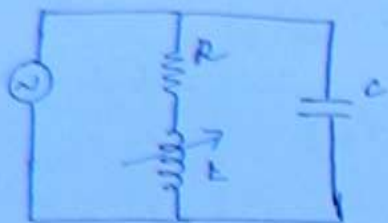

(252)

$$Z_{eq} = \frac{(R + jX_L)(-jX_C)}{R + jX_L - jX_C}$$

$$Z_{eq} = \frac{X_L X_C - j R X_C}{R + j(X_L - X_C)} \Rightarrow \frac{(X_L X_C - j R X_C)(R - j(X_L - X_C))}{R^2 + (X_L - X_C)^2}$$

$$= \frac{R X_L X_C - R X_C (X_L - X_C) - j [R^2 X_C + X_L X_C (X_L - X_C)]}{( )}$$

$$\text{Im}(Z_{eq}) = 0$$

$$R^2 X_C + X_L^2 X_C = 0$$

$$X_L^2 - X_L X_C + R^2 = 0$$

$$s^2 + 2\zeta \omega_n s + \omega_n^2 = 0$$

$$\omega_n = R, \quad 2\zeta \omega_n = -X_C \Rightarrow \zeta = \frac{-X_C}{2R}$$

$$\zeta < -1$$

$$\frac{-X_C}{2R} < -1 \Rightarrow \frac{X_C}{2R} > 1 \Rightarrow X_C > 2R$$

$$\underline{X_C > 10} \quad (b)$$

$$\zeta \geq 1$$


$$\frac{R}{2} \sqrt{\frac{C}{L}} \geq 1 \quad (c)$$

Note ① In over  $\zeta$ , critical damping, no oscillations are present.

In the underdamping system more than one oscillation are present.

Conv.

①

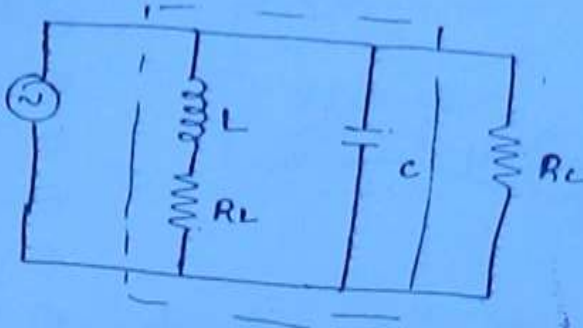


253

$R_C$  doesn't influence the imaginary part of  $Z_{eq}$ . Hence can be neglected.

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R_L^2}{L^2}}$$

②

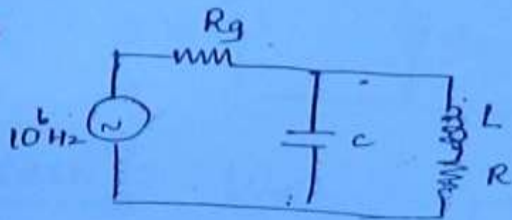

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R_g^2}{L^2}}$$

$R_g$  can be neglected ∵

it doesn't influence the  $\text{Im}(Z_{eq})$ .

$$10^6 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \rightarrow \textcircled{1}$$


$$Q = \frac{\omega L}{R} \Rightarrow \frac{R}{L} = \frac{\omega}{Q}$$

$$\frac{R}{L} = \frac{2\pi f}{7} \Rightarrow \frac{R}{L} = \frac{2\pi \times 10^6}{7} \rightarrow \textcircled{2}$$

Sub.  $\textcircled{2}$  in  $\textcircled{1}$ .

$$L = 0.2 \text{ mH}$$

$$R = 1.80 \Omega$$

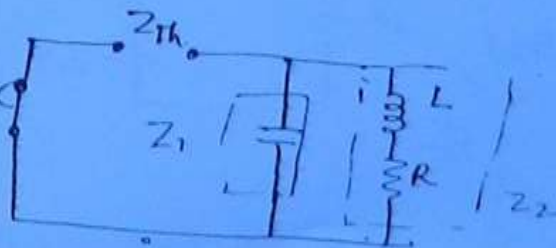


$$Z_1 = jX_C$$

$$Z_2 = R + jX_L$$

$$Z_{Th} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$




$$|Z_{Th}| = 5.3 \text{ k}\Omega$$



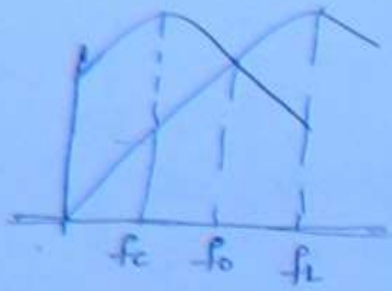

254


Maximum Power Transf.

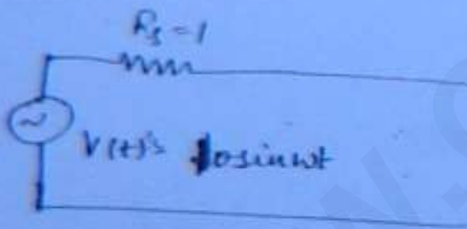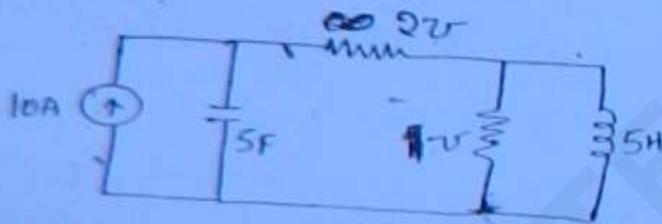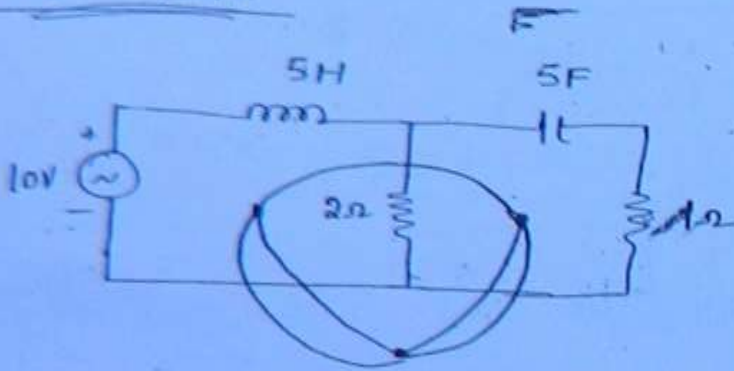

$$P_{max} = \frac{V_s^2}{4R_L}$$

$$R_L = R_s = 1$$

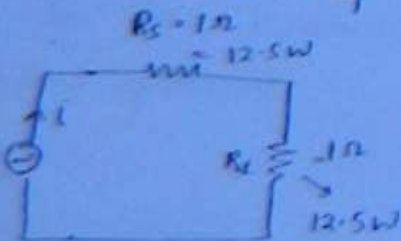
$$= \frac{(10/\sqrt{2})^2}{4} = \frac{100}{8} = 12.5W$$



$$P_T = 12.5 + 12.5$$

$$P_T = 25W$$

Q. 1)

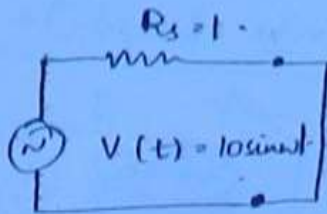


$$P_{av} = \frac{V_{eff}^2}{R_s}$$


$$= \frac{(10/\sqrt{2})^2}{1} = \underline{\underline{50W}}$$

(255)

## Proof of thevenin's theorem.

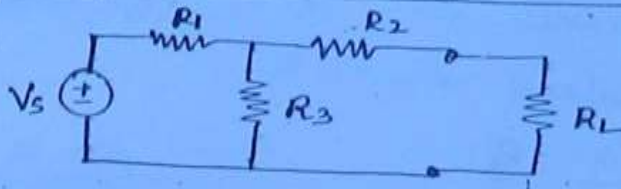


Case 1: ( $V_{Th}$ )

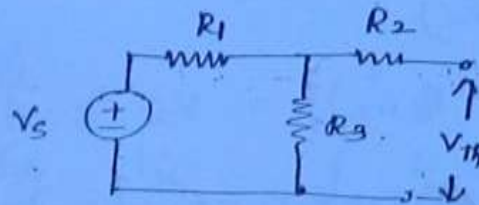


$$V_{Th} = \frac{V_s \cdot R_3}{R_1 + R_3} \rightarrow (1)$$

Case 2:

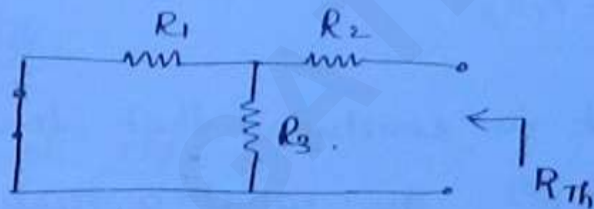

$$R_{Th} = R_2 + \frac{R_1 R_3}{R_1 + R_3} \rightarrow (2)$$

Case 3:

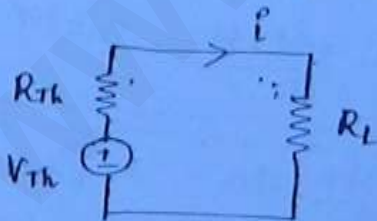


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$I_L = \frac{V_s \cdot R_3 / (R_1 + R_3)}{(R_2 + R_3)(R_1 + R_3) / (R_1 + R_3) + R_1 R_3 / (R_1 + R_3)}$$

$$I_L = \frac{V_s R_3}{(R_2 + R_3)(R_1 + R_3) + R_1 R_3}$$

$$\rightarrow (4)$$

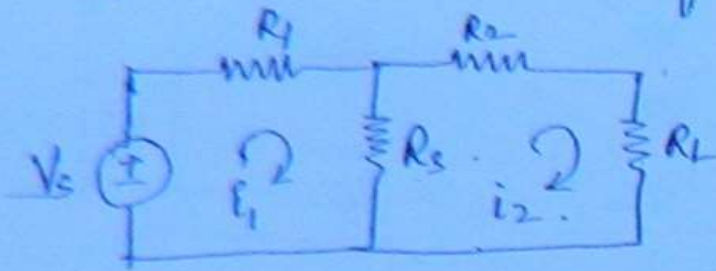using conventional method find out  $I_L$ .



(256)

$$V_S = (R_1 + R_3) i_1 - i_2 R_3$$

$$i_1 R_3 = i_2 (R_2 + R_3 + R_L)$$

$$i_2 (R_2 + R_3 + R_L) = \frac{V_S + i_2 R_3}{(R_1 + R_3)} \cdot R_3$$

$$i_2 [(R_2 + R_3 + R_L)(R_1 + R_3) - R_3^2] = V_S \cdot R_3$$

$$i_2 [R_2 R_1 + R_2 R_3 + R_1 R_3 + R_3^2 + R_L R_1 + R_L R_3 - R_3^2] = V_S R_3$$


$$i_2 = \frac{V_S R_3}{(R_1 + R_3)(R_L + R_2) + R_1 R_3} = I_L \rightarrow (8)$$

from the above calculation it is concluded that load current of eq (4) & eq (8) are equal. Hence, thevenin's theorem is proved.



# Magnetic Coupled circuits

Case (i)

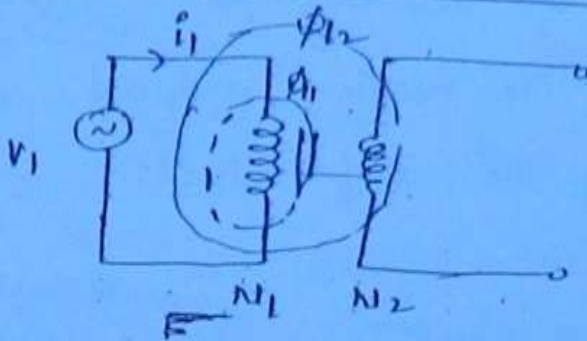

259

$I \Rightarrow \phi_1 \begin{cases} \phi_{11} \rightarrow \text{leakage flux} \\ \phi_{12} \rightarrow \text{useful flux (or) mutual flux} \end{cases}$

$$e_1 \propto \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{di_1} \cdot \frac{di_1}{dt}$$

$$\left( L = \frac{N\phi}{I} \right)$$

$$e_1 = -L_1 \frac{di_1}{dt}$$

$\rightarrow$  self induced emf.

$$e_2 \propto \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{di_1} \cdot \frac{di_1}{dt}$$


$$M_{21} = \frac{N_2 \phi_{12}}{i_1}$$

$$e_2 = -M_{21} \frac{di_1}{dt} \rightarrow \text{mutual induced emf}$$






Series opposing

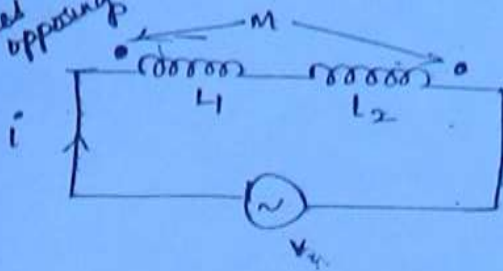

$$L_{eq} = L_1 + L_2 - 2M$$


259

parallel aiding

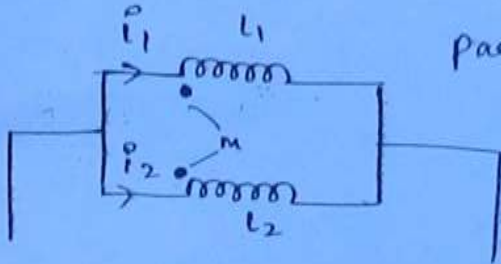


$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

parallel opposing

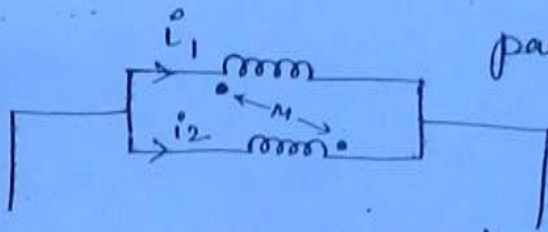

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

Q. Find eq. inductance wrt A & B.

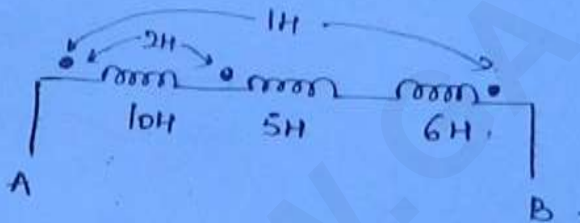


$$15 + 4 = 19$$

$$19 + 6 - 2 = \underline{23H}$$

$$L_{eq} = L_1 + L_2 + L_3 \pm 2M_1 \pm 2M_2 \pm 2M_3$$

$$L_{eq} = 10 + 5 + 6 + 4 - 2 = \underline{23H}$$

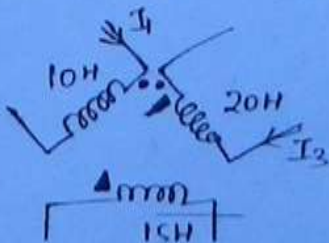Develop inductance matrix for the network shown.



$$\bullet 1H$$

$$\blacktriangle 2H$$



WWW.GATENOTES.IN

260